

14.75  
15



# NORTH SOUTH UNIVERSITY

Department of Mathematics & Physics

Experimental Physics

PHY-108L 12

Name of the Experiment: Charging and Discharging Characteristics of a Capacitor

Name: Jay kumar Ghosh

ID: 2211424 642

Serial No: 02

Group Member's Name: (i) Soykot Islam

ID: 2013928642

(ii)

ID:

Group Number: E

Date: (i) Experiment Performed: 27 February, 2023

(ii) Report Submitted: 06 March, 2023

---

Plot #15, Block # B, Bashundhara, Dhaka-1229, Bangladesh

Phone: +88 2 55668200, Fax: +88 2 55668202, Web: www.northsouth.edu

## Experiment Name: Charging and Discharging Characteristics

### of a Capacitor.


#### Objective:

- To observe charging and discharging characteristics of a capacitor using an oscilloscope.
- To verify the time constant in an RC circuit.
- Usage of Function Generator & Oscilloscope.

#### Apparatus:

- Breadboard
- Resistor:  $2\text{k}\Omega$
- Capacitor:  $0.1\mu\text{F}$
- Function Generator
- Oscilloscope
- wires

Position

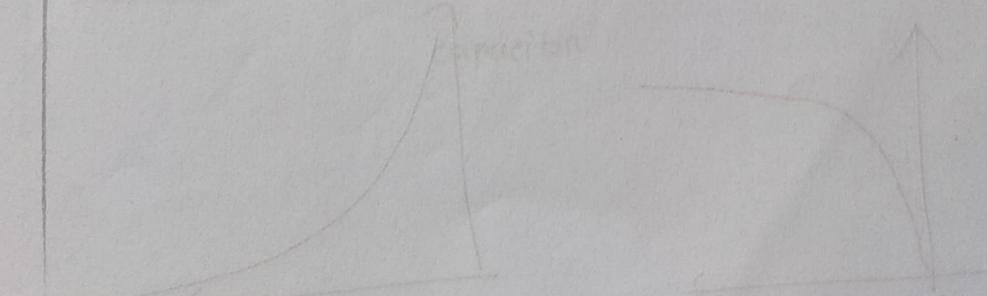

## Theory :

A capacitor is a passive device that stores energy in it in the form of an electric field. It can be charged and discharged through a resistor with the help of a power supply.


During charging, the voltage across the capacitor increases exponentially with time and is given by the following relation


$$V_c(t) = V_0 \left(1 - e^{-\frac{t}{RC}}\right)$$

Similarly, a charged capacitor can be discharged through a resistor and the voltage across the capacitor at any instant can be found by the following relationship

$$V_c(t) = V_0 e^{-\frac{t}{RC}}$$

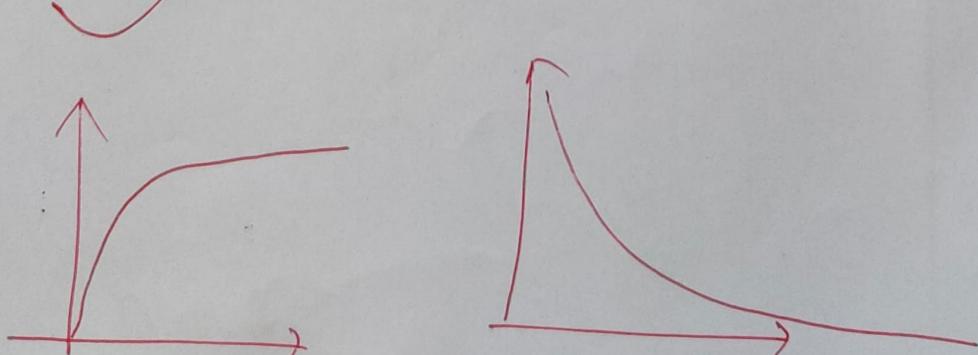Time constant is defined as the time required to charge the capacitor, through the resistor, to 63 percent of full charge; or to discharge it to 37% of its initial voltage.



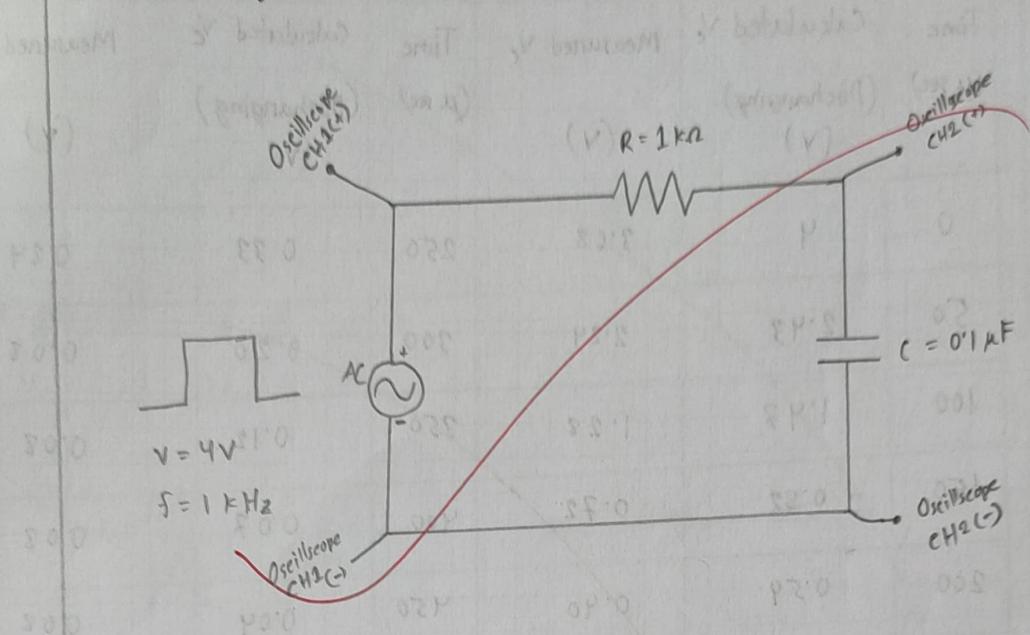Circuit Diagram:Data Table:

Time ( $\mu\text{sec}$ )	Calculated $V_c$ (Charging) (v)	Measured $V_c$ (v)	Time ( $\mu\text{sec}$ )	Calculated $V_c$ (Charging) (v)	Measured $V_c$ (v)
0	0	0.08	250	3.67	3.52
50	1.57	1.52	300	3.80	3.68
100	2.53	2.48	350	3.88	3.76
150	3.11	3.04	400	3.93	3.84
200	3.46	3.36	450	3.96	3.84

Table-1: Time dependent charging characteristic of a capacitor

Time (μ sec)	Calculated $V_c$ (Discharging) (v)	Measured $V_c$ (v)	Time (μ sec)	Calculated $V_c$ (Discharging) (v)	Measured $V_c$ (v)
0	4	3.68	250	0.33	0.24
50	2.43	2.24	300	0.20	0.08
100	1.47	1.28	350	0.12	0.08
150	0.89	0.72	400	0.07	0.08
200	0.54	0.40	450	0.04	0.08

Table 2: Time dependent discharging characteristic


Calculation:

For charging :

$$\text{when, } t = 50 \mu \text{sec}; V_c = V_0 (1 - e^{-\frac{t}{RC}})$$

$$= 4 (1 - e^{-\frac{50}{100}})$$


$$= 1.57 \text{ V}$$

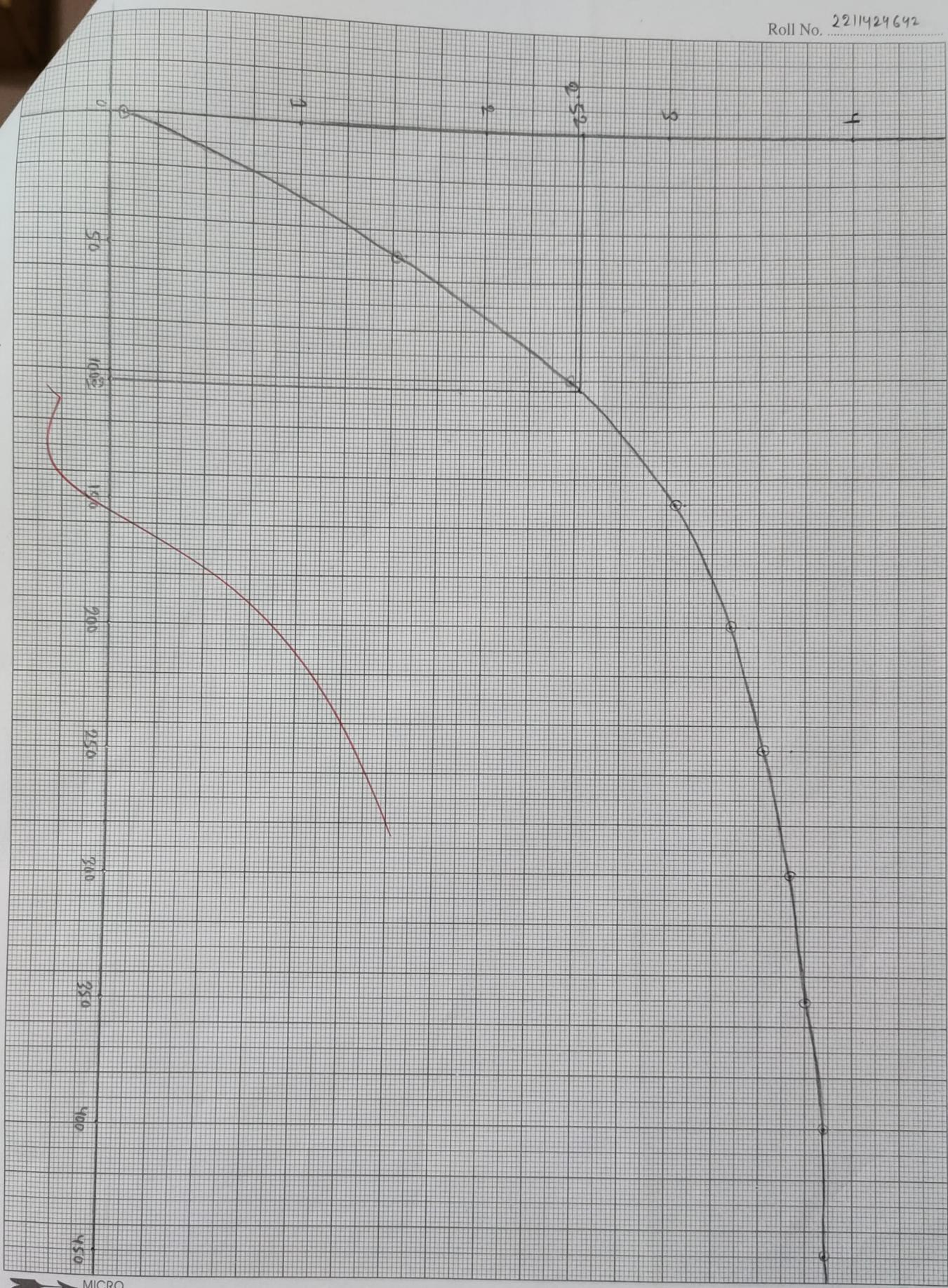

(N.P.) 20 cm x 25 cm

$\rightarrow V_c(v)$  $\rightarrow \text{Time } (\mu \text{ sec})$ 

Graph - 2: Discharging

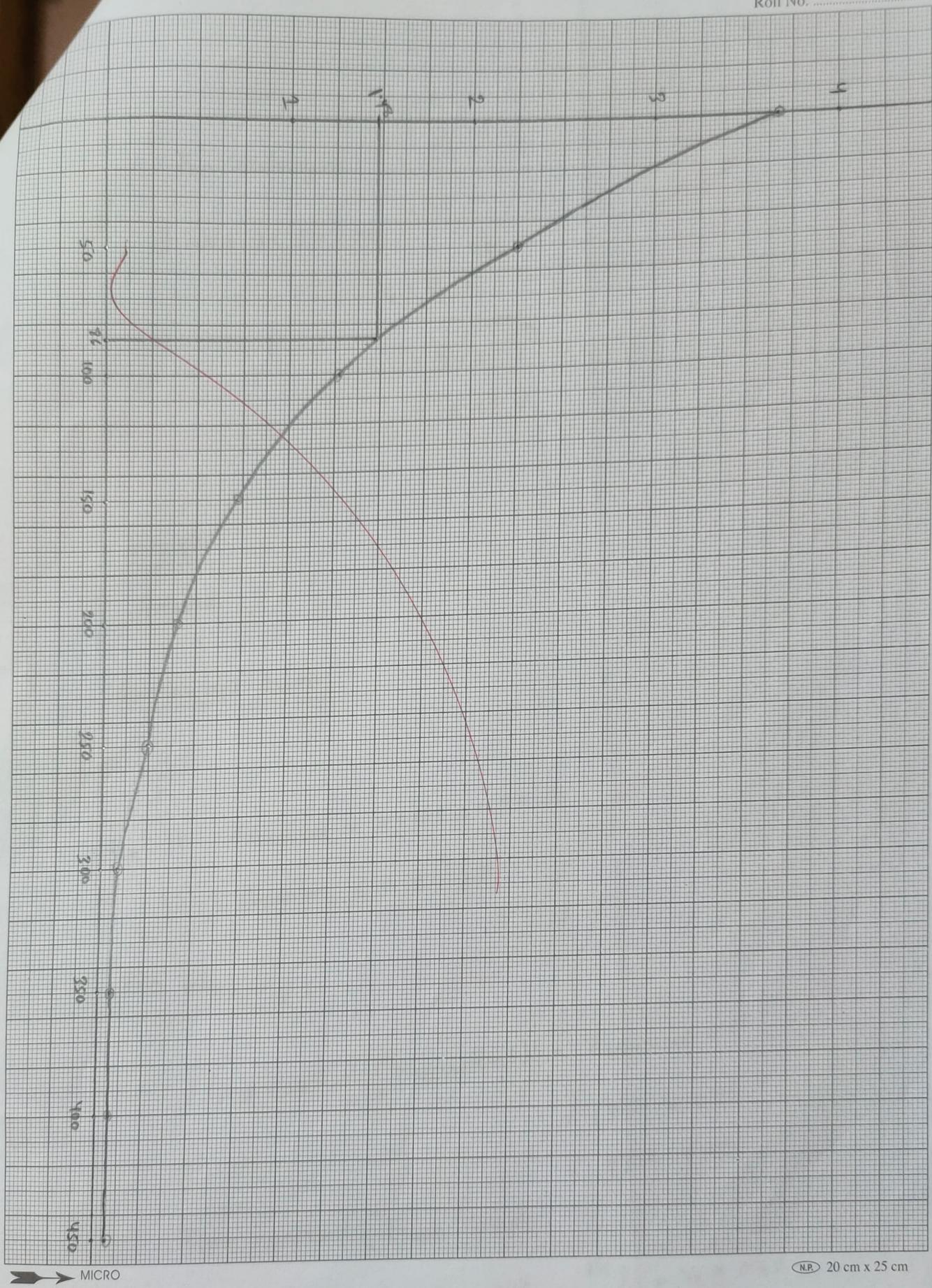

MICRO

(N.B.) 20 cm x 25 cm

For discharging:

when  $t = 50 \mu\text{sec}$ :

$$V_c = V_0 e^{-\frac{t}{RC}}$$

$-50/100$

$$= 4 \times e^{0.05}$$

$$= 2.43 \text{ V}$$

Graph:

Attached.

Questions and Answers:

1)

$$R_{\text{measured}} = 0.971 \text{ k}\Omega = 971 \Omega$$

$$\text{Capacitor, } C = 0.1 \mu\text{F}$$

For charging,

$$\text{Time constant (Theoretical)}: = R_{\text{measured}} \times C$$

$$= (971 \times 0.1)$$

$$= 97.1 \mu\text{sec}$$

Time constant (From Graph):

$$\text{When, } t = 1 \tau, \quad V_c = V_0 (1 - e^{-\frac{1}{RC}}) = V_0 \times 0.63$$

$$= 4 \times 0.63$$

$$= 2.52 \text{ V}$$

From the graph,

$$\text{when } V_c = 2.52 \text{ V}$$

$$\text{then, } t = 103 \mu\text{sec}$$

∴ time constant from graph:  $103 \mu\text{sec}$

$$\therefore \text{Error} = \left| \frac{\text{Time constant theoretical} - \text{Time constant from graph}}{\text{Time constant theoretical}} \right| \times 100\%$$
$$= \left| \frac{97.1 - 103}{97.1} \right| \times 100\% = 6.08\%$$

21

For discharging,

$$\text{Time constant theoretical} = 97.1 \mu\text{sec}$$

from graph:

$$\text{when } t = 1 \mu\text{sec}, V_c = V_0 e^{-t/\tau} = 1.48 \text{ V}$$

from the graph,

$$\text{when } V_c = 1.48 \text{ V}$$

$$\text{then, } t = 86 \mu\text{sec}$$

∴ time constant from graph:  $86 \mu\text{sec}$

$$\therefore \text{Error} = \left| \frac{97.1 - 86}{97.1} \right| \times 100\%$$

$$= 11.43\%$$

*To find error while discharging.*

31

Yes, there is a difference between theoretical and experimental values of time constants, as obtained from the charging and discharging of capacitors. There are

about 6.08% of error while charging and 11.43% of error while discharging. It happens because of the supply of voltage. We provided 4 V to the circuit but

in the set oscilloscope it was showing that 3.96 V.

Because of the wire there are some resistance which caused voltage drop. And also the graph was drawn by best feed line. That's why there are also some error.

By combining them we found 6.08% and 11.43% of error respectively for charging and discharging.

41

$$0.01 \times | \frac{20 - 1.8}{1.8} | = \text{time}$$

As we know,

$$\text{time constant}, \tau = RC$$

that means,  $\tau \propto R$

12

If we decreased the resistors then time constant will also be decreased. That means capacitor will charge very quickly than before also discharge faster than before.

In this experiment,

$$R = 1k\Omega$$



$$C = 0.1 \mu F$$

$$\therefore \tau = 1000 \times 0.1 = 100 \mu \text{sec}$$


If we decreased  $R$  to  $100\Omega$

$$\therefore \tau_0 = 100 \times 0.1 = 10 \mu \text{sec}$$

In graphical view,

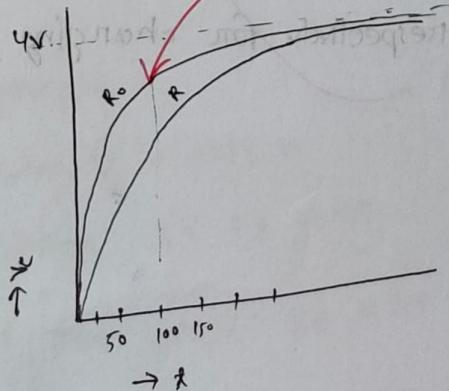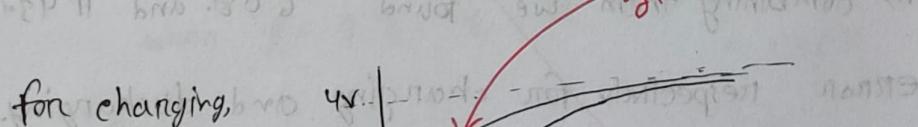

for discharging,

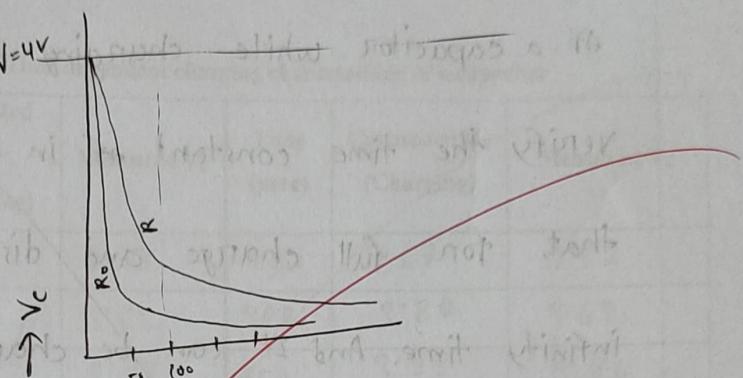

### Results:

From this experiment, we found that a capacitor can change  $C_{37\%}$  within  $1T$  (time constant) and also discharge  $37\%$  within  $1T$  (time constant). And we found ~~it~~ almost same ~~time constant~~ with some error. We found that our capacitor charge  $63\%$  within  $10^3 \mu\text{sec}$  and discharge  $37\%$  within  $86 \mu\text{sec}$ .

### Discussion :

From the experiment we learnt about the characteristics of a capacitor while charging and discharging. We also verify the time constant  $\tau$  in an  $RC$  circuit. We learn that, for full charge and discharge capacitors need infinity time. And it can be charge completely within one time constant. And in this experiment, we don't face any difficulty. But some time oscilloscope showing some abnormal behavior, but we fix it by rechecking the wire connection. In short, we learn about the charging and discharging characteristics of a capacitor.

Group - E

Name: Joy kumar Ghosh  
ID: 2211424 642

Name: Soykot Islam

ID: 2013928642

Data Tables:

Table 1: Time dependent charging characteristic of a capacitor

Time (μsec)	Calculated $V_C$ (Charging)	Measured $V_C$	Time (μsec)	Calculated $V_C$ (Charging)	Measured $V_C$
0	0	0.08	250	3.67	3.52
50	1.57	1.52	300	3.80	3.68
100	2.53	2.48	350	3.88	3.76
150	3.11	3.04	400	3.93	3.84
200	3.46	3.36	450	3.96	3.84

$$V_C = V_0 (1 - e^{-\frac{t}{RC}})$$

Table 2: Time dependent discharging characteristic of a capacitor

Time (μsec)	Calculated $V_C$ (Discharging)	Measured $V_C$	Time (μsec)	Calculated $V_C$ (Discharging)	Measured $V_C$
0	4	3.68	250	0.33	0.24
50	2.43	2.24	300	0.20	0.08
100	1.47	1.28	350	0.12	0.08
150	0.89	0.72	400	0.07	0.08
200	0.54	0.40	450	0.04	0.08

$$V_C = V_0 e^{-\frac{t}{RC}}$$

Point b