
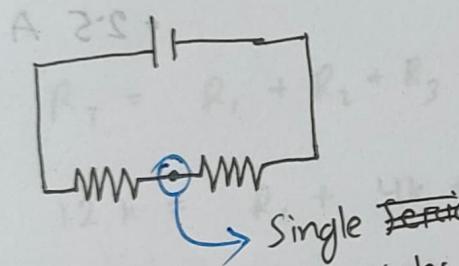



$$\frac{V}{R} = \frac{V}{8} = I$$

$$\frac{V}{R} = \frac{V}{9} = I$$


$$I = \frac{V}{9}$$

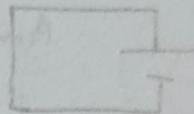

series line

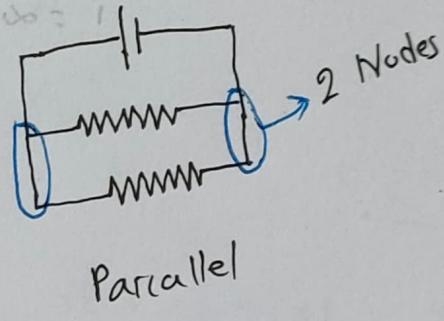

parallel

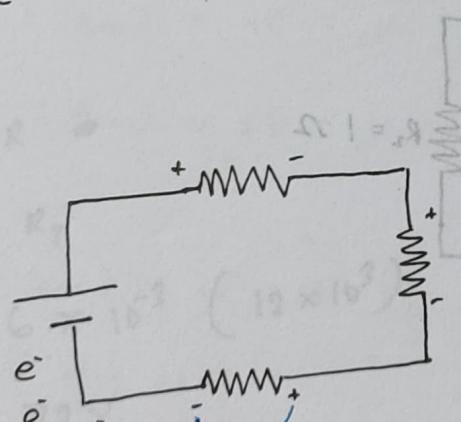


Potential Difference

$$i = \frac{q}{t}$$


$$i = \frac{V}{R} \Rightarrow i = \frac{V}{9}$$

$$\Rightarrow V = iR$$

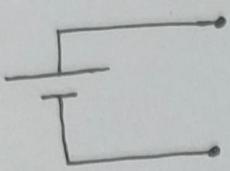


open circuit
infinity Resistance

$$R = \infty$$

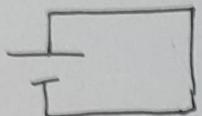

$$R = 0$$

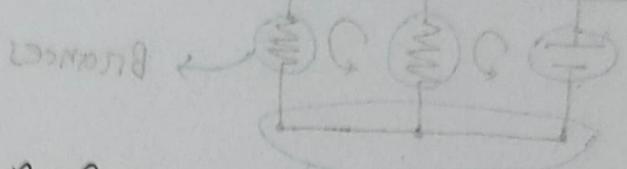

$$V = iR$$



$$i = \frac{V}{R}$$

$$V = i \cdot 0$$

$$= 0$$



$$i = \frac{V}{0}$$

$$i = \infty$$

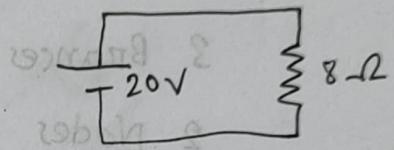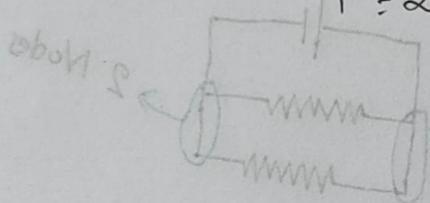

$$I = \frac{V}{R} = \frac{20}{8}$$

$$= 2.5 \text{ A}$$

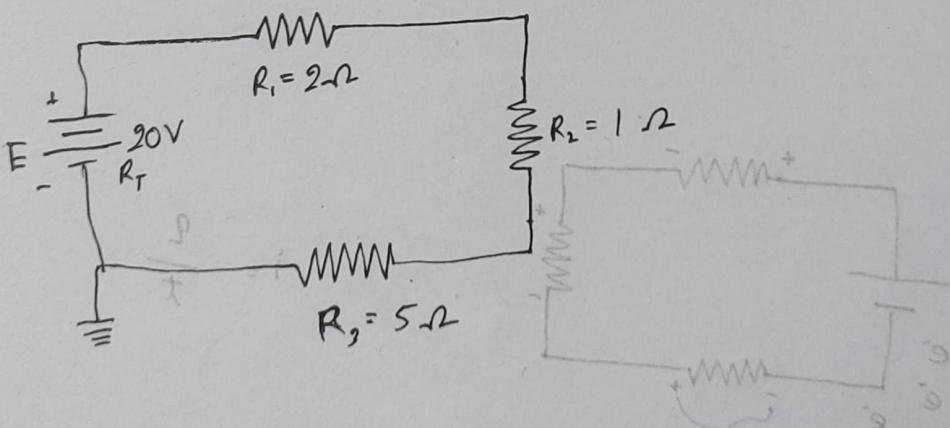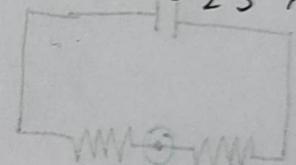

$$R_1 = 2 \Omega ; I = 2.5 \text{ A}$$

$$V_1 = 2 \times 2.5 = 5 \text{ V}$$

$$R_2 = 1 \Omega ; I = 2.5 \text{ A}$$


$$V_2 = 1 \times 2.5 = 2.5 \text{ V}$$

$$i = \frac{V}{R} = \frac{1}{R} \cdot V$$

$$i = \frac{V}{R}$$

$$R_3 = 5 \Omega ; I = 2.5 A$$

$$V_3 = 5 \times 2.5 = 12.5 V$$

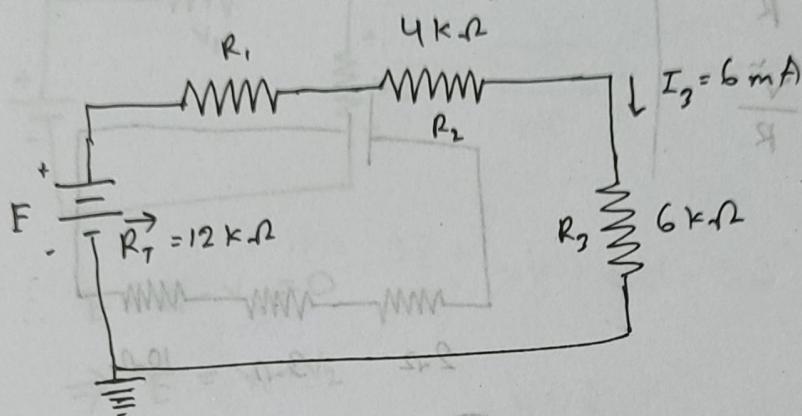

$$R_T = R_1 + R_2 + R_3$$

$$12\text{ k} = R_1 + 4\text{k} + 6\text{k}$$

$$R_1 = 2\text{k } \Omega$$

$$V_{81} = A_m d \times 4\Omega = 9\text{ V}$$

$$V = IR = A_m d \times 4\Omega = 9\text{ V} - 9 = 0$$

$$E = I R_T$$

$$= 6 \times 10^3 \text{ A} \times 12 \times 10^3 \Omega$$

$$= 72\text{ V}$$


$$A_m d = \frac{2\Omega}{k\Omega} = I$$

$$W_{m28} = A_m d \times 2 = 9$$

$$W_{m801} = A_m d \times 81 = 9$$

$$W_{m5F} = A_m d \times 51 = 9$$

L-2 / 02.02.2023

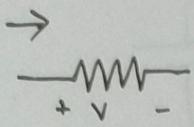


$$P = V I$$

$$P = (IR) I = I^2 R$$

$$P = V \left(\frac{V}{R} \right) = \frac{V^2}{R}$$

$$V = IR$$

$$I = \frac{V}{R}$$

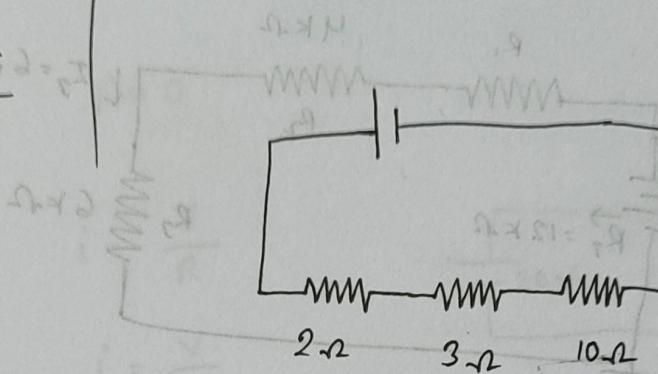

$$V = IR \quad \text{Same}$$

$$\therefore V \propto R$$

Example : 5.7

$$\begin{aligned} a) \quad R_T &= 1k + 2k + 3k \\ &= 6k \Omega \end{aligned}$$

$$c) \quad V_1 = 1k \times 6mA = 6V$$

$$V_2 = 3k \times 6mA = 18V$$

$$b) \quad 36 = I_s (6k)$$

$$V_3 = 2k \times 6mA = 12V$$

$$\therefore I_s = \frac{36}{6k} = 6mA$$

$$d) \quad P = 36 \times 6mA$$



$$= 216 mW$$

$$e) \quad P_1 = 6 \times 6mA = 36mW$$

$$P_2 = 18 \times 6mA = 108mW$$

$$P_3 = 12 \times 6mA = 72mW$$


$$f) \rightarrow 216mW$$

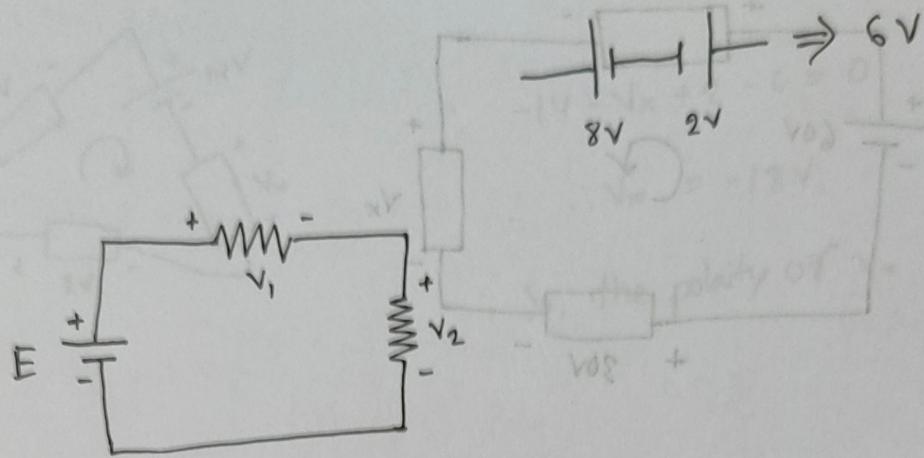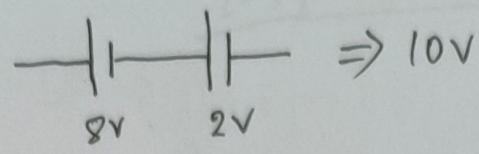

$$\therefore E - V_1 - V_2 = 0$$

$$\Rightarrow E = V_1 + V_2$$


Example : 5.8

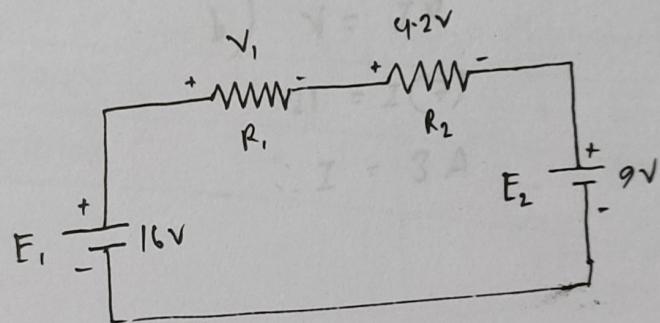

$$16 - V_1 - 4.2 - 9 = 0$$

$$\therefore V_1 = 2.8 \text{ V}$$

Example : 5.10

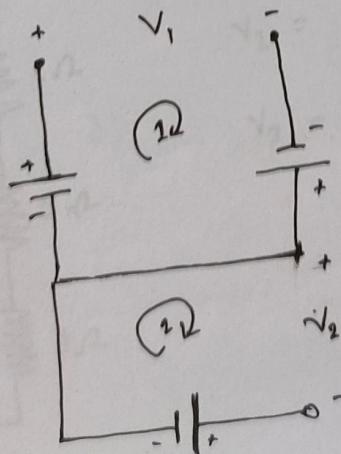


$$1: 25 - V_1 + 15 = 0$$

$$\therefore V_1 = 40 \text{ V}$$

$$2: -V_2 - 20 = 0$$


$$V_2 = -20 \text{ V}$$

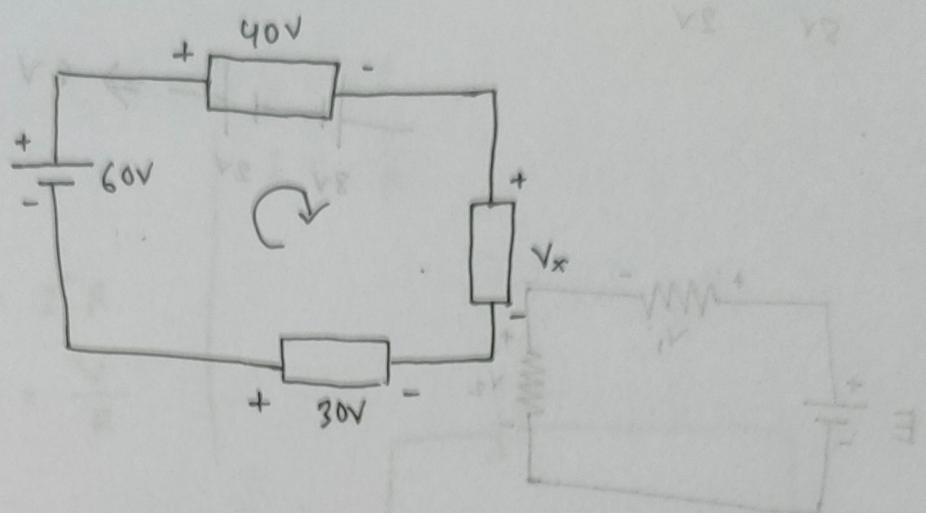

$$\therefore 60 - 40 - V_x + 30 = 0$$

$$V_x = 50 \text{ V}$$

$V = IR \rightarrow \text{Same}$

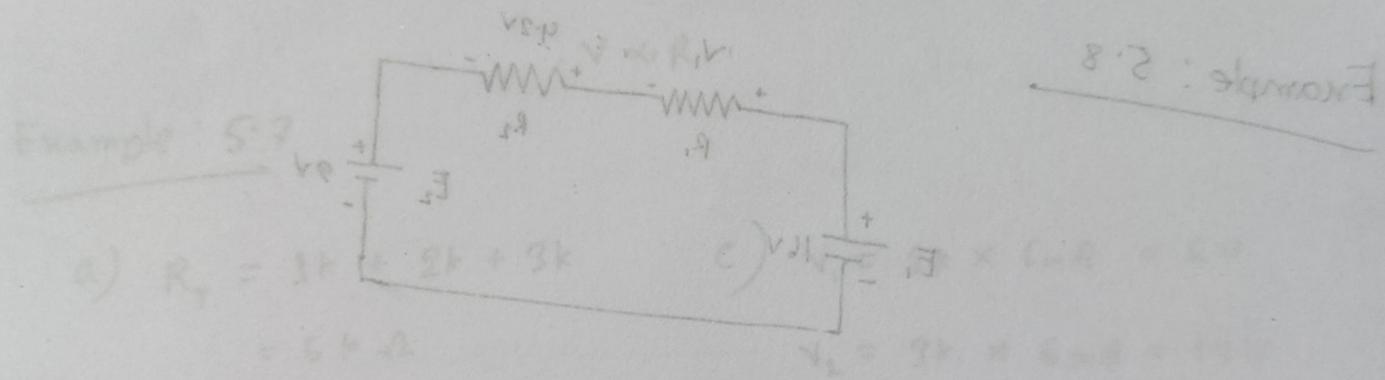

$$b) 36 = 3(6k)$$

$$0 = 36 - 54V/3 = 12 - 18V$$

$$18V = \frac{36}{6k} \times 6mA$$


$$0 = 21 + V - 22 \therefore 1$$


$$V_{DH} = 1V$$

$$P_D = 0.05 \times 6mA = 0.3W$$

$$P_{DH} = 0.05 \times 1V = 0.05W$$

$$P_{DH} = 0.05 \times 0.05A = 0.0025W$$

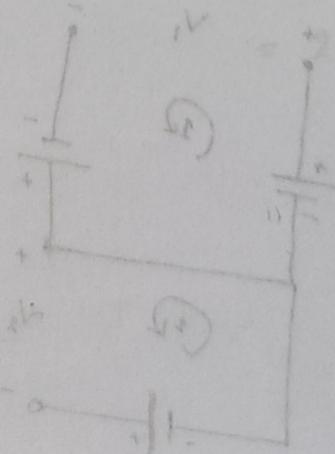


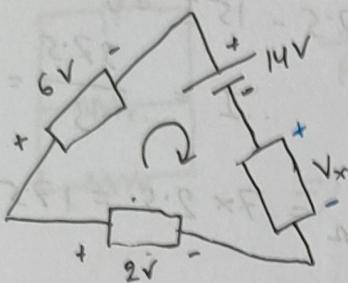

$$-14 - V_x + 2 - 6 = 0$$

$$\therefore V_x = -18V$$

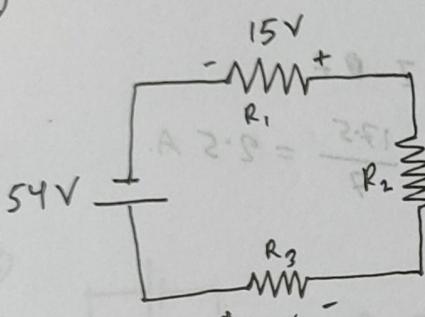\therefore So, the polarity of V_x will be change



$$a) -54 + 15 + V_2 + 18 = 0$$

$$\therefore V_2 = 21$$

$$c) 15 = I_2 R_1$$

$$\therefore R_1 = \frac{15}{3} = 5\Omega$$


$$18 = I_2 R_3$$

$$\therefore R_3 = \frac{18}{3} = 6\Omega$$


$$V_1 = \frac{6}{6+3+1} \times 20 = 12V$$

$$V_2 = \frac{3}{6+3+1} \times 20 = 6V$$

$$V_3 = \frac{1}{6+3+1} \times 20 = 2V$$

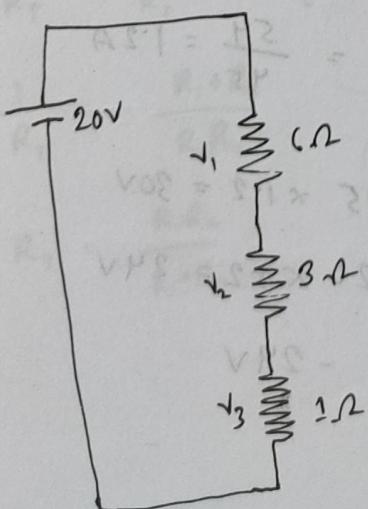

(*)

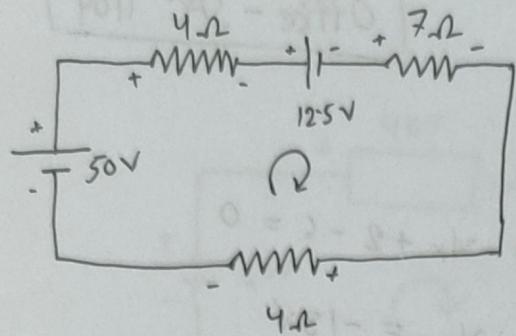


$$\therefore 50 - 4I - 12.5 - 7I - 4I = 0$$

$$\therefore 37.5 - 15I = 0$$

$$\therefore I = \frac{37.5}{15} = 2.5 \text{ A}$$

$$\therefore V_{7\Omega} = 7 \times 2.5 = 17.5 \text{ V}$$

(*)

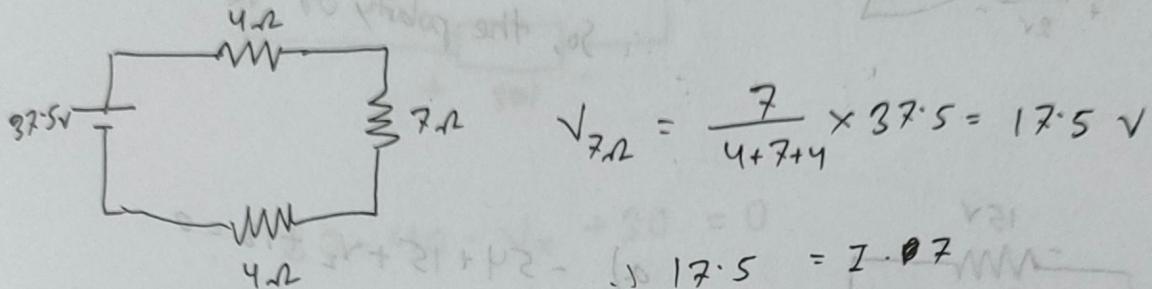


$$V_{7\Omega} = \frac{7}{4+7+4} \times 37.5 = 17.5 \text{ V}$$

$$\therefore 17.5 = I \cdot 7$$

$$\therefore I_2 = \frac{17.5}{7} = 2.5 \text{ A}$$

	Enters through	Exists (From)	
Current	+	-	negative
Current	-	+	positive

(*)

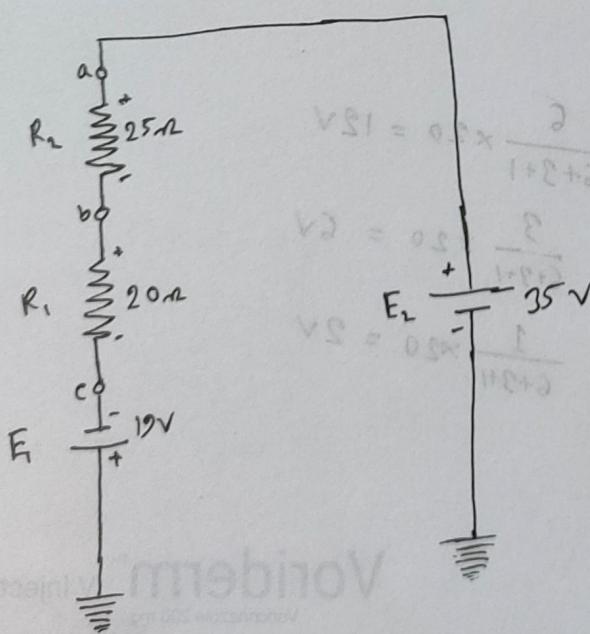

$$\therefore 35 = 25I + 20I - 19$$


$$\Rightarrow 54 = 45I$$

$$\therefore I = \frac{54}{45} = 1.2 \text{ A}$$

$$\therefore V_{ab} = 25 \times 1.2 = 30 \text{ V}$$

$$V_{bc} = 20 \times 1.2 = 24 \text{ V}$$

$$V_{bd} = -24 \text{ V}$$

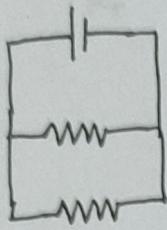

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2}$$


$$\Rightarrow R_T = \left(\frac{1}{R_1} + \frac{1}{R_2} \right)^{-1}$$

$$R_T = \left(\frac{1}{1} + \frac{1}{4} + \frac{1}{5} \right)^{-1}$$

$$= \left(\frac{20+5+4}{20} \right)^{-1}$$


$$= \left(\frac{29}{20} \right)^{-1}$$
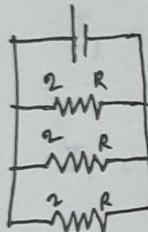
$$\left(\frac{1}{81} + \frac{1}{81} \right) = R_T$$



$$R_T = \left(\frac{1}{2} + \frac{1}{2} \right)^{-1}$$

$$= 1 \Omega$$

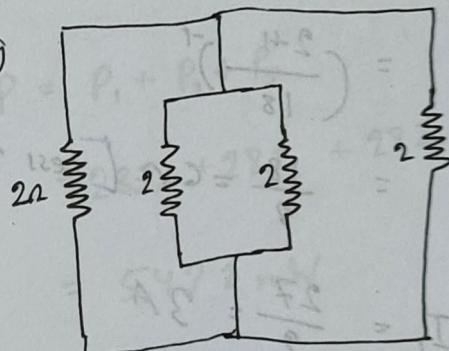


$$\frac{1}{R_T} = \frac{R}{N}$$

$$R_T = \frac{2}{4} = \frac{1}{2} \Omega$$

⊗

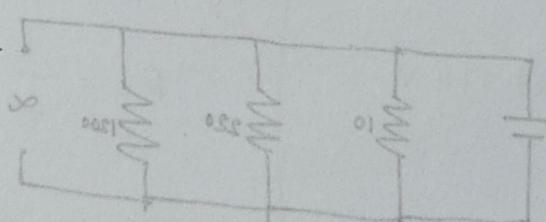
$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2}$$




$$\frac{1}{R_T} = \frac{R_1 + R_2}{R_1 R_2}$$

$$R_T = \frac{R_1 R_2}{R_1 + R_2}$$
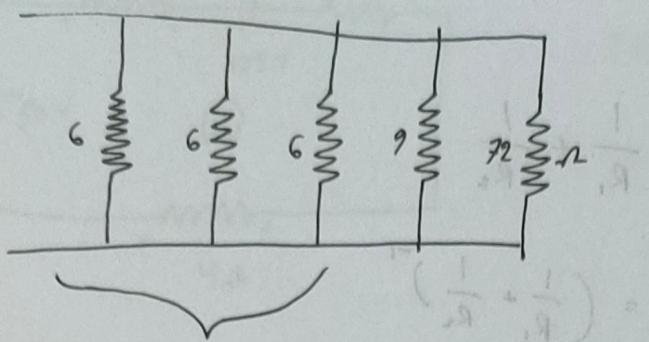
$$\left(\frac{1}{\infty} + \frac{1}{0.051} + \frac{1}{0.051} + \frac{1}{0.1} \right) = R_T$$



$$\frac{6}{3} = 2 \text{ ohms}$$

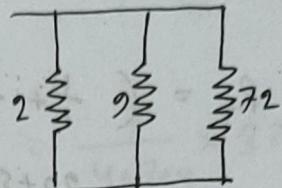

$$R_T = \left(\frac{1}{9} + \frac{1}{18} \right)^{-1}$$

$$I_s = \frac{E}{R_T} = \frac{27}{6} = 4.5 \text{ A}$$


$$= \left(\frac{2+1}{18} \right)^{-1}$$

$$= \frac{18}{3} = 6 \text{ ohms}$$

$$\therefore I_1 = \frac{27}{9} = 3 \text{ A}$$

$$I_2 = \frac{27}{18} = 1.5 \text{ A}$$

$$\frac{R}{R_1} = \frac{1}{R_2}$$

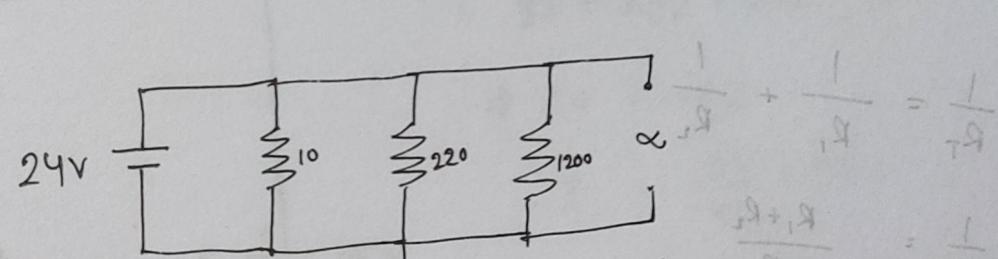

$$R_T = \left(\frac{1}{10} + \frac{1}{220} + \frac{1}{1200} + \frac{1}{\infty} \right)^{-1}$$

∞ can be ignored

$$= 9.49 \text{ ohms}$$


$$E = I_s R_T$$

$$\Rightarrow I_s = \frac{E}{R_T}$$

$$I_1 = \frac{24}{10} = 2.4 A$$

$$I_2 = \frac{24}{220} = 0.12 A$$

$$I_3 = \frac{24}{1.2k} = 20mA$$

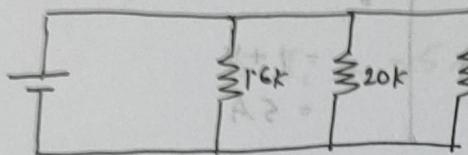

a) $R_T = \left(\frac{1}{1.6} + \frac{1}{20} + \frac{1}{56} \right)^{-1} = 1.4k\Omega$

b) $I_s = \frac{28}{1.4k} = 20mA$

$$I_1 = \frac{28}{1.4k} = 17.5mA$$

$$I_2 = \frac{28}{20k} = 1.4mA$$

$$I_3 = \frac{28}{56k} = 0.5mA$$

$$E = I_s R_T \quad (b)$$

$$28 \times 8.0 = \frac{21}{50} = 0.42$$

$$0 = I_1 - I_2 + I_3$$

$$17.5 - 1.4 = 16.1$$

$$A_2 =$$

$$1.4 \times 2 = 2.8$$

\rightarrow short circuit

\rightarrow short circuit

$$2I + rI = 25$$

$$rI - iI = 25$$

$$P = P_1 + P_2 + P_3$$

$$28I_1 + 28I_2 + 28I_3$$

$$28I_1 + 28I_2 + 28I_3$$

$$= 543.2 mW$$

$$A_{NO.5} = 2 + 0.1 + 8 = 10$$

$$VdI = (2)(0.5) = 1V = E$$

$$I^2 = R_2 \quad (c)$$

$$(0.5)^2 = 0.25$$

$$0.25 \times 8 = 2$$

L-5/11.02.2023/

(*) Kirchhoff's current Law:

6.17

$$I_1 + I_2 - I = 0 \quad \left| \begin{array}{l} I_3 = I_1 = 1A \\ I_4 = I_2 = 4A \end{array} \right| \quad \left| \begin{array}{l} I_5 = I_3 + I_4 \\ = 1+4 \\ = 5A \end{array} \right.$$

6.18/

From node a,

$$I_1 + I_2 = I_3$$

$$\therefore I_3 = 4+3$$

$$= 7A$$

From node b,

$$I_3 = I_4 + I_5$$

$$I_5 = I_3 - I_4$$

$$= 7-1 = 6A$$

6.19/

a) $I_s = 8+10+2 = 20mA$

b) $E = V_1 = (2)(8) = 16V$

c) $V_3 = R_3 I_s$

$$16 = R_3 (2)$$

$$\therefore R_3 = 8 k\Omega$$

d) $E = I_s R_T$

$$R_T = \frac{16}{20} = 0.8 k\Omega$$

6.20/


Let's assume that I_1 is entering.

$$\therefore I_1 + 10 + 4 + 8 = 5 + 4 + 2 + 6$$

$$\Rightarrow I_1 + 22 = 17$$

$$\therefore I_1 = -5A$$

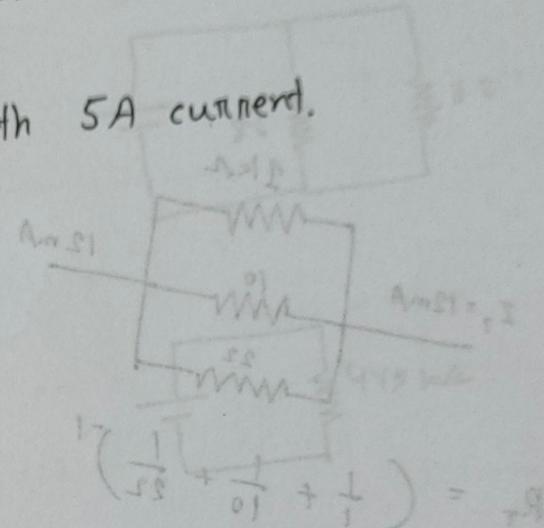$\therefore I_1$ is exiting with 5A current.



$$\therefore V = IR$$



$$I = \frac{V}{R} \quad R_{\text{eq}} = 12 \quad I = \frac{12}{12} = 1A$$

$$\therefore 258 =$$

$$\frac{(2.8)(4000)}{12} \quad [\text{Fahr} = \frac{I^2 R}{T \cdot A \text{ (area)}}]$$

$$AV = \left(\frac{1}{R_1} + \frac{1}{R_2} \right)$$

$$= 2.33 \text{ V}$$

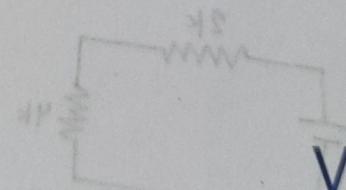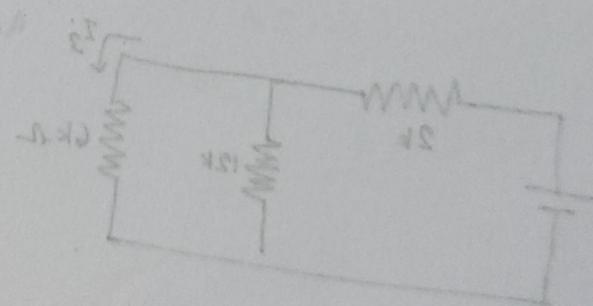

$$Am 21 = \frac{V}{R}$$


L-6 / 16.02.2023 /

⊗ Current devide Rule!

$$I \propto \frac{1}{R}$$

$$\Rightarrow I_x = I_T \cdot \frac{R_T}{R_x}$$

6.22

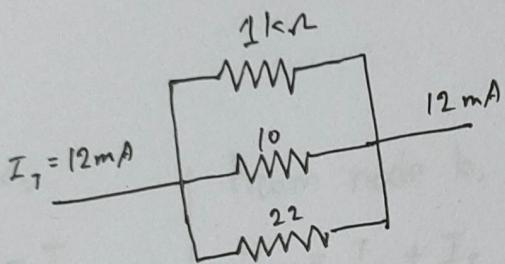


$$R_T = \left(\frac{1}{1} + \frac{1}{10} + \frac{1}{22} \right)^{-1}$$


$$= 873 \text{ } \Omega$$

$$I_x = \frac{I_T R_T}{R_x} = \frac{12 \times 10^{-3} \times 873}{1000} = 10.48 \text{ mA}$$

6.22

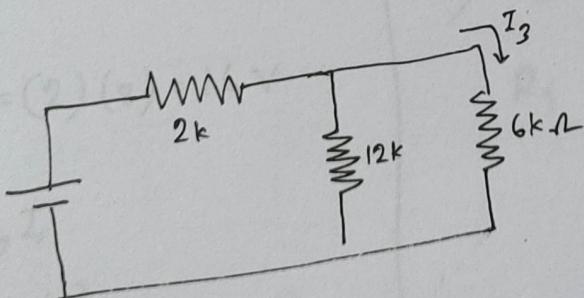
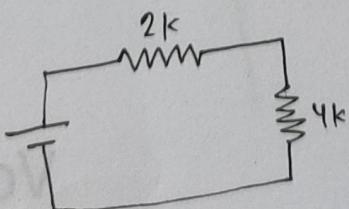
$$\left(\frac{1}{2} + \frac{1}{12} \right)^{-1} = 4\text{k}$$






$$\therefore I_T = \frac{54}{6} = 9 \text{ mA}$$

$$I_2 = \frac{I_T R_T}{R_2}$$

$$= \frac{9(4)}{6} = 6 \text{ mA}$$

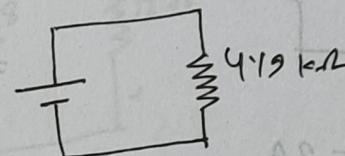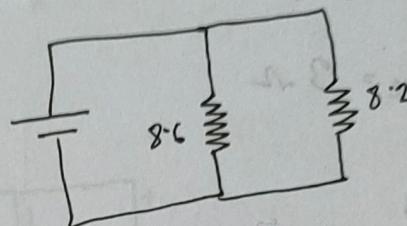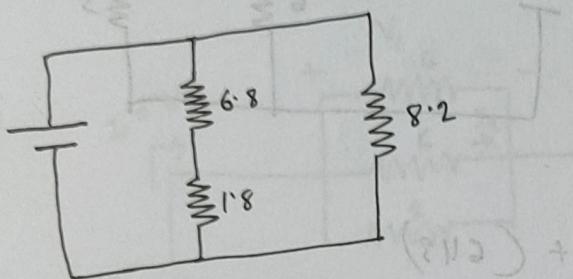7.2/

$$\left(\frac{1}{2} + \frac{1}{18}\right)^{-1} = 1.8$$



$$A.S = \frac{8.2}{22} = I \leftarrow$$

$$\therefore V = IR$$

$$I = \frac{V}{R} = \frac{12}{4.19} = 2.86 \text{ mA}$$

$$\frac{V+I}{22} = I$$

$$I_4 = \frac{I_T R_T}{R_4} = \frac{(2.86)(4.19)}{(8.2)} \quad [\text{From } 2^{\text{nd}} \text{ circuit}]$$

$$= 1.46 \text{ mA}$$

$$V_2 = 1.8 \times 1.4$$

$$= 2.52 \text{ V}$$

$$I_3 = \frac{V}{R} = \frac{12}{8} = 1.5 \text{ A}$$

$$I_4 = \frac{V}{R} = \frac{12.2}{8} = 2.4 \text{ A}$$

7.4/


$$R_A = \left(\frac{1}{6} + \frac{1}{9} \right)^{-1} = 3.6 \Omega$$

$$R_B = 4 + (6 \parallel 3)$$

$$= 4 + \left(\frac{1}{6} + \frac{1}{3} \right)^{-1}$$

$$= 6 \Omega$$

$$R_C = 3 \Omega$$


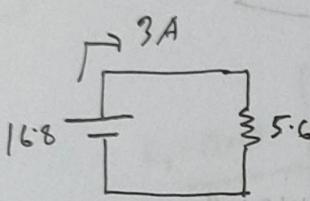


$$\Rightarrow I = \frac{16.8}{5.6} = 3A$$

$$= 3.6 + (6 \parallel 3)$$

$$= 3.6 + \left(\frac{1}{6} + \frac{1}{3} \right)^{-1}$$

$$= 5.6 \Omega$$

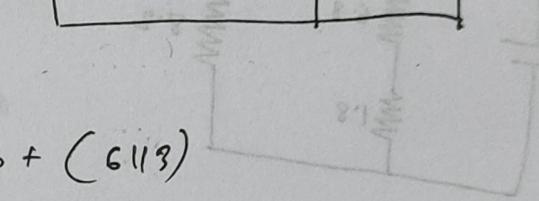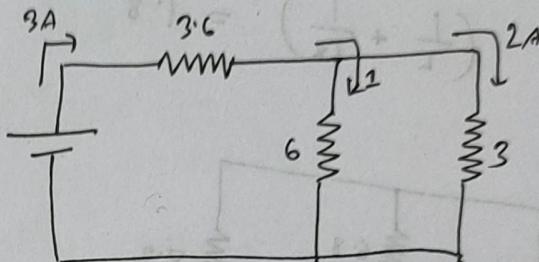

$$I_3 = \frac{I_T R_T}{R_3}$$

$$= \frac{3(2)}{(3)} = \frac{(0.6)(0.8)}{(0.8)} = \frac{0.48}{0.8} = 0.6$$

$$= 2A$$


A

A

$$P_1 \times 2.1 = V$$

$$V = 2.25$$

L-7 / 18.02.2023 /

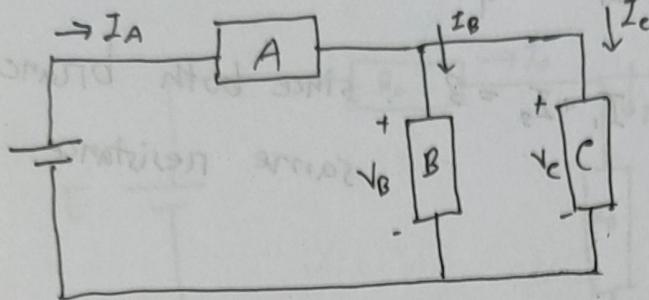


$$I_s = I_A$$

$$I_A = I_B + I_c$$


$$V_B = V_c$$

$$E = V_A + V_B$$

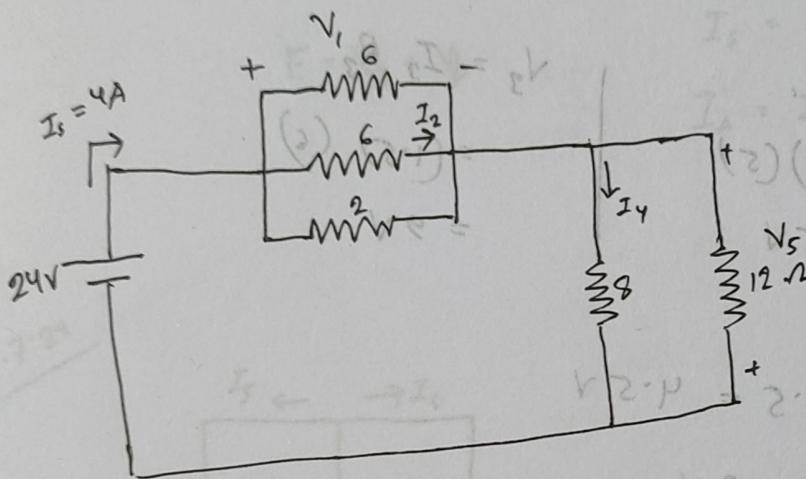

$$V_5 = \frac{24 - 5}{24} \times 24 = 3.33V$$

$$V_5 = 24 - 5 = 19.2V$$

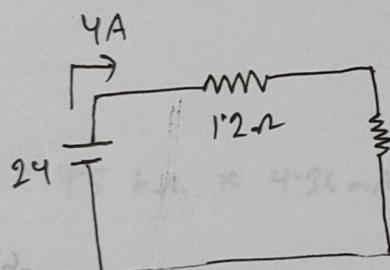


$$V_5 = \frac{4.8}{6} \times 24 = 19.2V$$

$$I_s = \frac{24}{6} = 4A$$

$$\therefore I_2 = \frac{I_s R'_T}{R_2} = \frac{4(1.2)}{6} = 0.8A$$

$$I_4 = \frac{V}{R} = \frac{19.2}{8} = 2.4A$$

(*)

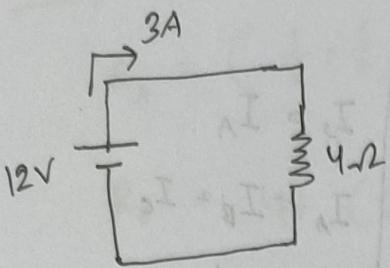

$$I_1 = \frac{12}{4} = 3A$$

$I_1 + I_2 = 3$: since both branches have same resistance.

$$I_1 = I_2$$

$$I_1 = 1.5A$$

$$V_1 = I_1 R_1$$

$$= (1.5)(5)$$

$$= 7.5V$$

$$V_3 = I_2 R_3$$

$$= (1.5)(6)$$

$$= 9V$$


$$\therefore V_a = 12 - 7.5 = 4.5V$$

$$\therefore V_b = 12 - 9 = 3V$$

$$\therefore V_{ab} = V_a - V_b$$



$$= 4.5 - 3$$

$$= 1.5V$$

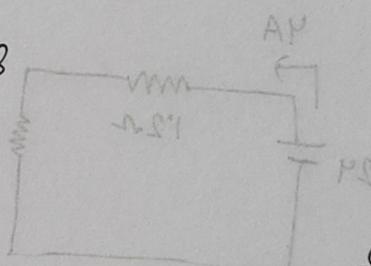


(*)

Figure- 7.22

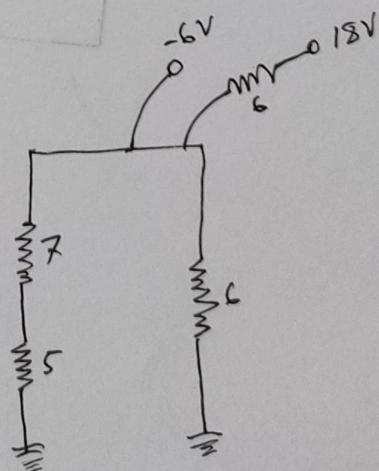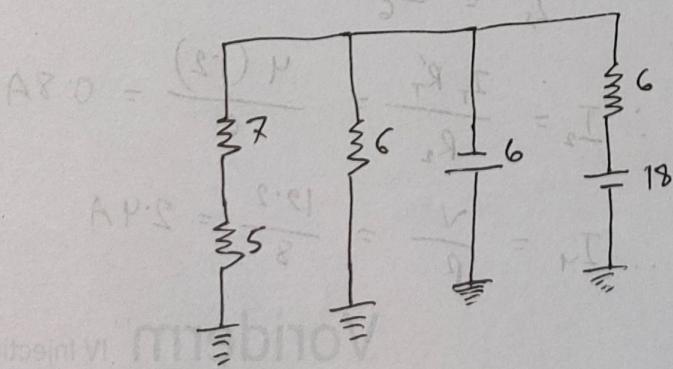

L-8 / 23.02.2023 /

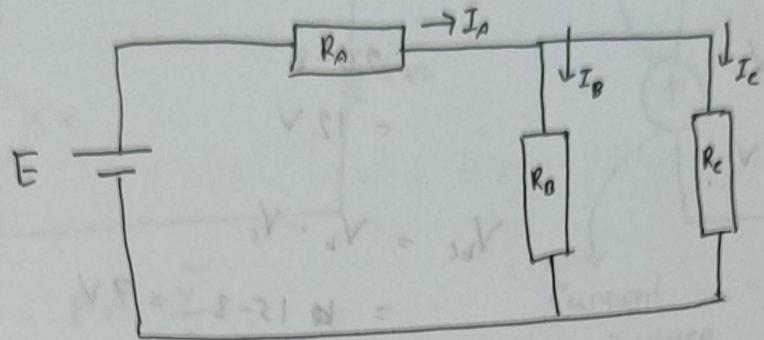


$$E = V_A + V_B$$

$$I_s = I_A$$

$$I_A = I_B + I_C$$



figure: 7.22

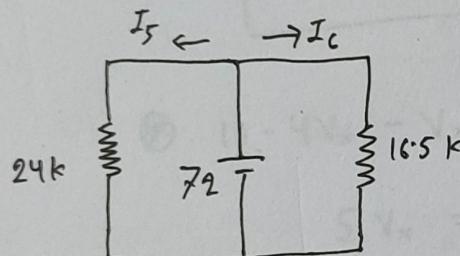


$$I_5 = \frac{72}{24k} = 3mA$$

$$I_C = \frac{72}{16.5k} = 4.36mA$$

$$I_s = 7.36mA$$

$$V_x = 4.5 \text{ k}\Omega \times 4.36mA$$

$$= 19.6V$$

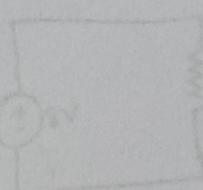

7.29

$$V_a = 20V$$

$$V_{ac} = V_a - V_c$$

$$V_c = 8V$$

$$= 20 - 8$$

$$V_b = 15V$$


$$= 12V$$

$$V_{bc} = V_b - V_c$$

$$= 15 - 8 = 7V$$

$$\text{Ansatz: } I_2 = \frac{V_{bc}}{R_2} = \frac{7}{4} = 1.75 A$$
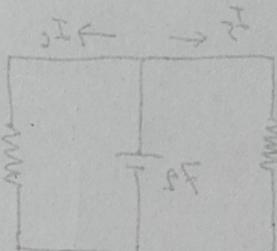
$$A_m \delta = \frac{\delta}{2\mu} = I^2$$






$$A_m \delta \cdot \mu = \frac{\delta}{2\mu} = I^2$$

$$A_m \delta \cdot \mu = I$$

$$A_m \delta \cdot \mu \times \mu \cdot \delta \cdot \mu = \delta V$$

$$V = 0.1 =$$

L-9 / 25.02.2023

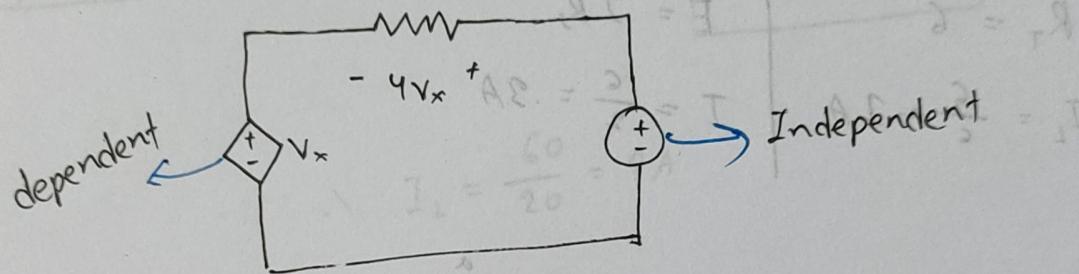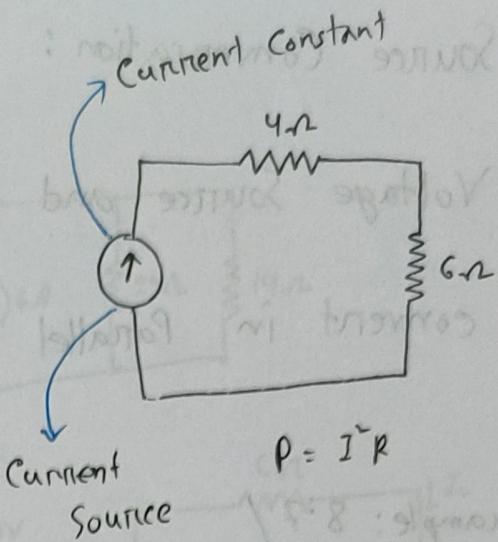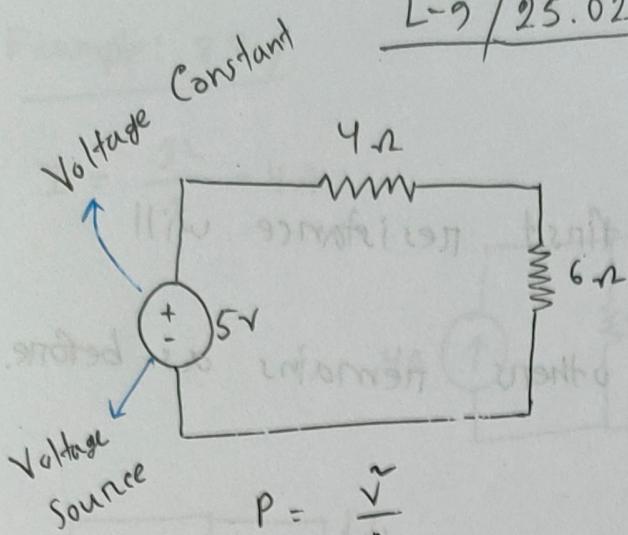


$$10 - 4V_x - V_x = 0$$

$$5V_x = 10$$

$$V_x = 2$$
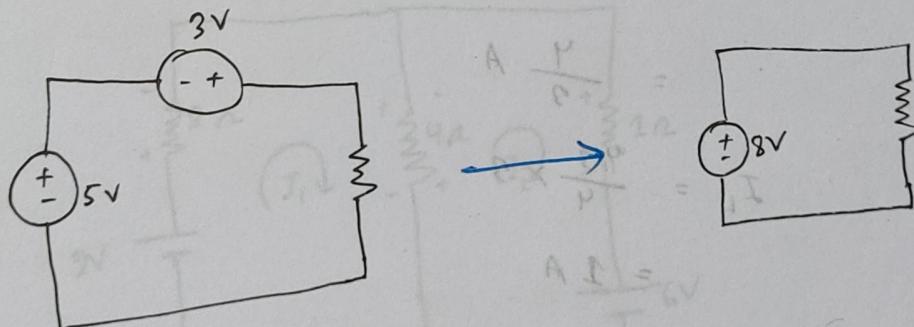
$$\left(\frac{1}{P} + \frac{1}{S} \right) = \frac{1}{T}$$



⊗ Source Conversion:

⊗ Voltage Source and the first resistance will convert in Parallel and others remains as before.


⊗ Example: 8.7 /

$$R_T = 6$$

$$I_L = \frac{6}{6} = 1 A$$




$$E = I R_s$$

$$I = \frac{6}{2} = 3 A$$

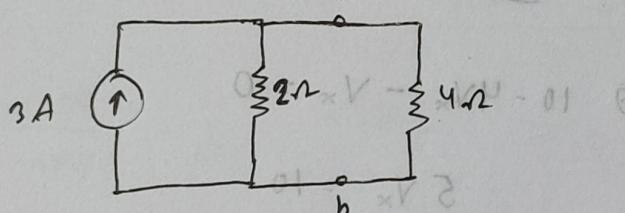



$$R_T = \left(\frac{1}{2} + \frac{1}{4} \right)^{-1}$$
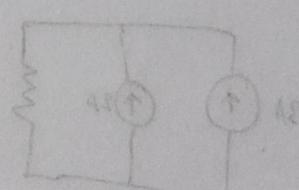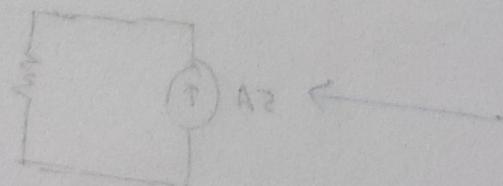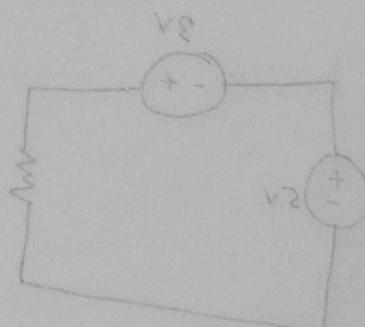
$$\begin{aligned} V_8 &= \frac{4}{3} A \\ I_L &= \frac{4/3}{4} \times 3 \\ &= 1 A \end{aligned}$$




Example: 89 /

$$I = \frac{32}{8} = 4A$$

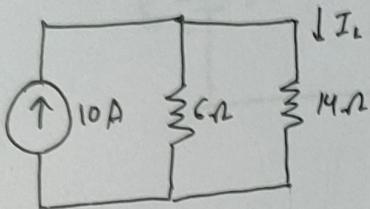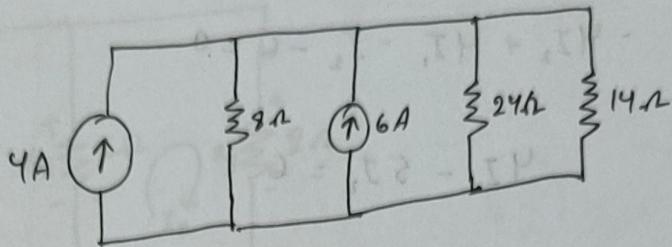


$$E = IR = 10 \cdot 6 = 60V$$

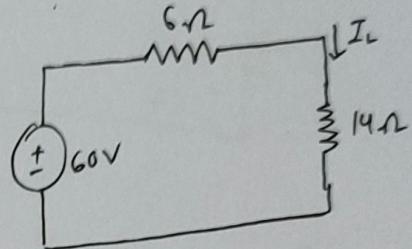

$$I_L = \frac{60}{20} = 3A$$

✖ Voltage Source cannot be in Parallel.

✖ Current Source cannot be in Series.

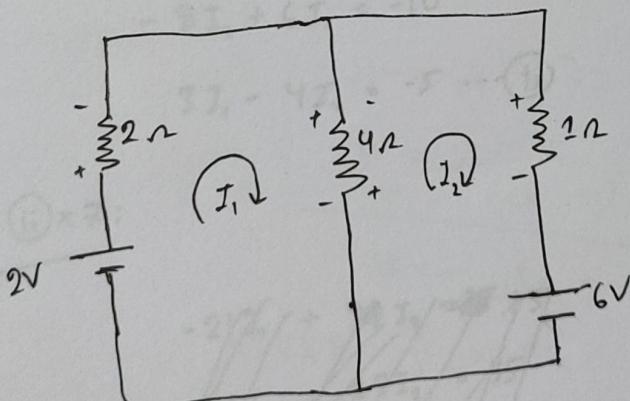

Loop-1!

$$2 - 2I_1 - 4(I_1 - I_2) = 0$$

$$2 - 6I_1 + 4I_2 = 0$$

$$3I_1 - 2I_2 = 2$$


Voriderm™ IV Injection
Voriconazole 200 mg

Loop-2:

$$-4(I_2 - I_1) - 2I_2 - 6V = 0$$

$$-4I_2 + 4I_1 - I_2 - 6 = 0$$

$$4I_1 - 5I_2 = 6$$

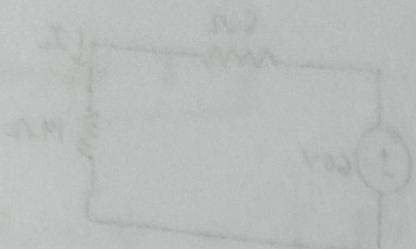


$$12V - 2 \cdot 0.1 = 8V = 8$$



$$A\Omega = \frac{0.2}{0.5} = 1$$

Current source cannot be in parallel

Current source cannot be in series

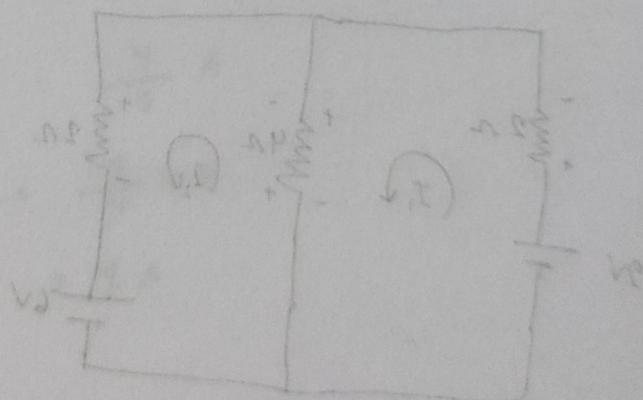


$$0 = (x - 1) \cdot 1 + 12 - 0$$

$$0 = 2P + 12 - 0$$

$$2P = 12 - 12$$

8.81/

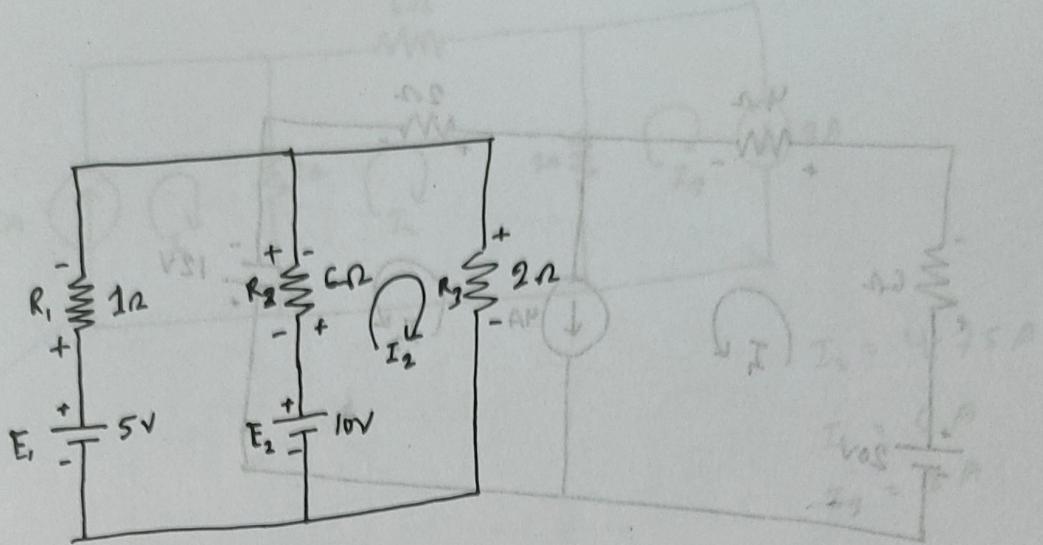

Loop 1:

$$5 - I_1 - 6(I_1 - I_2) - 10 = 0$$

$$-5 - I_1 - 6I_1 + 6I_2 = 0$$

$$-7I_1 + 6I_2 = 5 \quad \text{--- (i)}$$

Loop 2:

$$10 - 6(I_2 - I_1) - 2I_2 = 0$$

$$10 - 6I_2 + 6I_1 - 2I_2 = 0$$

$$-8I_2 + 6I_1 = -10$$

$$3I_1 - 4I_2 = -5 \quad \text{--- (ii)}$$

$$4 + I_2 = I_1$$

$$(i) \dots P = I_1 - I_2$$

(i) $\times 3 +$ (ii) $\times 7:$

$$\begin{aligned} -2I_1 + 4I_2 &= 15 \\ 21I_1 + 28I_2 &= 105 \end{aligned}$$

$$-21I_1 + 18I_2 = 15$$


$$21I_1 - 28I_2 = -35$$

$$-10I_2 = -20$$

$$\therefore I_2 = 2 \text{ A}$$

$$\therefore I_1 = \frac{-5 + 8}{3} = 1 \text{ A}$$

8.33

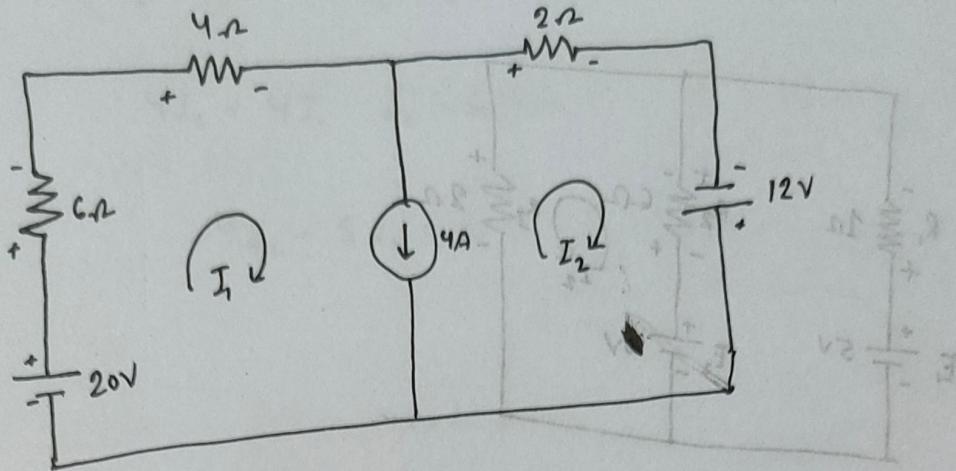Without $\textcircled{4A}$:

$$20 - 6I_1 - 4I_1 - 2I_2 + 12 = 0$$

$$\begin{aligned} -10I_1 - 2I_2 &= -32 \\ -5I_1 - I_2 &= -16 \quad \dots \textcircled{1} \end{aligned}$$

$$I_1 = I_2 + 4$$

$$I_1 - I_2 = 4 \quad \dots \textcircled{ii}$$

$$0 = 2I_2 - 2I_1 - 0 \quad \textcircled{0}$$

$$0 = 2I_2 + 2I_1 - 0 \quad \textcircled{0}$$

$$0 = I_2 + 2I_1 - 0$$

$$-5I_1 - I_2 = -16$$

$$\begin{array}{rcl} I_1 - I_2 & = & 4 \\ (-) & (+) & (-) \\ \hline -6I_1 & = & -20 \end{array}$$


$$8 \times \textcircled{ii} + 6 \times \textcircled{1}$$

$$I_1 = \frac{20}{6} = 3.33 \text{ A}$$

$$I_2 = 3.33 - 4 = -0.67 \text{ A}$$

$$A \text{ } \underline{I} = \frac{8 + 2}{8} = I$$

8:35/

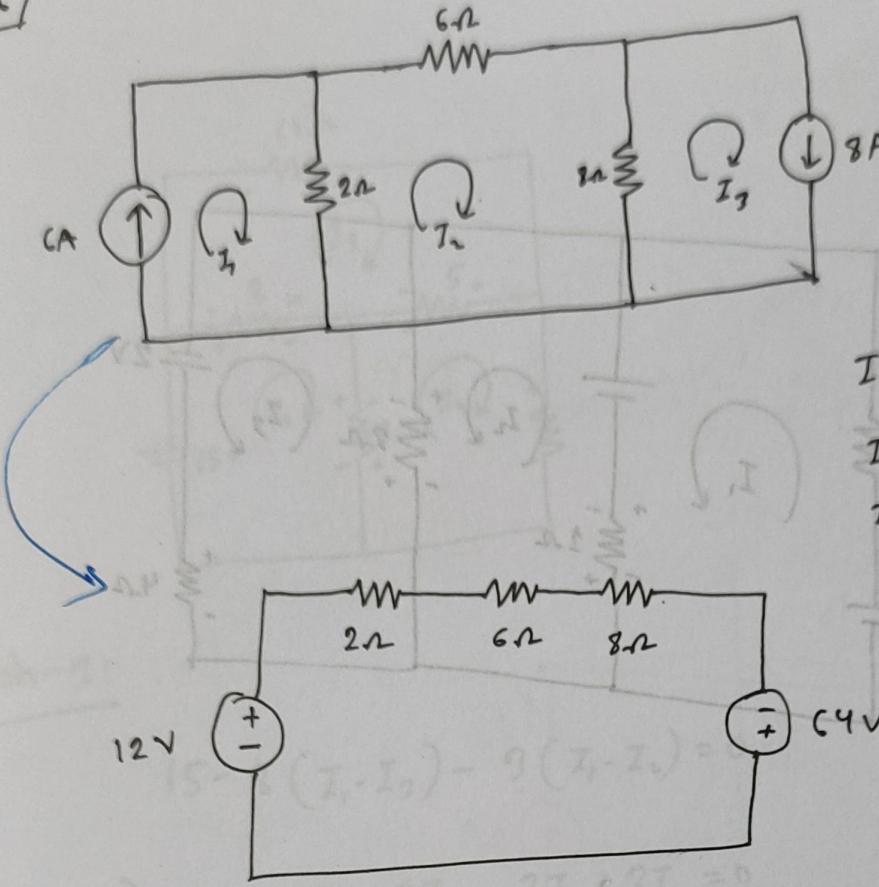

$$I_2 = 4.75 \text{ A}$$

$$I_1 = 6 \text{ A}$$

$$I_3 = 8 \text{ A}$$

$$\Rightarrow 15I_1 + 8I_2 - 3I_3 = (3I_1 - I_2) - 4 - 8 - 2$$

$$I = \frac{7c}{1c} = 4.75 \text{ A}$$

$$-11I_1 + 2I_2 + 8I_3 = 15I_1 + 8I_2 - 2$$

Mesh 1:

$$0 = (I_1 - I_2)3 - 2I_2 - (I_1 - I_2)3 - 4 - 8 - 2$$

$$\Rightarrow -3I_1 + 2I_2 - 5I_3 + 5I_2 - 2I_1 - I_2 = 0$$

$$-3I_1 + 10I_2 + 5I_3 = 0$$


$$0 = (I_1 - I_2)3 - 2I_2 - (I_1 - I_2)3 - 4 - 8 - 2$$

$$-10I_1 + 4(I_2 + I_3) - 5(I_2 - I_1) = 0$$

$$5 = 5I_2 - 5I_1$$

$$\Rightarrow -10I_1 + 9I_2 + 3I_3 - 5I_2 + 5I_1 = 0$$

8.41/

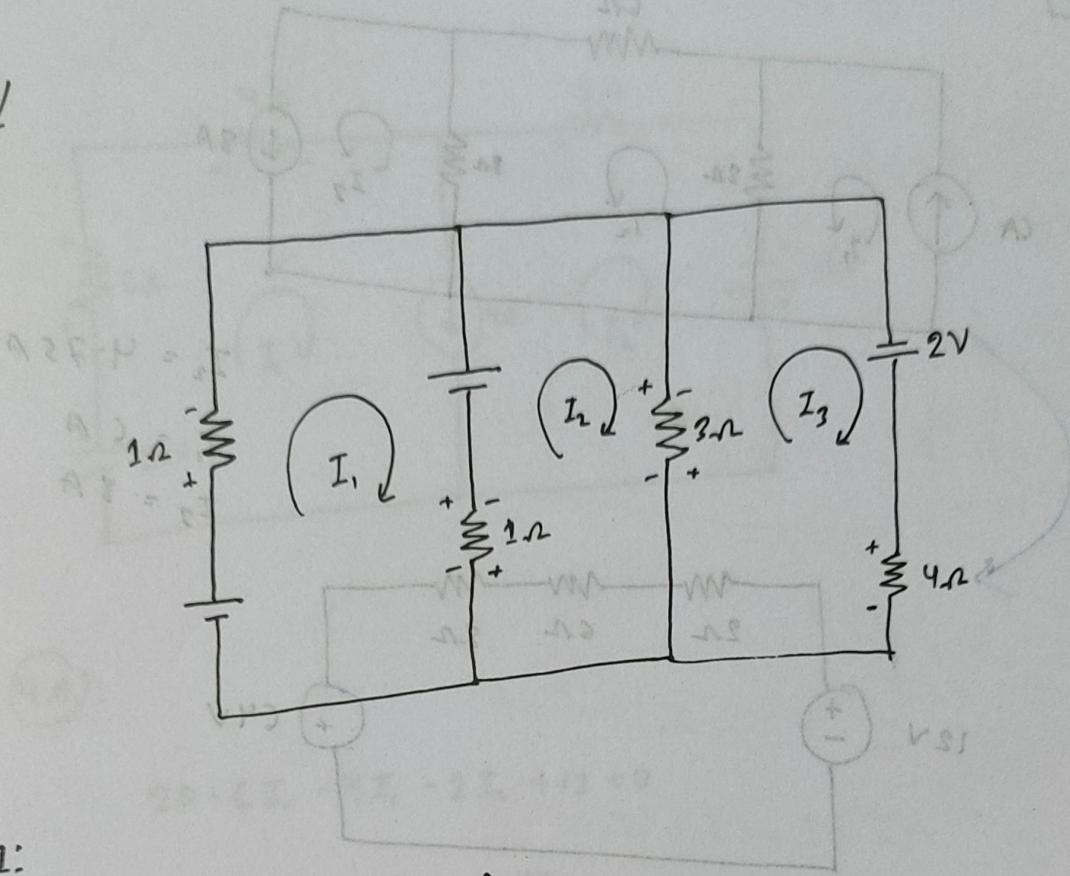

Mesh-1:

$$2 - I_1 - 4 - (I_1 - I_2) = 0$$

$$\Rightarrow -2I_1 + I_2 = 2$$

Mesh-2:

$$4 - 3(I_2 - I_3) - (I_2 - I_1) - 2I_2 = 0$$


$$\Rightarrow I_1 - 6I_2 + 3I_3 = -4$$

Mesh-3:

$$2 - 4I_3 - 3(I_3 - I_2) = 0$$

$$\Rightarrow 3I_2 - 7I_3 = -2$$

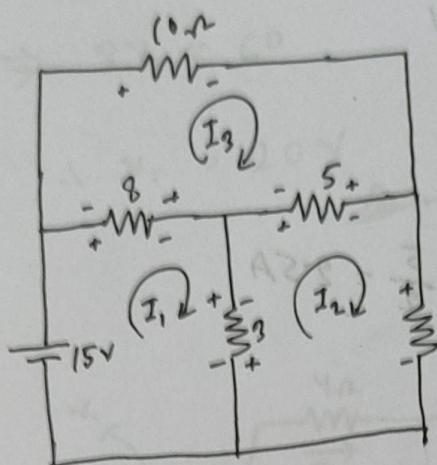\therefore Now we can use Crammer's Rule for solving this equation.



Mesh-1:

$$15 - 8(I_1 - I_3) - 3(I_1 - I_2) = 0$$

$$\Rightarrow 15 - 8I_1 + 8I_3 - 3I_1 + 3I_2 = 0$$

$$\therefore -11I_1 + 3I_2 + 8I_3 = -15 \quad \dots \text{(i)}$$

Mesh-2:

$$-3(I_2 - I_1) - 5(I_2 - I_3) - 2I_2 = 0$$

$$\Rightarrow -3I_2 + 3I_1 - 5I_2 + 5I_3 - 2I_2 = 0$$

$$\therefore 3I_1 - 10I_2 + 5I_3 = 0 \quad \dots \text{(ii)}$$


Mesh-3:

$$-10I_3 - 8(I_3 - I_1) - 5(I_3 - I_2) = 0$$

$$\Rightarrow -10I_3 - 8I_3 + 8I_1 - 5I_3 + 5I_2 = 0$$



$$\therefore 8I_1 + 5I_2 - 23I_3 = 0$$
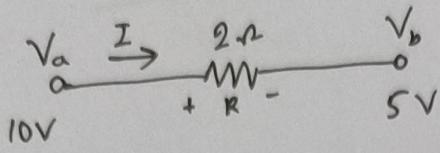
$$\begin{cases} I_1 = 2.63 \text{ A} \\ I_2 = 1.40 \text{ A} \\ I_3 = 1.22 \text{ A} \end{cases}$$



$$\therefore V_{ab} = 10 - 5 = 5 \text{ V}$$
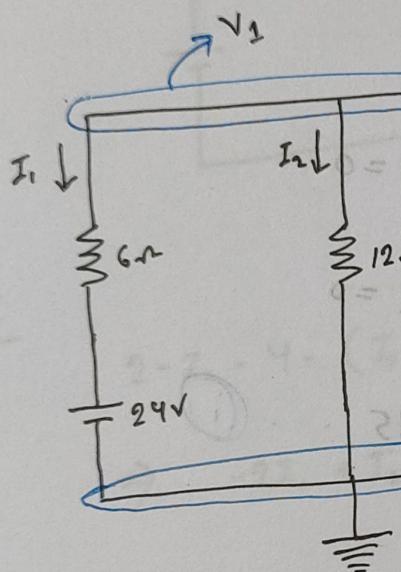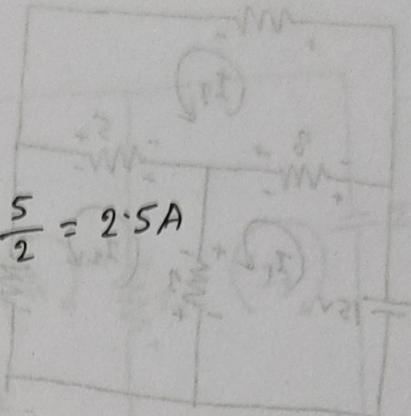
$$\therefore I = \frac{V_{ab}}{R} = \frac{5}{2} = 2.5 \text{ A}$$



Hence,

$$V_{Gn} = V_1 - 24$$

$$\therefore I_1 = \frac{V_1 - 24}{6}$$

$$\therefore I_2 = \frac{V_1 - 0}{12} = \frac{V_1}{12}$$

$\therefore \text{In node } - V_1 :$


$$I = I_1 + I_2$$

$$I = \frac{V_1 - 24}{6} + \frac{V_1}{12}$$

$$\Rightarrow I_2 = 2V_1 - 48 + V_1$$

$$\Rightarrow 3V_1 = 60$$

$$\therefore V_1 = 20V$$

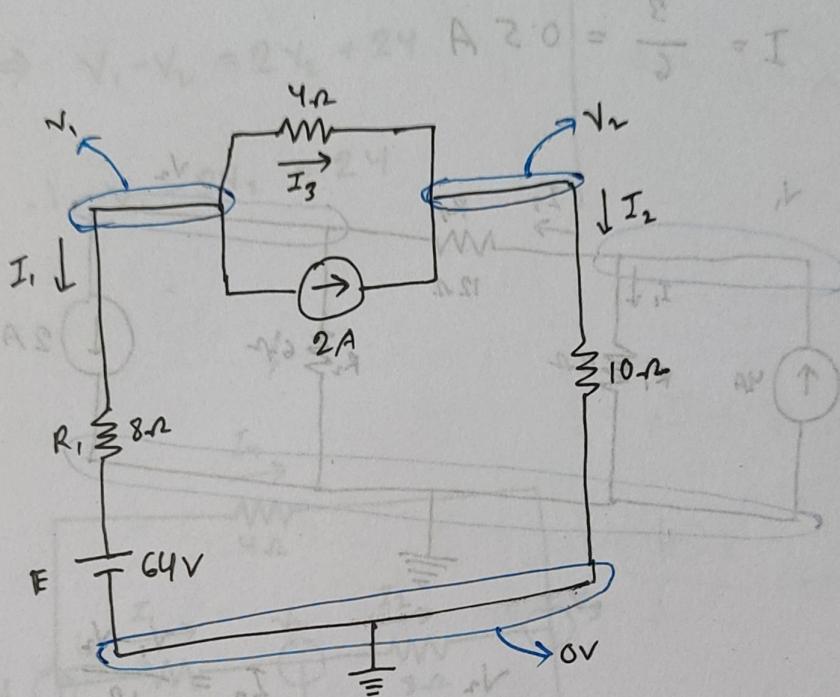

$$I_1 = \frac{V_1 - 64}{8}$$

$$I_2 = \frac{V_2}{10}$$

$$I_3 = \frac{V_1 - V_2}{4}$$

Node-1:

$$I_1 + I_3 + 2 = 0$$

$$\Rightarrow \frac{V_1 - 64}{8} + \frac{V_1 - V_2}{4} + 2 = 0$$

$$\Rightarrow V_1 - 64 + 2V_1 - 2V_2 + 16 = 0$$

$$\therefore 3V_1 - 2V_2 = 48 \dots (i)$$

Node-2:

$$I_3 + 2 = I_2$$

$$\frac{V_1 - V_2}{4} + 2 = \frac{V_2}{10}$$

$$\frac{V_1 - V_2 + 8}{4} = \frac{V_2}{10}$$


$$10V_1 - 10V_2 + 80 = 4V_2$$

$$\therefore 10V_1 - 14V_2 = -80 \dots (ii)$$


Voriderm™ IV Injection
Voriconazole 200 mg

(i) $\times 10$ - (ii) $\times 3$ then substitute.

L-13 / 11.03.2023 /

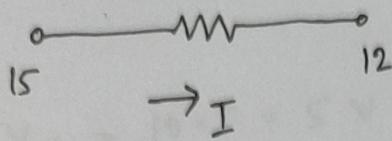

$$I = \frac{3}{6} = 0.5 \text{ A}$$

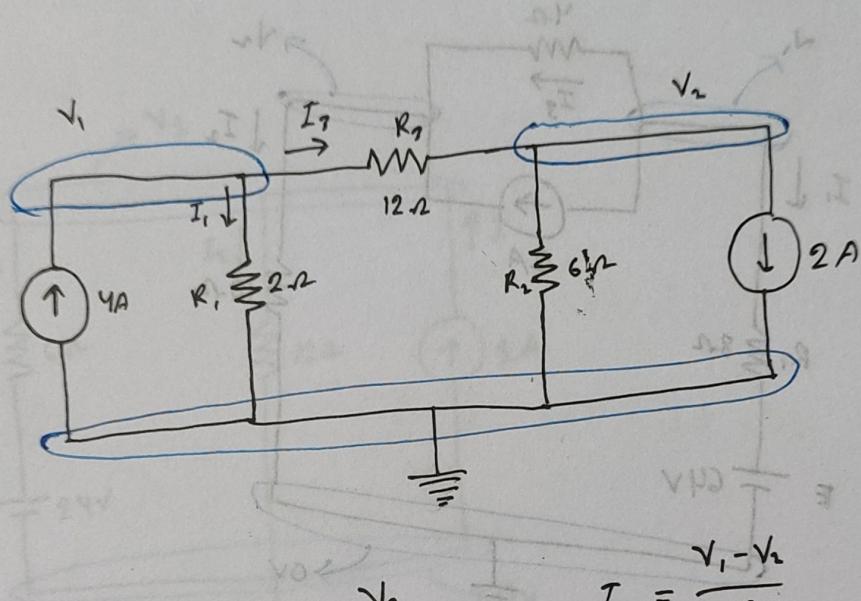

$$I_1 = \frac{V_1}{2}$$

$$I_2 = \frac{V_2}{6}$$

$$I_3 = \frac{V_1 - V_2}{12}$$

at node-1:

$$4 = I_1 + I_2$$

$$\Rightarrow 4 = \frac{V_1}{2} + \frac{V_2}{12}$$

$$\Rightarrow V_1 - V_2 + 6V_1 = 48$$

$$7V_1 - V_2 = 48$$

$$0 = I_2 + I_3$$

$$0 = \frac{V_2}{6} + \frac{V_1 - V_2}{12}$$

$$0 = 2I + V_2 - V_1 + V_2 - V$$

at node-2:

$$I_3 = I_2 + 2$$

$$\Rightarrow \frac{V_1 - V_2}{12} = \frac{V_2}{6} + 2$$

$$\Rightarrow V_1 - V_2 = 2V_2 + 24$$


$$\Rightarrow V_1 - 2V_2 = 24$$

$$V_1 = 6 \text{ V} + \frac{V_2 - V_1}{12} = 8 \text{ V}$$

$$V_2 = -6 \text{ V}$$

$$R_1 R_2 + R_2 R_3 + R_1 R_3$$

$$R_1 R_2$$

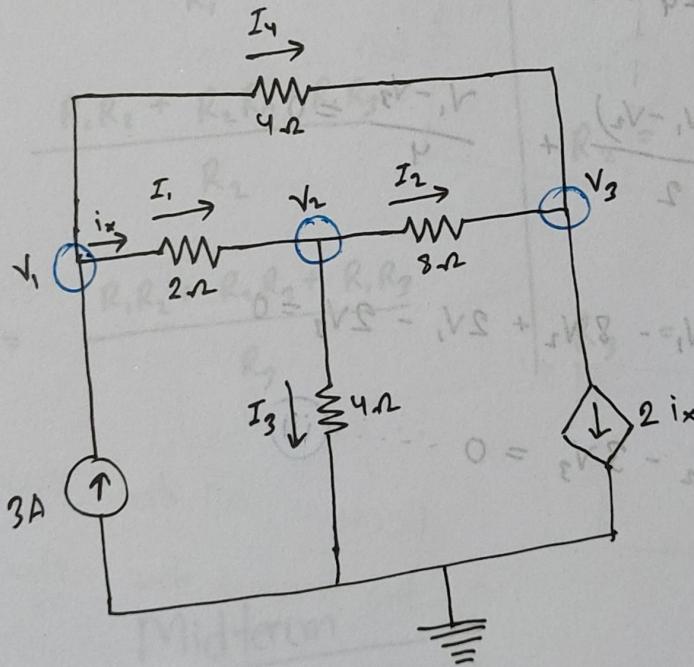

$$I_1 = \frac{V_1 - V_2}{2}$$

$$I_2 = \frac{V_2 - V_3}{8}$$

$$I_3 = \frac{V_2}{4}$$

$$I_4 = \frac{V_1 - V_2}{4}$$

$$i_x = \frac{V_1 - V_2}{2}$$

Node-1:

$$3 = I_1 + I_4$$

$$\Rightarrow 3 = \frac{V_1 - V_2}{2} + \frac{V_1 - V_3}{4}$$

$$\Rightarrow I_2 = 2V_1 - 2V_2 + V_1 - V_3$$

$$\therefore 3V_1 - 2V_2 - V_3 = 12 \quad \text{.....(i)}$$

Node-2:

$$I_1 = I_2 + I_3$$

$$\Rightarrow \frac{V_1 - V_2}{2} = \frac{V_2 - V_3}{8} + \frac{V_2}{4}$$


$$\Rightarrow 4V_1 - 4V_2 = V_2 - V_3 + 2V_2$$

$$\therefore 4V_1 - 7V_2 + V_3 = 0 \quad \text{.....(ii)}$$

$$PS = V_2 - V_1$$

Node-3:

$$I_2 + 2i_x + I_4 = 0$$

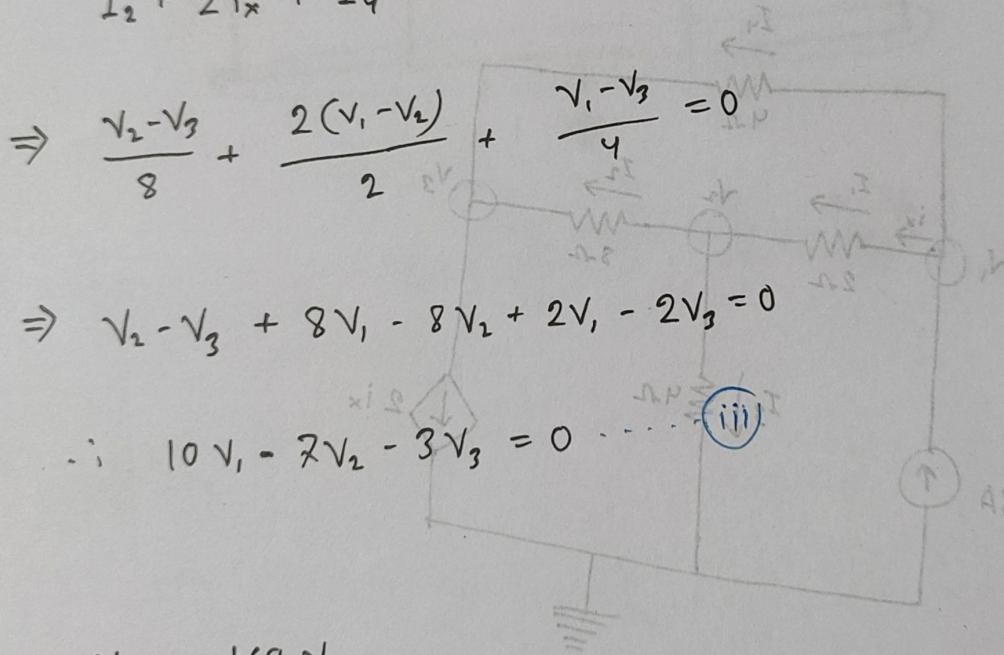

$$\therefore V_1 = -168 \text{ V}$$

$$V_2 = -132 \text{ V}$$

$$V_3 = -252 \text{ V}$$

$$\frac{V_1 - V_2}{2} = I$$


$$\frac{V_1 - V_3}{4} = i_x$$

$$\frac{V_1 - V_3}{8} = I$$

$$\frac{V_1 - V_2}{8} = i_x$$

$$\frac{V_1 - V_2}{2} = I$$

(*)

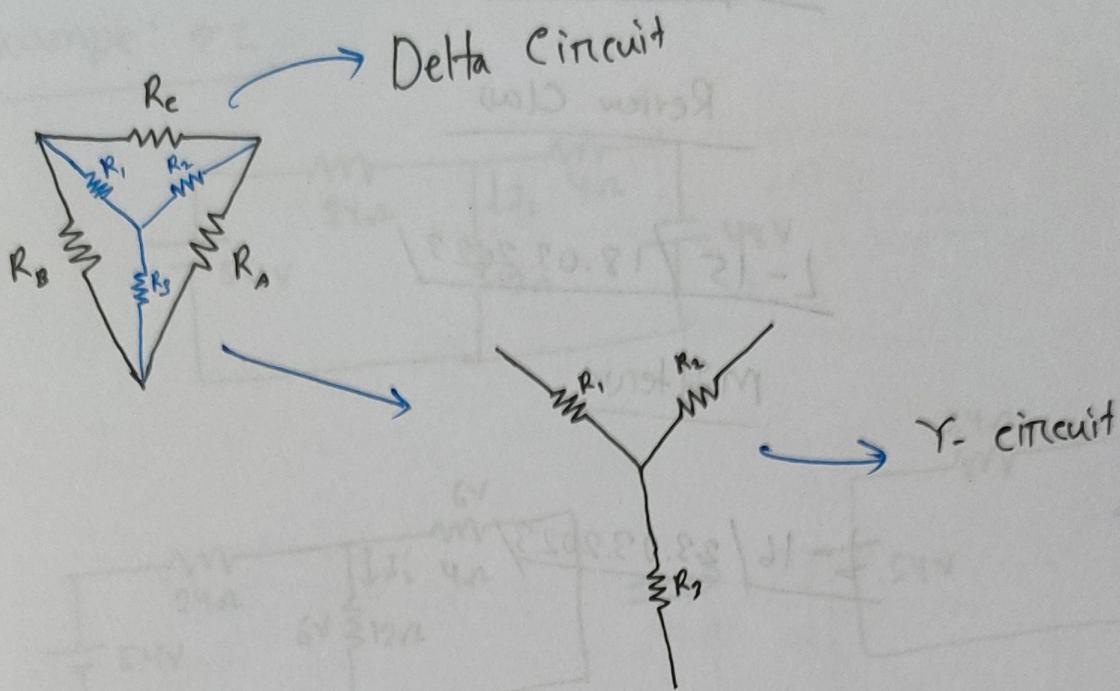

Hence,

$$R_A = \frac{R_1 R_2 + R_2 R_3 + R_1 R_3}{R_1}$$

$$R_B = \frac{R_1 R_2 + R_2 R_3 + R_1 R_3}{R_2}$$

$$R_C = \frac{R_1 R_2 + R_2 R_3 + R_1 R_3}{R_3}$$

$$R_1 = \frac{R_B R_C}{R_A + R_B + R_C}$$

$$R_2 = \frac{R_A R_C}{R_A + R_B + R_C}$$

$$R_3 = \frac{R_A R_B}{R_A + R_B + R_C}$$

Midterm

1. Quiz - 1

2. Quiz - 2

3. Node Analysis

4. Mesh Analysis