

CSE 331 / L-20 / 02.05.2024 /

ZC 138  $\Rightarrow$  D-MUX for interfacing RAM


Enable Pin  $\left\{ \begin{array}{l} A1 \Rightarrow 1 \\ \overline{A2A} \Rightarrow 0 \\ \overline{A2B} \Rightarrow 0 \end{array} \right\}$  Normal operation  
or  
mux is active

~~A B C~~      C B A  
                  MSB      LSB

PLA  $\Rightarrow$  Programmable Logic Array


EPROM  $\Rightarrow$  4x - each size 4k x 8
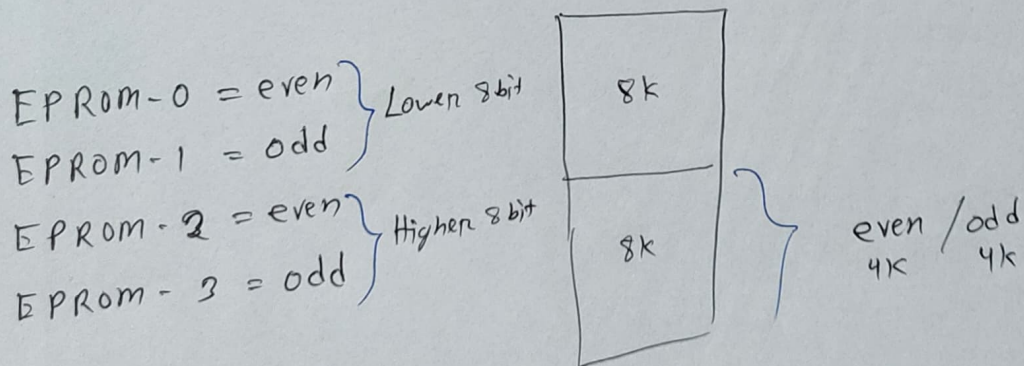
$$\text{total size} = \frac{4k \times 4}{16k \times 8}$$




$A_0$  used for even or odd.

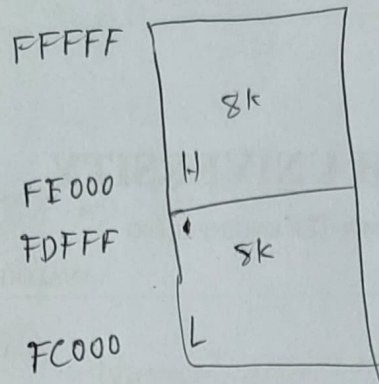Rom = Read only memory  $\Rightarrow$   $\overline{OE}$  = output Enable  
 $\overline{CE}$  = chip Enable



$A_0 - A_{12} \Rightarrow$  Already used

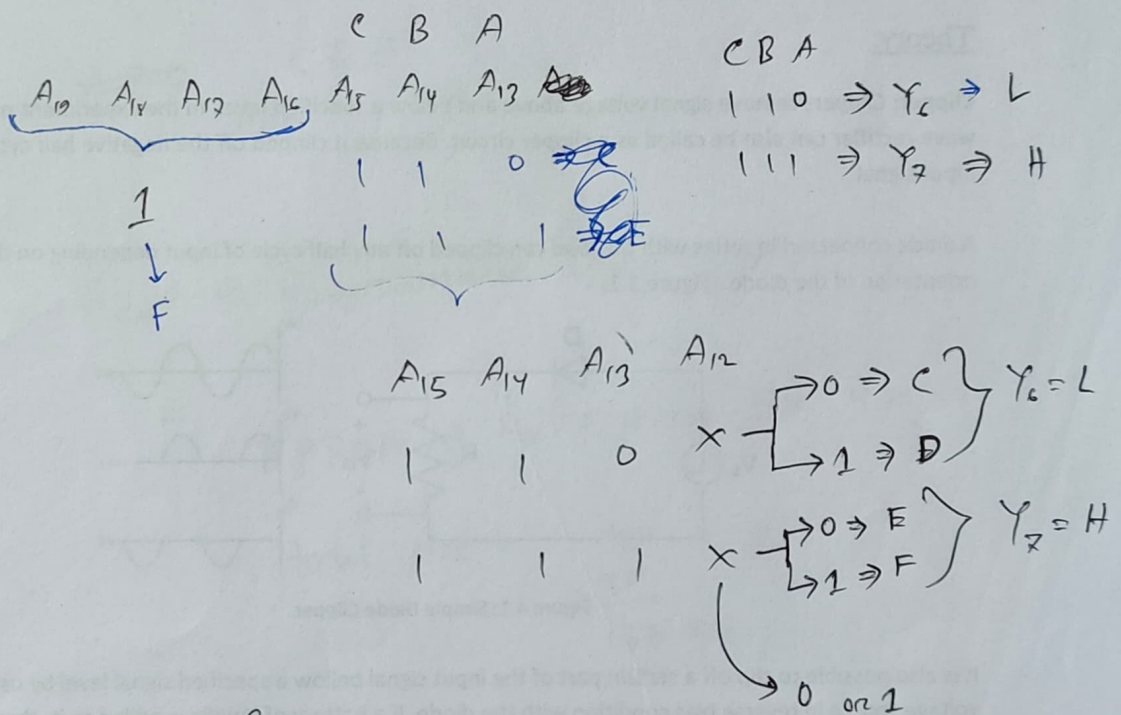

⊗ Configure Given, find out the address limit or according to address limit configure the circuit.

Configuration may change in mux output or mux enable and input pin.



PLA  $\Rightarrow$  16 LA

Fun LED,

0 = on

1 = off

Dot = Fixed

Cross = Programmable

PROM  $\Rightarrow$  AND fixed

OR Programmable

PAL  $\Rightarrow$  AND Programmable

OR fixed

PLA  $\Rightarrow$  Both Programmable  $\Rightarrow$  No Limitation


~~\*~~

L-21 / 04.05.2024 /


Midterm Exam

⊗ DAC  $\Rightarrow$  Digital to Analogue Converter.



⊗ R-2R Ladder Circuit

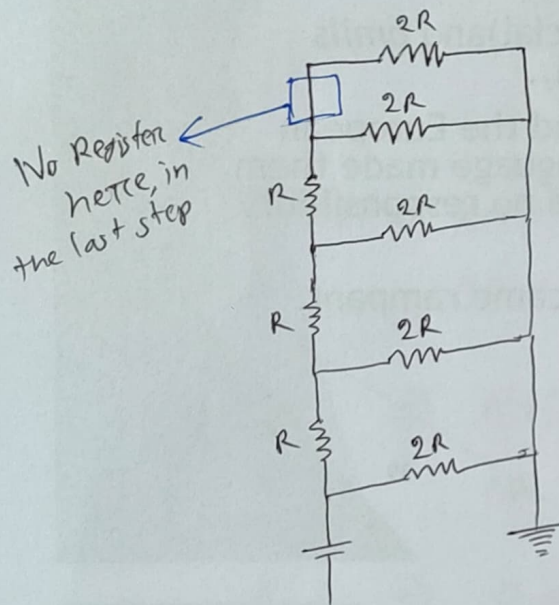

Looks Like a Ladder

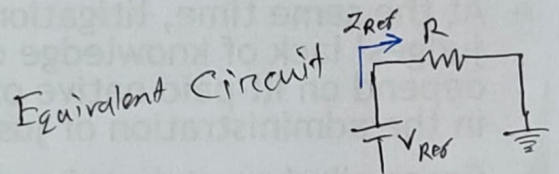

⊗ DAC

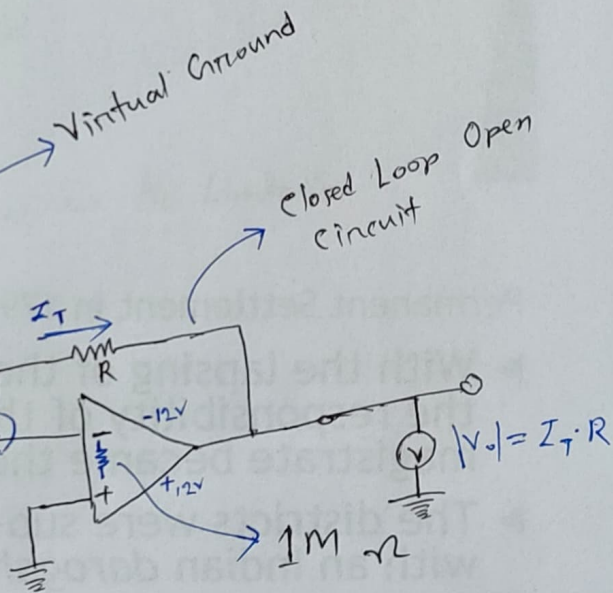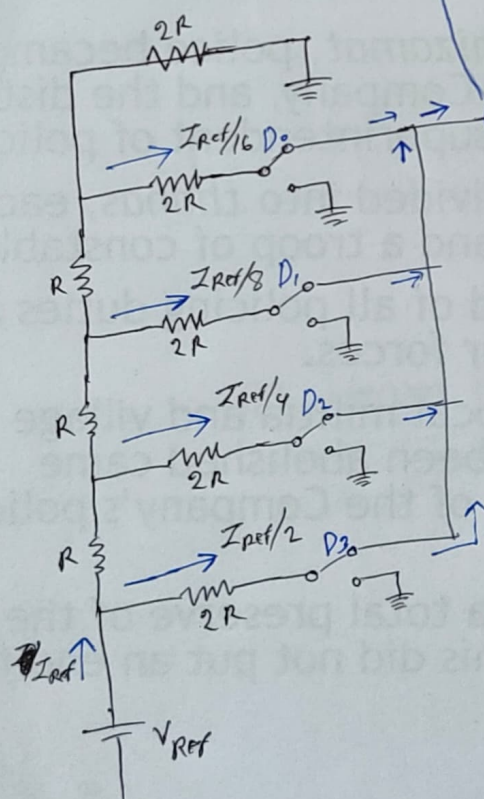

$$I_{ref} = \frac{V_{ref}}{R}$$



⊕ Lets say, Digital Input, total 4x  
 $D_3 = D_2 = D_1 = D_0 = 1 \Rightarrow$  means switch is on

Then,

$$I_T = \frac{I_{ref}}{2} + \frac{I_{ref}}{4} + \frac{I_{ref}}{8} + \frac{I_{ref}}{16}$$

$$= \frac{I_{ref}}{16} (8 + 4 + 2 + 1)$$

$$= \frac{V_{ref}}{R \times 16} (8 + 4 + 2 + 1)$$

$$= \frac{V_{ref}}{R \cdot 2^4} (8 + 4 + 2 + 1)$$

Number of digital input,  $n$

then,  $\frac{V_{ref}}{R \cdot 2^n} \left( \frac{\text{total } n}{\text{numbers}} \right)$

$\Rightarrow$  We can extend or reduce as our wish.

Now,

$$V_d = I_T \cdot R'$$

$$= \frac{V_{ref} \cdot R'}{R \cdot 2^4} (8 + 4 + 2 + 1)$$

For,

$$\begin{matrix} D_3 & D_2 & D_1 & D_0 \\ 1 & 1 & 1 & 1 \end{matrix} \Rightarrow |V_o| = \frac{V_{ref}}{2^4} \cdot \frac{R'}{R} (15)$$

$$0000 \Rightarrow |V_o| = 0$$

$$0001 \Rightarrow |V_o| = \frac{V_{ref}}{2^4} \cdot \frac{R'}{R} (1) \Rightarrow \text{Step Size Volt} = 1V$$


$\Rightarrow$  Possible when  $R' = R$

$$V_{ref} = 16V$$

$\Rightarrow$  if  $V_{ref}$  is fixed then we can adjust  $R'$  &  $R$  to make it 1V.

So we learn, how to set step up voltage by manipulating the circuit. But in our internal system we can easily do it by changing our Assembly Code.

Question Pattern:

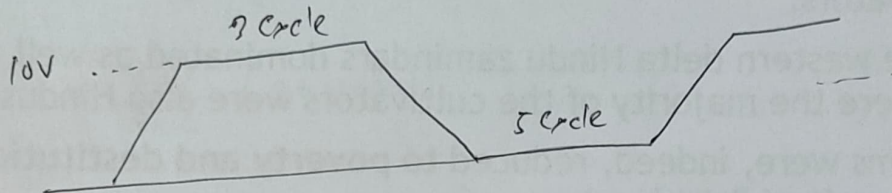

Write down the code. Use step up voltage as IV.  
⇒ some changes and hint  
L1:

```
cmp AL, 0AH
```

```
jnl L2
```

L2:

```
mov cx, 3
```

delay by running a loop

P=22

L3: decreasing part.

L4: again delay

~~L5~~ ~~JMP~~ L1.





Slide - Page - 22


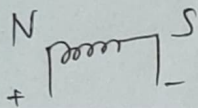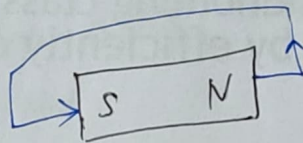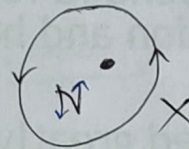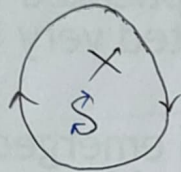
# ⊗ Stepper Motor

Here step size =  $20^\circ$

in reality, =  $1.8^\circ$  or close to  $1^\circ$




⊗ 3-8

for clock-wise = ROL


for anti-clock-wise = ROR

initial value  $\Rightarrow$

$S_4$	$S_3$	$S_2$	$S_1$
0	0	1	1

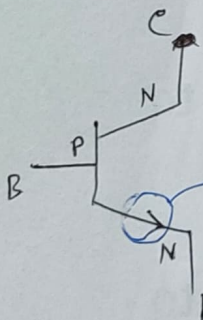

forward bias 0.7V need

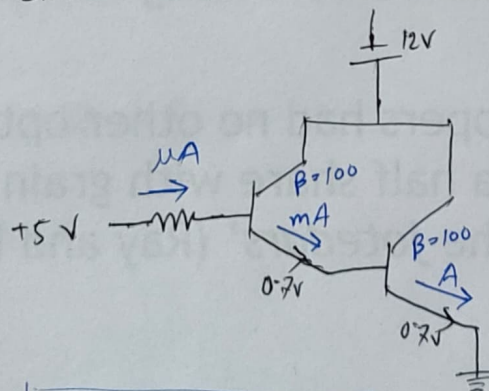

Quiz-2

Upto this

+ make-up exam

Nent 18.05.2024

Online class