

15.5  
15  
✓ good.



405

# NORTH SOUTH UNIVERSITY

Department of Mathematics & Physics

Experimental Physics

PHY-108L

Name of the Experiment: Induced EMF and Mutual Inductance

Name: Joy kumar Ghosh

ID: 2211424642

Serial No: 4

Group Member's Name: (i) Soykot Islam  
(ii)

ID: 2013928642

ID:

Group Number: E

Date: (i) Experiment Performed: 27.09.2023

(ii) Report Submitted: 03.04.2023

---

Plot #15, Block # B, Bashundhara, Dhaka-1229, Bangladesh

Phone: +88 2 55668200, Fax: +88 2 55668202, Web: [www.northsouth.edu](http://www.northsouth.edu)

## Experiment Name: Induced EMF and Mutual Inductance.

### Objective:

- To verify the concept of induced EMF.
- To calculate the turns-ratio of a transformer
- To verify the effect of frequency on a transformer.

### Apparatus:

- Transformer
- Function Generator
- Oscilloscope
- Wires

### Theory:

If two inductors are placed in the vicinity of each other, an induced EMF appears in one coil if the current is changed in the other coil. It obeys Faraday's law of induction and is given by the formula

$$E_L = -L \frac{di}{dt}$$



A transformer is a widely used device that works on the principle of mutual induction. It consists of two coils with different number of turns wound around an iron core. The primary winding of  $N_p$  turns is connected to an alternating current generator whose EMF at any time  $t$  is given by

$$E = E_m \sin \omega t$$

This sinusoidally changing primary current produces a sinusoidally changing magnetic flux in the iron core. The core acts to strengthen the flux and to bring it through the secondary winding. As the flux varies, it induces an EMF in each turn of the secondary. In fact, this EMF per turn  $E_{\text{turn}}$  is the same in the primary and the secondary.

Across the primary, the voltage  $V_p$  is the product of  $E_{\text{turn}}$  and the number of turns in the primary,


$$N_p.$$

$$V_p = E_{\text{turn}} \cdot N_p$$

Similarly, for the secondary side,  $V_s = E_{\text{turn}} \cdot N_s$

Thus, we can write,  $E_{\text{turn}} = \frac{V_p}{N_p} = \frac{V_s}{N_s}$

### Circuit Diagram:

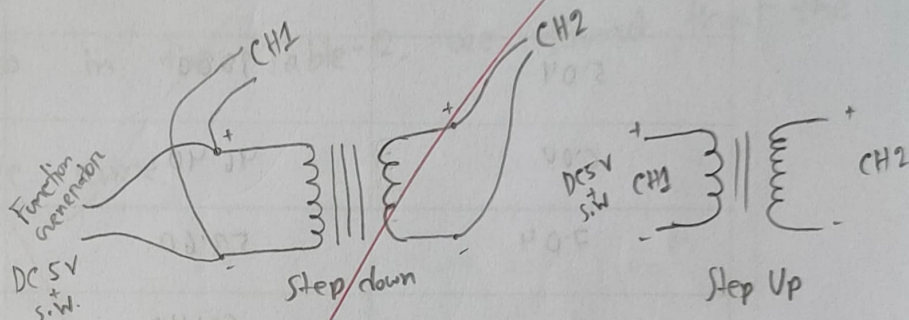

### Data Table:

Table-1:

Primary Voltage $V_p(\text{p-p})$ (V)	Secondary Voltage $V_s(\text{p-p})$ (mV)	$\frac{V_p(\text{p-p})}{V_s(\text{p-p})}$
1.04	128	8.125
2.08	248	8.387
3.04	368	8.261
4.08	488	8.361
5.04	600	8.400
6.00	728	8.242
7.04	848	8.302
8.0	968	8.264



Table-2:

Secondary Voltage $V_s$ (p-p) (V)	Primary Voltage $V_p$ (p-p) (V)	$\frac{V_p(p-p)}{V_s(p-p)}$
1.02	8.00	7.847
2.0	17.60	8.800
3.04	23.60	7.763
4.00	30.40	7.600
5.04	38.00	7.540
6.00	46.40	7.733
7.04	53.60	7.614
8.00	60.40	7.550

Table-1:

Primary Voltage $V_p$ (p-p) (V)	Secondary Voltage $V_s$ (p-p) (V)	$\frac{V_p(p-p)}{V_s(p-p)}$
1.04	8.00	7.692
2.08	17.60	8.462
3.12	23.60	7.564
4.16	30.40	7.308
5.20	38.00	7.308
6.24	46.40	7.436
7.28	53.60	7.363
8.32	60.40	7.259

Graph: N/A

Results: After completing this experiment, we construct two table. From Table-1, we found that, for each primary voltage the ratio of  $V_p$  and  $V_s$  are the same. Also in the Table-2, we found that the ratio are same.

### Questions & Answers:

Q1.

In part 1, we connect a transformer's primary side with a DC power supply, and the secondary part connected with the Oscilloscope. As DC power supply is constant we don't found any Induced EMF. But when we turn the switch ~~turn~~ on and off we found a little peak of EMF. That means we need changing current for EMF. When we use the Sineoidal wave, then we found the EMF. For input voltage of 1.04V we found 128 mV. ~~And~~ That means ~~we~~ the transformer



Q2. is ~~now~~ in step down transformer. At the  
ratio is on average 8.

Q2.

In the number of turns in the primary side of  
the transformer is reduced, the amplitude of the  
induced voltage in the secondary side will increase.

Because the number of turns the primary coil will be  
lower than the number of turns in the secondary coil.

In primary coil, if we reduce the turn then the  
voltage of each turn will be increase. That's why  
we ~~found~~ will found more EMF from the  
secondary coil.

Q3.

If a DC current flows through the primary coil,  
transformer will not work. Because, the DC current  
is constant. As we know,  $\mathcal{E} = -L \frac{di}{dt}$ .

Since, current is constant,  $\frac{di}{dt} = 0$

So,  $\mathcal{E} = 0 \text{ V.}$

4.

Average turns ratio

$$= \frac{8.125 + 8.387 + 8.201 + 8.301 + 8.400 + 8.242 + 8.382 + 8.209}{8}$$

$$= 8.293$$

05.

We know,

$$\frac{V_p}{V_s} = \frac{N_p}{N_s}$$

Given,

$$\frac{V_p}{V_s} = 8.293$$

$$N_p = 400$$

$$N_s = \frac{N_p V_s}{V_p}$$

$$N_s = \frac{400}{8.293} = 48.293 \text{ turns}$$



6.

If we increase the frequency such as  $250\text{ kHz}$ , the output will be reduced. The iron core used in the transformer is manufactured for low frequency. If we provide high frequency, iron core will produce heat. For we found some voltage loss due to heat. That's why the output will be reduced.

### Discussion:

From this experiment, we learn about the concept of Induced EMF. We learn how to calculate the turns ratio. And verify the effect of frequency on a transformer. In this experiment we don't face any technical problem. But at first we can't handle the Oscilloscope. With the help of instructor, finally we complete the experiment within time. Briefly, we learn about the step up and step down transformer.

Group - E

Soykot Islam

ID: 2013928642

Joy kuman Ghosh

ID: 2211424642

Data Tables:

Table 1 ( Use the set up shown in Figure 2)

Primary Voltage ( $V_{P(p-p)}$ ) (V)	Secondary Voltage ( $V_{S(s-s)}$ ) mV	$\frac{V_{P(p-p)}}{V_{S(s-s)}}$
1 1.04	128	8.125
2 2.08	248	8.387
3 3.04	368	8.261
4 4.08	488	8.361
5 5.04	600	8.40
6 6.00	728	8.242
7 7.04	848	8.302
8 8.0	968	8.264

Table 2 ( Use the set up shown in Figure 3)

Secondary Voltage ( $V_{S(s-s)}$ ) ✓	Primary Voltage ( $V_{P(p-p)}$ ) ✓	$\frac{V_{P(p-p)}}{V_{S(s-s)}}$
1 1.02	8.0	7.843
2 2.0	12.60	8.800
3 3.04	23.60	7.763
4 4.00	30.40	7.600
5 5.04	38.00	7.540
6 6.00	46.40	7.733
7 7.04	53.60	7.614
8 8.00	60.40	7.550

*Parik*