


L-14 / 16.02.2023 /

Review Class

L-15 / 18.02.2023 /


Midterm

L-16 / 23.03.2023 /

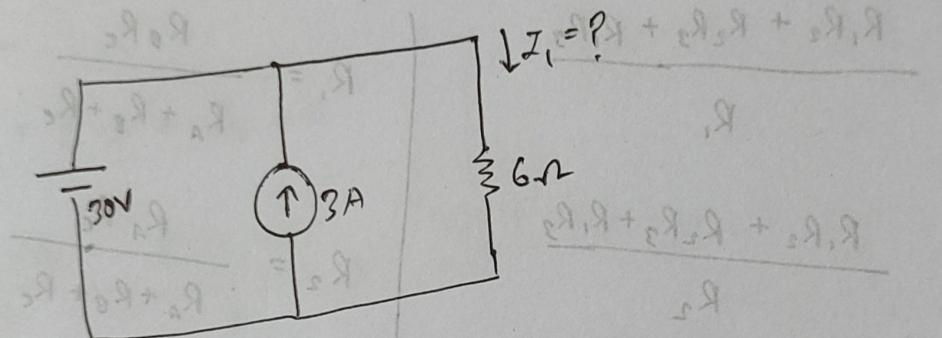


$$I_1 = \frac{30}{R_1 + R_2}$$

\Rightarrow

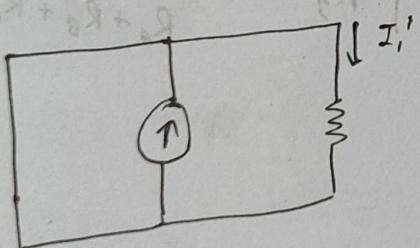

$$I_1' = \frac{30}{6} = 5 \text{ A}$$

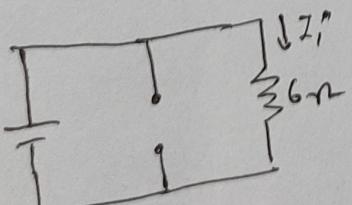Because all the current goes to the through the short.




$$I_1'' = \frac{30}{6} = 5 \text{ A}$$

Method shown?



$$I_1 = I_1' + I_1''$$

$$= 5 + 5 = 10 \text{ A}$$



Example: Q2

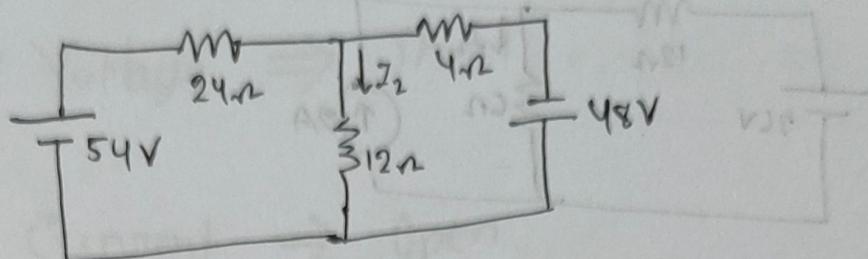

⇒

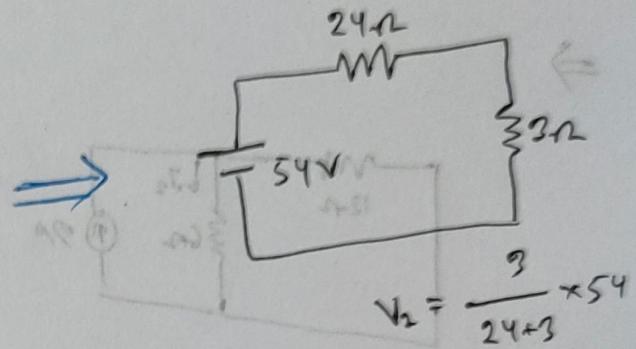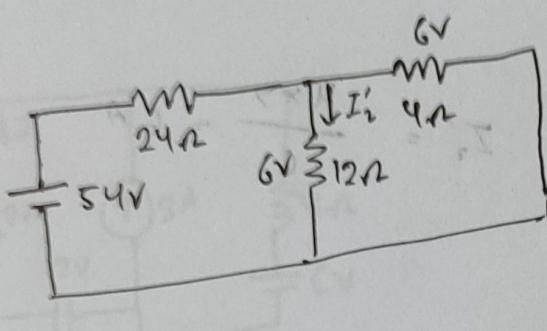
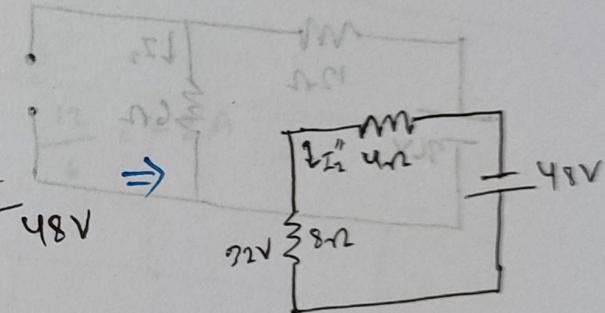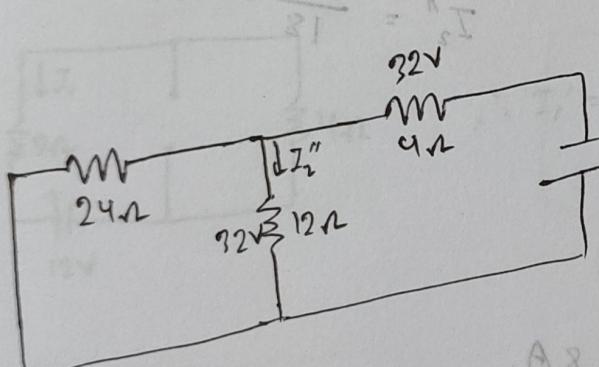
$$\therefore I_2' = \frac{6}{12} = 0.5 \text{ A} \quad = 6 \text{ V}$$



$$\therefore I_2'' = \frac{32}{12} = -2.67 \text{ A} \quad = 32 \text{ V}$$


$$\therefore I_2 = I_2' + I_2''$$

$$= 0.5 - 2.67$$


$$= -2.17 \text{ A}$$

Fig 2.21

Exercises 7

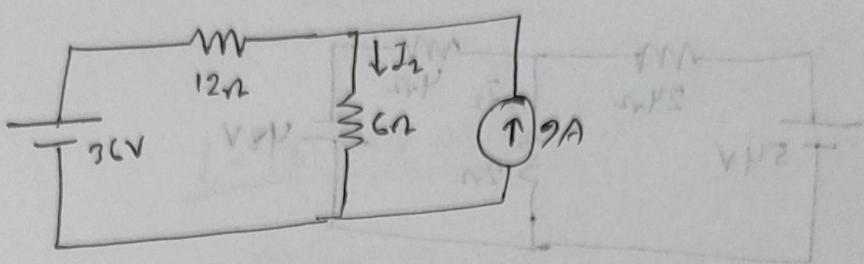

⇒

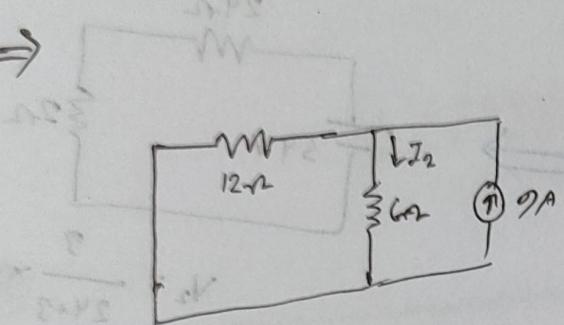


↔

$$V_2 = \frac{4 \times 9}{6} = 6 \text{ V}$$

$$V_2 =$$
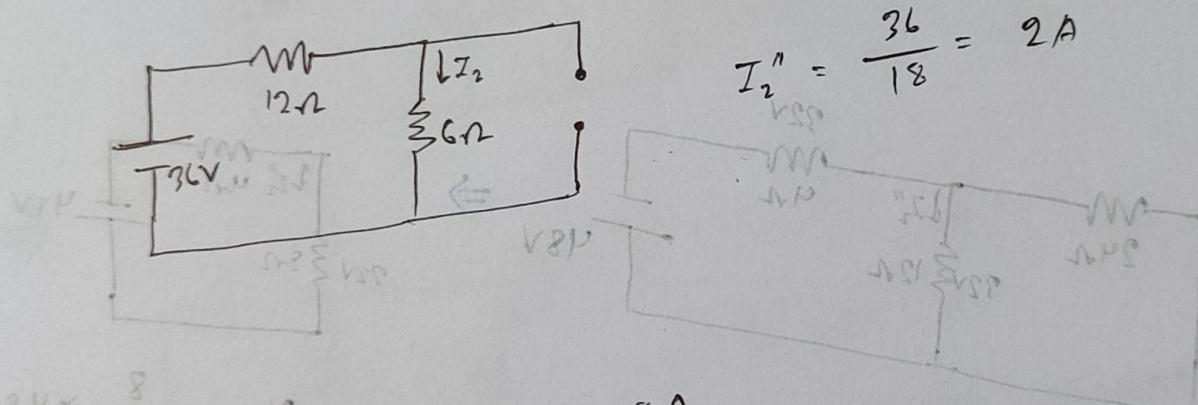
$$A 2 \cdot 0 = \frac{2}{36} = \frac{1}{18} \text{ I}$$



$$2H \times \frac{8}{18} = 5 \text{ V} \therefore I_2 = 6 + 2 = 8 \text{ A}$$

$$V_{SS} =$$

$$A 5 \cdot 0 = \frac{5}{36} = \frac{1}{7.2} \text{ I}$$

$$I_1 + I_2 = 5 \text{ A}$$


$$A 5 \cdot 0 = 0 \text{ A}$$

$$A 5 \cdot 0 = 0 \text{ A}$$



L-17/25.03.2023

⊗ Voltage \Rightarrow Short

⊗ Current \Rightarrow Open

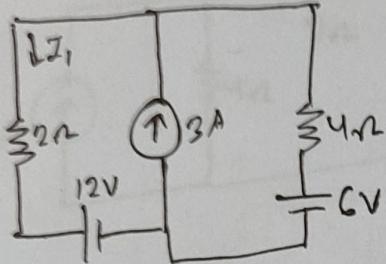


\Rightarrow

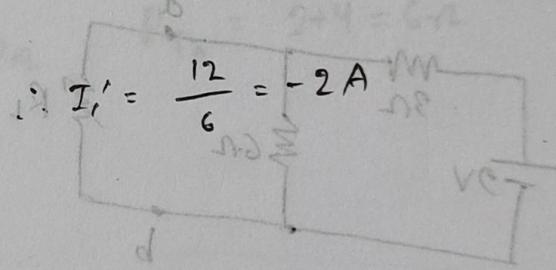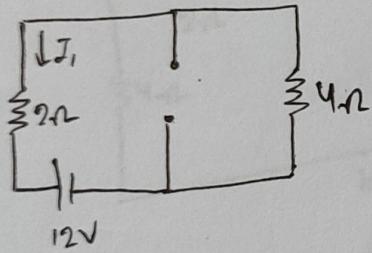


$$I_1'' = \frac{R_T}{R_x} \times I_s = \frac{\frac{4}{3} \times 3}{2} = 2A$$

$$R_T = \left(\frac{1}{2} + \frac{1}{4} \right)^{-1} = \frac{4}{3} \Omega$$
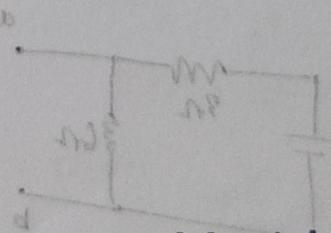
$$V_A = \infty \times \frac{2}{2+4} = \frac{2}{6} = \frac{1}{3}$$



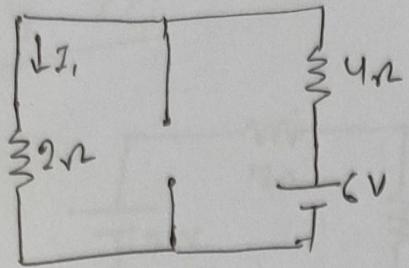

$$I_{1'''} = \frac{6}{6} = 1 \text{ A}$$

$\therefore I = I' + I'' + I'''$

$$= -2 + 2 + 1$$

$$= 1 \text{ A}$$



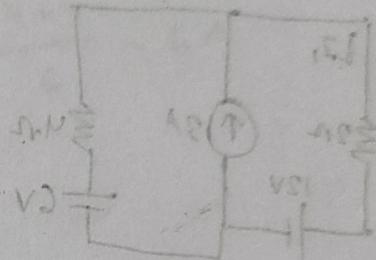
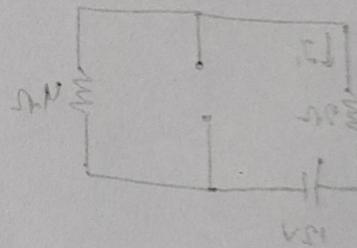


Fig - 26/

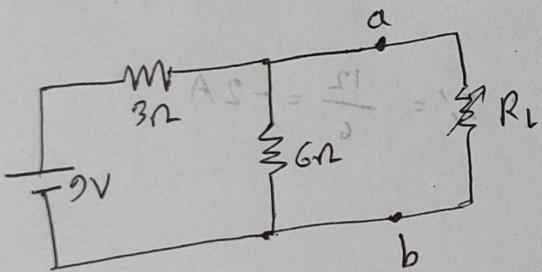
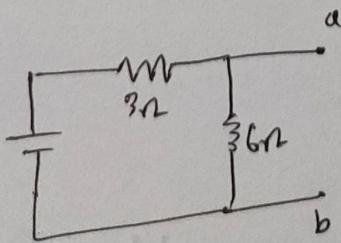
$$\Rightarrow R_{Th} = \left(\frac{1}{3} + \frac{1}{6} \right)^{-1} = 2 \Omega$$



$$E_{Th} = \frac{6}{3+6} \times 9 = 6 \text{ V}$$



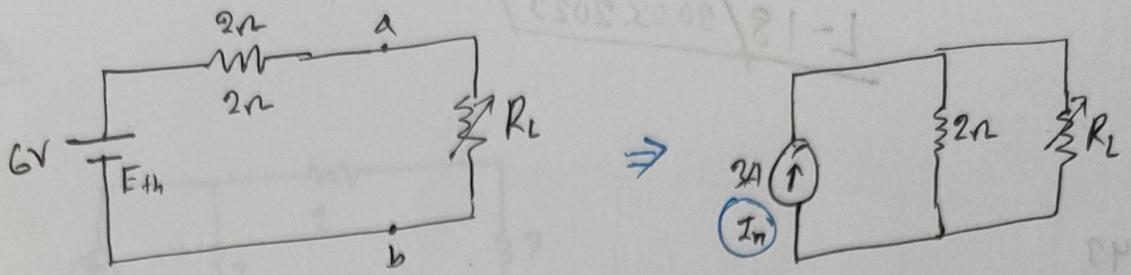
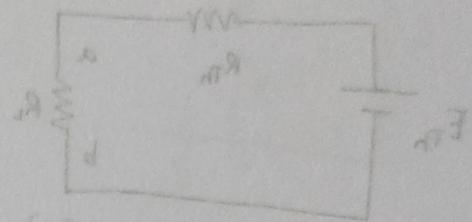





Fig - 2.32 /

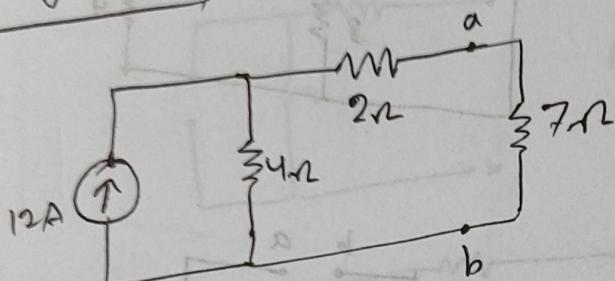

⇒

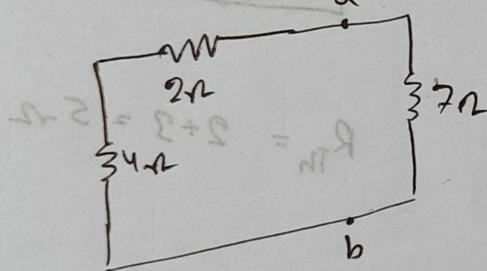

$$R_{Th} = 2 + 4 = 6\Omega$$

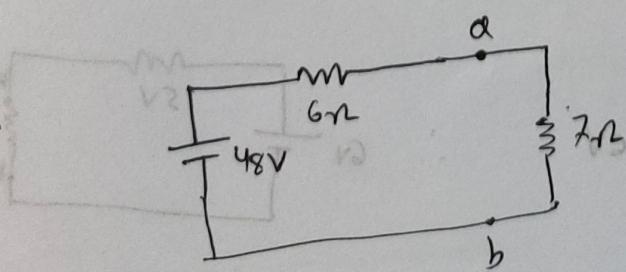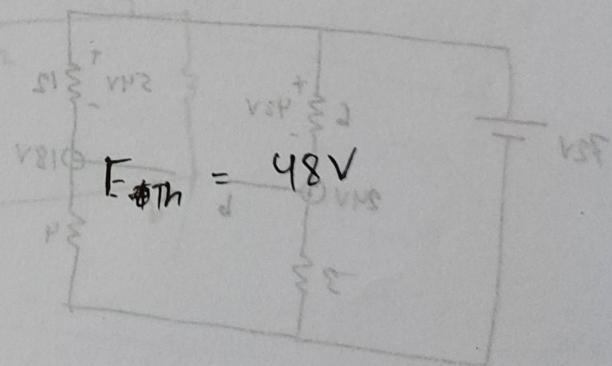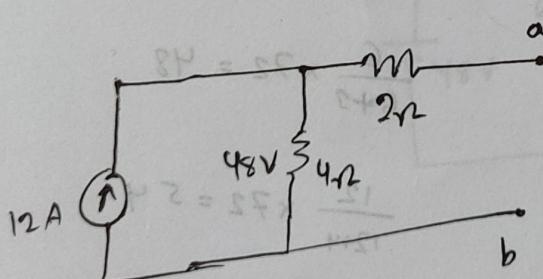

$$V_{MS} = V$$




$$V_{S1} = 0V$$

$$V_{S2} = 81 - 48 = 33V$$


Voriderm™ IV Injection
Voriconazole 200 mg

L-18 / 30.03.2023 /


9.43

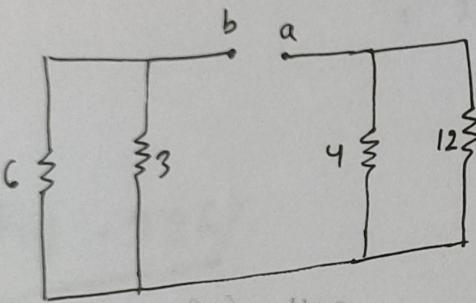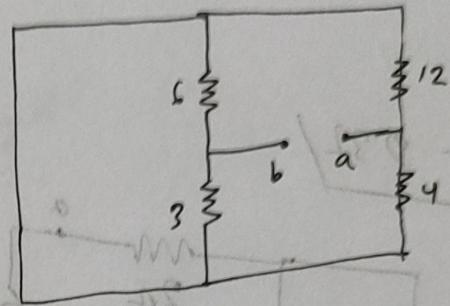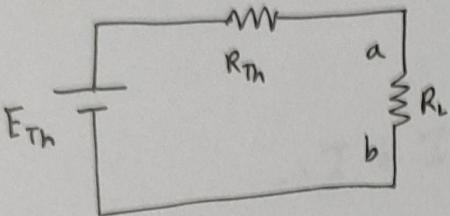

⇒

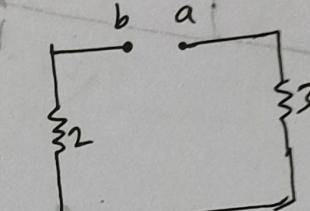

$$R_{Th} = 2 + 3 = 5 \Omega$$

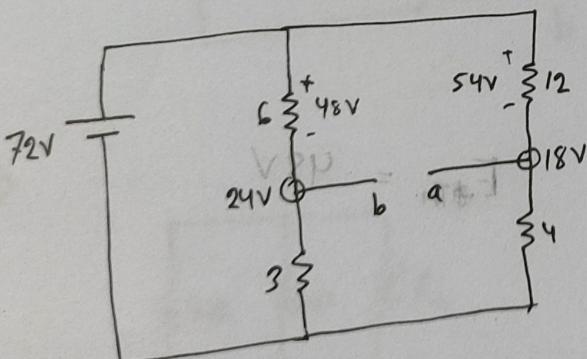

$$\frac{6}{6+3} \times 72 = 48$$


$$\frac{12}{12+4} \times 72 = 54$$

$$V_b = 24V$$

$$V_a = 18V$$




$$\therefore V_{ba} = 24 - 18 = 6V$$

$$\therefore E_{Th} = 6V$$

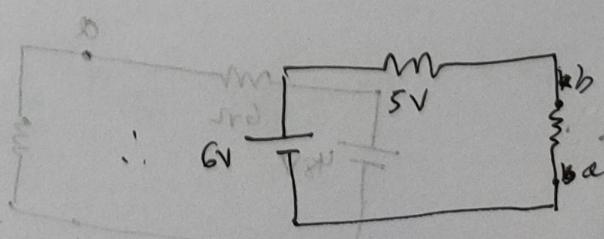


9.32

82.0

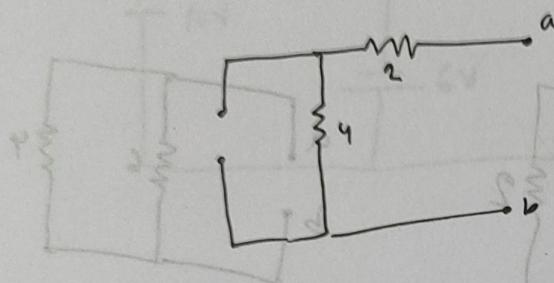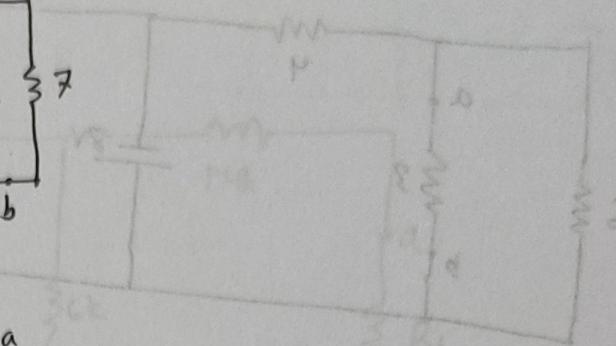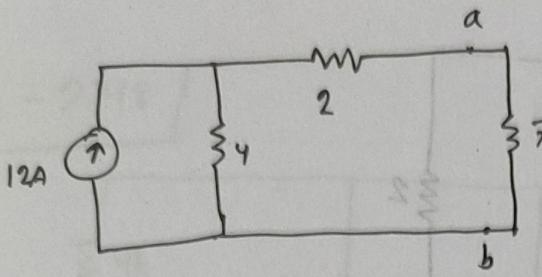

$$R_{Th} = 6\Omega$$

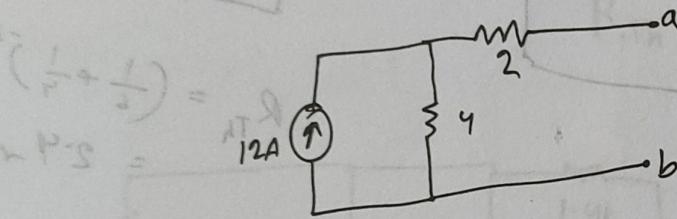


$$V_{ab} = 4 \times 12 = 48V$$





$$\Delta V_{ab} = 48V$$

$$\Delta E_{Th} = 48V$$
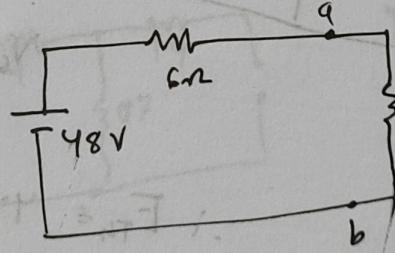
$$V_{8P} = 8 \times \frac{6\Omega}{6\Omega + 2\Omega}$$




9.38

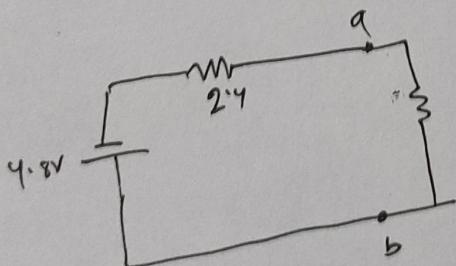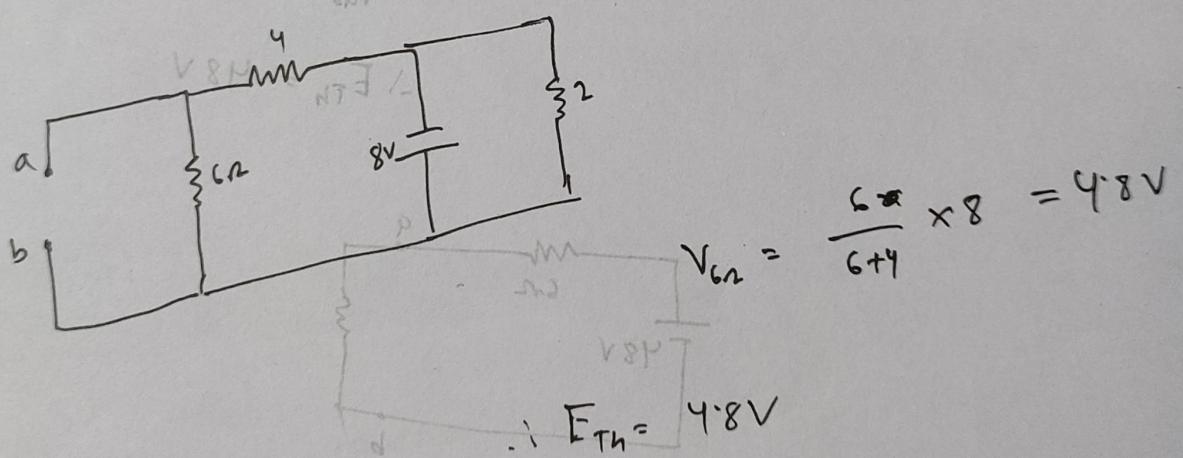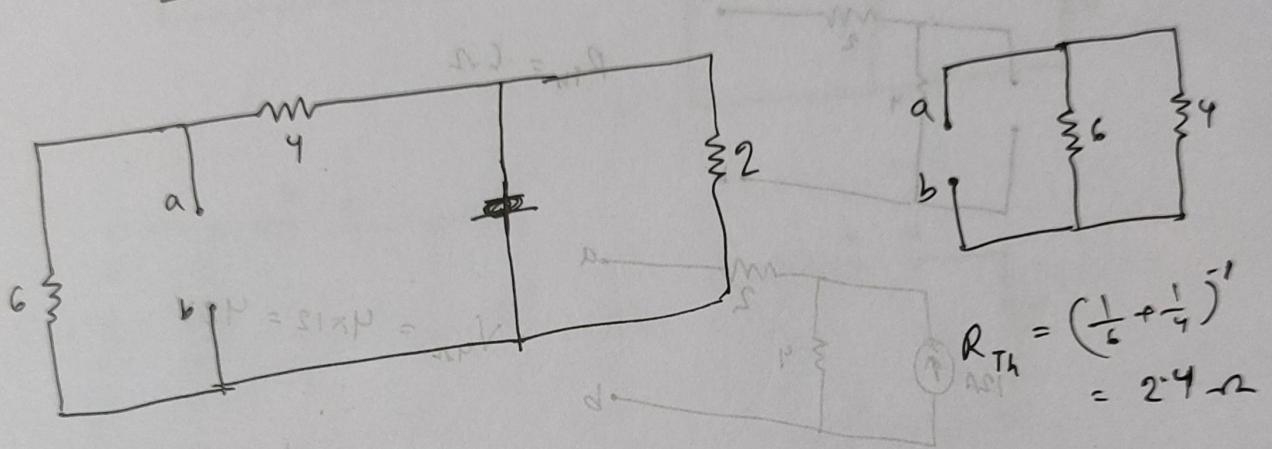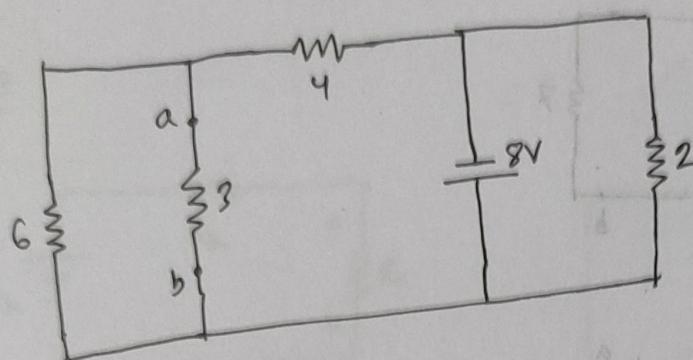


L-19 / 06.04.2023

Fig - 2.48

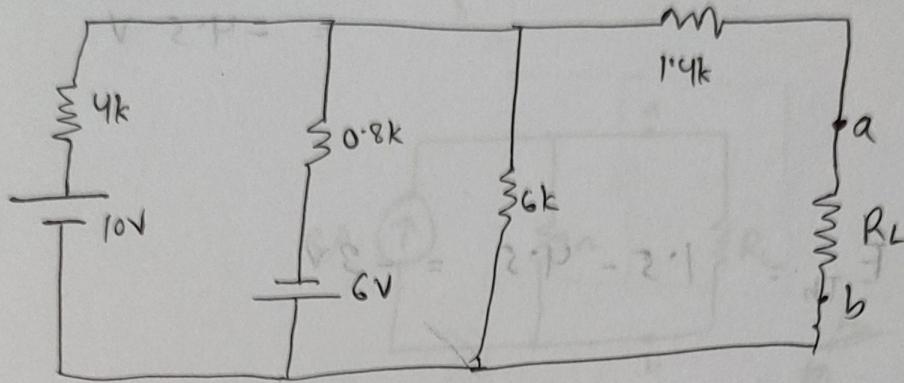

$$R_{Th} = \left(\frac{1}{4} + \frac{1}{0.8} + \frac{1}{6} \right)^{-1} + 1.4$$


$$= 2 \text{ k}\Omega$$

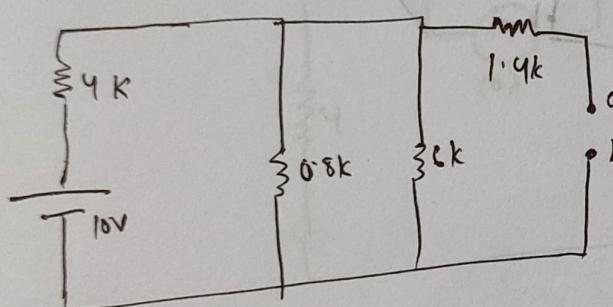


$$R_{ab} = \frac{0.7}{4+0.7} \times 10$$

$$= 1.48 \text{ V}$$

$$\approx 1.5 \text{ V}$$

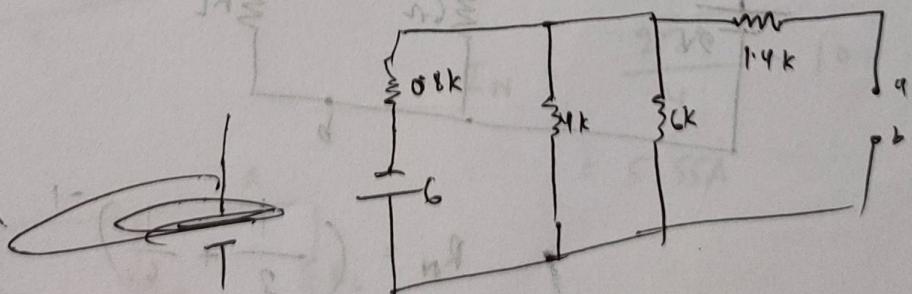


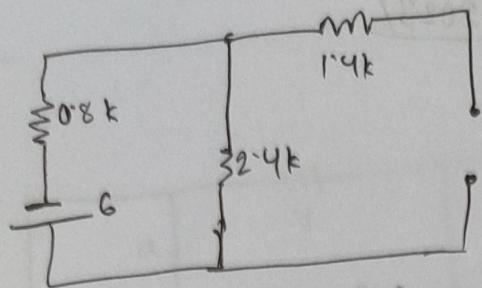



$$V_{ab}'' = \frac{2^4}{0.8 + 2^4} \times 6$$

$$= -4.5 \text{ V}$$

$$\therefore E_{Th} = 1.5 - 4.5 = -3V$$

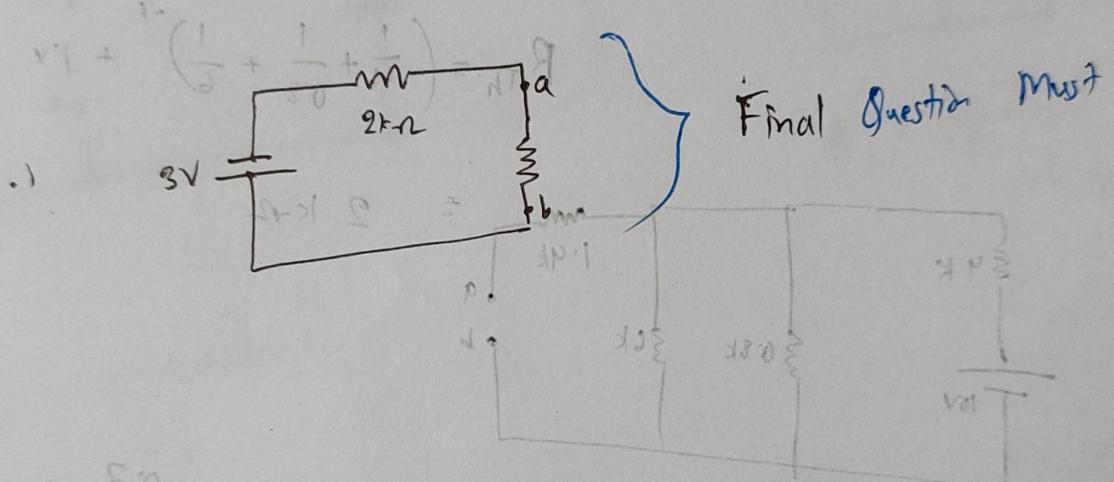


Norton's Theorem:

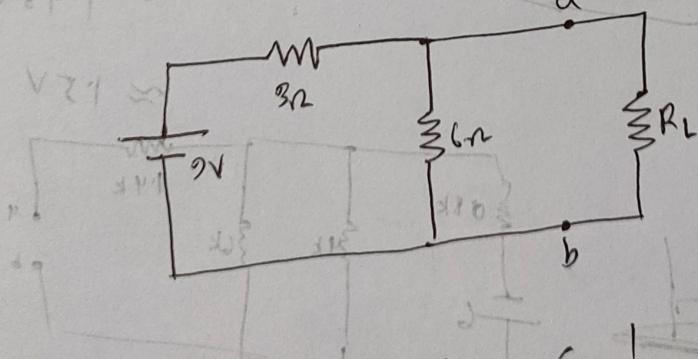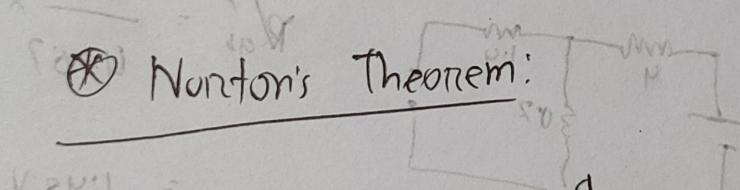


$$R_N = \left(\frac{1}{3} + \frac{1}{6} \right)^{-1}$$

= 2 n

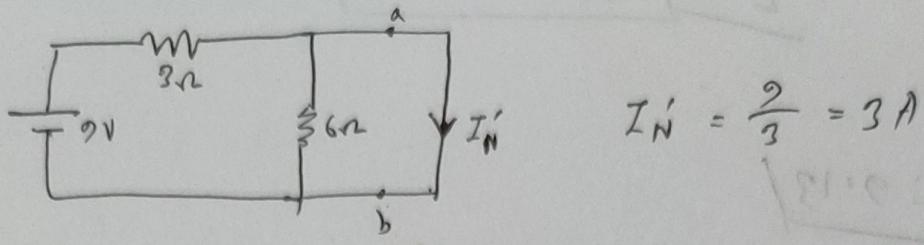


$$I_N' = \frac{9}{3} = 3A$$

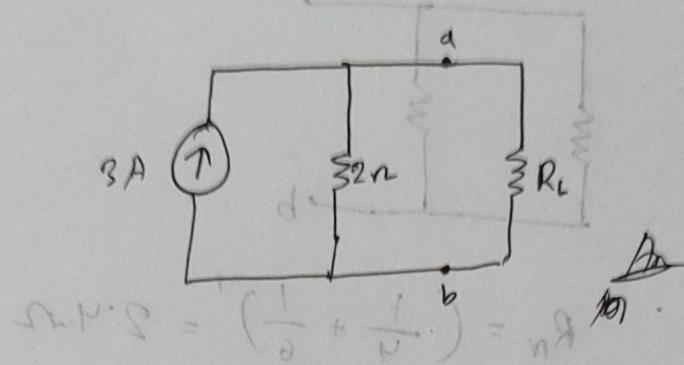


$$R_N = \left(\frac{1}{3} + \frac{1}{R_L} \right)^{-1}$$

9.67/

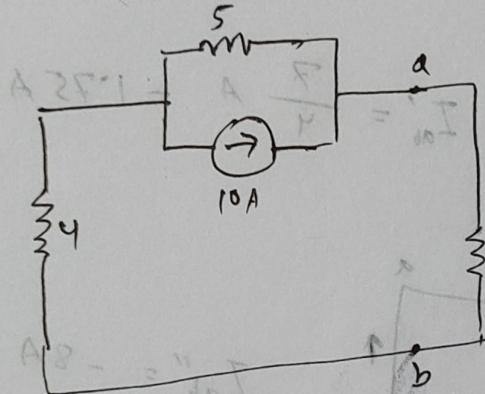

$$R_N = 4 + 5 = 9\Omega$$

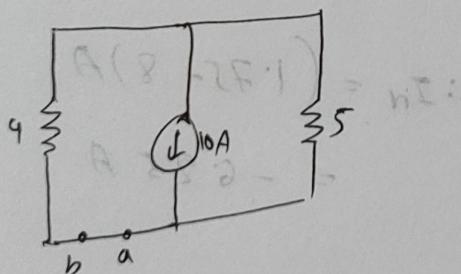


$$R_T = \left(\frac{1}{4} + \frac{1}{5} \right)^{-1}$$

$$= 2.22\Omega$$


$$I_N = \frac{2.22}{4} \times 10$$

$$= 5.55A$$

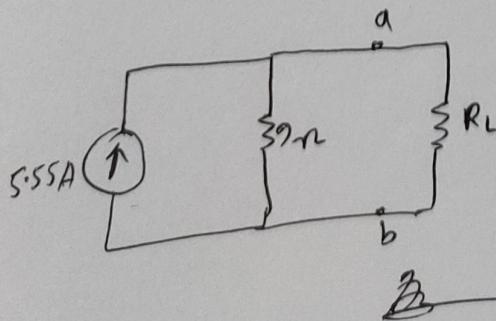


L-20 / 08.04.2023 /


Example : Q-13 /

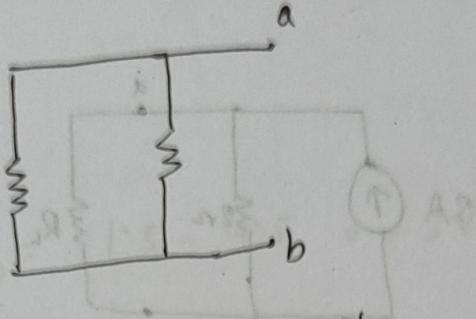


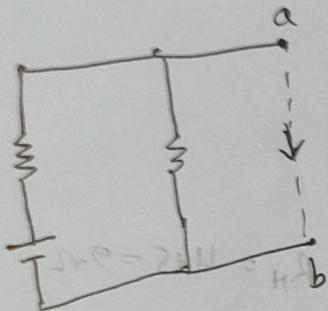
$$R_{\text{eq}} = \left(\frac{1}{3} + \frac{1}{6} \right)^{-1} = 2.4 \Omega$$



$$I_{ab}' = \frac{7}{2.4} A = 1.75 A$$

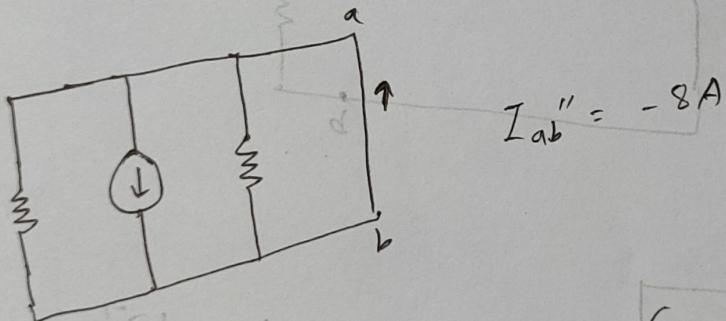


$$i_{In} = (1.75 - 8) A = -6.25 A$$

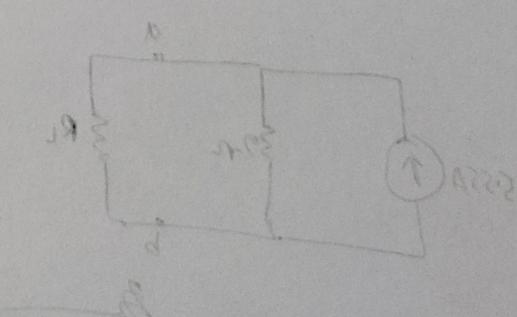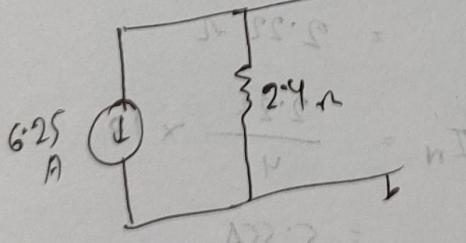

Maximum Power Transfer:

$$R_L = R_{Th}$$


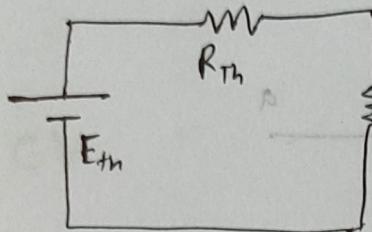


$$V_L = R_L \times \frac{E_{Th}}{R_L + R_{Th}}$$



$$P_L = R_L \times \frac{E_{Th}}{2R_L} = \frac{E_{Th}}{2}$$

$$\therefore P_L = \frac{V^2}{R} = \frac{(E_{Th}/2)^2}{R_L} = \frac{(E_{Th})^2}{4R_L}$$

Fig - 4.50/

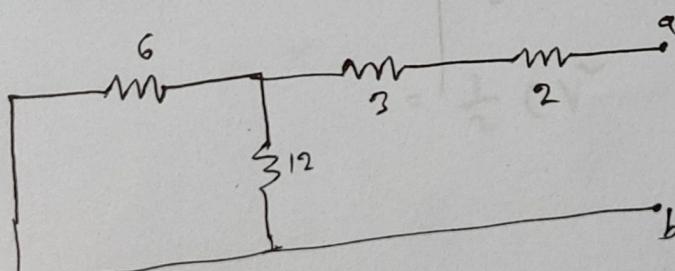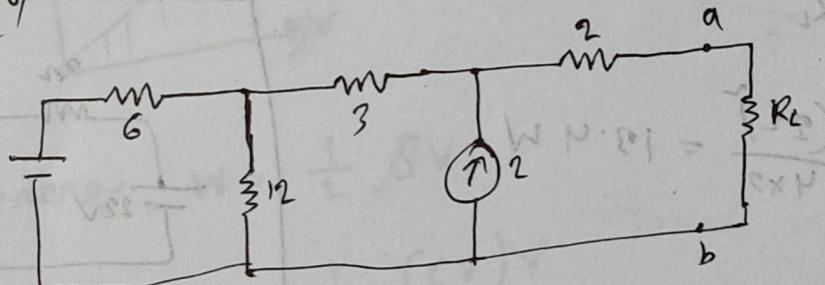

$$\therefore R_{Th} = 9\Omega$$

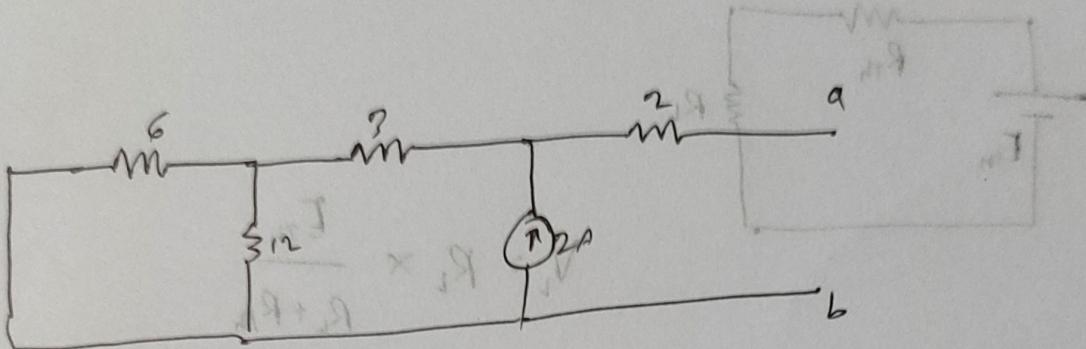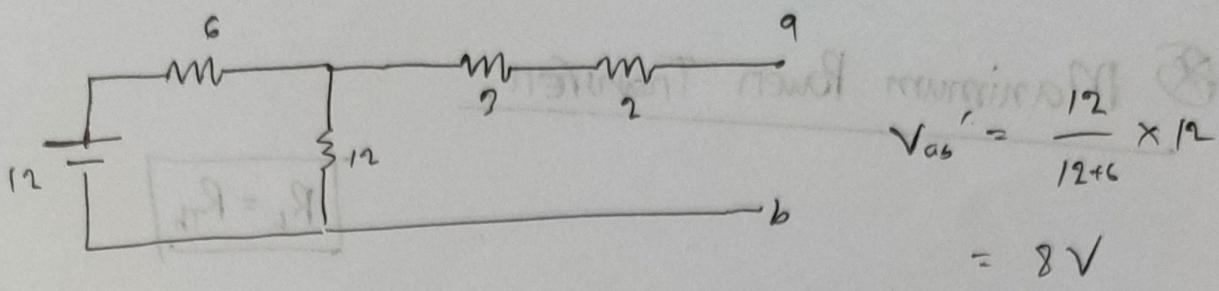


$$\frac{E}{R_L} = \frac{4E}{4R_L} \quad R_{Th} = 7\Omega$$

$$V_{ab}'' = \frac{7 \times 2}{7+2} = 14V$$


$$\rightarrow E_{th} = 8 + 14 = 22V$$

$$P_L = \frac{E_{th}^2}{4R_L}$$

$$= \frac{(22)^2}{4 \times 7} = 13.4W$$

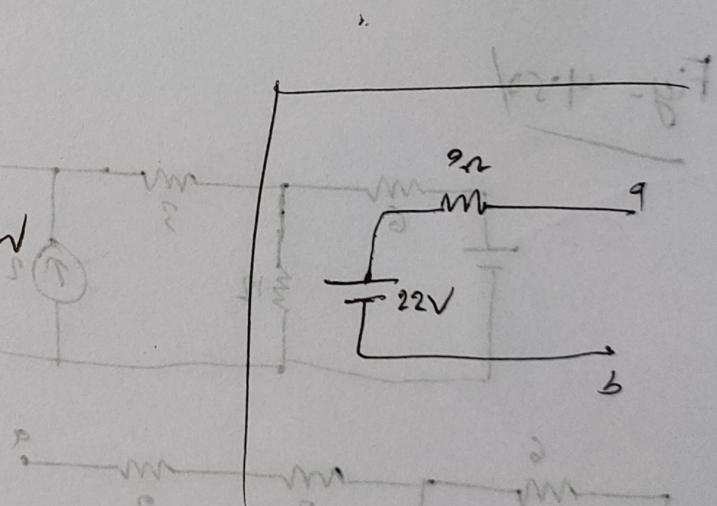

$$R_{Th} = 2\Omega$$

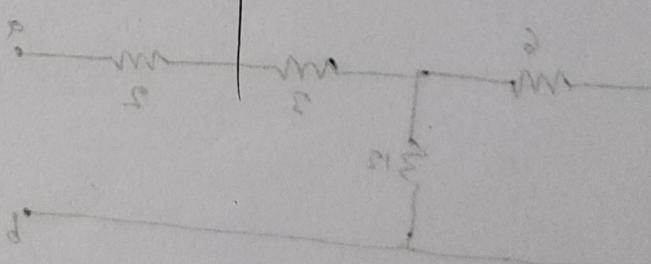

L-21 / 15.04.2023 /

$$V = 8$$

$\frac{Q}{d}$

$\frac{Q}{d}$

$\frac{Q}{d}$

$\frac{Q}{d}$

$\frac{Q}{d}$

$$Q = CV = 8V$$

$$C \propto \frac{A}{d}$$

$$C_x = \frac{A}{d} (7500 \text{ F})$$


$$C \propto A \cdot V + sV + , V = 3$$

$$= 7500 \frac{F}{m} G$$

$$\frac{C \propto}{e^2} \frac{A}{d} + \frac{Q}{d} = \frac{Q}{d} \Leftarrow$$

$$C = \epsilon \frac{A}{d}$$
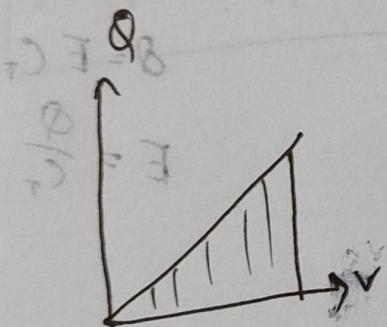
$$\frac{1}{e^2} + \frac{1}{e^2} + \frac{1}{e^2} \xrightarrow{\text{Permitivity}} (=)$$




$$1 - \left(\frac{1}{e^2} + \frac{1}{e^2} + \frac{1}{e^2} \right) = \rightarrow T$$

$$\text{Store energy, } W = \frac{1}{2} \cdot QV$$

$$= \frac{1}{2} (CV)V$$

$$= \frac{1}{2} C V^2$$

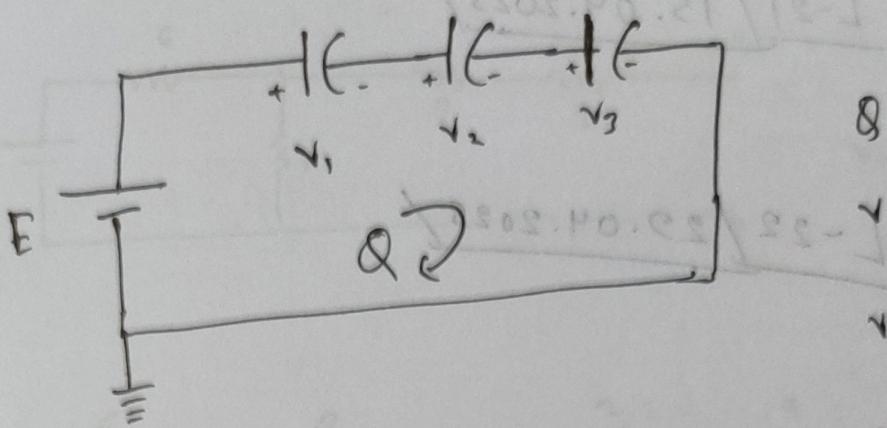


$$Q = C_1 V_1$$

$$V_1 = \frac{Q}{C_1}$$


$$V_2 = \frac{Q}{C_2}$$

$$V_3 = \frac{Q}{C_3} = \varnothing$$

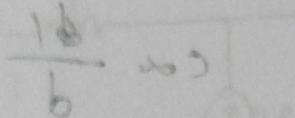

$$E = V_1 + V_2 + V_3 \rightarrow (\rightarrow 002F) \frac{A}{b} = \varnothing$$

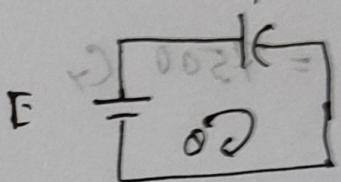
$$\Rightarrow \frac{Q}{C_1} = \frac{Q}{C_1} + \frac{Q}{C_2} + \frac{Q}{C_3}$$



$$\Rightarrow \frac{1}{C_T} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$$

$$C_T = \left(\frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} \right)^{-1}$$

Serielle Connection

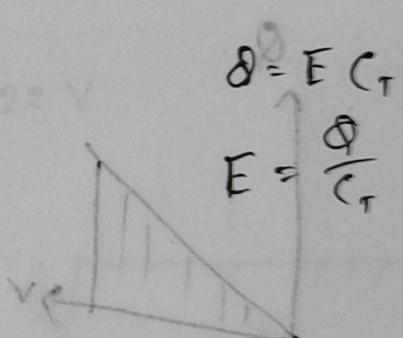


$$Q = E C_T$$

$$E = \frac{Q}{C_T}$$

$$V \cdot \frac{1}{C} = W, \text{ Vorsicht sonst?}$$

$$V \cdot \frac{1}{C} =$$

$$V \cdot \frac{1}{C} =$$

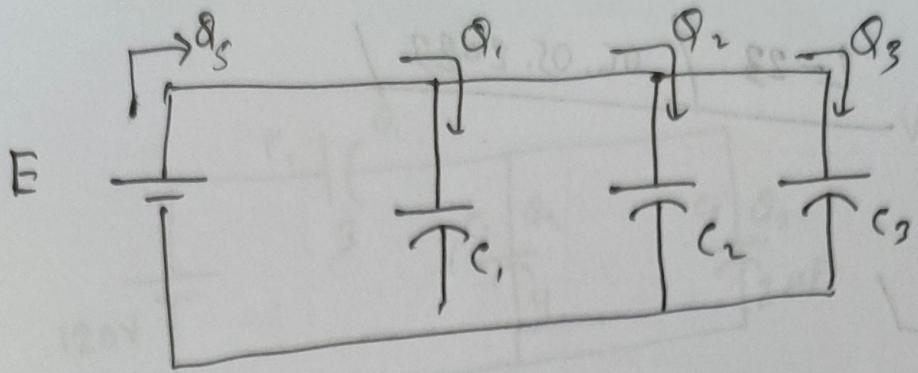

$$I_s = I_1 + I_2 + I_3$$

$$\delta_s = \delta_1 + \delta_2 + \delta_3$$

$$\Rightarrow EC_T = EC_1 + EC_2 + EC_3$$

$$EC_T = C_1 + C_2 + C_3$$


Parallel Connection

$$= (8\mu) (2 \times 10^{-1} \times 0.2)$$

$$= (8\mu) (2 \times 10^{-1} \times 0.2 \times 0.2) = V_s = 1.6$$

$$\frac{1}{R_s} + \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} = \frac{1}{R_T}$$

Example 10.6 /

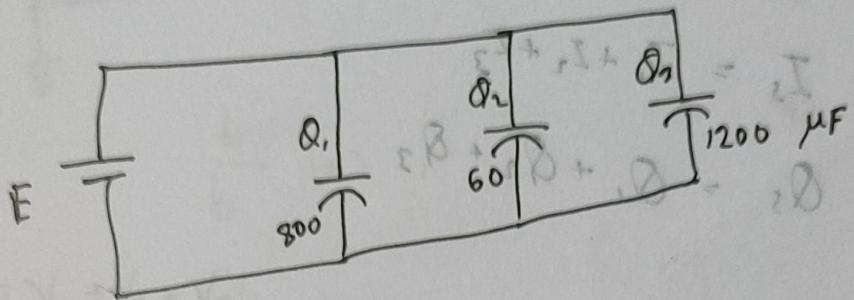

$$a) 800 + 60 + 1200 = 2060 \mu\text{F}$$


$$b) Q_1 = C_1 V = (800 \times 10^{-6}) (48) =$$

$$Q_2 = C_2 V = (60 \times 10^{-6}) (48) =$$


$$Q_3 = C_3 V = (1200 \times 10^{-6}) (48) =$$

$$c) Q_T = Q_1 + Q_2 + Q_3$$

=

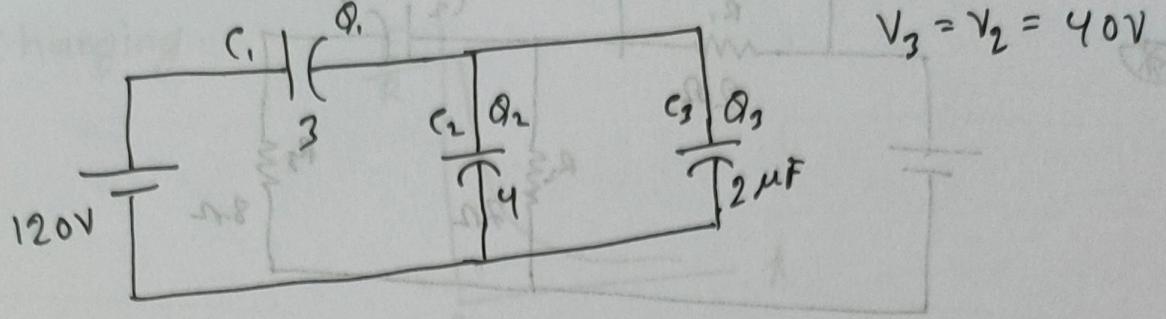

$$V_3 = V_2 = 40V$$

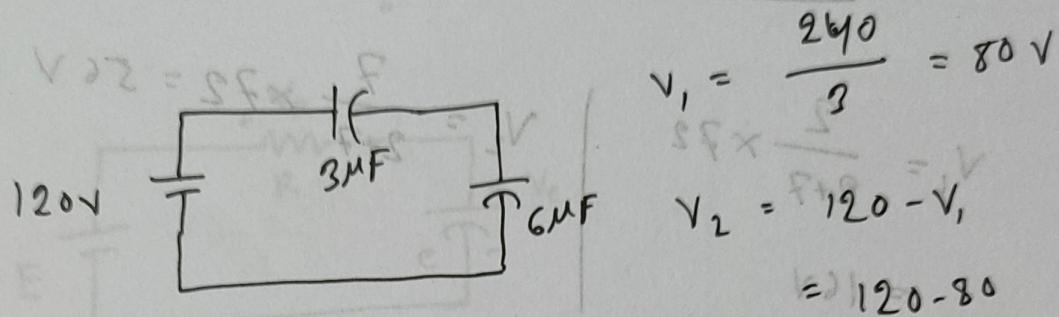


$$V_1 = \frac{240}{3} = 80V$$


$$V_2 = 120 - V_1$$

$$= 120 - 80$$
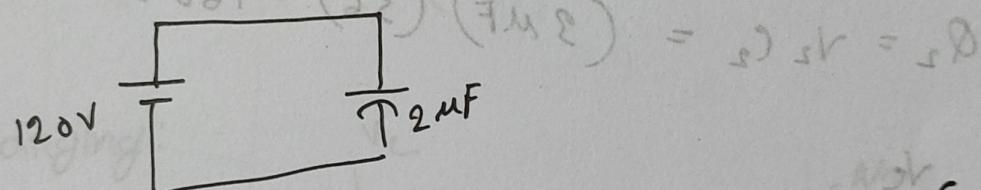
$$C_T = \left(\frac{1}{3} + \frac{1}{6} \right)^{-1} = \left(\frac{1}{2} \right)^{-1} = 2 \mu F$$



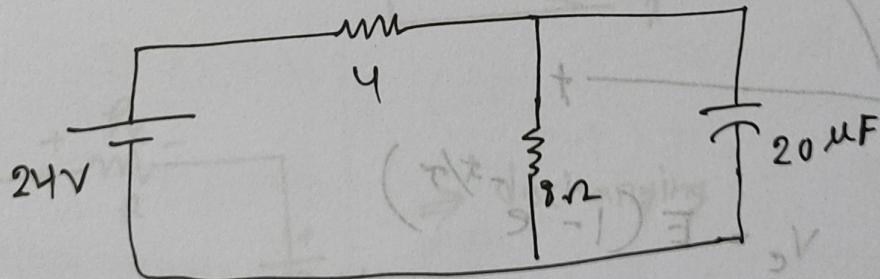
$$Q_T = C_T V = 120 \times 2 \times 10^{-6} = 240 \mu Coul.$$



$$V_C = \frac{8}{8+4} \times 24 = 16V$$
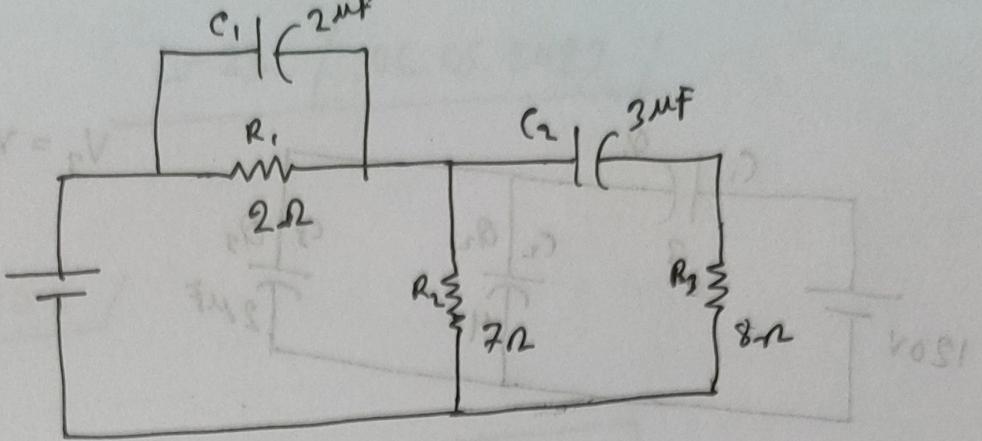
$$Q_1 = C_1 V_C = (20 \times 10^{-6}) (16) = 320 \mu Coul.$$




$$V_1 = \frac{2}{2+7} \times 72$$

$$= 16 \text{ V}$$

$$V_2 = \frac{7}{2+7} \times 72 = 56 \text{ V}$$

$$Q_1 = V_1 \times C_1 = (2 \times 10^{-6}) (16) = 32 \mu\text{C}$$
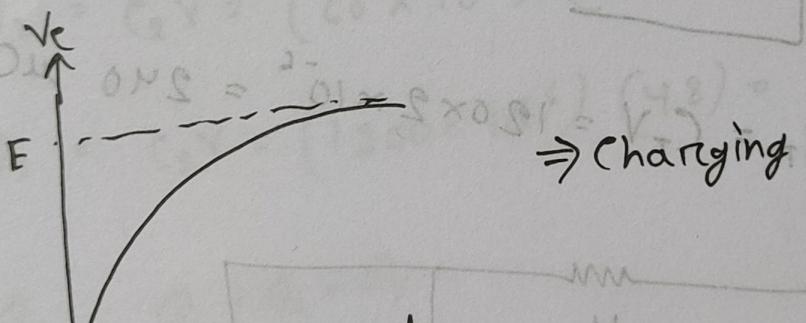
$$Q_2 = V_2 \times C_2 = (3 \mu\text{F}) (56) = 168 \mu\text{Coul.}$$




$$V_c = E (1 - e^{-t/\tau})$$

$$\text{at, } t=0, V_c = E (1 - e^0) = 0$$


$$\text{at, } t=\infty, V_c = E (1 - \frac{1}{e^\infty}) = 0$$

$$= E (1 - 0) = E_{\max}$$

④ Changing

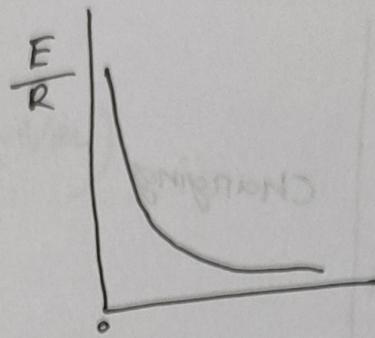



⑤

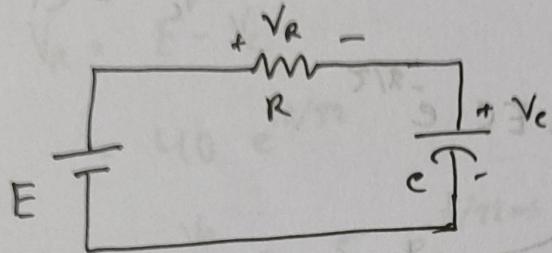


$$V_R = E - V_C = E - E(1 - e^{-t/\tau})$$

$$= (E e^{-t/\tau})$$


⑥ Discharging:

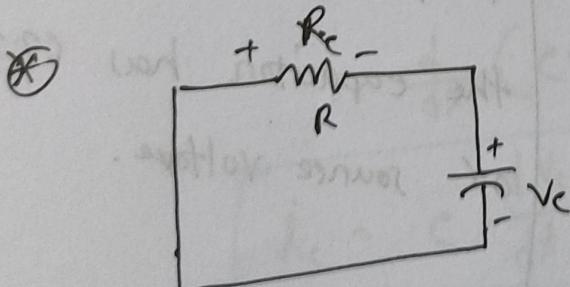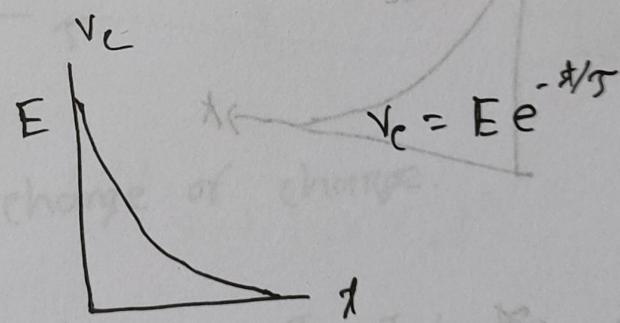



\Rightarrow discharging

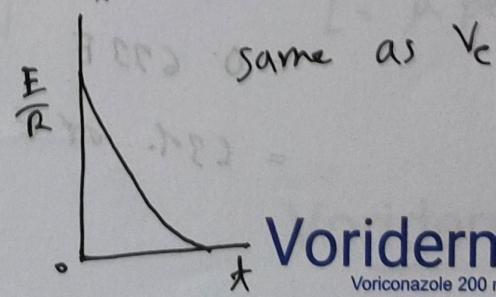



L-24 / 11.05.2023

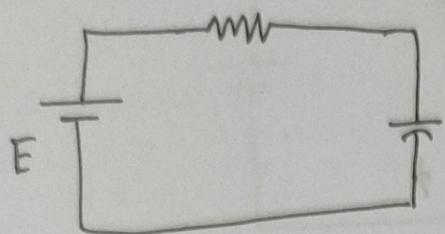

Charging

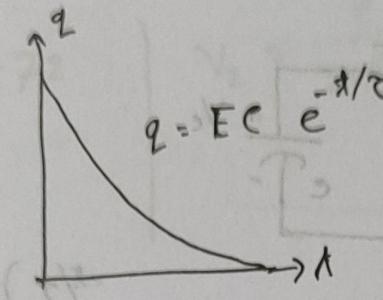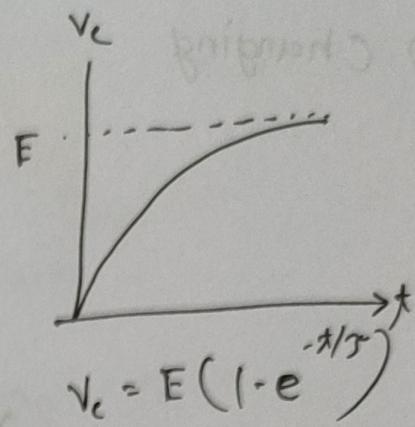

discharging:

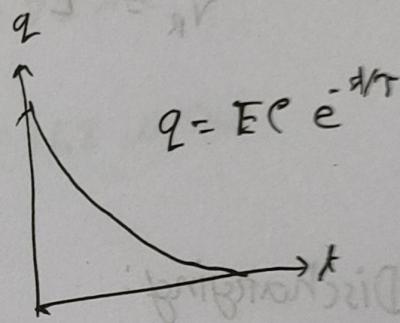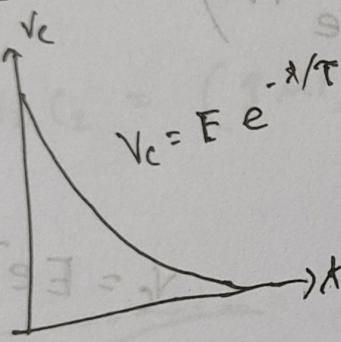

∴ When, $t = \tau$

at charging, $V_c = E(1 - e^{-\tau/\tau})$
= $E(1 - e^0)$
= $E(1 - 1)$
= $0.632 E$

= 63% of E

At, $t = \tau$

the capacitor has 63% of source voltage.

Example 10.6/

$$RC = 32 \text{ msec}$$

a) $V_C = 40(1 - e^{-t/RC})$



$$E = V_C + V_R$$

$$\Rightarrow V_R = E - V_C$$

$$= 40 e^{-t/32}$$

$$i_C = \frac{V_R}{R} = 5 e^{-t/32 \text{ ms}}$$

b)

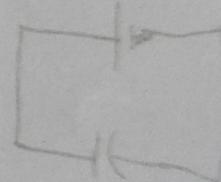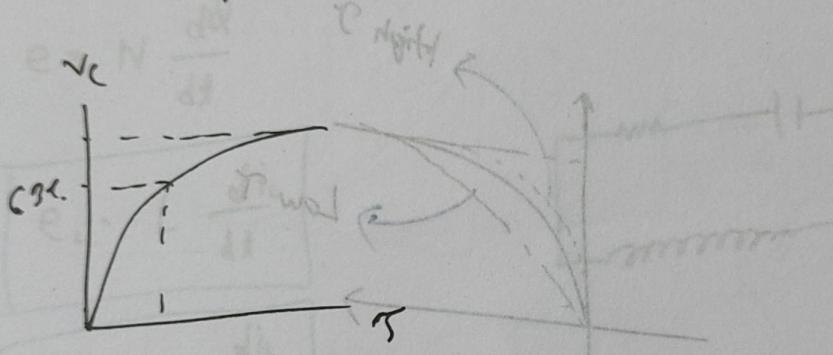


④ Current \rightarrow rate of change of charge.

$$i_C = \frac{dQ}{dt}$$

$$= \frac{d}{dt}(C V_C)$$

$i_C = C \frac{dV_C}{dt}$

④ Inductor

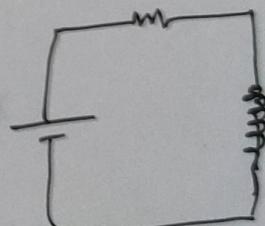

$C = \epsilon$ permittivity

$L = \mu$ permeability

L-25 / 13.05.2023 /



$$\varphi = CV$$

$$C = \frac{\varphi}{V}$$

$$C_{\text{parallel}} = C_1 + C_2 + C_3 + \dots + C_n$$


$$C_{\text{series}} = \left(\frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} + \dots + \frac{1}{C_n} \right)^{-1}$$

$$\tau = RC$$

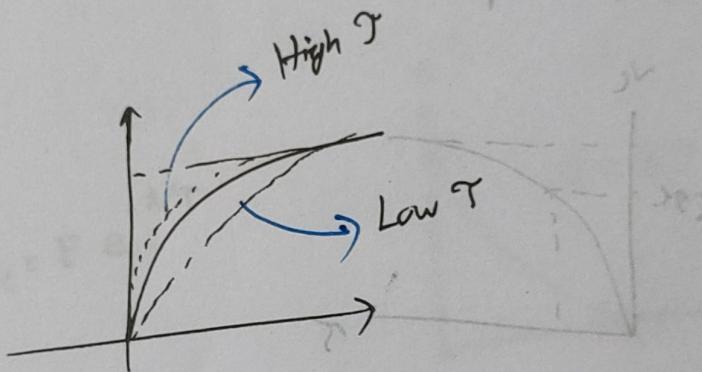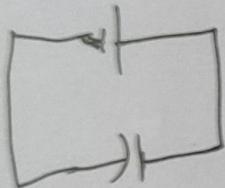



$$E_t = V_0 \left(1 - e^{-t/\tau} \right)$$

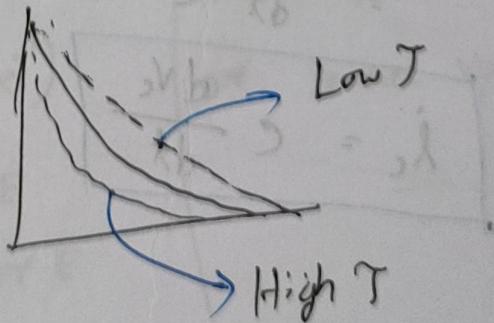notwendig
after, $\tau = \tau$, $E_t = 0.63 V_0$ $t = \tau$



$$C = \epsilon \frac{A}{d}; \quad \epsilon = \text{Permeability}$$

Inductor

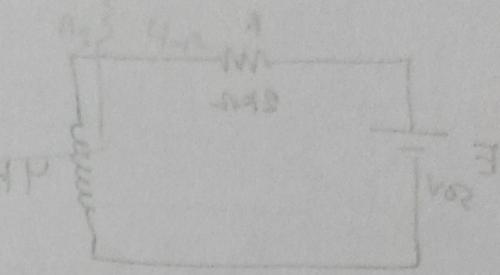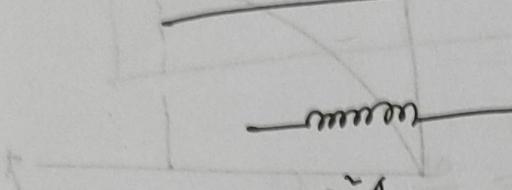




$$L = \mu \frac{N^2 A}{l}$$

$$L = \mu L_0$$




$$e = N \frac{d\Phi}{dt}$$

$$e_L = L \frac{di_L}{dt}$$

$$V_L = L \frac{di_L}{dt}$$

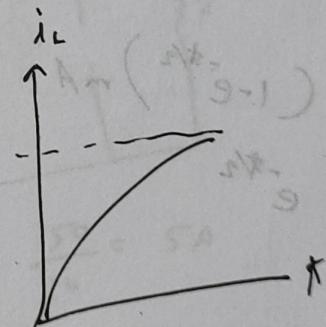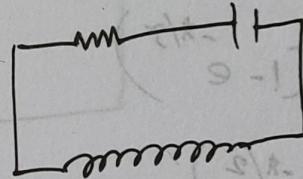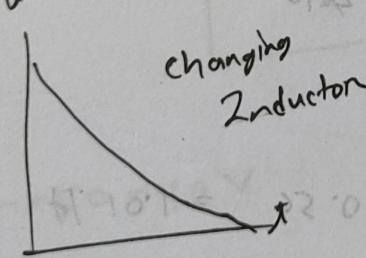

L-26 / 18.05.2023 /

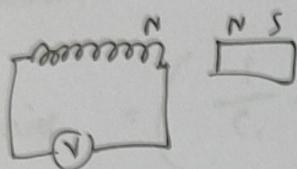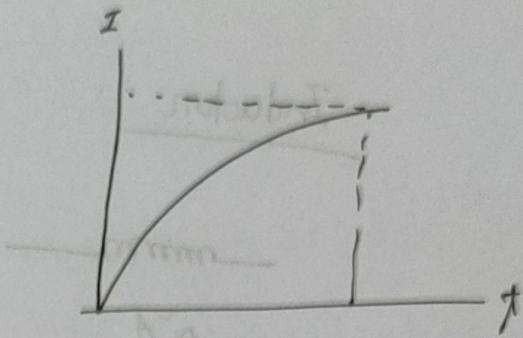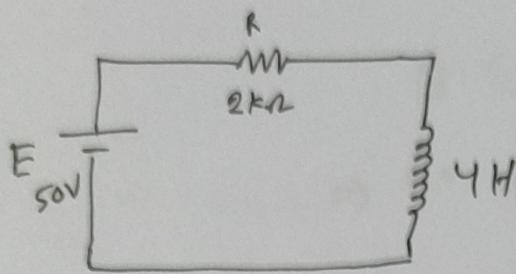

induced current oppose the source current.


$$i_L = \frac{E}{R} (1 - e^{-\frac{t}{T}})$$

$$i_L = \frac{50}{2 \times 10^3} (1 - e^{-\frac{t}{2}})$$

$$= 25 (1 - e^{-\frac{t}{2}}) \text{ mA}$$

$$v_L = 50 e^{-\frac{t}{2}}$$

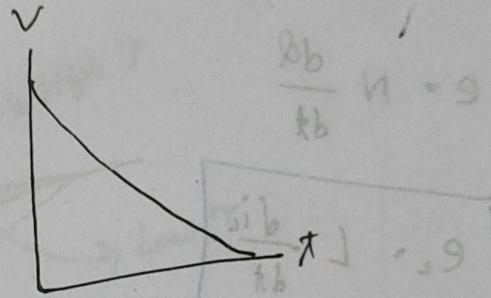
$$L_T = \left(\frac{1}{1.2} + \frac{1}{1.2} + \frac{1}{1.8} \right)^{-1} + 0.56 = 1.01 \text{ H}$$



$$\text{Here, } T = \frac{L}{R}$$

$$T = \frac{4}{2 \times 10^3} = 2 \text{ ms}$$



Moving
magnet

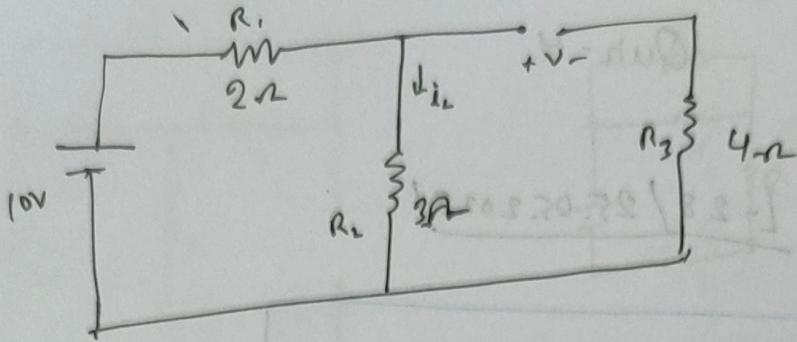

$$i_L = \frac{10}{2+3} = 2A$$

\downarrow (← marking node 2)

$$V_C = (3 \times 2) V = 6V$$

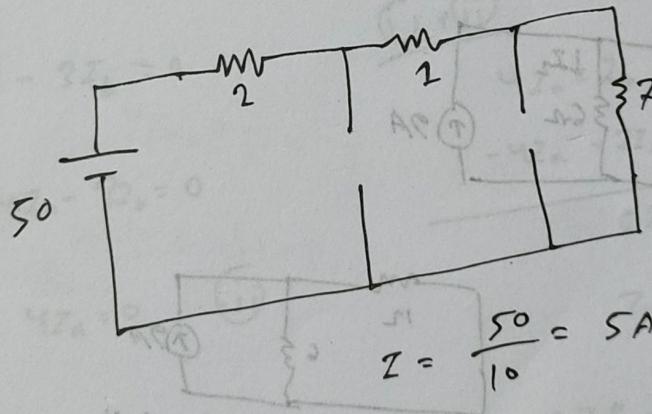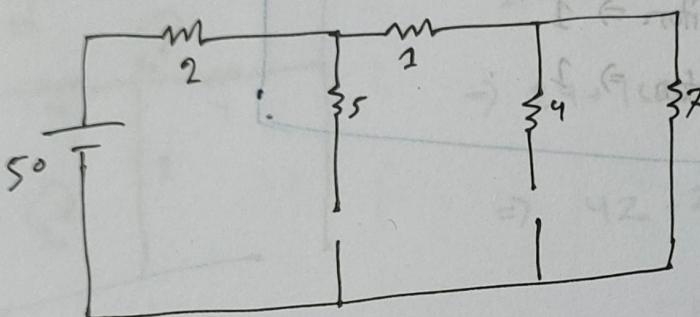

$$V_1 = \frac{8}{10} \times 50 = 40V$$

$$I_1 = I_2 = 5A$$

$$V_2 = \frac{7}{10} \times 50 = 35V$$

$$I = \frac{15}{3+2} = 3A$$

$$W = \frac{1}{2} (6 \times 10^{-3}) (3)^2 = 27 mJ$$

L-27 / 20.05.2023 /

Ques. 4

L-28 / 25.05.2023 /


Final Question Pattern

Super Position $\Rightarrow 1$



Norton's & Thévenin's Theorem $\Rightarrow 1$

Capacitor $\Rightarrow 1$


Inductor $\Rightarrow 2$

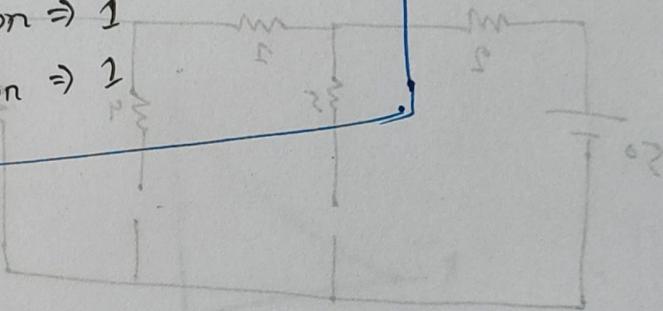

① Super Position:

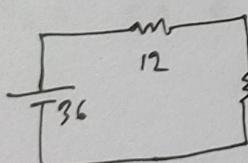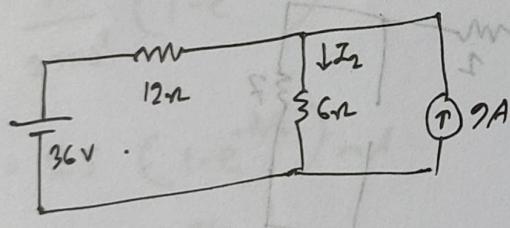

$$I_2' = \frac{36}{18} = 2A$$


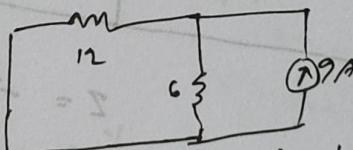


$$I_2'' = \frac{\left(\frac{1}{12} + \frac{1}{6}\right)^{-1}}{6} \times 4 = \frac{1}{6} \times 4 = \frac{2}{3} A$$


$$I_2 = I_2' + I_2'' = 2 + \frac{2}{3} = \frac{8}{3} A$$

$$\therefore I_2 = 2 + \frac{2}{3} = \frac{8}{3} A$$

(X)

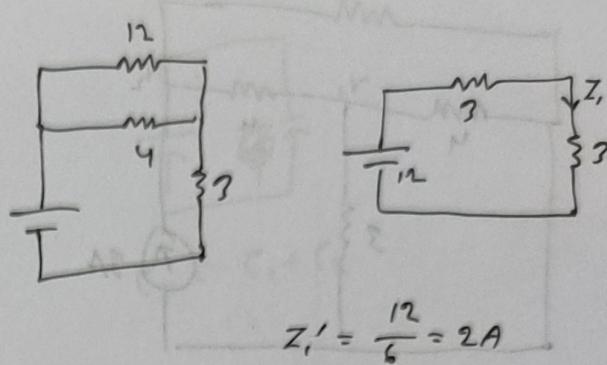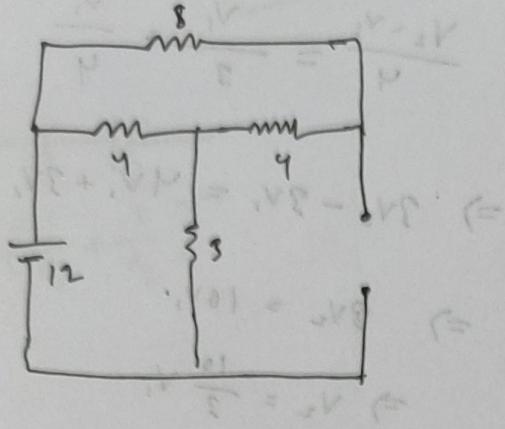

$$Z_1' = \frac{12}{6} = 2A$$

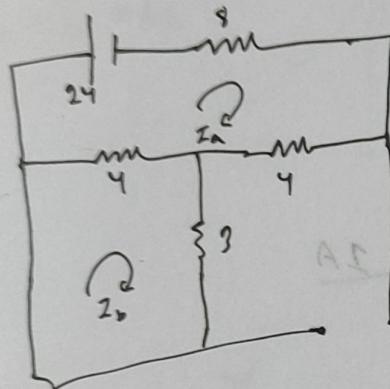

$$24 + 8Z_a + 4Z_a + 4(Z_a - Z_b) = 0$$

$$\Rightarrow 24 + 16Z_a - 4Z_b = 0$$

$$\Rightarrow 4Z_a - Z_b = -6 \quad \dots \textcircled{1}$$

$$-4(Z_a - Z_b) - 3Z_b = 0$$

$$\Rightarrow -4Z_b + 4Z_a - 3Z_b = 0$$

$$\Rightarrow 7Z_b - 4Z_a = 0 \quad \dots \textcircled{2}$$

① + ②,


$$4Z_a - Z_b = -6$$

$$-4Z_a + 7Z_b = 0$$

$$6Z_b = -6$$

$$Z_b = -1A$$

$$\therefore A Z_a'' = -1A$$

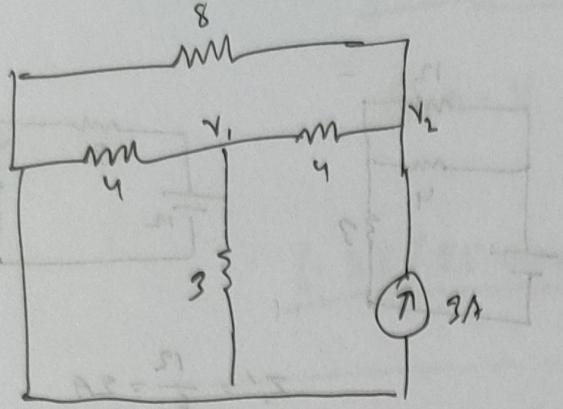

$$\frac{V_2 - V_1}{4} = \frac{V_1}{3} + \frac{V_1}{4}$$

$$\Rightarrow 3V_2 - 3V_1 = 4V_1 + 3V_1$$

$$\Rightarrow 3V_2 = 10V_1$$

$$\Rightarrow V_2 = \frac{10}{3}V_1$$


$$3 = \frac{V_2}{8} + \frac{V_2 - V_1}{4}$$

$$\Rightarrow 24 = V_2 + 2V_2 - 2V_1 + 8V_1 = 24$$

$$\Rightarrow -2V_1 + 3V_2 = 24$$

$$\Rightarrow -2V_1 + 3 \cdot \frac{10}{3}V_1 = 24 \quad \rightarrow I''' = \frac{3}{3} = 1A$$


$$-2V_1 + 10V_1 = 24$$

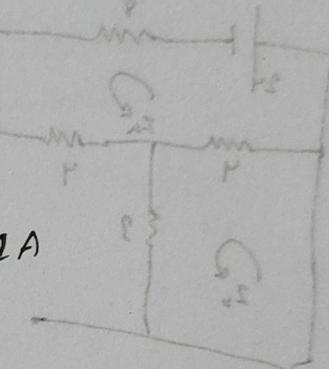


$$I = I' + I'' + I'''$$

$$= 2 - 1 + 1 = 2A$$

L-28/03.06.2023/

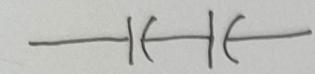

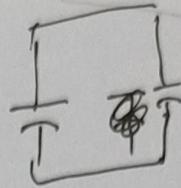
$$C_T = \left(\frac{1}{C_1} + \frac{1}{C_2} \right)^{-1}$$



$$C_T = C_1 + C_2$$



series series

$$L_T = L_1 + L_2$$


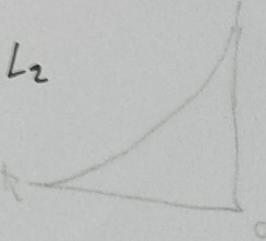


RC


Charging:

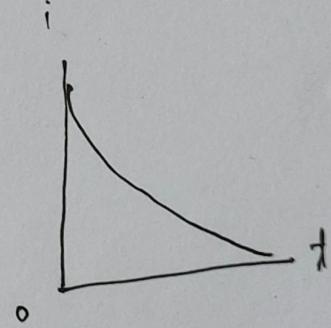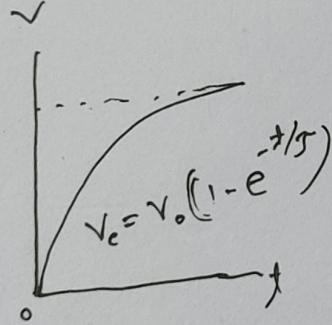



Discharging:

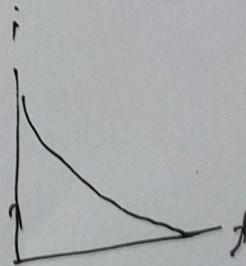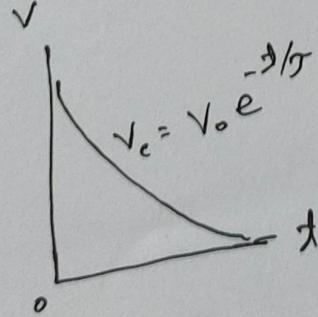

✓ 2023. 30. 26) 13-1

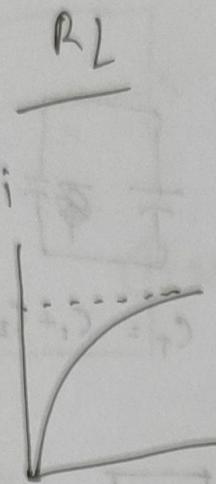

Charging:

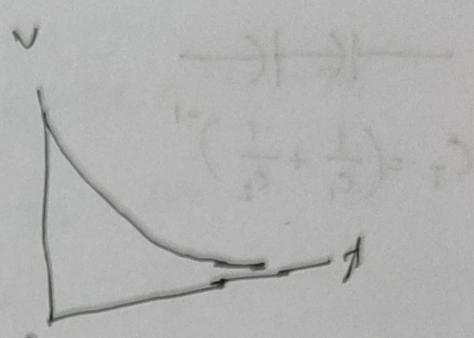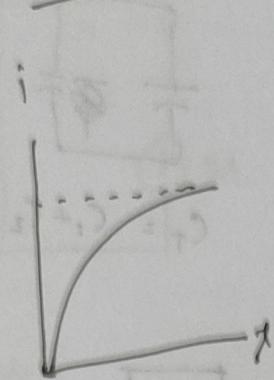

Discharging:

