

Gauss' Law


$$\textcircled{1} \quad \Phi_E = \oint \vec{E} \cdot d\vec{A} = \frac{q_{\text{enc}}}{\epsilon_0}$$

$$\Phi_E = \oint \vec{E} \cdot d\vec{A} = \frac{q}{\epsilon_0} \quad \dots \textcircled{i}$$

$$E_0 A = \frac{q}{\epsilon_0}$$

$$\therefore E_0 = \frac{q}{\epsilon_0 A} \quad \dots \textcircled{ii}$$

ii) With dielectric:

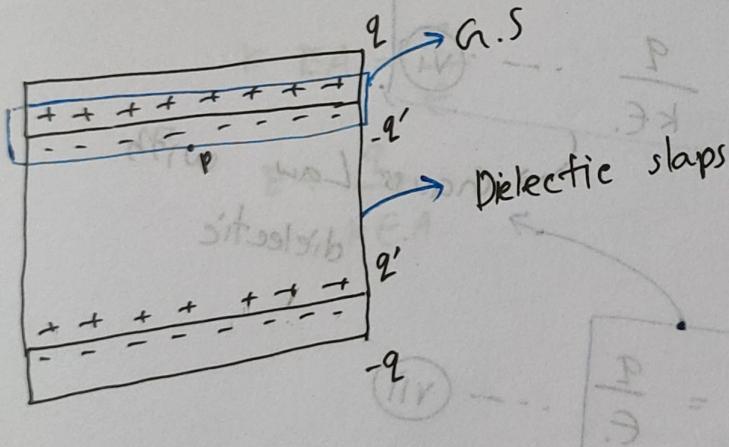

Gauss' Law:

$$\Phi_E = \oint \vec{E} \cdot d\vec{A} = \frac{q_{\text{enc}}}{\epsilon_0}$$

$$\Phi_E = \oint \vec{E} \cdot d\vec{A} = \frac{q - q'}{\epsilon_0} \quad \dots \textcircled{iii}$$

$$EA = \frac{q - q'}{\epsilon_0}$$

$$(E_0 - E')$$

$$E = \frac{q-q'}{\epsilon \cdot A} \quad \dots \dots \textcircled{iv}$$

$\otimes \quad \frac{E_0}{E} = k$

$$\therefore E = \frac{E_0}{k}$$

$$E = \frac{q}{k \cdot A} = \frac{q-q'}{\epsilon \cdot A}$$

$$\frac{q}{k} = \cancel{q-q'} \quad \textcircled{v}$$

From - iii,

$$\Phi_E = \oint \vec{E} \cdot d\vec{A} = \frac{q}{k\epsilon} \quad \textcircled{vi}$$

Gauss Law in

Law with
dielectric

$$\Rightarrow k \oint \vec{E} \cdot d\vec{A} = \frac{q}{\epsilon} \quad \textcircled{vii}$$

General form of Gauss' Law
(With or Without)

Prove:

① Without dielectric,

$$k = 1, \text{ Electric Field} = E.$$

$$\Phi_E = \oint \vec{E} \cdot d\vec{A} = \frac{q}{\epsilon_0}$$

$$E \cdot A = \frac{q}{\epsilon_0}$$

$$E = \frac{q}{\epsilon_0 A}$$

② With dielectric,

$$k = k, \text{ Electric Field}, E = E_0 - E'$$


$$k \oint \vec{E} \cdot d\vec{A} = \frac{q}{\epsilon_0}$$

$$k \cdot EA = \frac{q}{\epsilon_0}$$

$$E = \frac{q}{k \epsilon_0 A}$$

Voriderm™ IV Injection
Voriconazole 200 mg

$k_i = \frac{1}{2}$

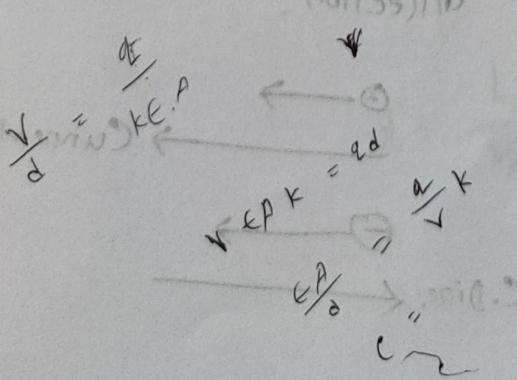


L-19 / 03. 04. 2023 /

Midterm Exam

L-19 / 05. 03. 2023 /
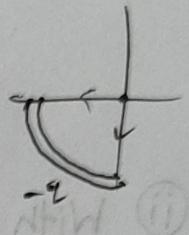
$$E = \int_0^{\pi/2} dE \cos\theta + \int_0^{\pi/2} dE \sin\theta$$




Example : On dielectric (Text Book) - Assignment.

⊗ Resistance and Current:

⊗ Current:

$$i = \frac{q}{t}$$

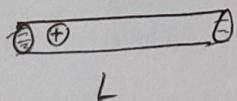

$$A = \pi R^2$$

$$V = A \cdot L$$

$$\therefore q = i t$$

$$dq \rightarrow dt ; i = \frac{dq}{dt}$$


$$\therefore \int dq = \int idt$$

$$\Rightarrow q = it$$

direction :




Current direction

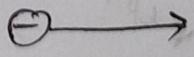

C. Direc: ←

(*)

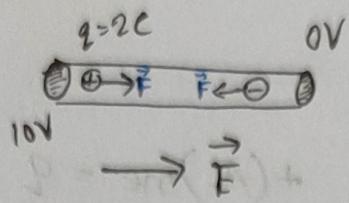


$$V = Ed$$

$$E = \frac{V}{d} = \frac{10}{2} = 5 \text{ V/m}$$

$$\vec{F} = q \vec{E} = \frac{q}{k}$$

(*)

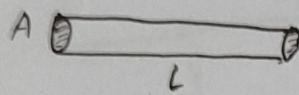


$$R \propto L$$

$$R \propto \frac{1}{A}$$


$$R \propto \frac{L}{A} = i$$
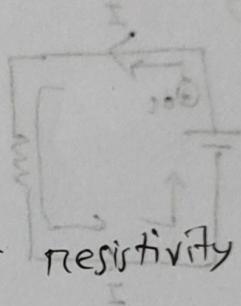
$$R = \rho \frac{L}{A}; \quad \rho = \text{resistivity}$$




(*)

$$(A, L)$$

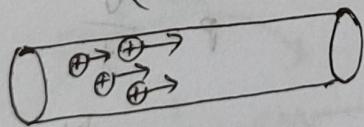

$$i = \frac{q}{t}$$

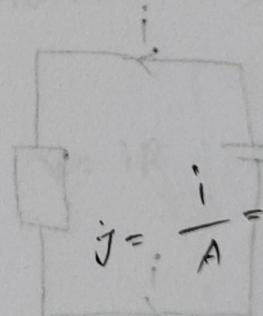

$$j = \frac{i}{A} = \text{current density}$$

$i = V$
 $iV = q$
 $iR = q$
 $iR = q$

$v_d = \text{drift velocity}, n = \text{number density of the electrons}$


$$A = \frac{L}{v_d}$$

$$IV = \frac{vb}{tb} = q$$

Voriderm™ IV Injection
Voriconazole 200 mg

(X)

$$bE = V$$

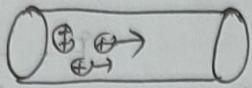

V_d

$$38 - p$$


~~Q = nAe~~

$$+ (AL)n e = Q$$

$$i = \frac{q}{t} = \frac{ALne}{\frac{L}{V_d}} = Ane V_d$$

Power:


10V

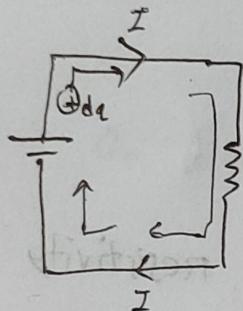

$$dq \rightarrow dt$$

$$i = \frac{dq}{dt} \therefore dq = i dt$$

$$\therefore \frac{q}{A} = R$$

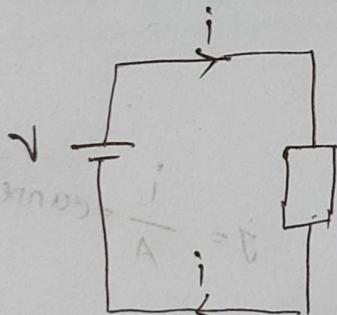

$$(J, A) \quad P = \frac{V}{I}$$

$$P = \frac{dU}{dt}$$

$$V = IR \quad P = VI$$

$$dU = V dq$$

$$\frac{dU}{V} = i dt$$

$$\therefore P = VI$$

Power

$$P = \frac{dU}{dt} = VI$$

$$V = IR$$


$$P = VI$$

$$P = iRi$$

$$\boxed{P = i^2 R}$$

L-20 / 10.04.2023

Circuits!

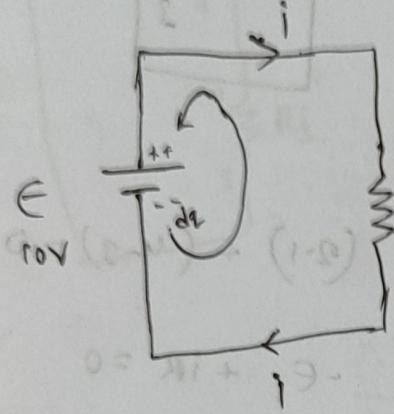

$$i = \frac{dq}{dt}$$

$$dq = dt$$

$$0 = (E - iR) + \frac{1}{C} \cdot \frac{1}{T}$$


$$\begin{aligned} dq &\rightarrow dw \\ \rightarrow \frac{dw}{dq} &= i \text{ per unit} \end{aligned}$$

$$0 = q_i - \rightarrow +$$

④ Charging RC circuit

$$q_i = \rightarrow$$

= $E - EMF$ (Electro motive Force)

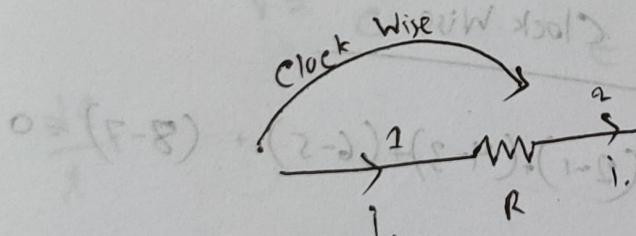


$$V = iR$$

$$0 = (E - iR) + (iR) + (iR) + \rightarrow$$


$$V_2 - V_1 = -iR$$

Kirchoff's Law

i) KCL:

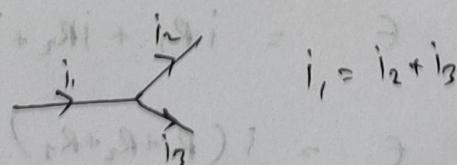

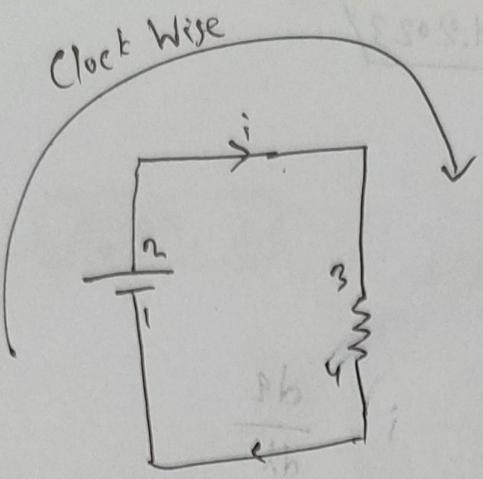ii) KVL: $\sum V_i = 0 \Rightarrow V_1 + V_2 = 0$





$$(2-1) + (4-3) = 0$$

$$+ \frac{E}{R} + (-iR) = 0$$

$$+ E - iR = 0$$

$$E = iR$$

$$i = \frac{E}{R}$$

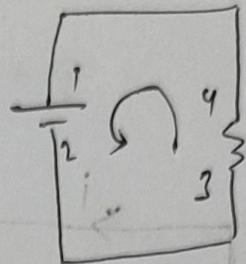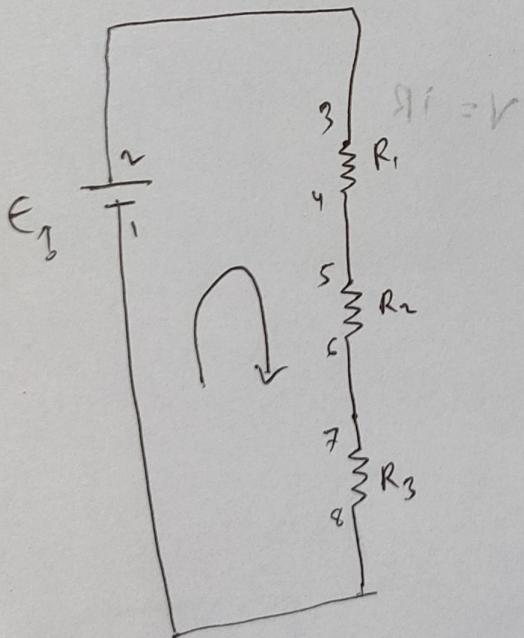

$$(2-1) + (4-3) = 0$$

$$-E_1 + iR = 0$$

$$E = iR$$

$$i = \frac{E}{R}$$

$$\text{time avg } \frac{wb}{pb} \leftarrow$$

Clock Wise

$$(2-1) + (4-3) + (6-5) + (8-7) = 0$$


$$E + (-iR_1) + (-iR_2) + (-iR_3) = 0$$

$$E - iR_1 - iR_2 - iR_3 = 0$$

$$E = iR_1 + iR_2 + iR_3$$

$$E = i(R_1 + R_2 + R_3)$$

$$i = \frac{E}{R_1 + R_2 + R_3}$$

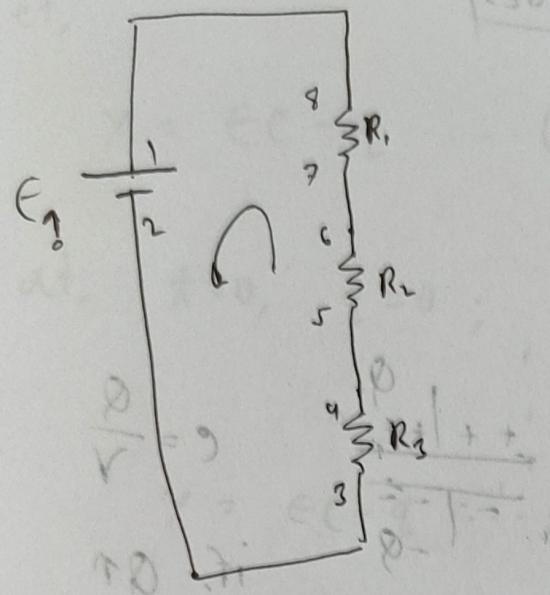

Anti Clock Wise

$$(2-1) + (4-3) + (6-5) + (8-7) = 0 \quad (i)$$

$$E + iR_3 + iR_2 + iR_1 = 0$$


$$E = -i(R_1 + R_2 + R_3)$$

$$i = \frac{E}{R_1 + R_2 + R_3}$$

IV

Induced = ?


$$\frac{dV}{dt} = V$$

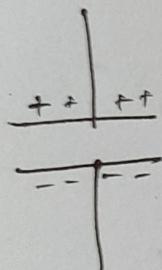

$$C = \left| \frac{\Phi}{V} \right|$$

① Changing RC circuit

$$r_b = \frac{\Phi}{Q}$$

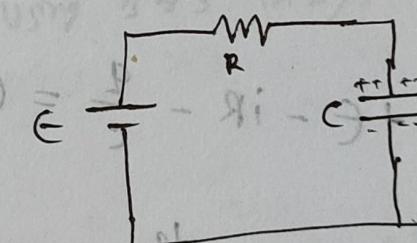

$$t = 0$$

$$q = 0$$

$$t \uparrow -q \uparrow$$

$$i = \frac{dq}{dt}$$

$$i = \frac{P}{V}$$

$$V = \frac{Q}{C} = 0$$

at point (P) separation


$$+E - iR - \text{loss} \frac{Q}{C} = 0 \rightarrow \text{point}$$

$$i = \frac{P}{V} = \frac{P}{V} - \rightarrow$$

$$(ii) \quad \frac{P}{V} = \frac{P}{V}$$

L-21 / 12.04.2023 /

i) Changing RC Circuit:

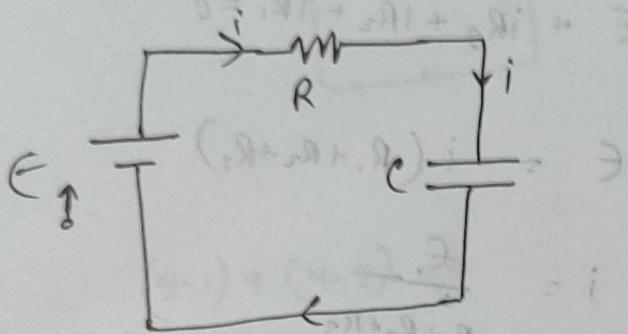

$$\frac{+ + | + +}{- - | - -} \quad q$$

$$c = \frac{q}{v}$$

if: $c \propto t$

$$\Rightarrow v \propto t$$

$\therefore c = \text{constant}$

$$\text{at, } t=0, q=0; v = \frac{q}{c} = 0$$

time t voltage v charge q

$t \uparrow, q \uparrow; v \uparrow$

$$v = \frac{q}{c}$$

$$\left| \frac{q}{v} \right| = \text{const}$$

$$\frac{q}{v} = \frac{\text{const}}{t}$$

$$+E - iR - \frac{q}{c} = 0; i = \frac{dq}{dt}$$

$$0 = E - \frac{dq}{dt} R - \frac{q}{c} = 0 \quad \text{--- (i)}$$

This is a differential equation of change (q) in time t .

$$E - \frac{q}{c} = -\frac{dq}{dt} R$$

$$\frac{c-q}{RC} = \frac{dq}{dt} \quad \text{--- (ii)}$$

Let,

$$y = EC - q \dots \text{iii}$$

$$\text{at, } t=0, q=0; \quad \text{iv} = EC = y_0 \dots \text{iv}$$

$$y = EC - q \dots \text{iii}$$

$$\frac{dy}{dt} = 0 - \frac{dq}{dt}$$

$$-\frac{dy}{dt} = \frac{dq}{dt} \dots \text{v}$$

$$\frac{y}{RC} = -\frac{dy}{dt} \quad (\text{using 3 & 5 in 2})$$

$$\Rightarrow \frac{dt}{RC} = \frac{-dy}{y}$$

$$\Rightarrow \frac{dy}{y} = -\frac{dt}{RC}$$

$$\Rightarrow \int \frac{dy}{y} = -\int \frac{dt}{RC} \quad \begin{matrix} \text{constant of integration} \\ \text{to evaluate} \end{matrix}$$

$$\ln y = -\frac{t}{RC} + k \dots \text{vi}$$

at $t=0$, $y = \epsilon c = y_0$

$$\ln y_0 = 0 + k$$

$$\textcircled{vi} \quad \ln c = -\frac{t}{RC} + \ln y_0 \quad \textcircled{vii} \quad 0 = p, 0 = t, f_n$$

$$\therefore \ln y = -\frac{t}{RC} + \ln y_0$$

$$\ln y - \ln y_0 = -\frac{t}{RC}$$

$$\ln \left(\frac{y}{y_0} \right) = -\frac{t}{RC}$$

$$\therefore \frac{y}{y_0} = e^{-\frac{t}{RC}}$$

$$y = y_0 \left(e^{-\frac{t}{RC}} \right)$$

$$\epsilon c - q = \epsilon c e^{-\frac{t}{RC}} \quad (\text{using } 3 \& 4)$$

$$\epsilon c - \epsilon c e^{\frac{t}{RC}} = q$$

$$q(t) = \epsilon c \left(1 - e^{-\frac{t}{RC}} \right)$$

$$\frac{q}{\epsilon c} = \frac{1 - e^{-\frac{t}{RC}}}{e^{-\frac{t}{RC}}} \quad \textcircled{viii}$$

$$\frac{q}{\epsilon c} = \frac{1 - e^{-\frac{t}{RC}}}{e^{-\frac{t}{RC}}} = \frac{e^{\frac{t}{RC}} - 1}{e^{\frac{t}{RC}}} = e^{\frac{t}{RC}} - 1$$

Solution of equation - 1

$$\frac{q}{\epsilon c} = e^{\frac{t}{RC}} - 1 = \frac{q}{\epsilon c} \left(1 + \frac{k}{\epsilon c} \right) \quad \textcircled{ix}$$

$$1 + \frac{k}{\epsilon c} = \frac{1}{e^{\frac{t}{RC}} - 1} \quad \textcircled{x}$$

$$E - \frac{dq}{dt} R - \frac{q}{C} = 0 \quad \text{--- (i)}$$

$$q(t) = EC \left(1 - e^{-\frac{t}{RC}}\right) \quad \text{--- (ii)}$$

$\otimes t=0;$

$$q(0) = EC \left(1 - e^0\right) \quad (\text{initial charge})$$

$$= EC (1-1) = 0$$

$\otimes t \rightarrow \infty$

$$t=\infty,$$


$$q(\infty) = EC \left(1 - e^{-\frac{\infty}{RC}}\right)$$

$$= EC (1-0) \quad (\text{maximum charge at } \infty \text{ time.})$$

$$= EC \rightarrow \text{Maximum charge at } \infty \text{ time.}$$

\otimes

$$E_{\uparrow} = 100V$$

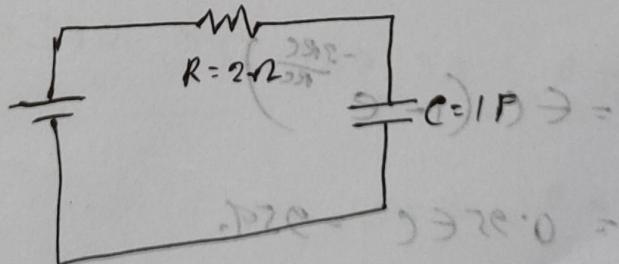

$$\otimes q(\infty) = EC = 100 \cdot 1 = 100 \text{ coul.}$$

$$q(RC) = EC \left(1 - e^{-\frac{RC}{RC}}\right) \quad (\text{at } t=RC)$$

$$= EC \left(1 - e^{-1}\right) = 0.63 EC \quad \Rightarrow 63 \text{ coul.}$$

$$= 63 \text{ coul.}$$

Voriderm™ IV Injection
Voriconazole 200 mg

$$\textcircled{X} \quad 1 \text{RC time} = \frac{C}{R} = \frac{1}{2} \text{ sec} \rightarrow$$

$R = 2$
 $C = 1$

$$RC = 2 \cdot 1 = 2 \text{ sec} = (k) P$$

$RC = \text{Time constant}$

$$\therefore Q(1\text{RC}) = 0.63 \times 100 \times 1$$

$$= 63 \text{ coul. } (2 \text{ sec}) \rightarrow = (6) P$$

$$\textcircled{X} \quad t = 2 \text{ RC}$$

$$Q(2\text{RC}) = EC \left(1 - e^{-\frac{2\text{RC}}{RC}} \right)$$

$$= EC \left(1 - e^{-2} \right)$$

$$= 0.86 EC = 86\% \text{ of } Q_{\text{max}} \rightarrow = (86) P$$

init $\Rightarrow 86 \text{ coul. } (4 \text{ sec}) \rightarrow$

$$\textcircled{X} \quad t = 3 \text{ RC}$$

$$Q(3\text{RC}) = EC \left(1 - e^{-\frac{3\text{RC}}{RC}} \right)$$

$$= 0.95 EC = 95\%$$

$$= 95 \text{ coul. } (3 \text{ sec}) \rightarrow = (95) P$$

$$\textcircled{X} \quad t = 5 \text{ RC}$$

$$Q(5\text{RC}) = EC \left(1 - e^{-\frac{5\text{RC}}{RC}} \right)$$

$$= 0.9932 EC \rightarrow 0.9932 \times 100 \rightarrow = (99.32) P$$

$$= 99.32 \text{ coul. } (10 \text{ sec})$$

$$\textcircled{X} \quad t = 10RC$$

1808.10.01 18-1

$$q(10RC) = \cancel{0.9999} \times 0.9999 \times C = 99.99 \text{ A.}$$

(charge RC circuit)

$$= 99.99 \text{ coul. (20 sec)}$$

\textcircled{X} In every RC time capacitor charged 63% of empty space. That's why RC is a time constant for a capacitor.

$$RC = 2.4 = 2 \text{ sec}$$

$$0 = \frac{P}{J} - q_i \rightarrow$$

$$10RC = 20 \text{ sec}$$

$$0 = \frac{P}{J} - q \frac{Pb}{kb} \rightarrow$$

$$20 \text{ sec} \quad 99.99 \quad \rightarrow \left(\frac{20}{99.99} - 1 \right) 33 = P$$


$$0 = P, \quad 0 = t$$

$$P = 0.03 EC, \quad t = 20 \text{ sec}$$

$$P = 0.03 \times 1000 = 30 \text{ W}, \quad t = 20 \text{ sec}$$

L-22 / 17.04.2023 /

⊗ Changing RC Circuits:

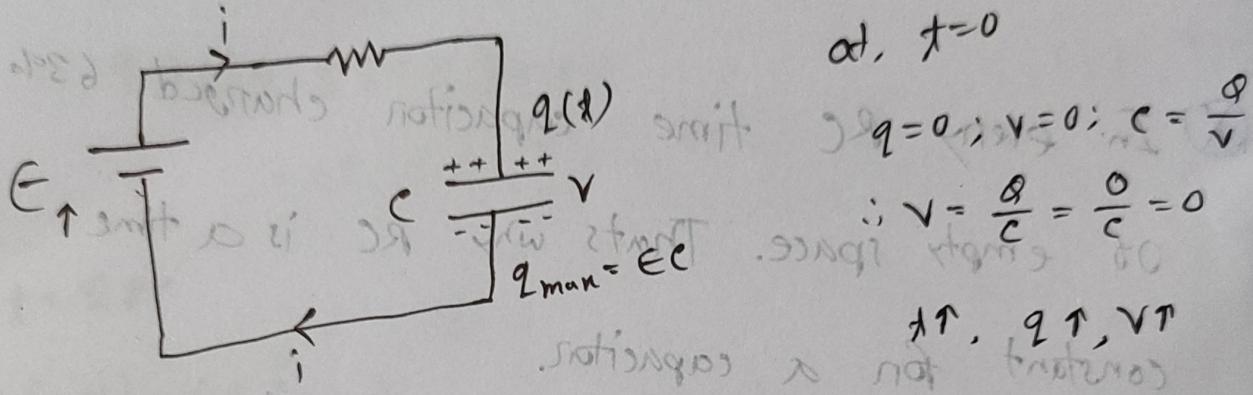

$$E - iR - \frac{q}{C} = 0$$

$$E - \frac{dq}{dt} R - \frac{q}{C} = 0$$

$$q = EC \left(1 - e^{-t/RC} \right)$$

⊗ $t=0, RC, 2RC, 5RC, 10RC, \infty$

$$t=0, q=0$$

$$t=RC, q = 0.63 EC$$

$$t=\infty, q = EC = q_{\max}$$

Example:

$$E = 100 \text{ Volts} \quad q_{\max} = E C = 100 \times 1 = 100 \text{ Coul} \quad \text{(i)}$$

$$R = 2 \Omega$$

$$C = 1 \text{ F}$$

$$t = \infty, V = 100 \text{ (stationary state at } 90^\circ)$$

$$t = 5RC, q = 0.9932 EC$$

$$= 99.32 \text{ C. V}$$


$$t = 10RC, q = 0.9999 EC$$

$$V = 99.99 \text{ V}$$

$$RC = 2 \cdot 1 = 2 \text{ sec}$$

$$10RC = 20 \text{ sec}$$

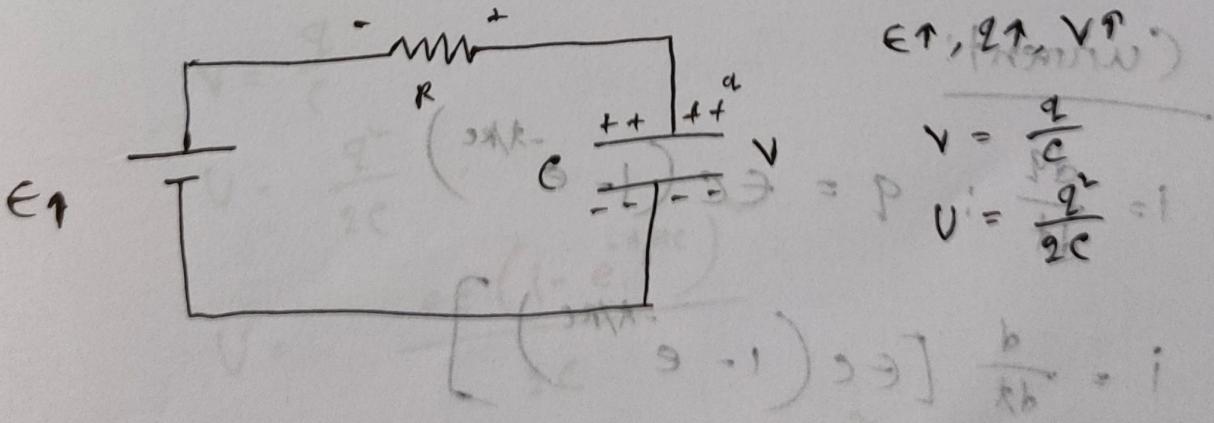in 20 sec $99.991 \Rightarrow q_{\max}$ $0 = (1-1) \Theta =$
 $\approx 100 \text{ C.} \quad \Theta = \text{the capacitor}$



$$E \uparrow, q \uparrow, V \uparrow \quad \text{(iii)}$$

$$V = \frac{q}{C}$$

$$V_i = \frac{q^2}{2C} = 1$$

i) Charge $q = \epsilon C (1 - e^{-\frac{t}{RC}})$

ii) Potential Difference between the plates or the

Capacitor (Voltage) V :

$$V = \frac{q}{C} = \frac{\epsilon C (1 - e^{-\frac{t}{RC}})}{C} = \epsilon (1 - e^{-\frac{t}{RC}})$$

$$V = \epsilon (1 - e^{-\frac{t}{RC}}) = V_c$$

$$t = 0,$$

$$V = \epsilon (1 - e^{\frac{0}{RC}})$$

$$= \epsilon (1 - 1) = 0$$

$$t = \infty, V = \epsilon \cdot 0 = 0$$

$$V = \epsilon (1 - e^{-\frac{\infty}{RC}})$$


$$= \epsilon \cdot 1$$

iii) Current:

$$i = \frac{dq}{dt} ; q = \epsilon C (1 - e^{-\frac{t}{RC}})$$

$$i = \frac{d}{dt} [\epsilon C (1 - e^{-\frac{t}{RC}})]$$
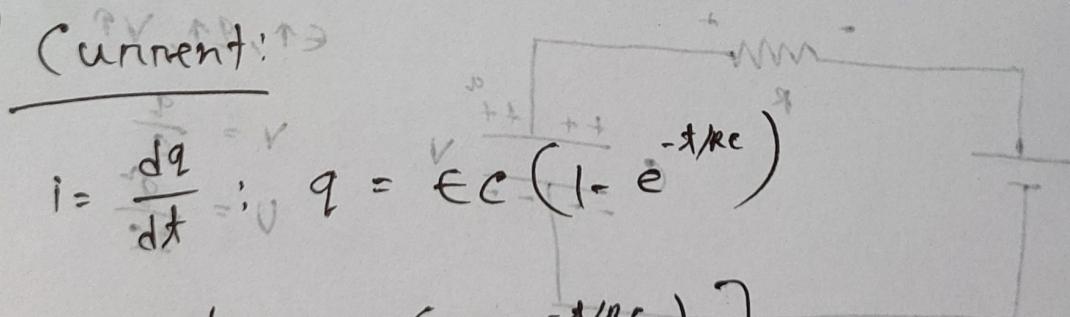
$$i = \epsilon C \left[0 - \frac{e^{-\frac{t}{RC}}}{-RC} \right]$$



$$i = \epsilon C \left[-\frac{e^{-t/RC}}{RC} \right]$$

$$i = \frac{\epsilon}{R} e^{-t/RC}$$

Now, $t=0, RC, 2RC, 3RC \dots$

$$i = ?$$

$$t = 10RC; \quad i = \frac{\epsilon}{R} e^{-10\frac{RC}{RC}}$$

$$i = \frac{\epsilon}{R} e^{-10} = 4.5 \times 10^{-5} \frac{\epsilon}{R}$$

$$i = \frac{100}{2} = 50 A$$

iv) Stored Energy in the capacitor:

$$V = \frac{Q}{C}$$

$$V = \frac{Q^2}{2C}$$

$$V = \frac{\epsilon C (1 - e^{-t/RC})}{2C}$$

$$V = \frac{1}{2} C \epsilon^2 (1 - e^{-t/RC})^2$$

$$t=0; V=0 \quad \left[\begin{array}{l} t=0, R_C, 2RC, C \rightarrow \infty \\ V=? \end{array} \right]$$

$$t=\infty; V = \text{max}$$

$$V = i$$

$$\frac{E}{R} = i \quad (10 \text{ V} - 1)$$

$$\frac{10}{2} = 0.2 \times 10^3 \quad i =$$

$$A_{02} = \frac{100}{5} = i$$

$\epsilon(i)$: Solution for current in the circuit

(ii) Current

$$\frac{V}{R} = i$$


$$\frac{V}{R} = i$$

$$\frac{(1-i)}{2} = i$$

$$\left(\frac{1}{2} - \frac{i}{2} \right) = i$$

L-23 / 26.04.2023 /

① Changing RC circuit:

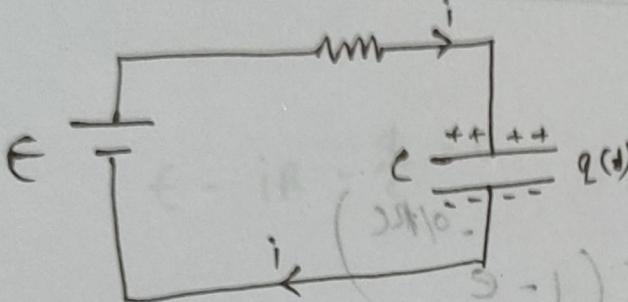

$$t=0, Q=0$$

$$t \uparrow, Q \uparrow$$

$$V = V_C \uparrow$$

$$f=\infty$$

$$Q = EC$$

$$= Q_{\max}$$

$$D=R$$

$$\text{① } Q = EC \left(1 - e^{-t/RC}\right)$$

$$\text{② } V = V_C = E \left(1 - e^{-t/RC}\right)$$

$$\text{③ } i = \frac{E}{R} e^{-t/RC}$$

④ Stored energy in the capacitor:

$$U = \frac{Q^2}{2C}; \quad Q = EC \left(1 - e^{-t/RC}\right)$$

$t \uparrow, U \uparrow,$

$$U = \frac{Q^2}{2C} =$$

$$\left(EC \left(1 - e^{-t/RC}\right) \right)^2 / 2C$$

$$V = V_C = V_E = \frac{E \tilde{C} (1 - e^{-t/RC})}{2C}$$


$$\therefore V(t) = \frac{1}{2} E \tilde{C} (1 - e^{-t/RC})$$

$$t=0, V(0)=?$$

$$t=0, V(0)=?$$

$$t=0, V(0)=?$$
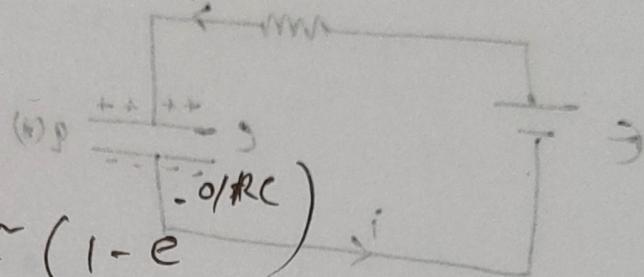
$$V(0) = \frac{1}{2} \cdot C \cdot E \tilde{C} (1 - e^{-0/RC})$$



$$= \frac{1}{2} C \cdot E \cdot 0 = 0 \Rightarrow = p \quad \textcircled{i}$$

During Charging:


$$\textcircled{i} \text{ Charge } q = E \tilde{C} (1 - e^{-t/RC}) \Rightarrow i$$

$$\textcircled{ii} \text{ Voltage } V = V_C = E (1 - e^{-t/RC})$$

$$\textcircled{iii} \text{ Current } i = \frac{E}{R} \cdot e^{-t/RC}$$

$$\textcircled{iv} \text{ Energy } U = V_C = V_E = \frac{1}{2} C E^2 (1 - e^{-t/RC})^2$$

Charging

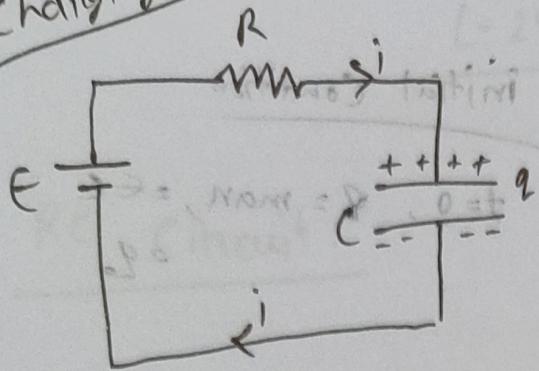

$$t=0, q=0$$

$$t \uparrow, q \uparrow \Rightarrow + = +, - = - \Rightarrow q = k \cdot t$$


$$q = EC \left(1 - e^{-\frac{t}{RC}}\right)$$

$$t = \infty, q = EC \left(1 - e^{-\frac{\infty}{RC}}\right) = EC$$

$$q = EC = q_{\text{max}}$$

$$E - iR - \frac{q}{C} = 0$$

Discharging:

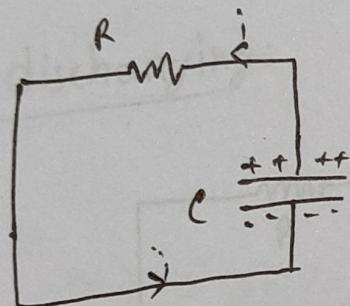

$$t=0, q = \frac{P_{\text{ini}}}{R} = EC$$

$$t \uparrow, q \downarrow$$

$$-iR - \frac{q}{C} = 0 \quad \text{--- (i)}$$

$$\left(-\frac{dq}{dt} R \right) - \frac{q}{C} = 0 \quad \text{--- (ii)}$$

(i) to natural

$$-\frac{dq}{dt} R = \frac{q}{C}$$

$$\int \frac{dq}{q} = - \int \frac{dt}{RC}$$

$$\ln q = -\frac{t}{RC} + K \quad \text{--- (iii)}$$

Voriderm™ IV Injection
Voriconazole 200 mg

~~K is a constant~~

~~on integral~~

Set, $t=0$, $q=q_0 = \epsilon C$ at $t=0$

$$\ln q_0 = 0 + k$$

$$\ln q_0 = k \quad \text{(iii)}$$

$$\ln q_0 = p = k$$


$$\therefore \ln q = -\frac{t}{RC} + \ln q_0 \quad 0 = \frac{p}{3} - q_i \rightarrow$$

$$\ln q - \ln q_0 = -\frac{t}{RC}$$

$$\ln \frac{q}{q_0} = -\frac{t}{RC}$$

$$\frac{q}{q_0} = e^{-t/RC}$$
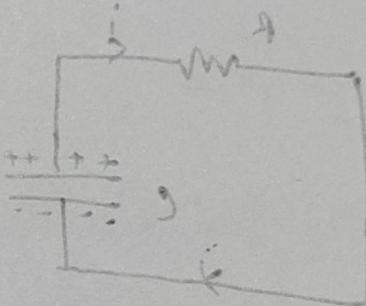
$$q = q_0 e^{-t/RC} \quad 0 = \frac{p}{3} - q_i \rightarrow$$



i) change:

$$q = \epsilon C e^{-t/RC} \quad \left| \begin{array}{l} t=0 \\ q=\epsilon C \end{array} \right. \quad \left(\frac{\epsilon b}{3} = q_0 \right)$$

solution of i)

$$t=0, q=\epsilon C = q_{\max}$$

$$\frac{p}{3} = \frac{\epsilon b}{k b}$$

$$t=RC, 2RC, \dots \infty$$

$$q = ?$$

$$\frac{k b}{3 b} = \frac{\epsilon b}{p}$$

initial condition

initial Condition

$$t=0, q=\max, \epsilon C \rightarrow$$

$$2q_0$$


~~prolonged time~~ \rightarrow $t \gg RC$

$$\frac{p}{3} + \frac{t}{25} = p_{\max}$$

L-24 / 03.05.2023

RC Circuit:

During Charging:

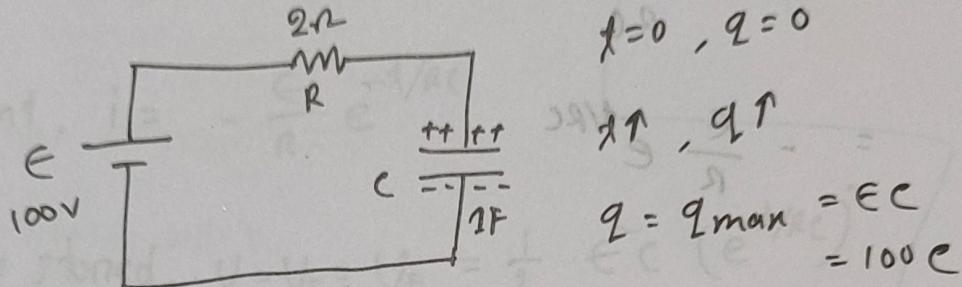


$$t=0, q=0$$

$$t \uparrow, q \uparrow$$

$$q = q_{\max} = EC \\ = 100\text{C}$$

During Discharging:

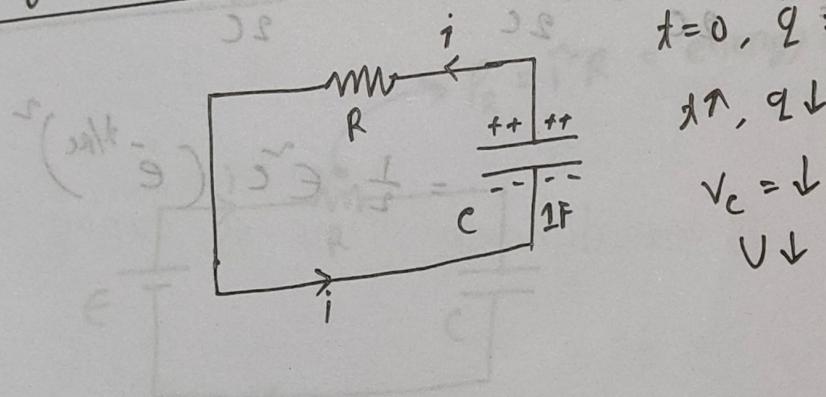

$$t=0, q=EC$$

$$t \uparrow, q \downarrow$$

$$V_C \downarrow \\ V \downarrow$$

i) $q(t) = q_0 e^{-t/RC}$

$$= EC e^{-t/RC}$$

ii) Potential Difference between the plates of the capacitor

(Voltage V_C)

$$V = V_C = \frac{q}{C} = \frac{EC e^{-t/RC}}{C} = EC e^{-t/RC}$$


iii Current:

$$i = \frac{dq}{dt}; q = \epsilon C e^{-Rt/RC}$$

$$= \frac{d}{dt} (\epsilon C e^{-Rt/RC})$$

$$= -\frac{\epsilon C e^{-Rt/RC}}{RC}$$

$$= -\frac{\epsilon}{R} e^{-Rt/RC}$$

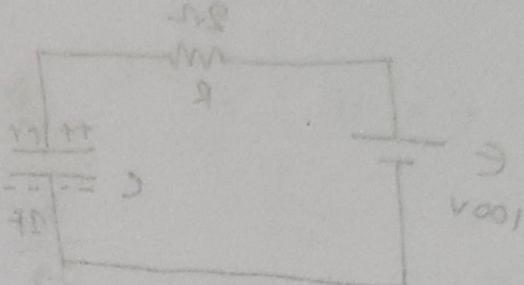

iv Energy stored in the capacitor:

$$U = U_C = U_E = \frac{Q^2}{2C} = \frac{q^2}{2C} = \frac{\tilde{\epsilon} C^2 e^{-2t/RC}}{2C}$$

$$= \frac{1}{2} \tilde{\epsilon} C (e^{-Rt/RC})^2$$

$$\Delta U_C = \tilde{\epsilon} C e^{-Rt/RC}$$


noticing that the initial difference between potential is zero

$$\Delta U_C = \frac{\tilde{\epsilon} C e^{-Rt/RC}}{C} = \frac{\tilde{\epsilon} C e^{-Rt/RC}}{C} = \frac{V_0 e^{-Rt/RC}}{C} = V = V_0 e^{-Rt/RC}$$

During Discharging:

- i) Charge, $q(t) = \epsilon C e^{-t/RC}$
- ii) Voltage, $V = V_C = \epsilon e^{-t/RC}$
- iii) Current, $i = -\frac{\epsilon}{R} e^{-t/RC}$
- iv) Energy stored, $V = V_E = \frac{1}{2} \epsilon^2 C (e^{-t/RC})^2$

More on energy:

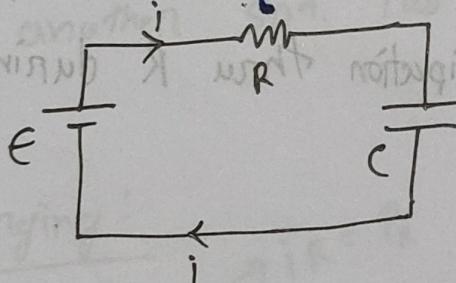

$$P_R = i^2 R = \text{energy consumed here}$$

$$V = VQ$$

- i) Supplied energy by the battery during charging process:

$$Q = Q_{max} = \epsilon C$$

Supplied energy by battery

$$V_E = \epsilon \cdot \epsilon C = \epsilon^2 C$$

(ii) Total stored energy in capacitor during charging

Process:

$$U_C = U = \frac{\tilde{q}}{2C} = \frac{\tilde{q}_{\text{max}}}{2C} = \frac{(\epsilon_0)}{2C}$$

$$= \frac{1}{2} \epsilon_0 C V$$

= Capacitor can store 50% of the supplied energy.

(iii) Energy loss thru the resistor R during charging

$$P = \frac{dU_R}{dt} = i^2 R = R i = R$$

= Power dissipation thru R during charging

$$= i^2 R dt$$

dU_R = energy loss in time dt

$$U_R = \int_{t=0}^{\infty} dU_R = \int i^2 R dt$$

$$U_R = \int_0^{\infty} \left(\frac{\epsilon_0}{R} e^{-t/RC} \right)^2 R dt$$


$$\Rightarrow U_R = \frac{\epsilon_0}{R} \cdot \frac{1}{2} C R^2 = \frac{1}{2} \epsilon_0 C V^2$$

$$\begin{aligned}
 &= \frac{\tilde{E}}{R} \cdot R \int_0^\infty e^{-2t/RC} dt \\
 &= \frac{\tilde{E}}{R} \int_0^\infty e^{-2t/RC} dt \\
 &= \frac{\tilde{E}}{R} \left[\frac{e^{-2t/RC}}{-\frac{2}{RC}} \right]_0^\infty = \frac{\tilde{E}}{R} \cdot \frac{1}{\frac{2}{RC}} = \frac{\tilde{E}RC}{2}
 \end{aligned}$$

$$\begin{aligned}
 &= \frac{\tilde{E}}{R} \cdot \frac{RC}{2} \cdot e^{-2t/RC} \Big|_0^\infty = \frac{\tilde{E}RC}{2} \cdot 0 = 0 \\
 &= -\frac{1}{2} \tilde{E}C \cdot (0-1) = \frac{1}{2} \tilde{E}C
 \end{aligned}$$

= another 50% loss during changing.

Discharging:

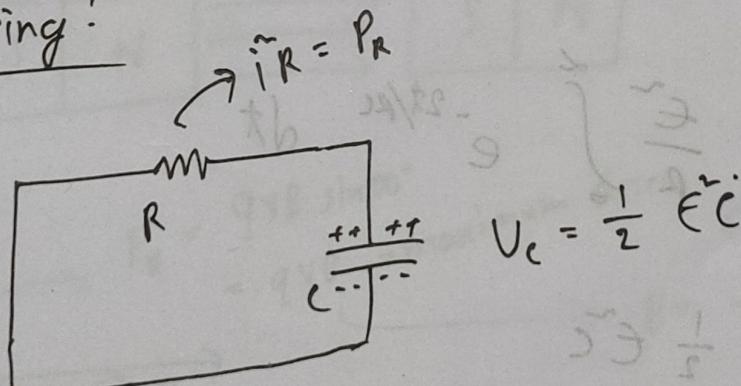

IV Energy loss during discharging thru the R.

$$P_R = \frac{dU_R}{dt} = \tilde{i}^2 R$$

$dU_R = \tilde{i}^2 R dt$ = energy loss in the time dt
during discharging.

$$U_R = \int dU_R = \int_0^\infty \tilde{i}^2 R dt$$

$$= \int_0^\infty \left(-\frac{\tilde{E}}{R} e^{-\frac{t}{RC}} \right) \tilde{R} dt$$

$$= \int_0^\infty \frac{\tilde{E}}{R} \cdot R \cdot e^{-\frac{2t}{RC}} dt$$



$$= \frac{\tilde{E}}{R} \int_0^\infty e^{-\frac{2t}{RC}} dt$$

$$= \frac{1}{2} \tilde{E} C$$

* After one cycle of charging and one cycle of discharging,
there is no remaining energy in the system.


L-25/08.05.2023/

✳ Magnetic Field (\vec{B})

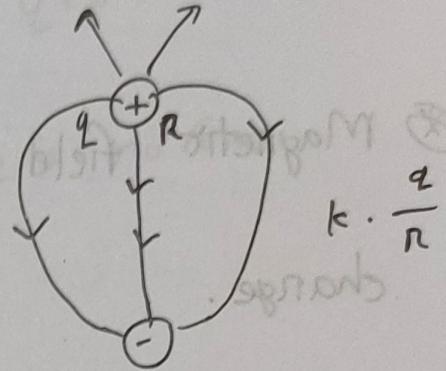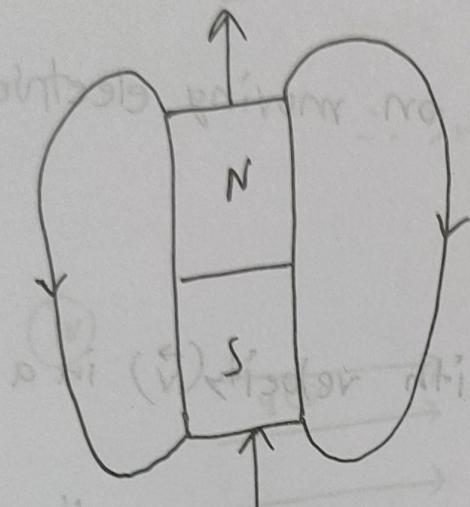

$\boxed{N} \rightarrow \times$ impossible

There is no isolated magnetic monopole.

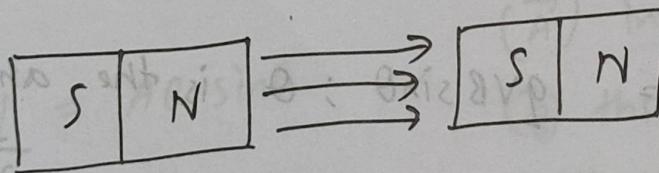



i)

$$F_B = qvB \sin 90^\circ$$

$= qvB$ = maximum force


$\theta = 90^\circ$

$$B = \frac{F_B}{qv}$$

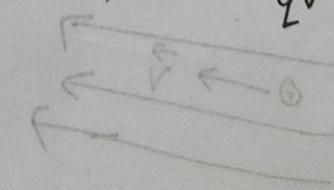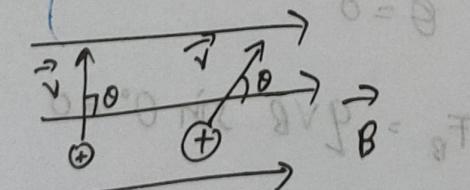


✳ A moving charge experiences magnetic force \vec{F}_B or

a ..

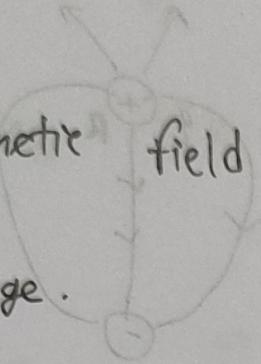

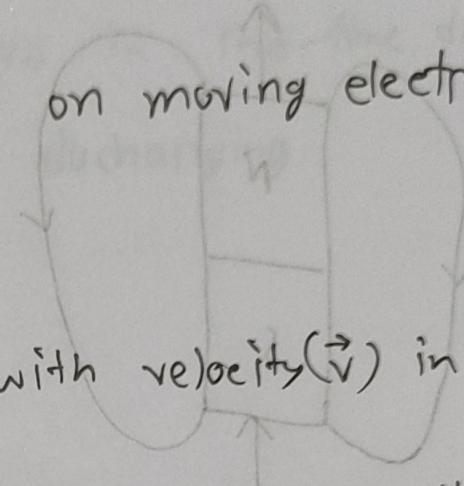✳ Magnetic field exerts force on moving electric charge.




✳ A charge (q) is moving with velocity (\vec{v}) in a magnetic field (\vec{B}) experiences a magnetic force (\vec{F}_B).

$$\vec{F}_B = q\vec{v} \times \vec{B}$$

$$|\vec{F}_B| = qvB \sin\theta ; \theta \text{ is the angle between } \vec{v} \text{ & } \vec{B}$$

ii

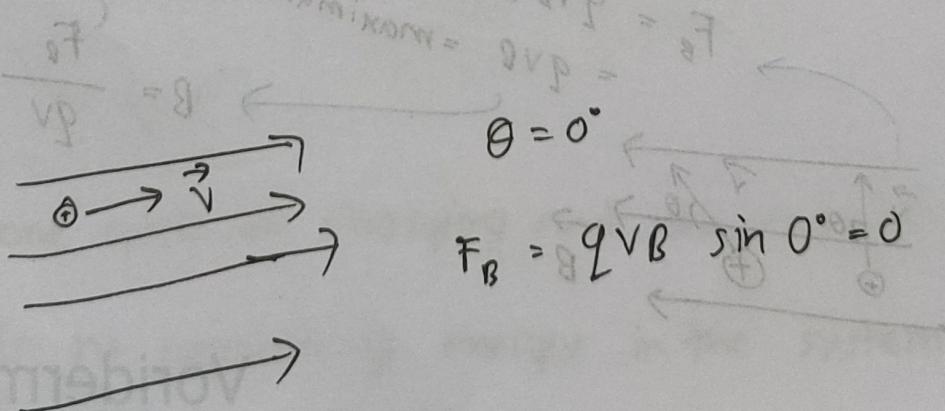

i

三

$$\theta = 180^\circ$$

$$F_B = QVB \sin 180^\circ = 0$$

\therefore In Parallel there is no force.

iv

$$\vec{F}_B = q\vec{v} \times \vec{B}$$

= 0

Cross Product:

 Right hand Rule:

$$\vec{C} = \vec{A} \times \vec{B}$$


$$|C| = AB \sin\theta$$

→ Sweep the 1st vector

(\vec{A}) into the second vector

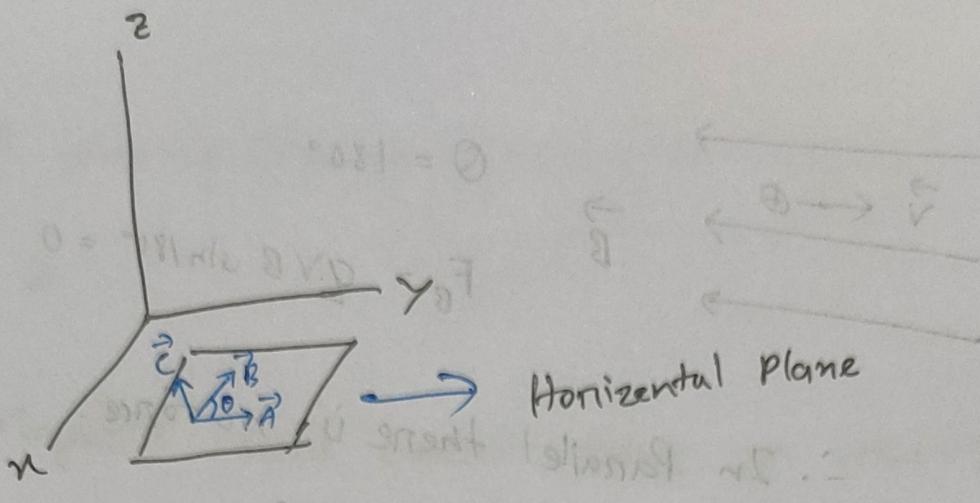
(B) thru smaller angle, ~~with~~
with the right hand

Direction of thumb is the direction of $\vec{C} = (\vec{A} \times \vec{B})$



$$\vec{C} = \text{up } (+z)$$

$$= AB \sin\theta$$

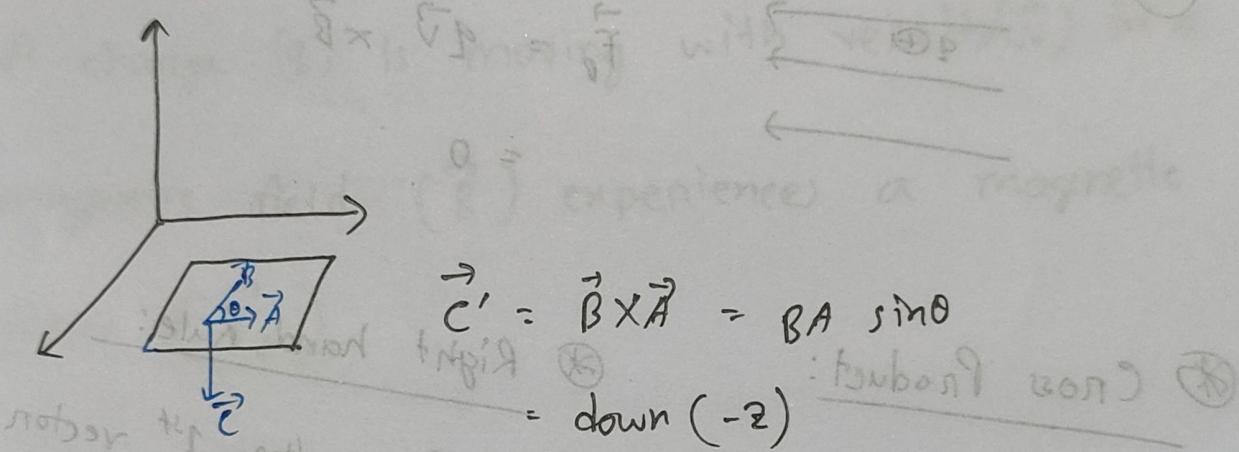


motor rotates anti-clockwise
current flows from left to right
cross product of current and magnetic field

$(\vec{B} \times \vec{A}) = 5$

$\vec{C} = \vec{A} \times \vec{B}$


out of the page

into the page

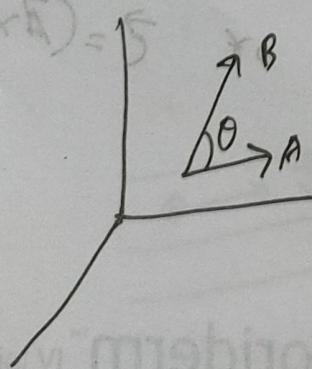

$$\vec{C} = \vec{A} \times \vec{B}$$

= towards me

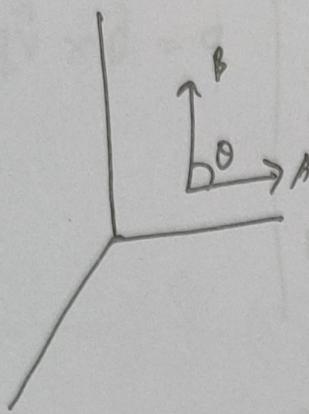


$$\vec{C} = \vec{B} \times \vec{A}$$

= from me

= \otimes

= Into the page
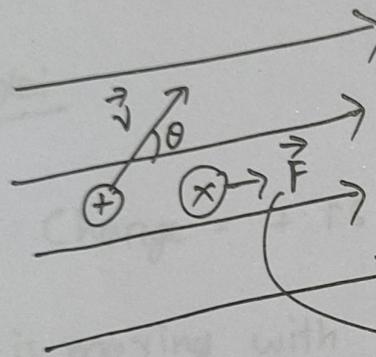
$$B_{\text{N}i \text{c} \text{S} \text{V} \text{P}} = 10^7$$



$$\vec{F}_B = q \vec{v} \times \vec{B}$$


$$(F_B) = qVB \sin\theta$$

into the page

$$(qB_A - qB_N) \hat{i} - (qB_A - qB_N) \hat{j} = \begin{vmatrix} \hat{i} & \hat{j} & \hat{k} \\ qB_A & qB_N & 0 \\ qB_A & qB_N & 0 \end{vmatrix} = \delta \times \vec{A}$$



$$(qB_A - qB_N) \hat{i} +$$

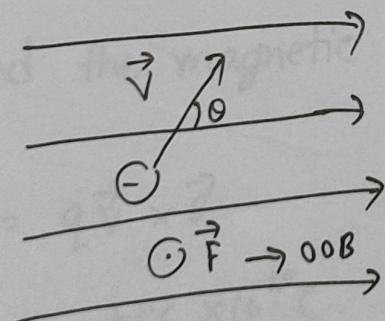

$$\vec{F}_0 = -q \vec{v} \times \vec{B}$$

= $-q$ (into the page)

= Out of the page

$$qB_A + qB_N + qB_0 = \delta$$