

<p>Spring 2023 EEE/ETE 141L Electrical Circuits-I Lab (Sec-19) Faculty: Mr. Saif Ahmed (SfA) Instructor: Md. Rabiul Karim Khan</p>
<p>Lab Report 05: Verification of Superposition Theorem.</p>

<p>Date of Performance: 02 April 2023</p> <p>Date of Submission: 09 April 2023</p>	<p><u>Group no.: 05</u></p> <ol style="list-style-type: none">1. Md. Mehedi Hossain - 19222256422. Sarith Chowdhury - 22125516423. Anindita Das Mishi - 22113646424. Joy Kumar Ghosh – 22114246425. Anisa Akter Meem - 2212538042
--	--

Experiment Name:- Verification of Superposition Theorem.

Objectives:- To verify Superposition Theorem.

Apparatus:-

- Breadboard
- Resistors ($1 \times 3.3 \text{ k}\Omega$, $1 \times 4.7 \text{ k}\Omega$, $1 \times 1 \text{ k}\Omega$)
- Digital multimeter
- DC power Supply
- wire.

Circuit Diagram:-

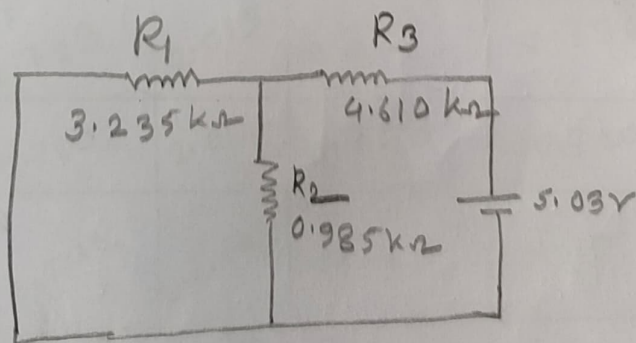
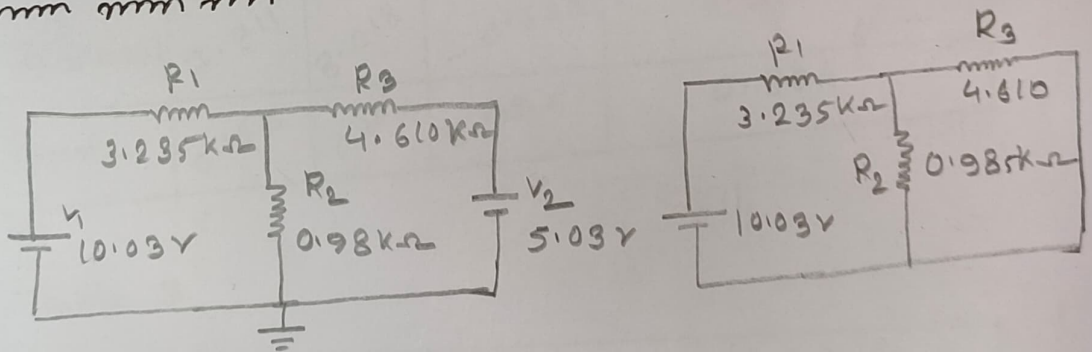


Table 1:

	I_1	I'_1	I''_1	$I'_1 + I''_1$
measured Data	2.780	2.040	0.740	2.780
Theoretical Data	2.761	2.043	0.719	2.762
Error	0.69%	0.15%	2.92%	0.65%

Table 2

	V_{R_1}	V'_{R_1}	V''_{R_1}	$V'_{R_1} + V''_{R_1}$
measured	7.300	8.010	-0.722	7.288
Theoretical	7.311	8.018	-0.708	7.310
Error	0.15%	0.10%	1.98%	0.304


Table 3

	V_{R_2}	V'_{R_2}	V''_{R_2}	$V'_{R_2} + V''_{R_2}$
measured	2.728	2.013	0.723	2.736
Theoretical	2.720	2.012	0.708	2.720
Error	0.29%	0.05%	2.12%	0.59%

Table-4

	V_{R3}	V'_{R3}	V''_{R3}	$V'_{R3} + V''_{R3}$
measured	2.375	-2.014	4.410	2.396
Theoretical	2.310	-2.012	2.310 4.322	2.310
Error	2.81%	0.10%	2.04%	3.72%

From circuit 1:-

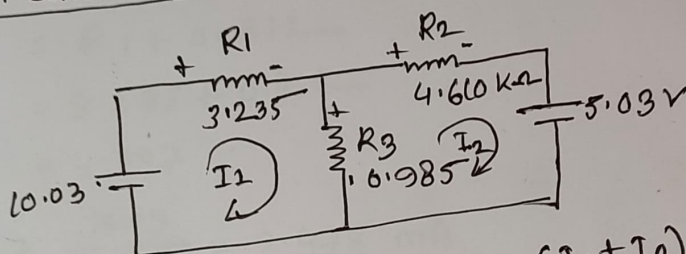

loop 1 $10.03 - 3.25 I_1 - 0.985 (I_1 + I_2) = 0$
 $\Rightarrow 10.03 - 3.25 I_1 - 0.985 I_1 - 0.985 I_2 = 0$
 $\Rightarrow -4.22 I_1 - 0.985 I_2 = -10.03$
 $4.22 I_1 + 0.985 I_2 = 10.03 \dots (i)$

loop 2: $5.03 - 4.610 I_2 - 0.985 (I_1 + I_2) = 0$
 $\Rightarrow 5.03 - 4.610 I_2 - 0.985 I_1 - 0.985 I_2 = 0$
 $0.985 I_1 + 5.595 I_2 = 5.03 \dots (ii)$

using calculator

$$I_1 = 2.260 \text{ mA}$$

$$I_2 = 0.501 \text{ mA}$$


$$I_{R3} = (2.260 + 0.501) \text{ mA} = 2.761 \text{ mA}$$

$$V_{R1} = 2.260 \times 3.235 = 7.34 \text{ V}$$

$$V_{R2} = 2.761 \times 0.985 = 2.720 \text{ V}$$

$$V_{R3} = 0.501 \times 4.610 = 2.310 \text{ V}$$

circuit 2:-

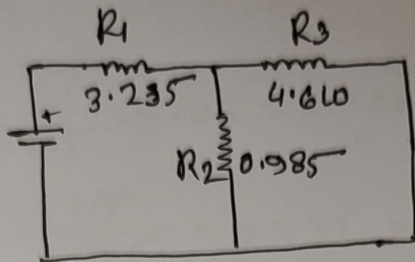

$$R_T = R_1 + (R_2 \parallel R_3)$$

$$= R_1 + \left(\frac{1}{\frac{1}{0.985} + \frac{1}{4.610}} \right)^{-1}$$

$$= R_1 + 0.812$$

$$= 3.235 + 0.812$$

$$= 4.047$$

$$I_S = \frac{10.03}{4.047} = 2.478 \text{ mA}$$


$$V_{R_1} = \frac{3.235}{4.047} \times 10.03 = 8.018 \text{ V}$$

$$V_{R_2} = \frac{0.812}{4.047} \times 10.03 = 2.012 \text{ V}$$

$$V_{R_3} = -V_{R_1} = -2.012 \text{ V}$$

$$I'_1 = \frac{0.812}{0.985} \times 2.478 = 2.043 \text{ mA}$$

circuit 3:-

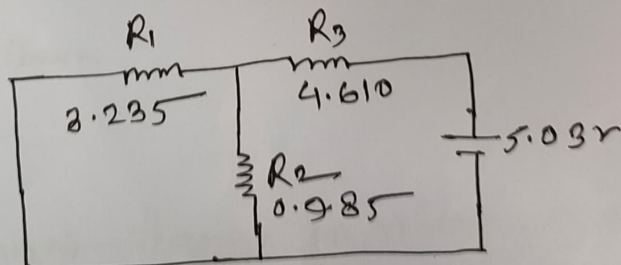

$$R_T = R_3 + (R_1 \parallel R_2)$$

$$= R_3 + \left(\frac{1}{\frac{1}{3.235} + \frac{1}{0.985}} \right)^{-1}$$

$$= R_3 + 0.755$$

$$= 4.610 + 0.755$$

$$= 5.365 \text{ k}\Omega$$

$$I_5 = \frac{5.03}{5.365} = 0.938 \text{ mA} \quad V''_{R3} = \frac{4.610}{5.365} \times 5.03 = 4.322 \text{ V}$$

$$V'_{R2} = \frac{0.755}{5.365} \times 5.03 = 0.708 \text{ V} \quad V_{R1}' = -V_{R1}'' = +0.708 \text{ V}$$

$$I_1' = \frac{0.755}{5.985} \times 0.933 = 0.719 \text{ mA}$$

Error:

$$I_2 = \left| \frac{2.76 - 2.780}{2.761} \right| \times 100$$

$$= 0.69\%$$

$$V_{R1} = \left| \frac{7.311 - 7.360}{7.311} \right| \times 100$$

$$= 0.15\%$$

$$V_{R2} = \left| \frac{2.720 - 2.728}{2.720} \right| \times 100$$

$$= 0.29\%$$

$$V_{R3} = \left| \frac{2.310 - 2.375}{2.310} \right| \times 100$$

$$= 2.81$$

Result Analysis:- we measured the current I_2 when two sources were connected and when only one source was connected at a time. After measurement we found value I_2 is the same as the algebraic I_2' and I_2'' . That means our circuit superposition theorem.

Question:

① The current through or voltage across any element of network is equal to the algebraic sum of the current or voltage produced independently by each source.

② Already showed in Data Table section.

08. In our experiment circuit we found I_2 was 2.78 mA when two sources were connected. we found I_2' of 2.04 we removed the second source. After reconnecting the second source and removing the first source. we find $2.04 + 0.74 = 2.78 \text{ mA}$.

V_{R_1}

$$V_{R_1}' + V_{R_1}'' = 8.01 \text{ V} (-0.722 \text{ V}) = 7.288 \text{ V} = V_{R_1}$$

V_{R_2}


$$V_{R_2}' + V_{R_2}'' = 2.013 \text{ V} + 0.723 \text{ V} = 2.736 \text{ V} = 0.728 \text{ V} = V_{R_2}$$


V_{R_3}


$$V_{R_3}' + V_{R_3}'' = -2.014 + 4.410 \text{ V} = 2.396 \text{ V} = 2.375 \text{ V} = V_{R_3}$$

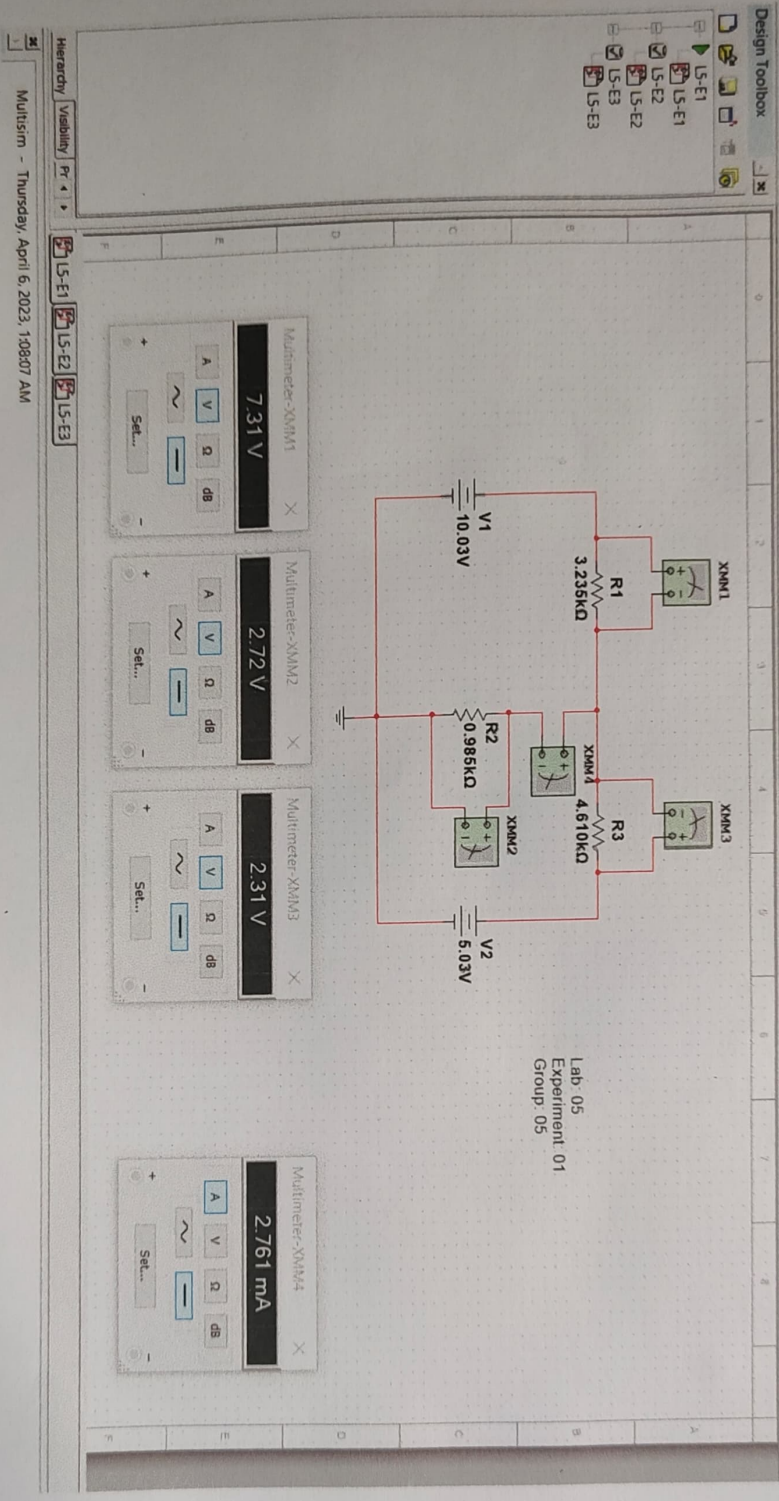04. Already showed in Data Table.

Discussion:- After completing this experiment we successfully verify the Superposition Theorem. That means we now find a solution for a current or voltage using only one source at a time. we need to combine the result to find the final solution. In this experiment we don't face any severe difficulty we encountered a problem with DC power supply it was continuously. Finally we completed the experiment with in the time.



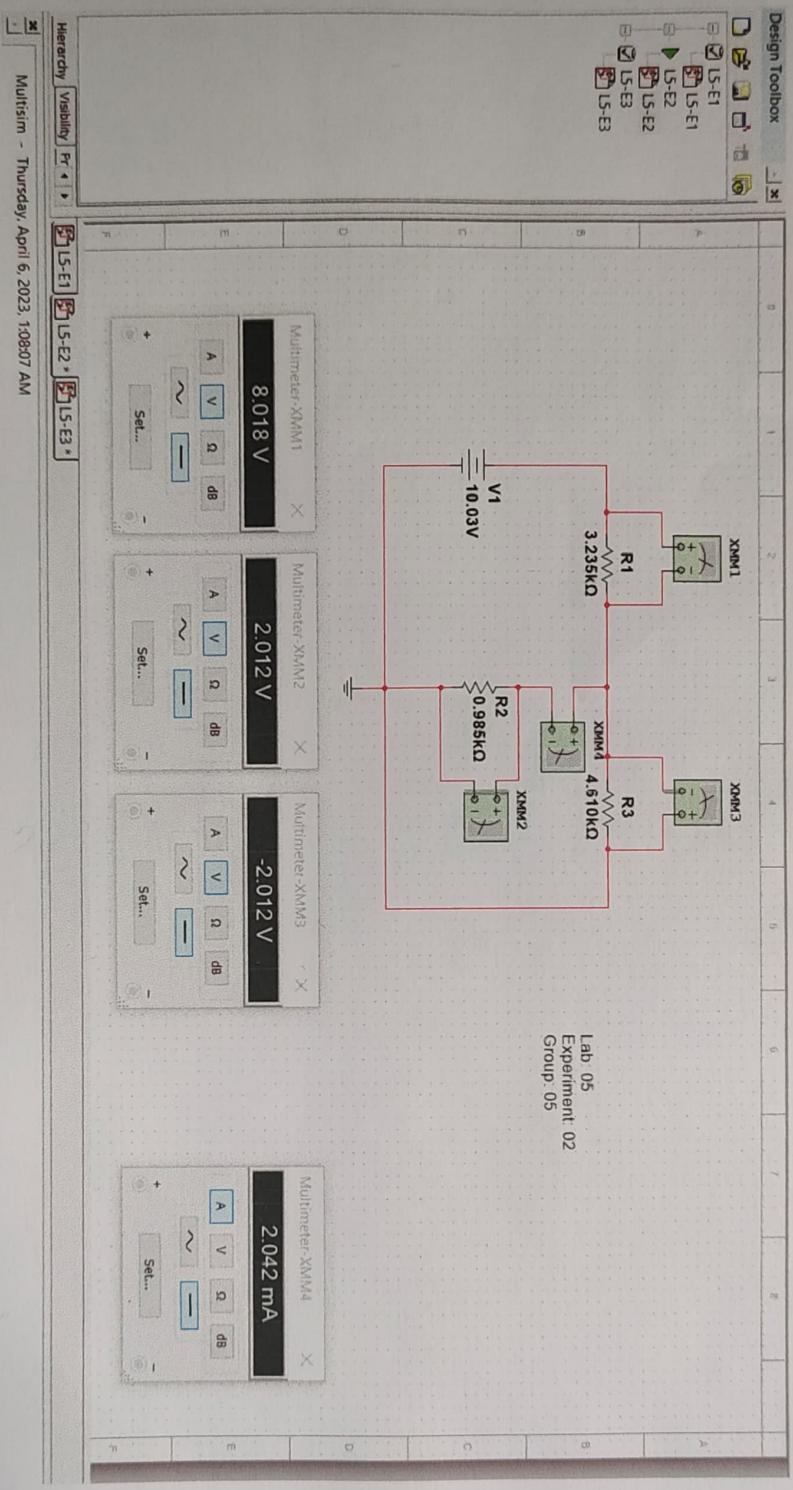

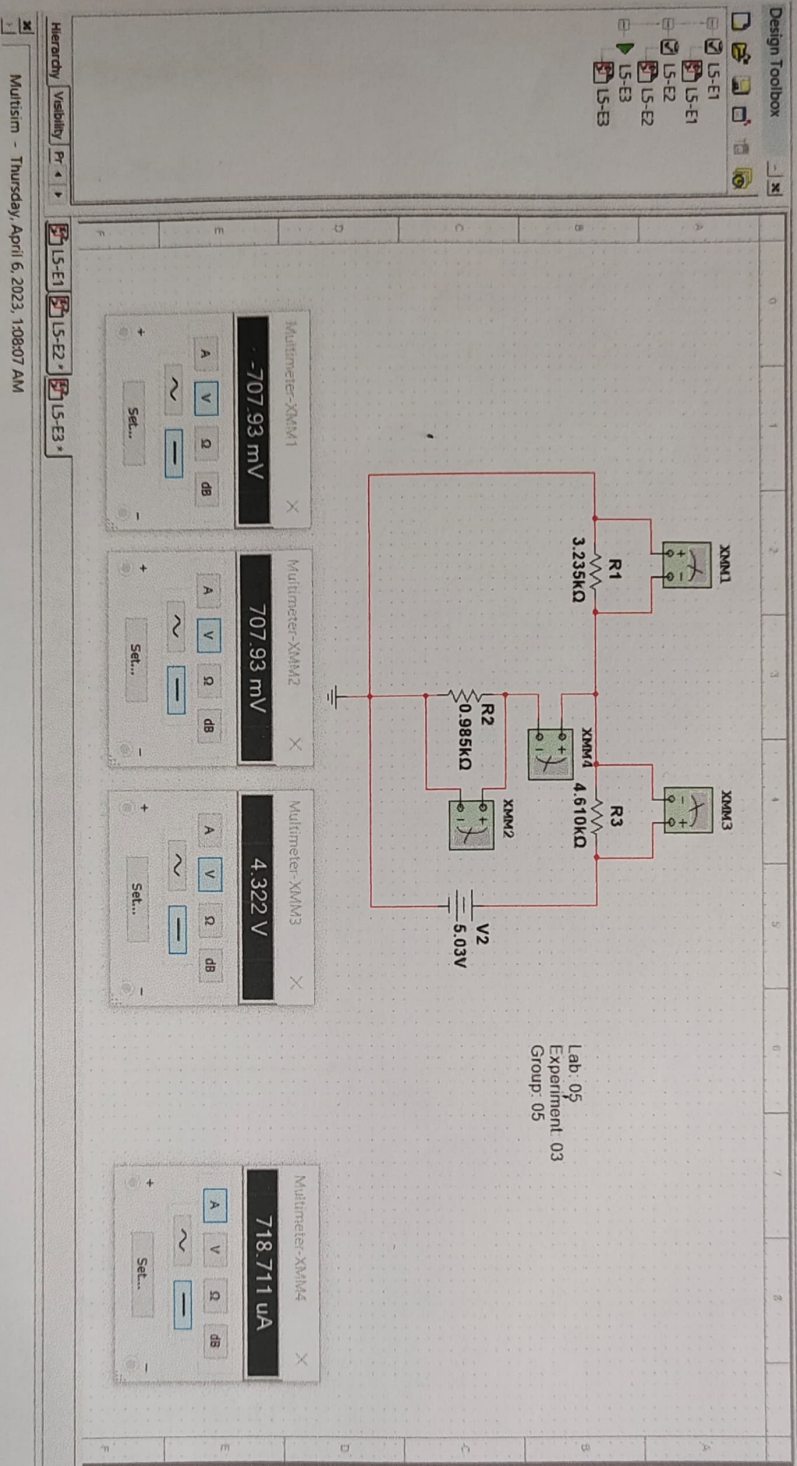

NORTH SOUTH UNIVERSITY

DEPARTMENT OF ELECTRICAL & COMPUTER ENGINEERING



Electrical Circuit I Lab

Lab 5: Verification of Superposition Theorem

Objective:

- To verify Superposition Theorem.

List of Equipment


- Trainer Board
- DMM
- 1 x 3.3k Ω resistor
- 1 x 4.7k Ω resistor
- 1 x 1K Ω resistor

$$R_1 = 3.235 \text{ k}\Omega$$


$$R_2 = 4.440 \text{ k}\Omega$$

$$R_3 = 4.610 \text{ k}\Omega$$


Circuit Diagram

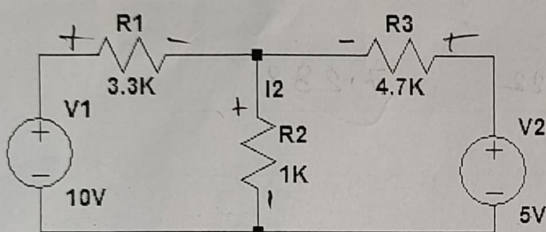

Circuit 1

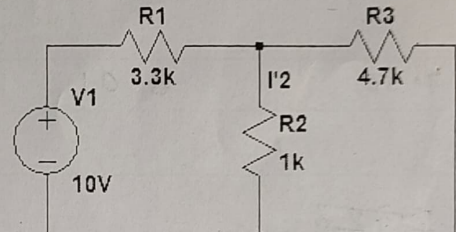

Circuit 2

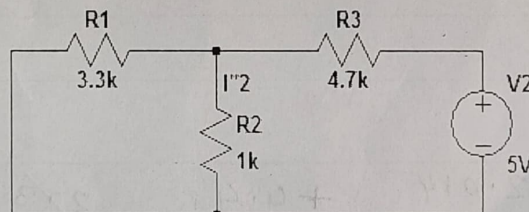

Circuit 3

Procedure:

- Set up Circuit 1.
- Mark the polarities of each resistor.
- With both the voltage source connected to the circuit, measure I_2 , V_{R1} , V_{R2} , V_{R3} and record the values in appropriate tables.
- Setup Circuit 2. Measure and record I'_2 , V'_{R1} , V'_{R2} , V'_{R3} .
- Setup Circuit 3. Measure and record I''_2 , V''_{R1} , V''_{R2} , V''_{R3} .

NORTH SOUTH UNIVERSITY

DEPARTMENT OF ELECTRICAL & COMPUTER ENGINEERING



Electrical Circuit I Lab

Data Collection for Lab 5:

Group No. _____

Instructor's Signature _____

Table 1:

I_2	I_2'	I_2''	$I_2' + I_2''$
2.78	2.04	0.74	$2.04 + 0.74$ $= 2.78$

Table 2:

V_{R1}	V_{R1}'	V_{R1}''	$V_{R1}' + V_{R1}''$
7.90	8.01	-0.722	7.288

Table 3:

V_{R2}	V_{R2}'	V_{R2}''	$V_{R2}' + V_{R2}''$
2.728 2.728	2.013	0.723	2.736

Table 4:

V_{R3}	V_{R3}'	V_{R3}''	$V_{R3}' + V_{R3}''$
2.375	-2.014	+4.41	2.396

Report:

1. What is Superposition Theorem?
2. Theoretically Calculate all values of Table 1 to Table 4. Show all the steps in details.
3. Using measured data, show that your circuit followed superposition theorem.
4. Find the % Error between your theoretical and experimental values.

Rabin
02/04/23