
IC Number	IC Name	Input	Gate Count	Pin Details	
7400	NAND	2	4	1,2 = 3	9,10 = 8
7408	AND	2	4	4,5 = 6	12,13 = 11
7432	OR	2	4		
7486	XOR	2	4		
7402	NOR	2	4	2,3 = 1	8,9 = 10
				5,6 = 4	11,12 = 13
				1 = 2	9 = 8
7404	NOT	1	6	3 = 4	11 = 10
				5 = 6	13 = 12
4073	AND	3	3	1,2,8 = 9	
4075	OR	3	3	3,4,5 = 6	
				11,12,13 = 10	
7410	NAND	3	3	1,2,13 = 12	
7411	AND	3	3	3,4,5 = 6	
				9,10,11 = 8	

IC 7483 4-bit binary adder

 

New Apparatus:

IC 74151 (8:1 Multiplexer):

The 74151 is a 16 pin IC which requires a Ground connection at pin 8 and $V_{\rm CC}$ at pin 16. Pins 4, 3, 2, 1 and 15, 14, 13, 12 are the inputs, pins 9, 10 and 11 are used to select a particular input and pin 5 is the output. Pin 6 is provides the inverse of the output at pin 5. An input at pin 7 is used to Enable the IC.

 


Figure B.3: Pinout of IC74151

IC 74138 (3 to 8 Line Decoder):

The 74138 is also a 16 pin IC which requires Ground at pin 8 and VCC at pin 16. Pins 15, 14, 13, 12, 11, 10, 9 and 7 are used as the outputs and pins 3, 2 and 1 are used to take input. A combination of the inputs at pins 6, 4 and 5 is used to enable the device. In order for the IC to function as intended, pin 6 (G1) must have a high value and both pins 4 and 5 (G2A and G2B) must have low values.

Unlike some of the other ICs used so far, the outputs of the 74138 IC are ACTIVE-LOW which means that they provide a 0 or LOW output when they are activated and a 1 or High output when they are inactive.

 


Figure B.4: Pinout of IC74138

 


Figure D.1.1: 4:1 Multiplexer

IC 7474 (Dual D Flip-Flops):

 


Figure B.1: Pinout of IC7474

D.1 Procedure

 


Figure D.1.1: JK Flip-Flop implemented using AND and NOR gates

 


Figure D.3.1: Right Shift Register

IC 74107 (Dual JK Flip-Flops):

 


Figure B5: Pinout of IC74107

The 74107 is a 14 pin IC which requires a Ground connection at pin 7 and $V_{\rm CC}$ at pin 14. Pins 1 and 4 serve as the J and K inputs for the first Flip-Flop and pins 8 and 11 act as the J and K inputs for the second Flip-Flop. Pins 2 and 5 are the outputs of Flip-Flop 1 and Flip-Flop 2 respectively. Pin 12 is the clock input for the first Flip-Flop and pin 9 is the clock input for the second Flip-Flop. The CLR 1 and CLR 2 inputs (pin 13 and pin10, respectively) have to be supplied with logic 1 or 0 depending on the internal implementation of the paticular IC.