

***BOLD and Underline Word should be written with color pen. Use pencil margin, Page number with color pen, all drawing with pencil, table body with pencil but text will be ball pen, write both sides.***

**Experiment Name:** Verification of Maximum Power Transfer Theorem.


**Objectives:**

- Experimentally perform Maximum Power Transfer theorem.
- Perform theoretical calculations.
- Verify the experimental values with theoretical values.

**Apparatus:**

- Breadboard
- Resistors (2x 10 k $\Omega$ )
- Variable Resistors (0 k $\Omega$  - 10 k $\Omega$ )
- Digital Multimeter (DMM)
- DC Power Supply
- Wires

**Circuit Diagram:**

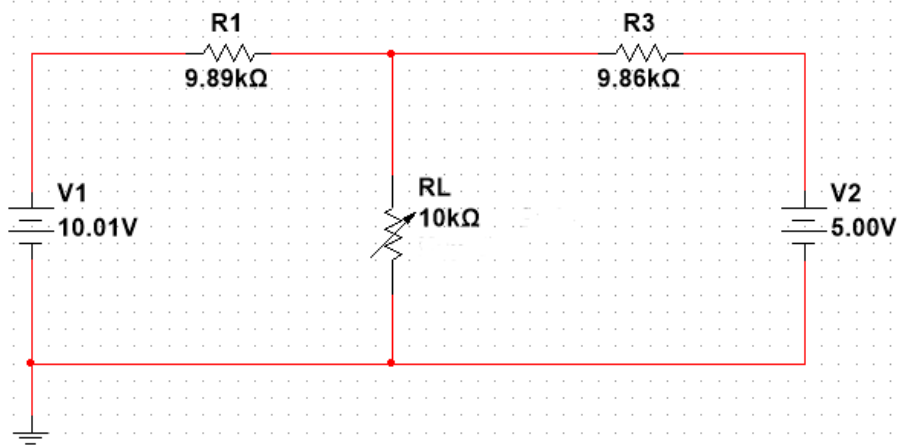


### Data Table & Calculation:


Table - 1:

$R_L (k\Omega)$	$V_L$ Experimental (V)	$V_L$ Theoretical (V)	$P_L$ Experimental	$P_L$ Theoretical
1.037	1.240	1.302	1.4827	1.6347
2.018	2.146	2.176	2.2821	2.3464
3.073	2.870	2.978	2.6804	2.6254
4.00	3.345	3.357	2.7973	2.8174
5.02	3.770	3.782	2.8313	2.8493
5.97	4.100	4.106	2.8157	2.8240
6.97	4.380	4.391	2.7524	2.7662
7.99	4.630	4.636	2.6830	2.6999
9.00	4.840	4.844	2.6028	2.6071
10.06	5.030	5.032	2.5150	2.5170


# Theoretical Value Calculation:

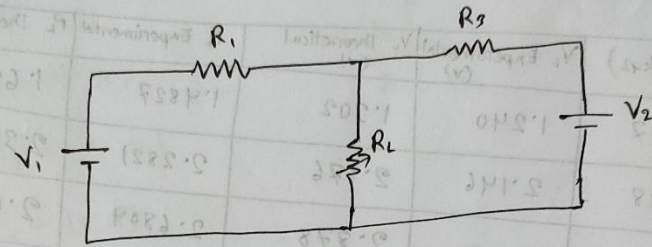

Using Superposition Theorem,

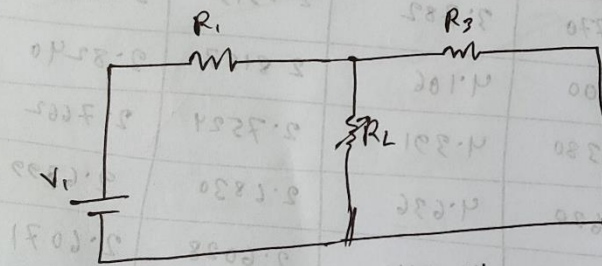
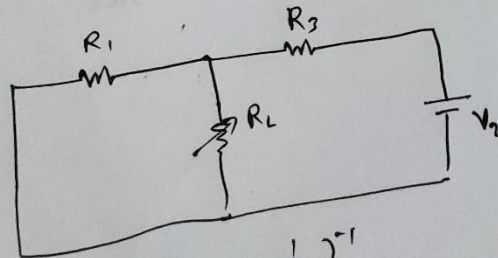
$$V_L' = \frac{\left(\frac{1}{R_L} + \frac{1}{R_2}\right)^{-1} \times V_1}{R_1 + \left(\frac{1}{R_L} + \frac{1}{R_2}\right)^{-1}}$$



$$V_L'' = \frac{\left(\frac{1}{R_L} + \frac{1}{R_1}\right)^{-1} \times V_2}{R_2 + \left(\frac{1}{R_L} + \frac{1}{R_1}\right)^{-1}}$$

$$\therefore V_L = V_L' + V_L''$$

$$= \frac{\left(\frac{1}{R_L} + \frac{1}{R_2}\right)^{-1}}{R_1 + \left(\frac{1}{R_L} + \frac{1}{R_2}\right)^{-1}} \times V_1 + V_2 \frac{\left(\frac{1}{R_L} + \frac{1}{R_1}\right)^{-1}}{R_2 + \left(\frac{1}{R_L} + \frac{1}{R_1}\right)^{-1}}$$

$$\text{And } P_L = \frac{(V_L)^2}{R_L}$$

Here,

$$R_1 = 9.89 \text{ k}\Omega$$

$$R_2 = 9.86 \text{ k}\Omega$$

$$V_1 = 10.01 \text{ V}$$

$$V_2 = 5.00 \text{ V}$$

Now,

$$\text{For } R_L = 1.037 \text{ k}\Omega,$$

$$\therefore V_L = 10.01 \frac{\left(\frac{1}{1.037} + \frac{1}{9.86}\right)^{-1}}{9.89 + \left(\frac{1}{1.037} + \frac{1}{9.86}\right)^{-1}} + 5.00 \frac{\left(\frac{1}{1.037} + \frac{1}{9.89}\right)^{-1}}{9.86 + \left(\frac{1}{1.037} + \frac{1}{9.89}\right)^{-1}}$$

$$= 1.362 \text{ V}$$

$$\therefore P_L = \frac{(1.362)^2}{1.037} = 1.6947 \text{ mW}$$

For  $R_L = 2.018 \text{ k}\Omega$

$$V_L = 10.01 \frac{\left(\frac{1}{2.018} + \frac{1}{9.86}\right)^{-1}}{9.89 + \left(\frac{1}{2.018} + \frac{1}{9.86}\right)^{-1}} + 5.00 \frac{\left(\frac{1}{2.018} + \frac{1}{9.89}\right)^{-1}}{9.86 + \left(\frac{1}{2.018} + \frac{1}{9.89}\right)^{-1}}$$

$$= 2.176 \text{ V}$$

$$\therefore P_L = \frac{(2.176)^2}{2.018} = 2.3464 \text{ mW}$$

For  $R_L = 3.073 \text{ k}\Omega$

$$V_L = 10.01 \frac{\left(\frac{1}{3.073} + \frac{1}{9.86}\right)^{-1}}{9.89 + \left(\frac{1}{3.073} + \frac{1}{9.86}\right)^{-1}} + 5.00 \frac{\left(\frac{1}{3.073} + \frac{1}{9.89}\right)^{-1}}{9.86 + \left(\frac{1}{3.073} + \frac{1}{9.89}\right)^{-1}}$$

$$= 2.878 \text{ V}$$

$$P_L = \frac{(2.878)^2}{3.073} = 2.6954 \text{ mW}$$



For,  $R_L = 4.00 \text{ k}\Omega$ ,

$$V_L = 10.01 \frac{\left(\frac{1}{4} + \frac{1}{2.86}\right)^{-1}}{2.82 + \left(\frac{1}{4} + \frac{1}{2.86}\right)^{-1}} + 5.00 \frac{\left(\frac{1}{4} + \frac{1}{2.86}\right)^{-1}}{2.86 + \left(\frac{1}{4} + \frac{1}{2.86}\right)^{-1}}$$

$$= 3.357 \text{ V}$$

$$P_L = \frac{(3.357)^2}{4.00} = 2.8174 \text{ mW}$$

For  $R_L = 5.02 \text{ k}\Omega$ ,

$$V_L = 10.01 \frac{\left(\frac{1}{5.02} + \frac{1}{2.86}\right)^{-1}}{2.82 + \left(\frac{1}{5.02} + \frac{1}{2.86}\right)^{-1}} + 5.00 \frac{\left(\frac{1}{5.02} + \frac{1}{2.86}\right)^{-1}}{2.86 + \left(\frac{1}{5.02} + \frac{1}{2.86}\right)^{-1}}$$

$$= 3.782 \text{ V}$$

$$P_L = \frac{(3.782)^2}{5.02} = 2.8493 \text{ mW}$$

For  $R_L = 5.97 \text{ k}\Omega$

$$V_L = 10.01 \frac{\left(\frac{1}{5.97} + \frac{1}{2.86}\right)^{-1}}{2.82 + \left(\frac{1}{5.97} + \frac{1}{2.86}\right)^{-1}} + 5.00 \frac{\left(\frac{1}{5.97} + \frac{1}{2.86}\right)^{-1}}{2.86 + \left(\frac{1}{5.97} + \frac{1}{2.86}\right)^{-1}}$$

$$= 4.106 \text{ V}$$

$$P_L = \frac{(4.106)^2}{5.97} = 2.8240 \text{ mW}$$

**Seacal-D**

Calcium Carbonate (From Coral Source) and  
Vitamin D<sub>3</sub> (Colecalciferol)

**Seacal-DX**

Calcium Carbonate (From Coral Source)  
and Vitamin D<sub>3</sub> (Colecalciferol)

For  $R_L = 6.27 \text{ k}\Omega$

$$V_L = 10.01 \frac{\left(\frac{1}{6.27} + \frac{1}{9.86}\right)^{-1} + 5.00}{9.86 + \left(\frac{1}{6.27} + \frac{1}{9.86}\right)^{-1}} \frac{\left(\frac{1}{6.27} + \frac{1}{9.86}\right)^{-1}}{\left(\frac{1}{6.27} + \frac{1}{9.86}\right)^{-1}}$$

$$= 4.391 \text{ V}$$

$$P_L = \frac{(4.391)^2}{6.27} = 2.7662 \text{ mW}$$

For  $R_L = 7.27 \text{ k}\Omega$

$$V_L = 10.01 \frac{\left(\frac{1}{7.27} + \frac{1}{9.86}\right)^{-1} + 5.00}{9.86 + \left(\frac{1}{7.27} + \frac{1}{9.86}\right)^{-1}} \frac{\left(\frac{1}{7.27} + \frac{1}{9.86}\right)^{-1}}{\left(\frac{1}{7.27} + \frac{1}{9.86}\right)^{-1}}$$

$$= 4.636 \text{ V}$$

$$P_L = \frac{(4.636)^2}{7.27} = 2.6822 \text{ mW}$$

For  $R_L = 9.60 \text{ k}\Omega$

$$V_L = 10.01 \frac{\left(\frac{1}{9} + \frac{1}{9.86}\right)^{-1} + 5.00}{9.86 + \left(\frac{1}{9} + \frac{1}{9.86}\right)^{-1}} \frac{\left(\frac{1}{9} + \frac{1}{9.86}\right)^{-1}}{\left(\frac{1}{9} + \frac{1}{9.86}\right)^{-1}}$$

$$= 4.844 \text{ V}$$

$$P_L = \frac{(4.844)^2}{9.60} = 2.6071 \text{ mW}$$

For  $R_L = 10.06 \text{ k}\Omega$

$$V_L = 10.01 \frac{\left(\frac{1}{10.06} + \frac{1}{9.86}\right)^{-1}}{9.89 + \left(\frac{1}{10.06} + \frac{1}{9.86}\right)^{-1}} + 5.00 \frac{\left(\frac{1}{10.06} + \frac{1}{9.89}\right)^{-1}}{9.86 + \left(\frac{1}{10.06} + \frac{1}{9.89}\right)^{-1}}$$

$$= 5.032 \text{ V}$$

$$P_L = \frac{(5.032)^2}{10.06} = 2.5170 \text{ mW}$$

Theoretical Value of maximum power,

$$R_{TH} = 4.74 \text{ k}\Omega$$

$$V_{TH} = 7.520 \text{ V}$$

$$\therefore P_{max} = \frac{(V_{TH})^2}{4 R_{TH}} = \frac{(7.520)^2}{4 \times 4.74}$$

$$= 2.8619 \text{ mW}$$

From Graph,

$$R_{TH} = 4.7 \text{ k}\Omega$$

$$P_{max} = 2.8500 \text{ mW}$$

$$\therefore \text{Error} : \left| \frac{2.8619 - 2.8500}{2.8619} \right| \times 100\%$$

$$= 0.42\%$$

**Graph:**

Attached.



**Result Analysis:**

From the data table of this experiment, we found that the theoretical and measured values of  $V_L$  and  $P_L$  are approximately the same. We also get that the theoretical value of  $P_{max}$  and the  $P_{max}$  from the graph are also approximately the same. Therefore, our circuits completely follow the Maximum Power Transfer theorem.

**Questions and Answers:**

**01.**Already showed in Data Table Section.

**02.**Already showed in Data Table Section.

**Discussion:**

After completing this experiment, we learnt to verify the Maximum Power Transfer Theorem. Now we can calculate the maximum Power of a circuit using this theorem. We need to remove the load and measure the  $R_t$  and the voltage of Thevenin's Theorem at points a and b; then, using the maximum power transfer formula, we can calculate the maximum power. In this experiment, we don't face any difficulties. We completed this experiment on time.

**Attachment:**

**01.**Signed Data Table.

**02.**Simulation using Multisim.

**03.**Graph of  $R_L$  vs  $P_{max}$ .