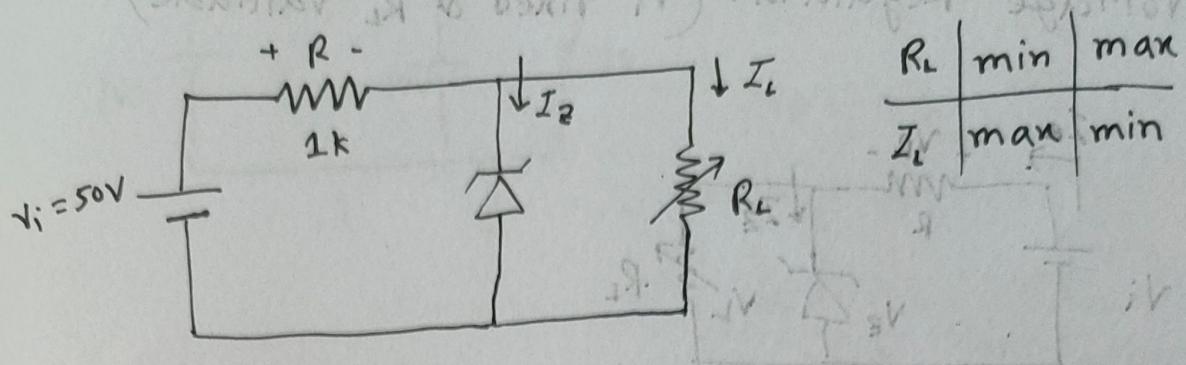


L-12 / 02.09.2023 /



$$V_z = V_L = \frac{V_i \times R_{L\min}}{R + R_{L\min}} = 1V = 3V$$

$$\Rightarrow 10 = \frac{50 \times R_{L\min}}{R + R_{L\min}} = \frac{5V}{5V - 1V} = 10$$

$$\Rightarrow 50 R_{L\min} = 10R + 10R_{L\min}$$

$$\Rightarrow 40 R_{L\min} = 10R$$

$$\therefore R_{L\min} = \frac{10R}{40} = \frac{10k\Omega}{40} = 0.25k\Omega$$

$$I_{L\max} = \frac{V_L}{R_{L\min}} = \frac{10}{0.25} = 40mA$$

$$I_R = \frac{V_R}{R} = \frac{50 - 10}{1k\Omega} = 40mA$$


$$I_R = I_2 + I_L \quad | \quad R_{L\max} = \frac{V_L}{I_{L\min}} = \frac{10}{8mA} = 1.25k\Omega$$

$$I_{L\min} = I_R - I_2$$

$$= I_R - I_{2M}$$



$$= 40 - 32 = 8mA$$

AC Regulator

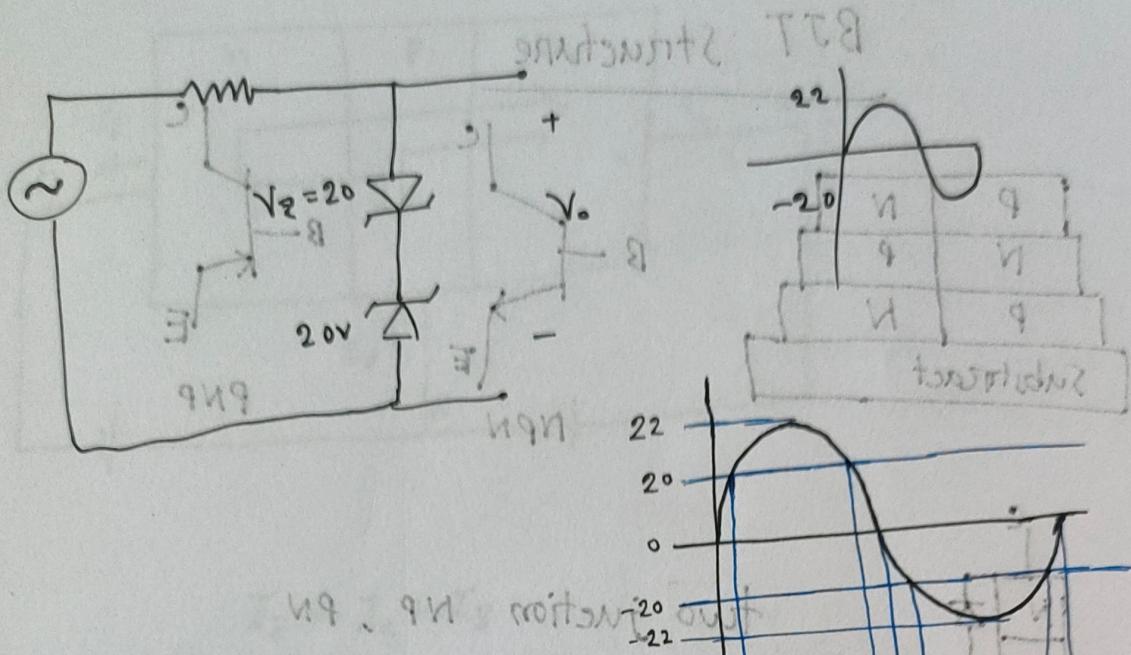

④ Transistor: Transfer energy

from low to high

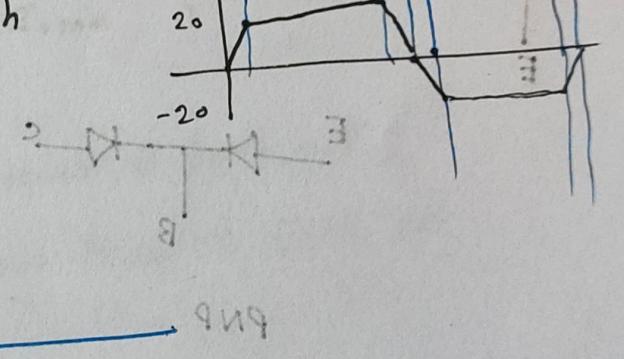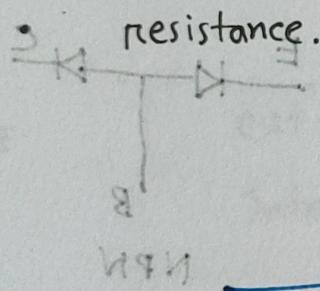

(will most) return to show ④

switch = mitverhindern ④

mitverhindern & filtern = abfiltern

Seacal-D


Calcium Carbonate (From Coral Source) and
Vitamin D₃ (Colecalciferol)

Seacal-DX

Calcium Carbonate (From Coral Source)
and Vitamin D₃ (Colecalciferol)

L-13/07.09.2023/

BJT Structure

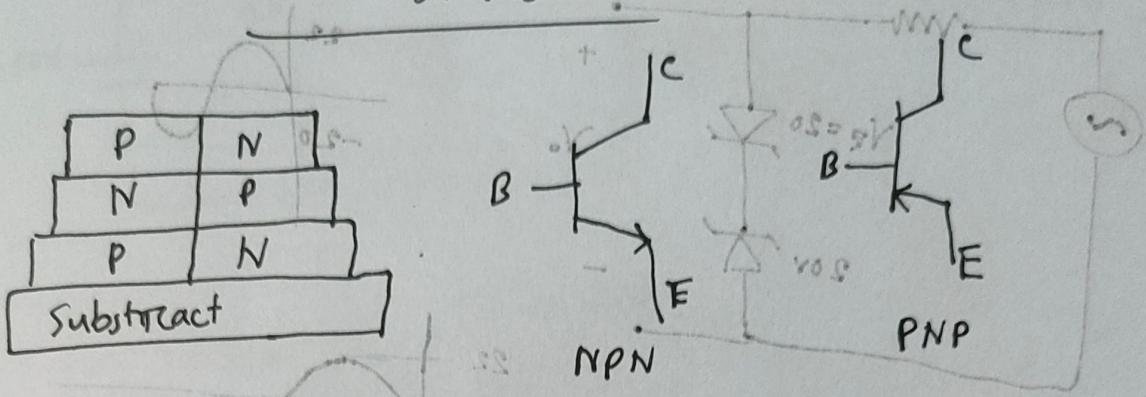


two junction NP, PN

CB, BE

forward bias : not invert



inversion of w/o invert

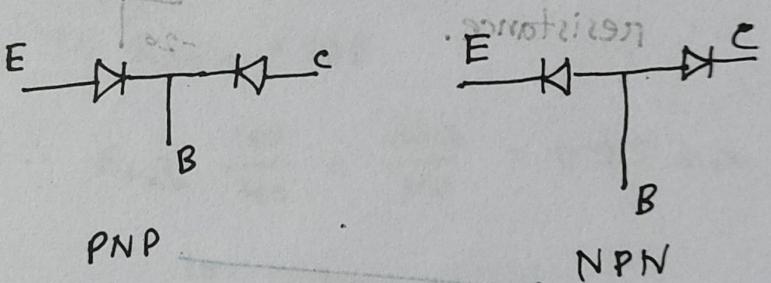

✳ Mode of Operation (from slide)

✳ Amplification = Active

Switch = cut off & saturation

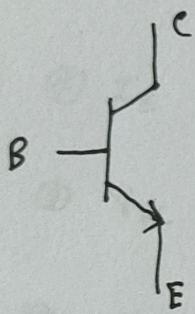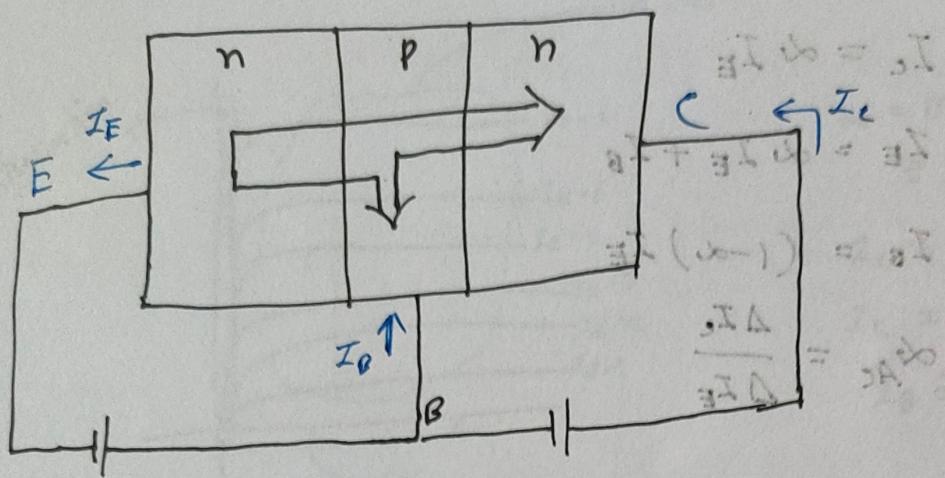

$$I_E = I_C + I_B$$

$$I_C = I_{C\max} + I_{C\min}$$

cut off mode \Rightarrow Both off

Saturation Mode \Rightarrow Both on

④ PNP \Rightarrow Active Mode \Rightarrow Holes are injected in place of electron.

⑤ Common emitter used for amplification.

⑥ if 100 electrons injected and 98 electrons passed

then,

$$\alpha = \frac{98}{100} \rightarrow I_C$$

$$I_E$$

Seacal-D

Calcium Carbonate (From Coral Source) and Vitamin D₃ (Colecalciferol)

Seacal-DX

Calcium Carbonate (From Coral Source) and Vitamin D₃ (Colecalciferol)



From previous circuit,

$$I_c = \alpha I_E$$

$$I_E = \alpha I_E + I_B$$

$$I_B = (1-\alpha) I_E$$

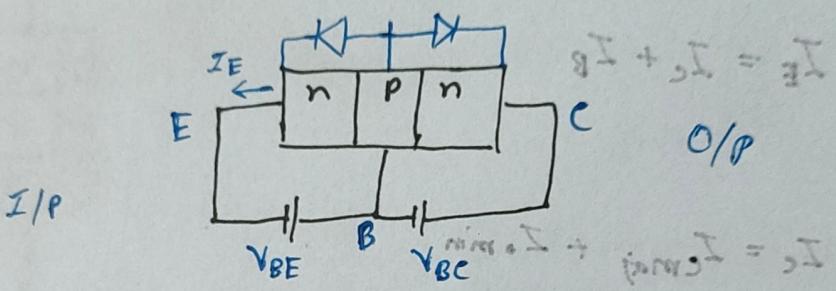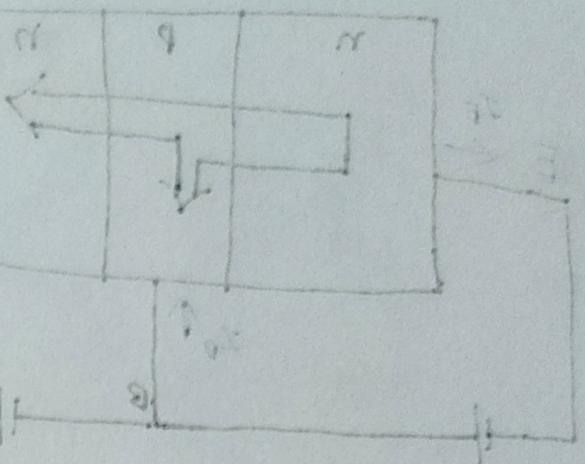
$$\alpha_{AC} = \frac{\Delta I_c}{\Delta I_E}$$



I_E vs V_{BE} ~~for n-p-n~~ \neq I_E vs V_{BC}

no I_B \leftarrow ~~shunt M~~ no collector

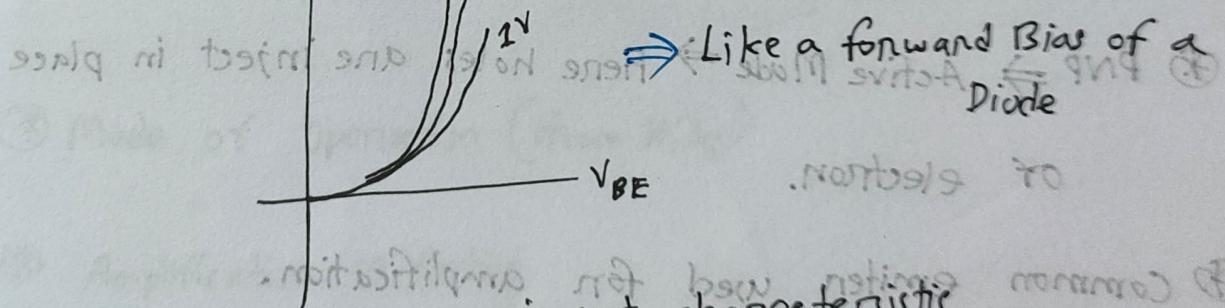
I_E $\xrightarrow{20V}$
 $\xrightarrow{10V} V_{BC}$



input characteristic curve

$$\frac{\partial I}{\partial V} = \frac{8e}{100} = \infty$$

Output Characteristic

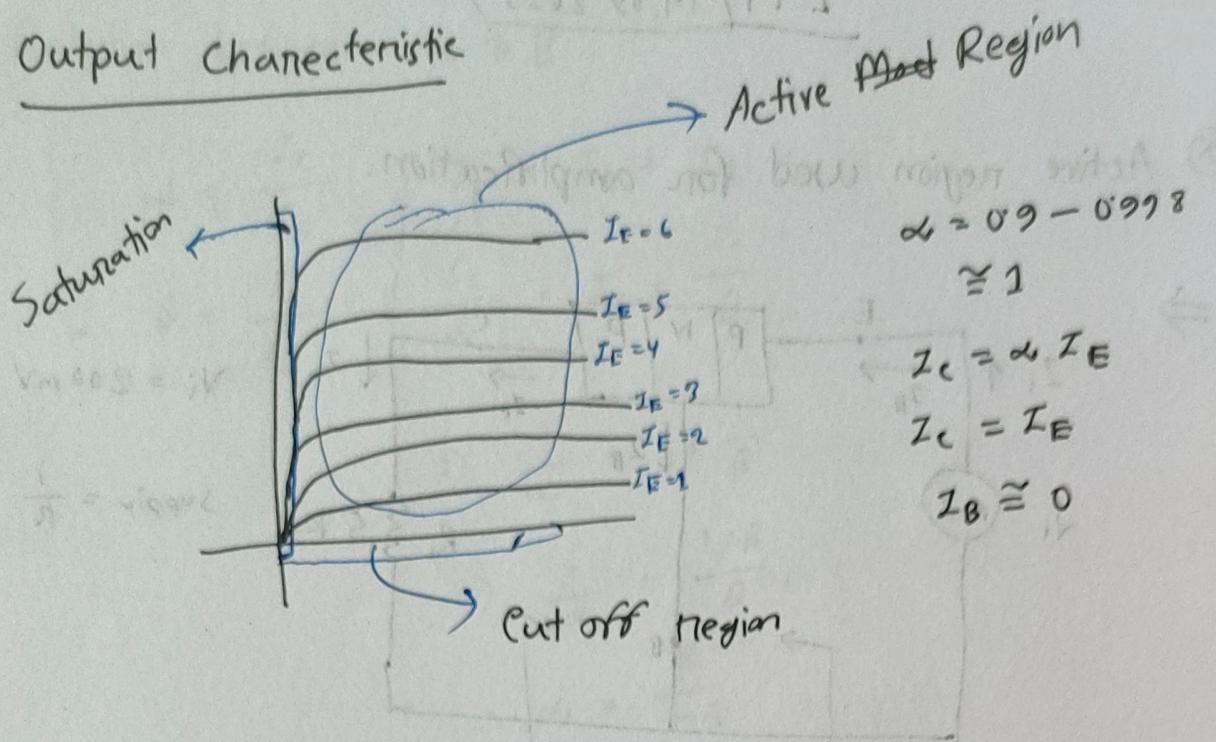

- ⊗ I_C dependent on I_E
- ⊗ I_E dependent on V_{BE}
- ⊗ V_{DC} is negligible
- ⊗ When, $I=0$, But voltage present (cut off)
- ⊗ Voltage 0 But current present (saturation)

Quiz-2 END

Quiz-2 \Rightarrow 16. 09. 2023

Midterm \Rightarrow 21. 09. 2023


Seacal-D

Calcium Carbonate (From Coral Source) and
Vitamin D₃ (Colecalciferol)

Seacal-DX

Calcium Carbonate (From Coral Source)
and Vitamin D₃ (Colecalciferol)

* Active region used for amplification.

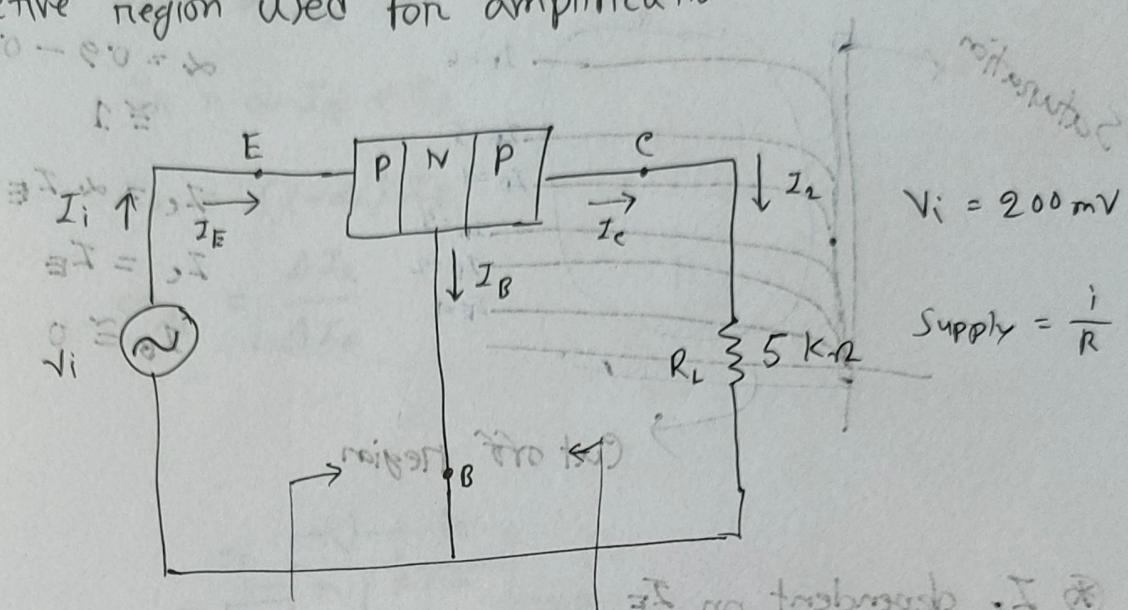

$$R_i = 20\Omega$$

$$R_o = ?$$

$$I_i = \frac{V_i}{R_i} = \frac{200\text{mV}}{20\Omega}$$

$$I_E = I_i + I_C \approx 30\text{mA}$$

$$= 10\text{mA}$$

$$I_C = I_E$$

$$V_L = (5\text{k}\Omega \times 10\text{mA})$$

$$= 50\text{V}$$

$$\rightarrow \text{voltage gain}, A_v = \frac{V_L}{V_i} = \frac{50\text{V}}{200\text{mV}} = 250$$

* Common Emitter Configuration:

$$\text{Amplification factor, } \beta = \frac{I_C}{I_B}$$

Relation between α & β

$$\left. \begin{array}{l} \alpha = \frac{I_c}{I_E} \\ \beta = \frac{I_c}{I_B} \end{array} \right| \quad \begin{array}{l} I_E = I_c + I_B \\ \frac{I_c}{\alpha} = I_c + \frac{I_c}{\beta} \end{array}$$

$$\Rightarrow \frac{1}{\alpha} = 1 + \frac{1}{\beta}$$

$$\Rightarrow \frac{1}{\alpha} = \frac{1+\beta}{\beta}$$

$$\therefore \alpha = \frac{\beta}{1+\beta}$$

Common Emitter Characteristic

Input


I_B vs V_{BE}

Output

I_c vs V_{CE}

$$I_c = \beta I_B$$

50, 100, etc

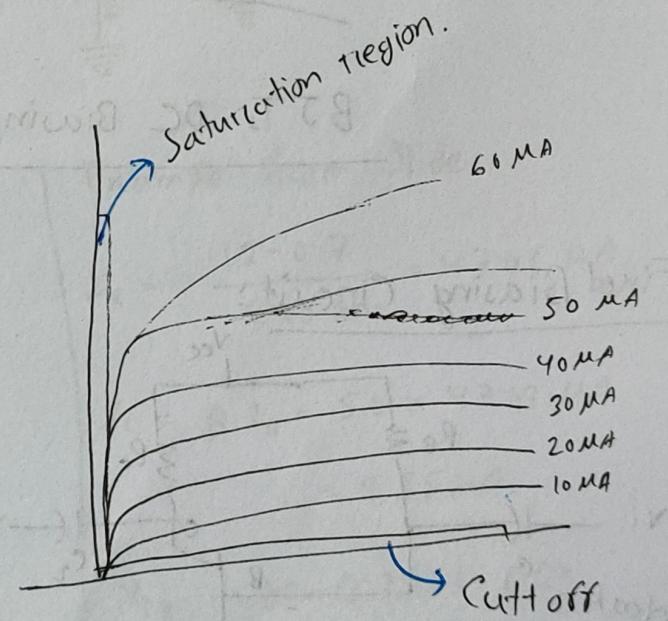

Next Class - Quiz-2

Only Lecture-5

Seacal-D

Calcium Carbonate (From Coral Source) and
Vitamin D₃ (Colecalciferol)

Seacal-DX

Calcium Carbonate (From Coral Source)
and Vitamin D₃ (Colecalciferol)

L-15 / 16.09.2023/

Quiz - 02
No Class

Next Class Midterm

L1-6


L-16 / 21.09.2023/

Midterm Exam

L-17 / 23.09.2023/

BJTs DC Biasing

Fixed Biasing Circuit:

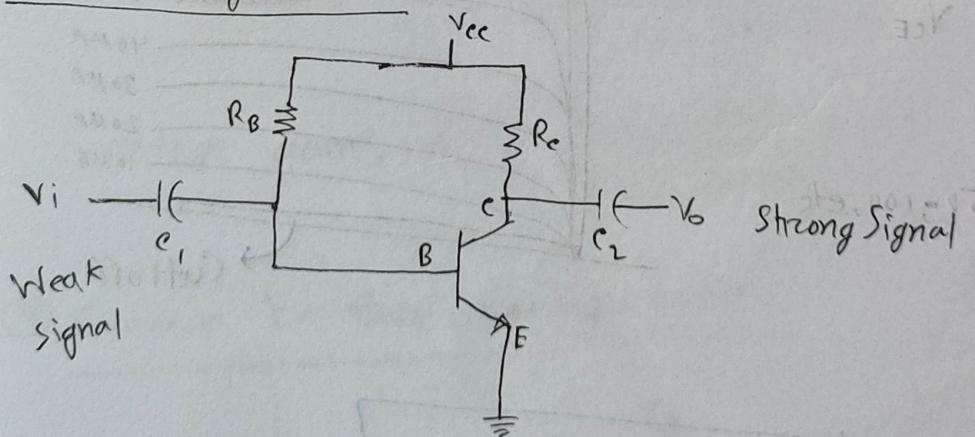


Step - 1: DC Analysis

Step - 2: AC Apply


④ DC Analysis

$$f = 0$$

$$X_C = \frac{1}{2\pi f C} = \infty$$

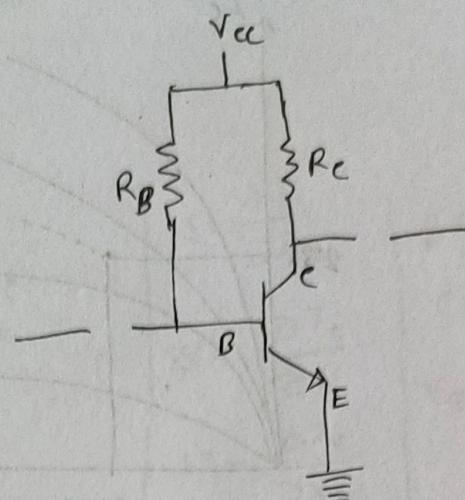

④ Simplify:

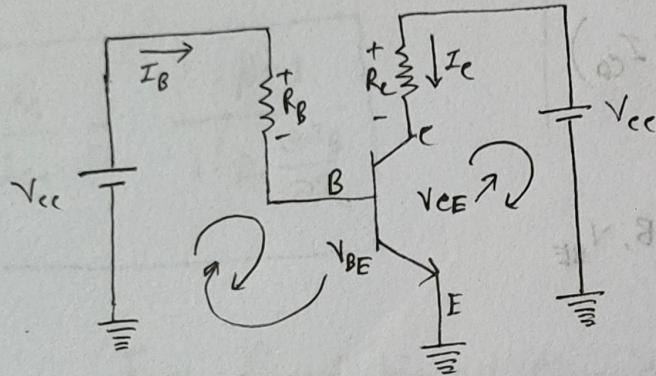

$$V_{CC} - I_B R_B - V_{BE} = 0$$

$$I_B = \frac{V_{CC} - V_{BE}}{R_B} \quad \text{--- (1)}$$

$$V_{CE} + I_c R_c - V_{CC} = 0$$

$$V_{CE} = V_{CC} - I_c R_c$$

$$I_c = \beta I_B$$


Example from Slide

$$I_B = \frac{12 - 0.7}{240 \text{ k}\Omega} = 47.08 \text{ mA}$$

$$\begin{aligned} I_c &= \beta \cdot I_B = 50 \times 47.08 \text{ mA} \\ &= 2.35 \text{ mA} \end{aligned}$$


$$\begin{aligned} V_{CE} &= 12 - 2.35 \text{ mA} \cdot 2.2 \text{ k} \\ &= \dots \end{aligned}$$

$$V_{BC} =$$

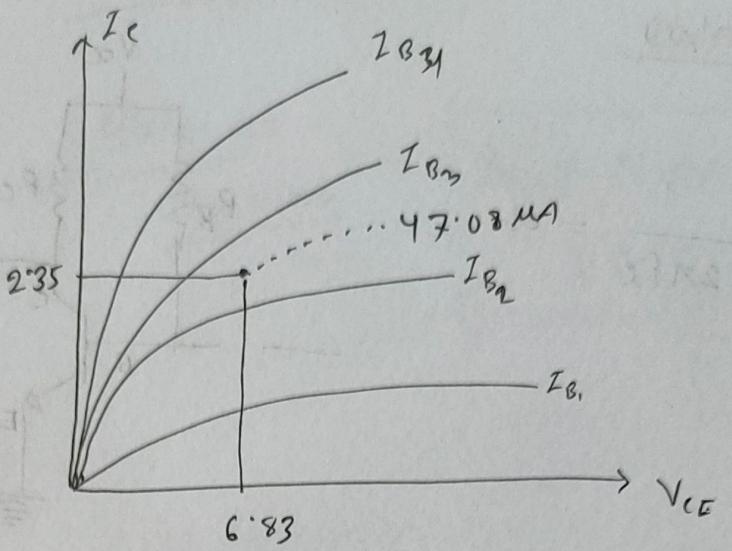

$$I_c = f(B, I_B, I_{C0})$$
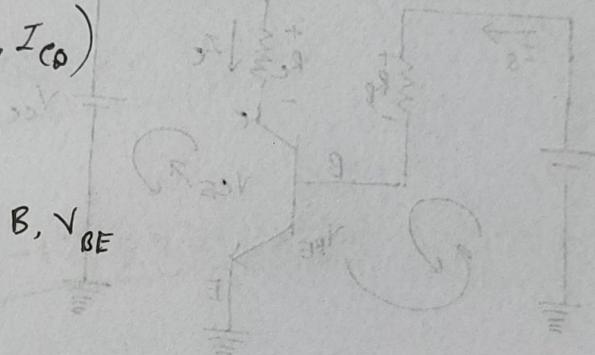
$$S = \frac{\partial I_c}{\partial I_{C0}}$$



shunt load approximation

$$0 = 38V - 28.5V - 2.5V$$

$$R_{out} = \frac{V_{out}}{I_B} = \frac{2.5V}{2.35mA} = 1060 \Omega$$

$$\textcircled{1} \quad I_B = \frac{38V - 28.5V}{R_L} = 1mA$$

$$R_{load} = 10.2 \times 10^3 \Omega = 10.2k\Omega$$

$$0 = 38V - 28.5V - 2.5V$$

$$10.2k\Omega \cdot 1mA = 10.2V$$

$$0.2V = 1.5V$$

$$= 3.9V$$

L-18 / 30. 09. 2023 /

$$I_c = \beta I_B + (\beta + 1) I_{co}$$

$$1 = \beta \frac{\partial I_B}{\partial I_c} + (\beta + 1) \frac{\partial I_{co}}{\partial I_c}$$

$$\frac{\partial I_{co}}{\partial I_c} = \frac{1 - \beta \frac{\partial I_B}{\partial I_c}}{(\beta + 1)}$$

$$S = \frac{\partial I_c}{\partial I_{co}}$$

$$S' = \frac{\partial I_c}{\partial \beta}$$


$$S'' = \frac{\partial I_c}{\partial V_{BE}}$$

β & V_{BE}
constant
 V_{BE} and I_{co}

$$S = \frac{\partial I_c}{\partial I_{co}} = \frac{\beta + 1}{1 - \beta \frac{\partial I_B}{\partial I_c}}$$

For fixed biased circuit

$$I_B = \frac{V_{cc} - V_{BE}}{R_B}$$

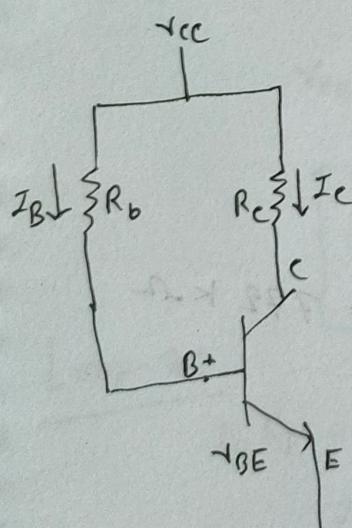

$$\frac{\partial I_B}{\partial I_c} = 0$$

$$S = \frac{\beta + 1}{1 - \beta \cdot 0} = \beta + 1$$

$$I_c = \frac{V_{cc} - V_{CE}}{R_c}$$

$$= I_{c, \text{set}} = \frac{V_{cc}}{R_c}$$


Seacal-D

Calcium Carbonate (From Coral Source) and
Vitamin D₃ (Colecalciferol)

Seacal-DX

Calcium Carbonate (From Coral Source)
and Vitamin D₃ (Colecalciferol)

LOAD Line Analysis

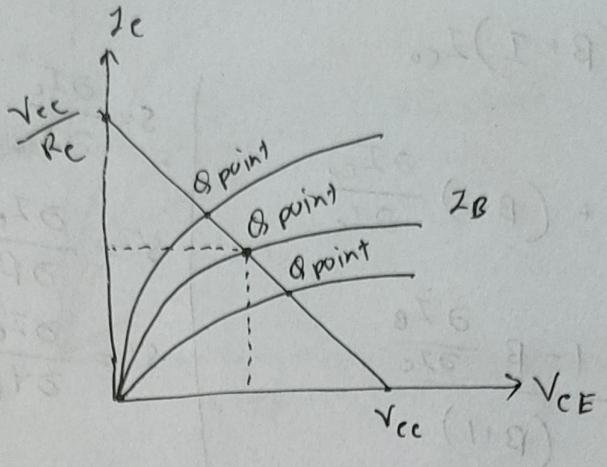

$$I_c = \frac{V_{cc} - V_{ce}}{R_c}$$

I_{CQ}	$\beta_{DC} = \frac{I_{CQ}}{Z_{BQ}}$
----------	--------------------------------------

From Slide

$$\frac{V_{cc}}{R_c} = 10 \text{ mA}$$

$$V_{cc} = 20 \text{ V}$$



$$R_c = \frac{20}{10} = 2 \text{ k}\Omega$$

$$I_B = \frac{V_{cc} - V_{BE}}{R_B}$$

$$R_B = \frac{V_{cc} - V_{BE}}{I_B}$$

$$= \frac{20 - 0.7}{25 \text{ mA}} = 772 \text{ k}\Omega$$

④ Emitter Stabilized Bias Circuit

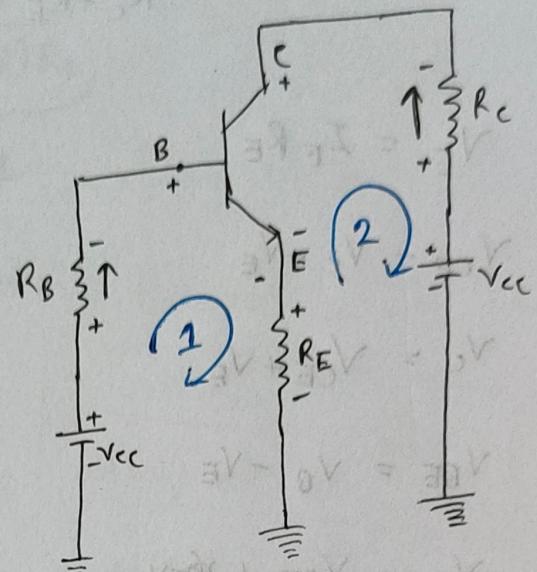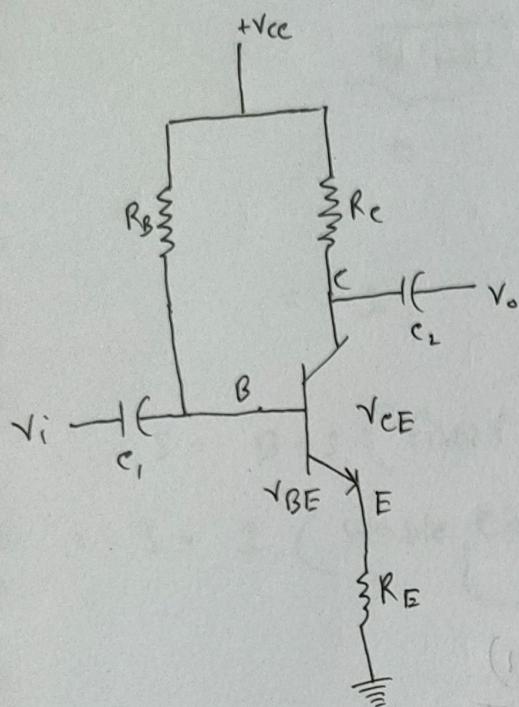

Loop-1:

$$V_{CC} - I_B R_B - V_{BE} - I_E R_E = 0$$

$$I_E = I_B + I_C = I_B + \beta I_B = (\beta + 1) I_B$$

$$V_{CC} - I_B R_B - V_{BE} - (\beta + 1) I_B R_B = 0$$

$$\therefore I_B = \frac{V_{CC} - V_{BE}}{R_B + (\beta + 1) R_E}$$

Loop-2:

$$I_E R_E + V_{CE} + I_C R_C - V_{CC} = 0$$

$$I_C \approx I_E$$

$$I_C R_E + V_{CE} - I_C R_C - V_{CC} = 0$$

Seacal-D

Calcium Carbonate (From Coral Source) and
Vitamin D₃ (Colecalciferol)

Seacal-DX

Calcium Carbonate (From Coral Source)
and Vitamin D₃ (Colecalciferol)

or

$$Z_C = \frac{V_{CC} - V_{CE}}{R_C + R_E}$$

$$\therefore V_E = I_E R_E$$

$$V_{CE} = V_C - V_E$$

$$V_C = V_{CE} + V_E$$

$$V_{BE} = V_B - V_E$$

$$V_B = V_{BE} + V_E$$

$$S = \frac{\partial Z_C}{\partial I_{CO}} = \frac{(\beta+1)}{1 - \beta \frac{\partial Z_B}{\partial I_C}}$$

$$I_B = \frac{V_{CC} - V_{BE}}{R_B + (\beta+1) R_E}$$

$$V_{CC} - Z_B R_B - V_{BE} - I_E R_E = 0$$

$$I_C \cong Z_E$$

$$V_{CC} - Z_B R_B - V_{BE} - I_C R_E = 0$$

$$\frac{\partial Z_B}{\partial I_C} / R_B I_B = V_{CC} - V_{BE} - Z_C R_E$$

$$I_B = \frac{V_{CC}}{R_B} - \frac{V_{BE}}{R_B} - \frac{Z_C R_E}{R_B}$$

$$\frac{\partial Z_B}{\partial I_C} = - \frac{R_E}{R_B}$$

$$\therefore S = \frac{\partial Z_C}{\partial I_{CO}} = \frac{\beta+1}{1 + \beta \frac{R_E}{R_B}} = \frac{(\beta+1) R_B}{R_B + \beta R_E}$$

$$\frac{\frac{R_B}{R_B(1+\beta)}}{1} + \frac{\frac{\beta R_E}{(1+\beta) R_B}}{1}$$

= 1


$\therefore s = \beta + 1$ (fixed bias)

$\therefore s = 1$ (stable circuit)


→ independent.

L-19 / 05.10.2023

⊗ Emitter Stabilized Bias Circuit.

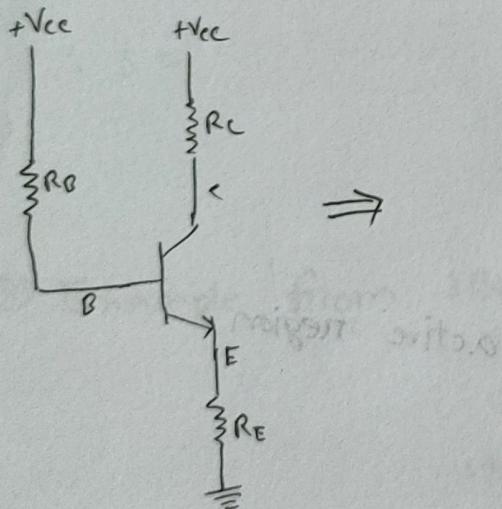

⇒

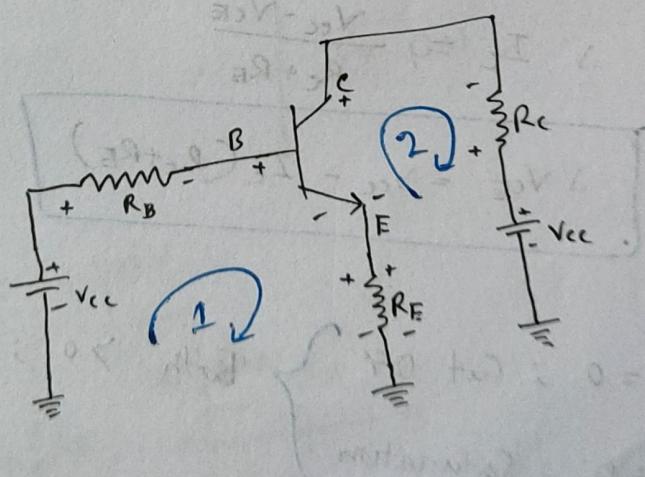

Loop-1 /

$$V_{CC} - R_B I_B - V_{BE} - R_E I_E = 0$$

$$I_C = \beta I_B$$

$$I_E = I_C + I_B$$

$$= \beta I_B + I_B = I_B (\beta + 1)$$

$$\therefore V_{CC} - I_B R_B - V_{BE} - (\beta + 1) I_B R_E = 0$$

$$\therefore I_B = \frac{V_{CC} - V_{BE}}{R_B + (\beta + 1) R_E}$$

(cold bias) \rightarrow

(forward biased)

transistor region

Loop-2 /

$$I_E R_E + V_{CE} + I_C R_C - V_{CC} = 0$$

$$I_C \approx I_E$$

$$\therefore I_C (R_C + R_E) + V_{CE} - V_{CC} = 0$$

$$\therefore I_C = \frac{V_{CC} - V_{CE}}{R_C + R_E}$$

$$\therefore V_{CE} = V_{CC} - I_C (R_C + R_E)$$

* $I_C = 0$; Cut Off } Both > 0 ; active region

$V_{CE} = 0$; Saturation }

Stability Factor for Emitter Bias Circuit

$$I_B = \frac{V_{CC} - V_{BE}}{R_B}$$

$$I_C = \beta I_B + (\beta+1) I_{CO}$$

$$\Rightarrow S = \boxed{\frac{\partial I_C}{\partial I_{CO}}}$$

$$S' = \frac{\partial I_C}{\partial \beta}$$


$$S'' = \frac{\partial I_C}{\partial V_{BE}}$$

for advance level, not in this course.

$$\therefore I = \beta \frac{\partial I_B}{\partial I_C} + (\beta+1) \frac{\partial I_{CO}}{\partial I_C} \quad \left| \begin{array}{l} \text{fixed bias circuit,} \\ \frac{\partial I_B}{\partial I_C} = 0 \end{array} \right.$$

$$\therefore S = \beta + 1$$

Example from slide:

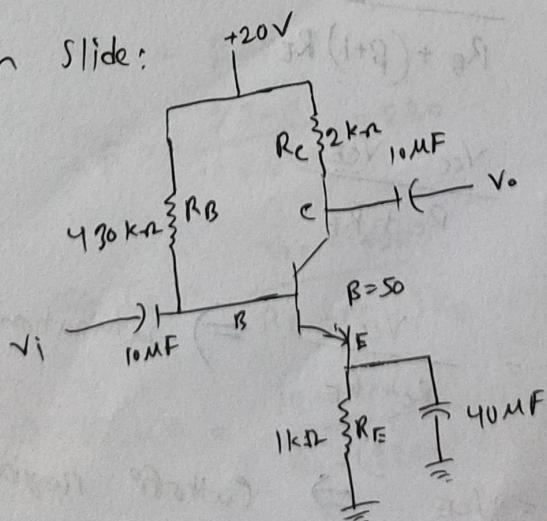

$$I_B = \frac{V_{CC} - V_{BE}}{R_B + (\beta+1)R_E} = \frac{20 - 0.7}{430\text{k}\Omega + (50+1)2\text{k}\Omega}$$

always in micro

$$= 40.1 \text{ mA}$$

→ always in milli
 $I_C = \beta I_B = 50 \times (40.1 \text{ mA})$

$$= 2.005 \text{ mA}$$

$$V_{CE} = V_{CC} - I_C (R_C + R_E)$$

$$= 20 - 2 \text{ mA} (2+1) \text{ k}\Omega$$

$$= 13.982 \text{ V}$$

⇒ See slide for more

L-20/07.10.2023.


Load Line analysis for Emitter stabilized bias circuit

$$I_B = \frac{V_{CC} - V_{BE}}{R_B + (\beta+1)R_E}$$

$$I_C = \frac{V_{CC} - V_{CE}}{R_C + R_E}$$

$$I_{C\text{sat}} = \frac{V_{CC}}{R_C + R_E} \Rightarrow \text{Saturation Region}$$
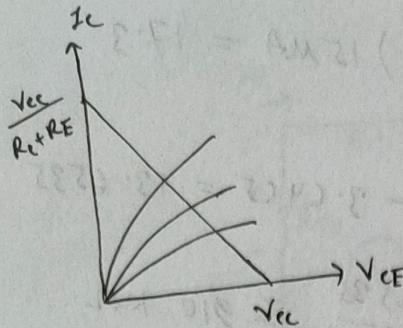
$$V_{CC} = V_{CE} \Rightarrow \text{Cutoff Region}$$



Example from slide,

$$V_{CE} = 18V$$


$$R_C = 2.2k\Omega$$

$$R_E = 1.1k\Omega$$

$$R_B = ?$$

$$I_{C\text{sat}} = \frac{V_{CE}}{R_C + R_E} = \frac{18}{2.2 + 1.1} = 5.45mA$$

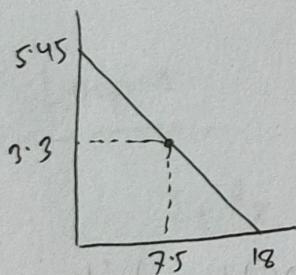Now plot load line and find out Q point. And I_{CQ} and V_{CEQ}



$$I_{CQ} = 3.3mA$$

$$V_{CEQ} = 7.5mA$$

$$I_{BQ} = 15\mu A$$

$$I_c \approx \beta I_B$$

$$\beta = \frac{3.3mA}{15 \times 10^{-6}A} = 220$$

$$I_B = \frac{V_{CC} - V_{BE}}{R_B + (\beta + 1)R_E}$$

$$\Rightarrow 15\mu A = \frac{18 - 0.7}{R_B + (220 + 1)1.1k}$$



$$\therefore 15 \text{ mA } R_B + (221 \times 11 \text{ k}) 15 \text{ mA} = 17.3$$

$$\therefore 15 \text{ mA } R_B = 17.3 - 3.64 \text{ V} = 13.6535$$


$$\therefore R_B = \frac{13.6535}{15 \text{ mA}} \approx 910 \text{ k}\Omega$$

Now reverse for this approximation, Q point will be shift. Reverse and find out Q point.

Voltage Divider Bias

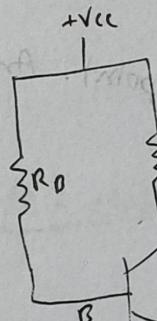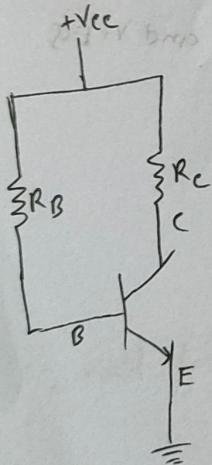

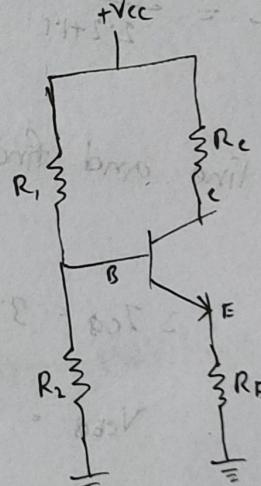
$$A_{voltage} = \frac{R_C}{R_E + R_C} = \frac{81}{39 + 81} = 0.65$$



Voltage divider


Simplify

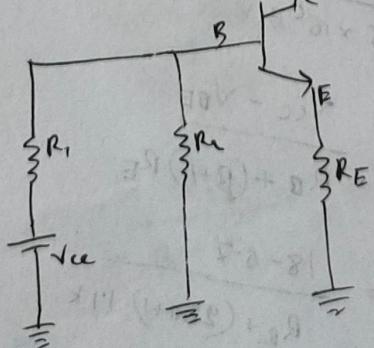

$$R_{TH} = R_1 \parallel R_2$$

$$= \frac{R_1 R_2}{R_1 + R_2}$$
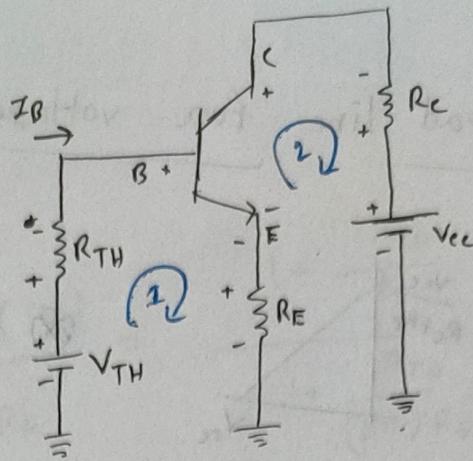
$$V_{TH} = \frac{R_2 \times V_{cc}}{R_1 + R_2}$$



Using KVL,

Loop-1,

$$V_{TH} - I_B R_{TH} - V_{BE} - I_E R_E = 0$$

$$I_E = (\beta + 1) I_B$$

$$\therefore V_{TH} - I_B R_{TH} - V_{BE} - (\beta + 1) I_B R_E = 0$$

$$\therefore I_B = \frac{V_{TH} - V_{BE}}{R_{TH} + (\beta + 1) R_E}$$

Loop-2,

$$I_E R_E + V_{CE} + I_c R_C - V_{cc} = 0$$

$$V_{CE} = V_{cc} - I_c R_C - I_E R_E$$

$$I_c \approx I_E$$

$$\therefore V_{CE} = V_{cc} - I_c (R_C + R_E)$$

$$\therefore I_c = \frac{V_{cc} - V_{CE}}{R_C + R_E}$$


Seacal-D

Calcium Carbonate (From Coral Source) and
Vitamin D₃ (Colecalciferol)

Seacal-DX

Calcium Carbonate (From Coral Source)
and Vitamin D₃ (Colecalciferol)

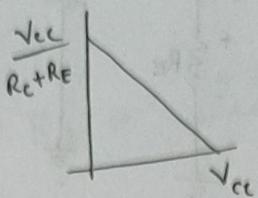④ DC Load line for voltage divider Bias circuit



④ Do some example from slide.

⑤ Stability factor for voltage Divider Bias circuit.

$$S = \frac{\beta + 1}{1 - \beta \frac{\partial I_B}{\partial I_C}}$$

$$\Rightarrow V_{TH} - V_{BE} - R_{TH} I_B - I_C R_E = 0$$

$$I_E = I_B + I_C$$

$$V_{TH} - V_{BE} - R_{TH} I_B - I_C R_E - I_B R_E = 0$$

$$I_B (R_{TH} + R_E) = V_{TH} - V_{BE} - I_C R_E$$

$$\therefore I_B = \frac{V_{TH}}{R_{TH} + R_E} - \frac{V_{BE}}{R_{TH} + R_E} - \frac{I_C R_E}{R_{TH} + R_E}$$

$$\therefore \frac{\partial I_B}{\partial I_C} = - \frac{R_E}{R_{TH} + R_E}$$

$$.1 \quad S = \frac{\beta+1}{1 + \beta \frac{R_E}{R_{TH} + R_E}}$$

$$= \frac{(R_{TH} + R_E) (\beta+1)}{R_{TH} + (\beta+1) R_E} = \frac{1 + \frac{R_{TH}}{R_E}}{1 + \frac{R_{TH}}{(\beta+1) R_E}}$$

$$\therefore R_E \gg R_{TH}$$

$\therefore S = 1$ (Independent) (stable)

④ Collector Feedback Config.

L-21 / 12.10.2023 /

Voltage divider Bias Circuit

Analysis

$$I_{C\text{sat}} = I_{C\text{max}} = \frac{V_{CC}}{R_C + R_E}$$

$$I_C = \frac{V_{CC}}{R_C + R_E} \quad [\text{Now load Line Analysis}]$$

$$V_{CE} = V_{CC}$$

Seacal-D

Calcium Carbonate (From Coral Source) and
Vitamin D₃ (Colecalciferol)

Seacal-DX

Calcium Carbonate (From Coral Source)
and Vitamin D₃ (Colecalciferol)

Design Operation

From slide,

$$V_{cc} = 20 \text{ V}$$

$$8 \text{ mA} = \frac{V_{cc}}{R_c}$$

$$R_c = \frac{20 \text{ V}}{8 \text{ mA}} = 2.5 \text{ k}\Omega$$

$$I_B = \frac{V_{cc} - V_{BE}}{R_B}$$

$$R_B = \frac{V_{cc} - V_{BE}}{I_B} = \frac{20 - 0.7}{40 \text{ mA}} = 47.5 \text{ k}\Omega$$

But standard value of R ,

$$R_c = 2.4 \text{ k}\Omega$$

$$R_B = 470 \text{ k}\Omega$$

$$I_B = \frac{V_{cc} - V_{BE}}{R_B} = \frac{20 - 0.7}{470 \text{ k}\Omega} = 4.1 \text{ mA} \approx 40 \text{ mA}$$

(We can consider upto
5%)



$$I_{CQ} = \frac{1}{2} I_{esat} = \frac{1}{2} \times 8 \text{ mA}$$

$$I_{BQ} = \frac{I_{CQ}}{\beta} = \frac{4 \text{ mA}}{110} = 36.36 \text{ mA}$$

$$I_{BQ} = \frac{V_{cc} - V_{BE}}{R_B + (\beta+1) R_E}$$

$$I_{RC} = \frac{V_{cc} - V_C}{R_C} = \frac{28 - 18}{R_C}$$

$$36.36 \text{ mA} = \frac{28 - 18}{R_B + (111 \times 1) \cdot 4 \text{ mA}}$$

$$R_B = 639.8 \text{ k}\Omega$$

$$\therefore R_B = 639.8 \text{ k} \approx$$

$$R_C = 2.5 \text{ k}\Omega \approx 2.4 \text{ k}\Omega$$

$$R_E = 1 \text{ k}\Omega$$

$$4 \text{ mA} = \frac{28 - 18}{R_C}$$


$$R_C = 2.5 \text{ k}\Omega$$

$$I_{esat} = \frac{V_{cc}}{R_C + R_E}$$

$$R_E = \frac{V_{cc} - R_C I_{esat}}{I_{esat}}$$

$$= \frac{28 - 2.5 \cdot 8}{8}$$

$$= 1 \text{ k}\Omega$$

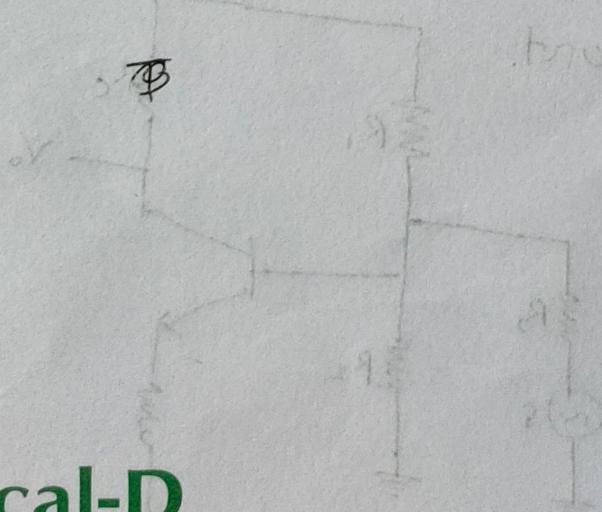


Seacal-D

Calcium Carbonate (From Coral Source) and
Vitamin D₃ (Colecalciferol)

Seacal-DX

Calcium Carbonate (From Coral Source)
and Vitamin D₃ (Colecalciferol)

Transistor Switching Networks

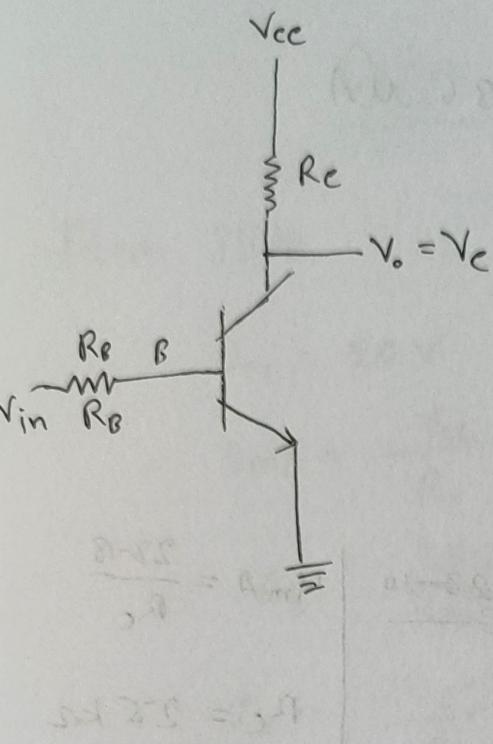

$$I_{c\text{sat}} = \frac{V_{cc}}{R_c}$$

$$I_B = \frac{I_{c\text{sat}}}{\beta} = 40$$

Assume
then
 $I_B > \frac{I_{c\text{sat}}}{\beta}$

$$I_B = \frac{V_{cc} - V_{BE}}{R_B}$$


find out


$$h_{fc} \Rightarrow \beta_{DC}$$

for PNP, just polarity will change

AC Analysis

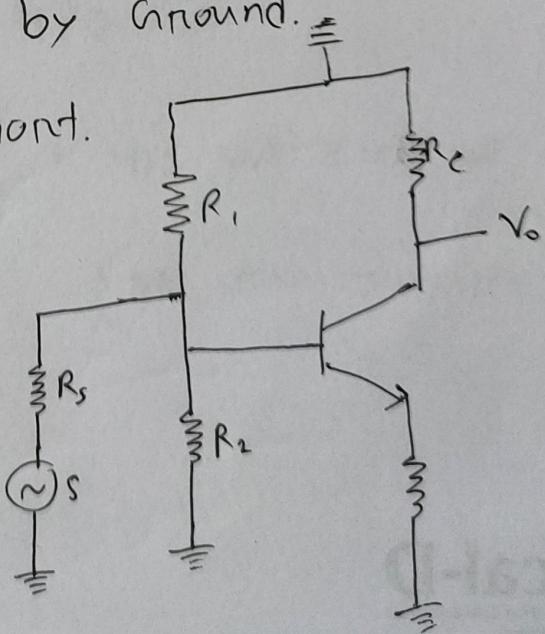- ① Replace DC source by ground.
- ② Capacitor will be short.



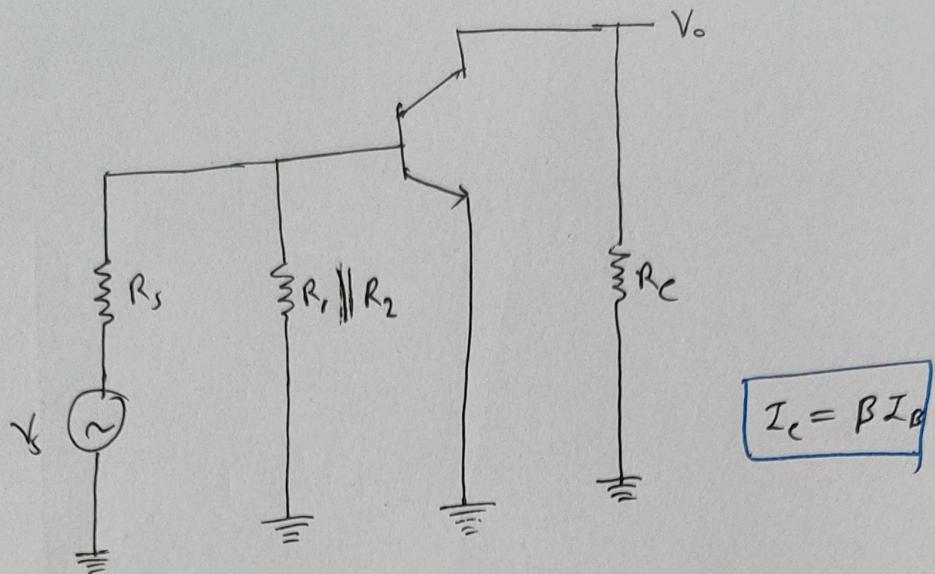

⌚ Why called - controlled - device?

L-23/

Seacal-D

Calcium Carbonate (From Coral Source) and
Vitamin D₃ (Colecalciferol)

Seacal-DX

Calcium Carbonate (From Coral Source)
and Vitamin D₃ (Colecalciferol)