

Spring 2023
EEE/ETE 141L
Electrical Circuits-I Lab (Sec-19)
Faculty: Mr. Saif Ahmed (SfA)
Instructor: Md. Rabiul Karim Khan

Lab Report 07: Verification of Maximum Power Transfer Theorem.

Date of Performance: 30 April 2023	Group no.: 05 <ol style="list-style-type: none">1. Anisa Akter Meem - 22125380422. Sarith Chowdhury - 22125516423. Anindita Das Mishi - 22113646424. Md. Mehedi Hossain – 19222256425. Joy Kumar Ghosh – 2211424642
Date of Submission: 07 May 2023	

Experiment Name: Verification of Maximum Power Transfer Theorem.


Objectives :

- Experimentally Perform Maximum Power Transfer Theorem.
- Perform theoretical calculations.
- Verify the experimental values with theoretical values.

Apparatus :

- Breadboard
- Resistors ($2 \times 10\text{ k}\Omega$)
- Variable Resistors ($0\text{ k}\Omega - 10\text{ k}\Omega$)
- Digital Multimeter (DMM)
- DC Power supply
- Wires


Circuit Diagram:

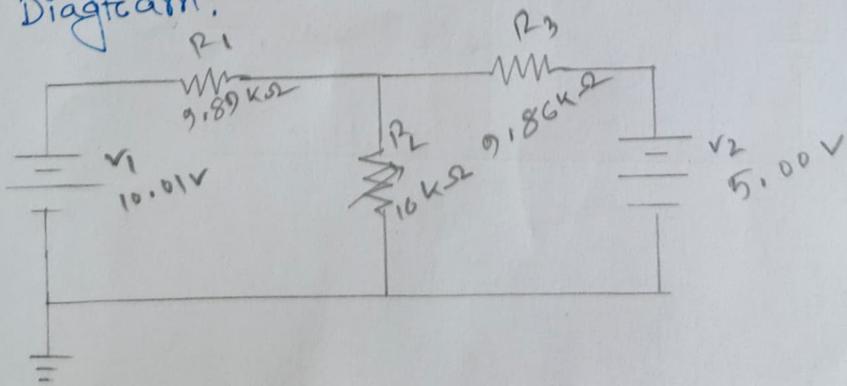


Data table 8 Calculation:

$R_L(k\Omega)$	V_L Experimental (V)	V_2 Theoretical (V)	P_L Experimental (mW)	P_L Theoretical (mW)
1.037	1.240	1.302	1.4827	1.6317
2.018	2.146	2.176	2.2821	2.3464
3.073	2.870	2.878	2.6804	2.6954
4.00	3.345	3.357	2.7973	2.8174
5.02	3.770	3.782	2.8313	2.8493
5.97	4.100	4.106	2.8152	2.8240
6.97	4.380	4.391	2.7524	2.7662
7.99	4.630	4.636	2.6830	2.6899
9.00	4.840	4.844	2.6028	2.6071
10.06	5.030	5.032	2.5150	2.5170


Theoretical value calculation:

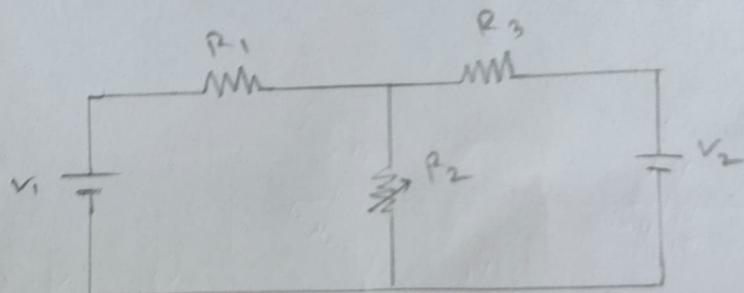

using superposition theorem

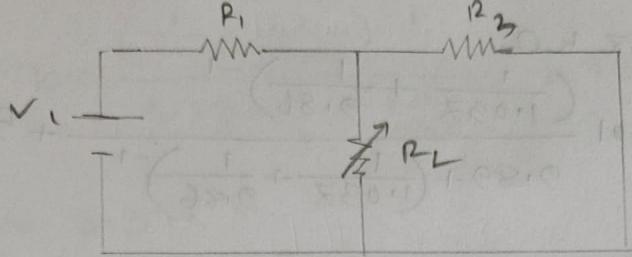
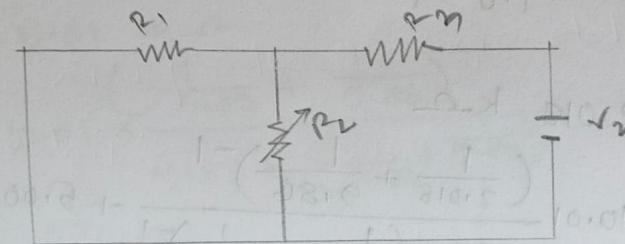
$$V_L' = \frac{\left(\frac{1}{R_L} + \frac{1}{R_3}\right)^{-1}}{R_1 + \left(\frac{1}{R_2} + \frac{1}{R_3}\right)^{-1}} \times V_1$$



$$V_L'' = \frac{\left(\frac{1}{R_L} + \frac{1}{R_1}\right)^{-1}}{R_3 + \left(\frac{1}{R_L} + \frac{1}{R_1}\right)^{-1}} \times V_2$$

$$\begin{aligned} \therefore V_L &= V_L' + V_L'' \\ &= \frac{\left(\frac{1}{R_L} + \frac{1}{R_3}\right)^{-1}}{R_1 + \left(\frac{1}{R_L} + \frac{1}{R_3}\right)^{-1}} \times V_1 + V_2 - \frac{\left(\frac{1}{R_L} + \frac{1}{R_1}\right)^{-1}}{R_3 + \left(\frac{1}{R_L} + \frac{1}{R_1}\right)^{-1}} \end{aligned}$$

$$\text{And } P_L = \frac{(V_L)^2}{R_L}$$

Hence,

$$R_1 = 9.89 \text{ k}\Omega$$

$$R_3 = 9.86 \text{ k}\Omega$$

$$V_1 = 10.01 \text{ V}$$

$$V_2 = 5.00 \text{ V}$$

Now,

For $R_L = 1.032 \text{ k}\Omega$

$$\therefore V_L = 10.01 \frac{\left(\frac{1}{1.032} + \frac{1}{0.86}\right)^{-1}}{0.86 + \left(\frac{1}{1.032} + \frac{1}{0.86}\right)^{-1}} + 5.00 \frac{\left(\frac{1}{1.032} + \frac{1}{0.86}\right)^{-1}}{0.86 + \left(\frac{1}{1.032} + \frac{1}{0.86}\right)^{-1}}$$

$$= 1.302 \text{ V}$$

$$\therefore P_L = \frac{(1.302)^2}{1.032} = 1.6342 \text{ mW}$$

For $R_L = 2.018 \text{ k}\Omega$

$$\therefore V_L = 10.01 \frac{\left(\frac{1}{2.018} + \frac{1}{0.86}\right)^{-1}}{0.86 + \left(\frac{1}{2.018} + \frac{1}{0.86}\right)^{-1}} + 5.00 \frac{\left(\frac{1}{2.018} + \frac{1}{0.86}\right)^{-1}}{0.86 + \left(\frac{1}{2.018} + \frac{1}{0.86}\right)^{-1}}$$

$$= 2.176 \text{ V}$$

$$\therefore P_L = \frac{(2.176)^2}{2.018} = 2.3464 \text{ mW}$$

For $R_L = 3.073 \text{ k}\Omega$

$$\therefore V_L = 10.01 \frac{\left(\frac{1}{3.073} + \frac{1}{0.86}\right)^{-1}}{0.86 + \left(\frac{1}{3.073} + \frac{1}{0.86}\right)^{-1}} + 5.00 \frac{\left(\frac{1}{3.073} + \frac{1}{0.86}\right)^{-1}}{0.86 + \left(\frac{1}{3.073} + \frac{1}{0.86}\right)^{-1}}$$

$$= 2.878 \text{ V}$$

$$\therefore P_L = \frac{(2.878)^2}{3.073} = 2.6954 \text{ mW}$$

For $R_L = 4.00 \text{ k}\Omega$,

$$V_L = 10.01 \frac{\left(\frac{1}{4} + \frac{1}{0.86}\right)^{-1}}{0.86 + \left(\frac{1}{4} + \frac{1}{0.86}\right)^{-1}} + 5.00 \frac{\left(\frac{1}{4} + \frac{1}{0.86}\right)^{-1}}{0.86 + \left(\frac{1}{4} + \frac{1}{0.86}\right)^{-1}}$$
$$= 3.352 \text{ V}$$

$$P_L = \frac{(3.352)^2}{4.00} = 2.8124 \text{ mW}$$

For $R_L = 5.02 \text{ k}\Omega$,

$$V_L = 10.01 \frac{\left(\frac{1}{5.02} + \frac{1}{0.86}\right)^{-1}}{0.86 + \left(\frac{1}{5.02} + \frac{1}{0.86}\right)^{-1}} + 5.00 \frac{\left(\frac{1}{5.02} + \frac{1}{0.86}\right)^{-1}}{0.86 + \left(\frac{1}{5.02} + \frac{1}{0.86}\right)^{-1}}$$
$$= 3.782 \text{ V}$$

$$P_L = \frac{(3.782)^2}{5.02} = 2.8493 \text{ mW}$$

For $R_L = 5.92 \text{ k}\Omega$,

$$V_L = 10.01 \frac{\left(\frac{1}{5.92} + \frac{1}{0.86}\right)^{-1}}{0.86 + \left(\frac{1}{5.92} + \frac{1}{0.86}\right)^{-1}} + 5.00 \frac{\left(\frac{1}{5.92} + \frac{1}{0.86}\right)^{-1}}{0.86 + \left(\frac{1}{5.92} + \frac{1}{0.86}\right)^{-1}}$$
$$= 4.106 \text{ V}$$

$$P_L = \frac{(4.106)^2}{5.92} = 2.8240 \text{ mW}$$

For $R_L = 6.92 \text{ k}\Omega$,

$$V_L = 10.01 \frac{\left(\frac{1}{6.92} + \frac{1}{0.86}\right)^{-1}}{0.86 + \left(\frac{1}{6.92} + \frac{1}{0.86}\right)^{-1}} + 5.00 \frac{\left(\frac{1}{6.92} + \frac{1}{0.86}\right)^{-1}}{0.86 + \left(\frac{1}{6.92} + \frac{1}{0.86}\right)^{-1}}$$
$$= 4.391 \text{ V}$$

$$P_L = \frac{(4.391)^2}{6.92} = 2.7662 \text{ mW}$$

$$\text{For } R_L = 2.99 \text{ k}\Omega$$

$$V_L = 10.01 \frac{\left(\frac{1}{2.99} + \frac{1}{9.86}\right)^{-1}}{9.89 + \left(\frac{1}{2.99} + \frac{1}{9.86}\right)^{-1}} + 5.00 \frac{\left(\frac{1}{2.99} + \frac{1}{9.86}\right)^{-1}}{9.86 + \left(\frac{1}{2.99} + \frac{1}{9.86}\right)^{-1}}$$

$$= 4.636 \text{ V}$$

$$P_L = \frac{(4.636)^2}{2.99} = 2.6899 \text{ mW}$$

$$\text{For } R_L = 9.00 \text{ k}\Omega$$

$$V_L = 10.01 \frac{\left(\frac{1}{9} + \frac{1}{9.86}\right)^{-1}}{9.89 + \left(\frac{1}{9} + \frac{1}{9.86}\right)^{-1}} + 5.00 \frac{\left(\frac{1}{9} + \frac{1}{9.86}\right)^{-1}}{9.86 + \left(\frac{1}{9} + \frac{1}{9.86}\right)^{-1}}$$

$$= 4.844 \text{ V}$$

$$P_L = \frac{(4.844)^2}{9.00} = 2.6071 \text{ mW}$$

$$\text{For } R_L = 10.06 \text{ k}\Omega$$

$$V_L = 10.01 \frac{\left(\frac{1}{10.06} + \frac{1}{9.86}\right)^{-1}}{9.89 + \left(\frac{1}{10.06} + \frac{1}{9.86}\right)^{-1}} + 5.00 \frac{\left(\frac{1}{10.06} + \frac{1}{9.86}\right)^{-1}}{9.86 + \left(\frac{1}{10.06} + \frac{1}{9.86}\right)^{-1}}$$

$$= 5.032 \text{ V}$$

$$P_L = \frac{(5.032)^2}{10.06} = 2.5170 \text{ mW}$$

Theoretical value of maximum power.

$$R_{TH} = 1.94 \text{ k}\Omega$$

$$V_{TH} = 2.520 \text{ V}$$

$$P_{\max} = \frac{(V_{TH})^2}{4 R_{TH}}$$

$$= \frac{(2.520)^2}{4 \times 1.94}$$

$$= 2.8619 \text{ mW}$$

From graph

$$R_{TH} = 4.7 \text{ k}\Omega$$

$$R P_{max} = 2.8500 \text{ mW}$$

Error :
$$\left| \frac{2.8619 - 2.8500}{2.8619} \right| \times 100\% = 0.421\%$$

Graph: Attached

Result Analysis: From the table of this experiment we found that the theoretical and measured values of V_L and P_L are approximately the same. We also get that the theoretical value of P_{max} and the P_{max} from the graph are also approximately the same. Therefore, our circuits completely follow the maximum power transfer theorem.

Questions and Answers:

1. Already showed in data-table.
2. Already showed in data-table.

Discussion:

After completing this experiment, we learnt to verify the Maximum Power Transfer Theorem. Now we can calculate the maximum power of a circuit using this theorem. We need to remove the load and measure the R_L and the voltage of Thevenin's Theorem at points a and b; then, using the maximum power transfer formula, we can calculate the maximum power. In this experiment, we don't face any difficulties. We completed this experiment on time.

Attachment:


① signed Data table.

② simulation using Multisim.

③ Graph of R_L vs P_{max} .

$\rightarrow P(\text{mW})$

Group - 5
Roll No.

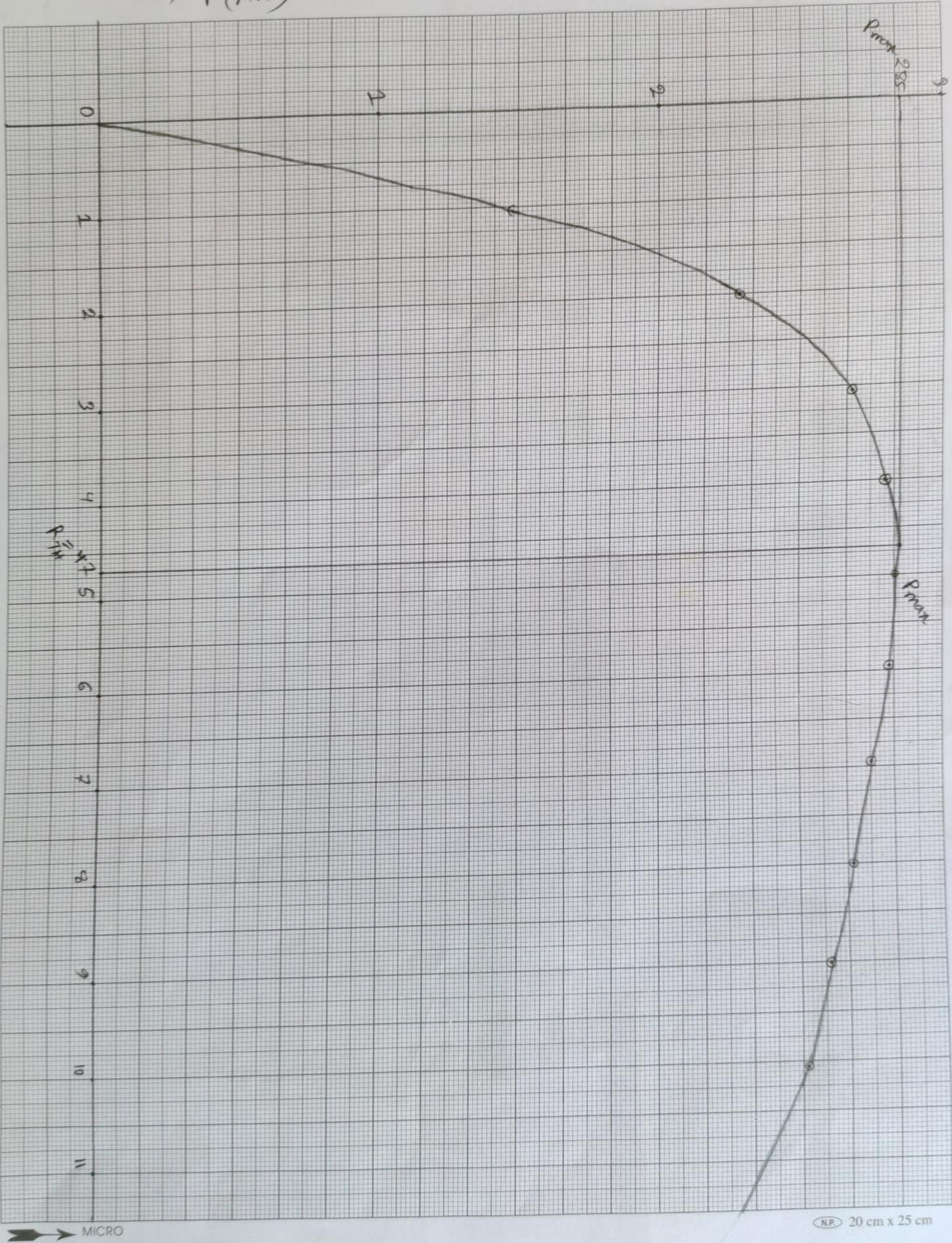


MICRO

(N.P.) 20 cm x 25 cm

Design Toolbox

 L7-E1


Hierarchy Visibility Pr ▲ ▼

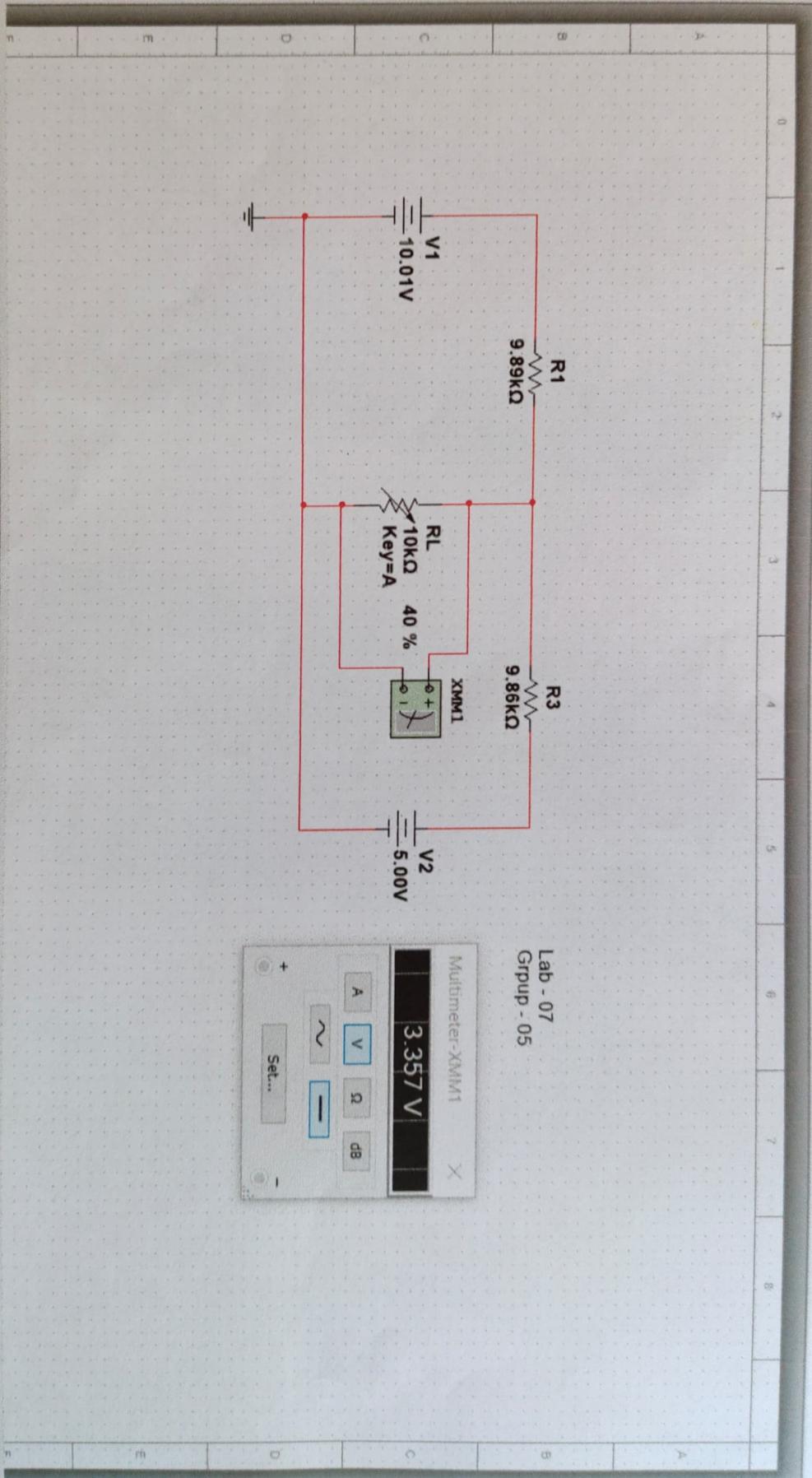 L7-E1

Hierarchy Visibility Pr ▲ ▼

Multisim - Wednesday, May 3, 2023, 7:51:48 PM

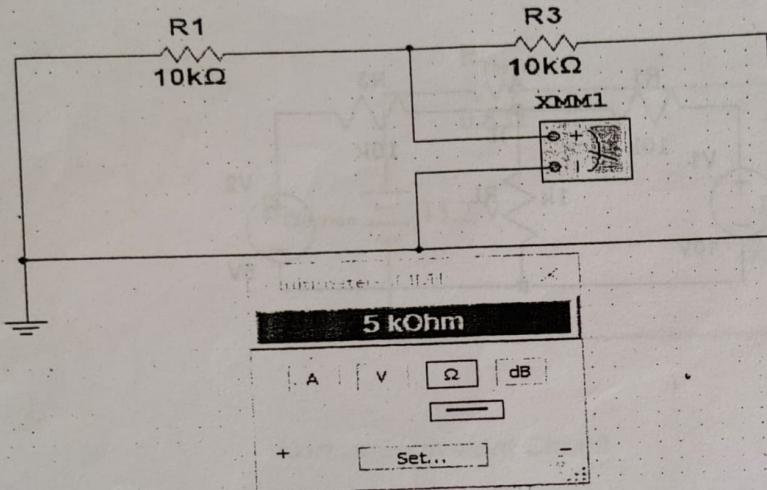Thevenin's equivalent resistance, R_{TH} :



Data Collections:

Group No. _____

Instructor's Signature _____

Table 1:

Theoretical R	Measured R	% Error
	$R_i = 9.77 \text{ k}\Omega, R_3 = 10.150 \text{ k}\Omega$	
	$R_L = 1.005 \text{ k}\Omega, R_{Th} = 4.730 \text{ k}\Omega$	

Table 2:

Value	Measured	% Error
$V_L(V)$	1.263V	
$I_L(\text{mA})$		


Table 3:

Measurement	Measured	Calculated	% Error
$V_{TH}(V)$	7.520		
$I_N(\text{mA})$	1.520		
$R_{TH}(\text{k}\Omega) = R_N(\text{k}\Omega)$	4.980		
$V_L(V)$	1.274		
$I_L(\text{mA})$			

$$I_m = 1.55 \text{ mA}$$

$$\sqrt{R_L} = 1.293 \text{ V}$$

Norton's equivalent circuit:

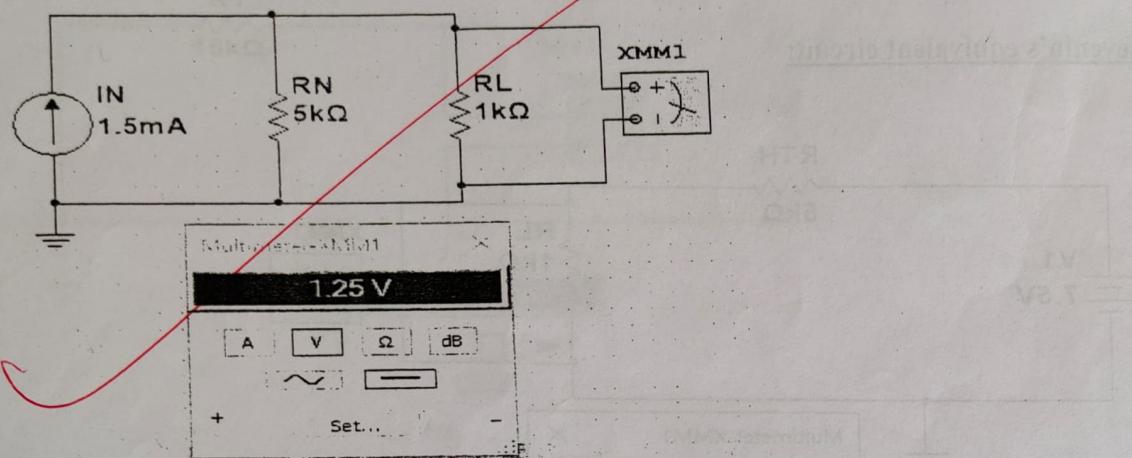


Rahul
9/4/23

Table 4:

$R_L (k\Omega)$	$V_L (\text{Experimental})$	$P_L (\text{Experimental})(mW)$
1.0 (1.037)	1.240	1.4927 ✓
2.0 (2.018)	2.146	2.2821
3.0 (3.073)	2.870	2.6804
4.0 (4.88)	3.345	2.7973
5.0 (5.82)	3.770	2.8313
6.0 (5.97)	4.100	2.8157
7.0 (6.97)	4.38	2.7524
8.0 (7.99)	4.63	2.6830
9.0 (9.80)	4.84	2.6029
10 (10.06)	5.03	2.5150

Graph :

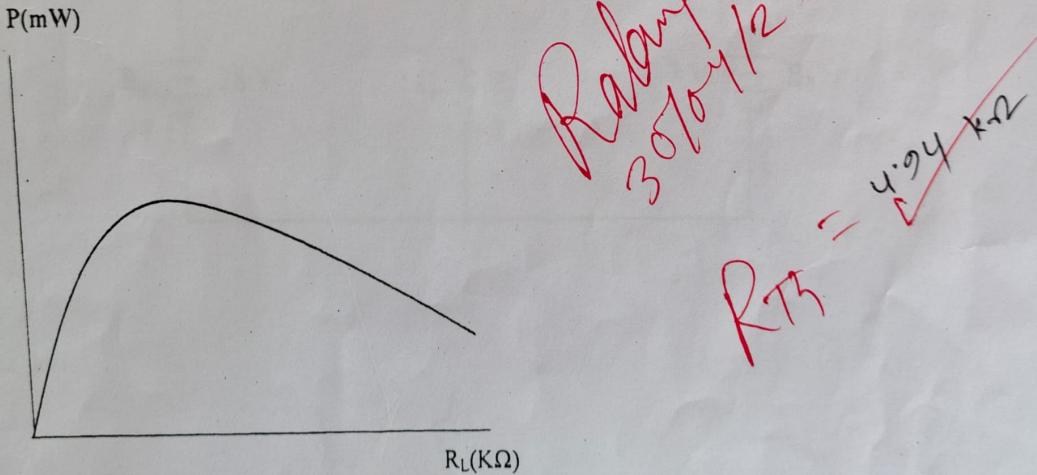

Report :

- Find the theoretical values of V_L , R_{TH} , V_{TH} , P_{MAX} and I_N .
- Compare the theoretical values with practical values.