



North South University
Department of Electrical & Computer Engineering

LAB REPORT

Course Code : EEE111L

Course Title: Analog Electronics-1

Course Instructor: DMM

Experiment Number: 06

Experiment Name:

The input-output characteristics of CE (common emitter) configuration of BJT

Date of Experiment: 23rd of September, 2023

Date of Submission: 30th of September, 2023

Section: 11

Group Number: 05

Submitted By		Score
	Student Name	ID
1.	Afrin Akter	2112246642
2.	Joy Kumar Bhosh	2211424642
3.	Sazid Hasan	2211513642
4.	Sabrina Haque Tithi	2031265642
5.	Mahmudul Hasan	2011551043

Name of the Experiment: The input-output characteristics of CE (common emitter) configuration of BJT.

Objectives: Study of the input-output characteristics of CE (common emitter) configuration of BJT

Equipment & Components:

Serial	Component Details	Specification	Quantity
1	Transistor	BC 548	1 Piece
2	Resistor	100 kΩ, 1 kΩ	1 piece each
3	Trainer Board		1 unit
4	DC Power Supply		1 unit
5	Digital Multimeter		1 unit
6	Cords & Wire		as required.

Theory: A resistor has three doped regions, namely Emitter, Base and Collector. In common emitter configuration, base is the input terminal, collector is the output terminal, and emitter is the common terminal for both input and output. That means the base terminal and common emitter are known as input terminals whereas collector terminal and common emitter terminal are known as output terminals. The emitter terminal is grounded and it is regarded as the CE configuration. CE is the most

Widely used transistor.

The emitter is heavily doped so that it can eject free majority carrier to the base. The base being the most lightly doped, it passes the most of the emitter injected electron into the collector. When V_{BB} is greater than barrier potential, emitter electrons will also enter base region. So, the free electrons can follow either into the base or into the collector. There are three different current in a transistor namely emitter current (I_E), collector current (I_c) and the base current (I_B).

$$\text{The Formula, } I_E = I_c + I_B$$

$$\text{current gain} = \frac{I_c}{I_B}$$

→ The characteristics is measured by two characteristics of

a. Input characteristics

b. Output characteristics

→ ~~and~~ Input characteristics Curve: It describes the relationship between the input current and input voltage on base-emitter voltage for the constant output voltage (V_{CE})

The input voltage V_{BE} is increased from zero to different voltage.

→ Output characteristics: It describes the relationship between output current (I_c) and output voltage (V_{CE}).

- The input current is kept constant at 0 mA and the output voltage V_{CE} is increased from zero volts to different voltage levels.
- It has three regions namely Saturation, Active and cut off region
- The input current is increased from 0 mA to 20 mA by adjusting the output voltage. The input current is kept constant at 20 mA
- When the collector diode of the transistor becomes reverse biased, the graph becomes horizontal. This region is called active region.
- The base current being zero there is some collector current. This region of the transistor curve is known as the cut off region. The small current is called the collector cut off current.
- Different values of ~~I_B~~ I_B creates individual curves.

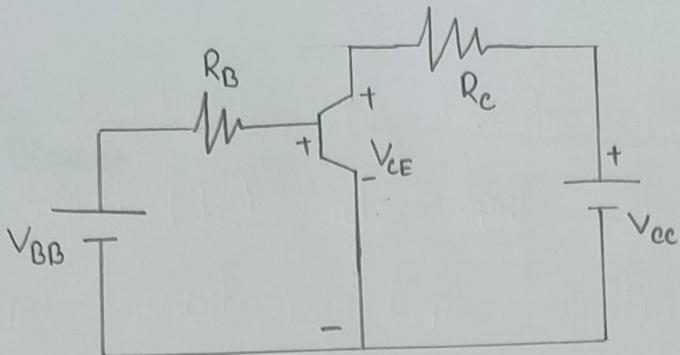


Figure: Biasing of a NPN transistor

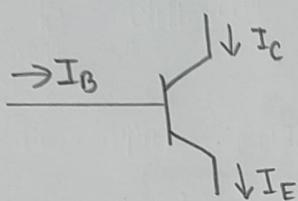


Figure: Different current in transistor

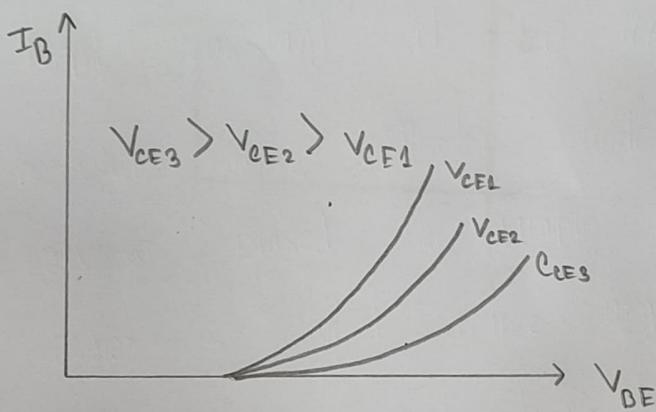


Figure: Input Characteristics


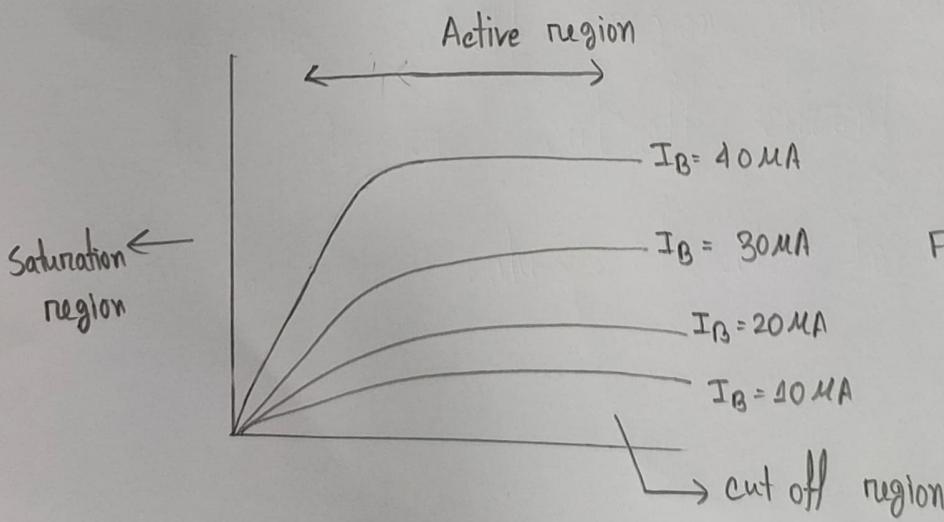


Figure: Output Characteristics

Circuit Diagram

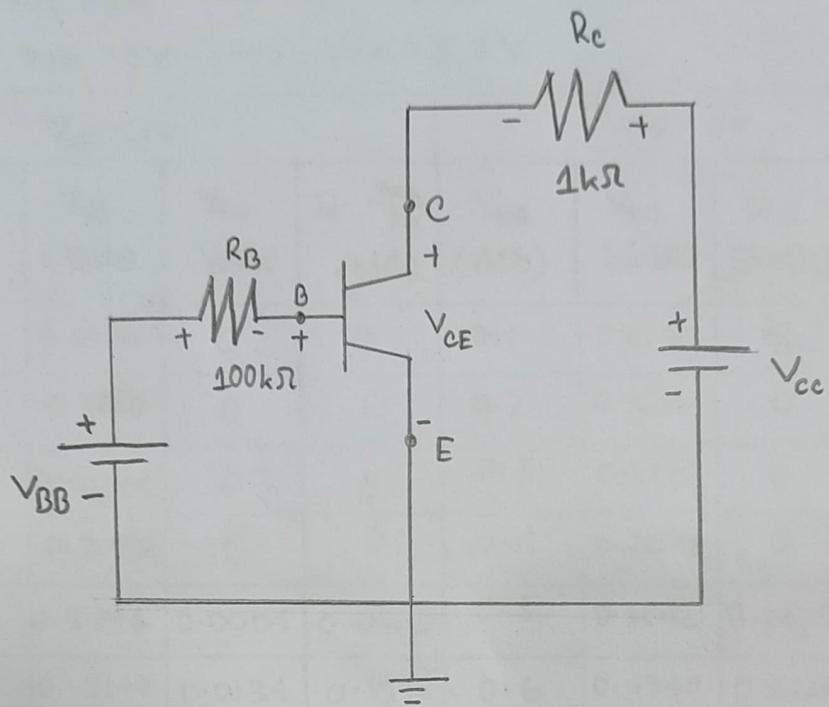

Data Table

$$R_B = 100.2 \text{ k}\Omega$$

$$R_C = 1.63 \text{ k}\Omega$$

Table -1

When, $V_{CE} = 2V \rightarrow V_{CC} = 1.9V$

When, $V_{CE} = 5V \rightarrow V_{CC} = 5.0V$

$V_{CE} = 2V$				$V_{CE} = 5V$			
V_{BB} (Volts)	V_{BE} (Volts)	V_{RB} (Volts)	$I_B = \frac{V_{RB}}{R_B}$ (μA)	V_{BB} (Volts)	V_{BE} (Volts)	V_{RB} (Volts)	$I_B = \frac{V_{RB}}{R_B}$ (μA)
0.1	0.0106	0	0	0.1	0.0235	0	0
0.2	0.1770	0	0	0.2	0.9610	0	0
0.3	0.1894	0	0	0.3	0.2377	0	0
0.4	0.3496	0	0	0.4	0.2893	0	0
0.5	0.3996	0.0004	0.0040	0.5	0.3842	0.0185	0.1846
0.6	0.5140	0.0134	0.1340	0.6	0.4940	0.0600	0.5958
0.7	0.5770	0.0862	0.8618	0.7	0.5600	0.1243	1.2408
0.8	0.5920	0.1331	1.3307	0.8	0.5870	0.2430	2.4251
0.9	0.6130	0.2560	2.5595	0.9	0.6110	0.2852	2.8630
1.0	0.6160	0.2924	2.9234	1.0	0.6330	0.5490	5.4790
1.2	0.6310	0.9370	9.3681	1.2	0.6663	0.6780	6.7665
1.4	0.6410	0.9980	9.9780	1.4	0.6840	0.8820	8.8024
1.6	0.6430	1.1090	11.0878	1.6	0.6950	1.0500	10.5190
1.8	0.6460	1.3470	13.4673	1.8	0.6980	1.2960	12.9341
2.0	0.6480	1.5350	15.3469	2.0	0.6930	2.2440	22.3952
3.0	0.6510	2.3290	23.2853	3.0	0.6980	3.3150	22.3952
4.0	0.6560	3.2950	32.9434	4.0	0.7110 0.6930	4.3700	33.0838
5.0	0.6560	4.3500	43.4913	5.0	0.7110	4.3700	43.6127

Table - 2

when $V_{RB} = 2V \longrightarrow V_{BB} = 2.6V$

when $V_{RB} = 5V \longrightarrow V_{BB} = 5.6V$

$I_B = 20\mu A$				$I_B = 50\mu A$			
V_{ee} (Volts)	V_{CE} (Volts)	V_{RE} (Volts)	$I_C = \frac{V_{RE}}{R_E}$ (mA)	V_{ee} (Volts)	V_{CE} (Volts)	V_{RE} (Volts)	$I_C = \frac{V_{RE}}{R_E}$ (mA)
0.1	0.0037	0.0172	0.0167	0.1	0.0070	0.0409	0.0392
0.2	0.0994	0.0752	0.0730	0.2	0.0103	0.1103	0.1070
0.3	0.0340	0.1945	0.1488	0.3	0.0171	0.1619	0.1571
0.4	0.0438	0.3160	0.3067	0.4	0.0238	0.2679	0.2600
0.5	0.0510	0.3440	0.3370	0.5	0.0325	0.3964	0.3848
0.6	0.1012	0.4940	0.4310	0.6	0.0321	0.4680	0.4543
0.7	0.1223	0.5700	0.5530	0.7	0.0358	0.6160	0.5980
0.8	0.0649	0.6280	0.6097	0.8	0.0385	0.6510	0.6320
0.9	0.0691 0.0658	0.7560	0.7339	0.9	0.0417	0.7970	0.7732
1.0	0.0756 0.0691	0.8270	0.8029	1.0	0.0446	0.9210	0.8941
1.2	0.0825 0.0756	1.0800	1.0485	1.2	0.0495	1.0970	1.0650
1.5	0.0975 0.0825	1.3190	1.2805	1.5	0.0564	1.3780	1.3378
2.0	0.1094 0.0975	1.7920	1.7398	2.0	0.0654	1.8720	1.8223
2.5	0.1193 0.1094	2.4055 2.3320	2.1640	2.5	0.0729	2.3250	2.2570
3.0	0.1291 0.1193	2.18050	2.7233	3.0	0.0790	2.8750	2.7869
5.0	4.4800 0.1691	4.7900	4.6504	5.0	0.1034	4.7800	4.6407
10.0	9.3100 4.4800	5.4000	5.2427	10.0	0.1761	9.6500	9.3689
15.0	15.3100	5.6300	5.4660	15.0	0.2300	10.2300	9.9320
20.0	14.0900	5.8800	5.6893	20.0	0.1820	11.1800	10.8573
				23.0	10.7500	11.9000	10.1592
				26.0	12.9870	12.3600	10.3252
				30.0	13.7580	16.6500	10.6720

Answer to the question no: 3

When $I_B = 50 \text{ mA}$

$$I_C = 10 \text{ mA}$$

$$\therefore \beta = \frac{I_C}{I_B} = \frac{10}{50} = 0.2$$

When

$$I_B = 20 \text{ mA}$$

$$I_C = 5.68 \text{ mA}$$

$$\therefore \beta = \frac{I_C}{I_B} = \frac{5.68}{20} = 0.284$$

Answer to the ques no:4

From graph of I_c vs V_{CE}

$$V_{cc} = V_{CE} = \text{---} 15 V$$

At saturation region

$$I_c (\text{sat}) = \frac{V_{cc}}{R_c}$$

$$= \frac{15}{1k\Omega}$$

$$= \text{---} 15 \text{ mA}$$

$$\therefore V_{CE} = 0 V$$

At cut off region

$$V_{CE} (\text{cut off}) = V_{cc} = \text{---} 15 V$$

$$I_c = 0 \text{ mA}$$

From graph we draw the load line and obtain Q point at $(14.09, 5.68)$
 $(5, 10)$

Discussion:

In this experiment, we have observed the input-output characteristics of common emitter configuration of BJT. We start by building the circuit given on the manual, where we use two resistors of resistance $R_B = 100\text{ k}\Omega$ and $R_C = 1\text{ k}\Omega$. Initially, we set V_{BB} to 0V and then vary V_{CC} until V_{CE} becomes 2V. We kept checking V_{CE} using a DMM to check if it was close to 2V. After doing this, we vary V_{BB} from 0.1V to 5V and record V_{BE} and V_{RB} where V_{BE} is the voltage across the base and emitter and V_{RB} is the voltage across the resistor R_B . We repeat the same steps for $V_{CE} = 5\text{ V}$ where we set V_{BB} to 0V and then make $V_{CE} 5\text{ V}$ and then take the readings of V_{BE} and V_{RB} . For both V_{CE} , we calculate I_B by dividing V_{RB}/R_B . In this way, we obtain all the data for the input characteristics of BJT.

For the output characteristics of BJT, we use the same circuit as before. However, we now set the V_{CC} to 0V and

in order to achieve $I_B = 20 \mu A$, we vary V_{BB} until V_{RB} becomes 2V. After doing this, we vary V_{CC} from 0.1V to 20V and record the corresponding V_{CE} and V_{RE} and calculate I_C by dividing V_{RE}/R_E where, V_{CE} is the voltage across collector and emitter and V_{RE} is the resistance across the resistor R_E . We follow the same steps for $I_B = 50 \mu A$


During the measurement of table-2 when $I_B = 20 \mu A$, we had faced some problems. DMM was not giving stable output. Then we rechecked the circuit, and found that, for continuous measurement, some pins of the breadboard got damaged. Then we re-construct the circuit and started to measure again. This time we didn't face any problems. DMM was working fine. Hence, we complete our experiment successfully.


Table of Contribution


No.	Name	ID	Contribution
01	Afrin Akter	2112246642	Took the measurement of table-1 when $V_{CE} = 2V$, Report writing, Graph plotting, Simulation.
02	Sazid Hasan	2211513642	Took the measurement of table-1 when $V_{CE} = 5V$, Built the circuit
03	Joy Kumar Ghosh	2211424642	Took the measurement of table-2 when $I_B = 20 \mu A$, monitoring all the process, Operating the dc power supply, I_B calculation.
04	Sabrina Hague Tithi	2031265642	Took the measurement of table-2 when $I_B = 50 \mu A$, monitoring process, I_C calculation
05	Mahmudul Hasan	2011551043	-


Attachment:

1. Simulation
2. Graph
3. Data Sheet.

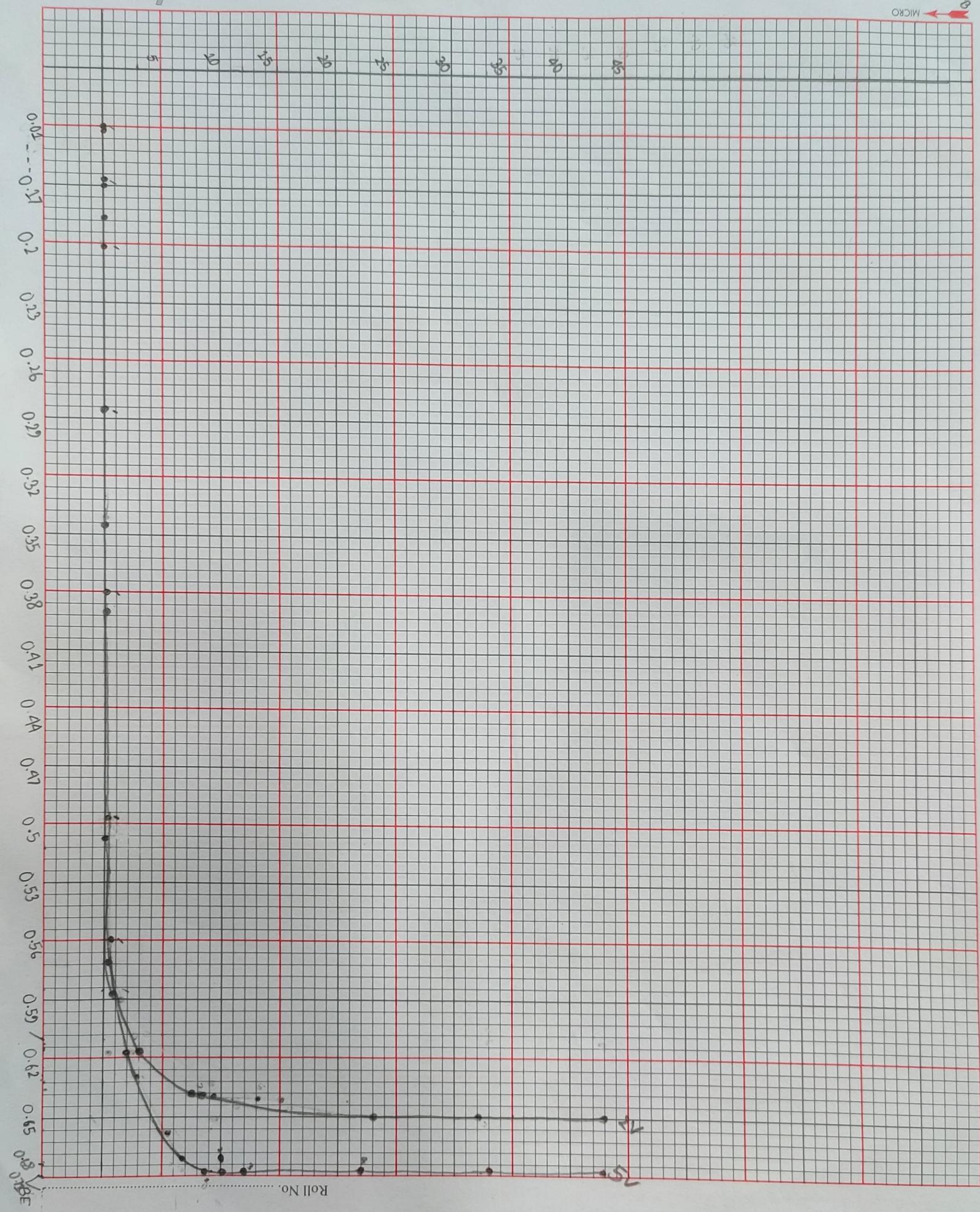


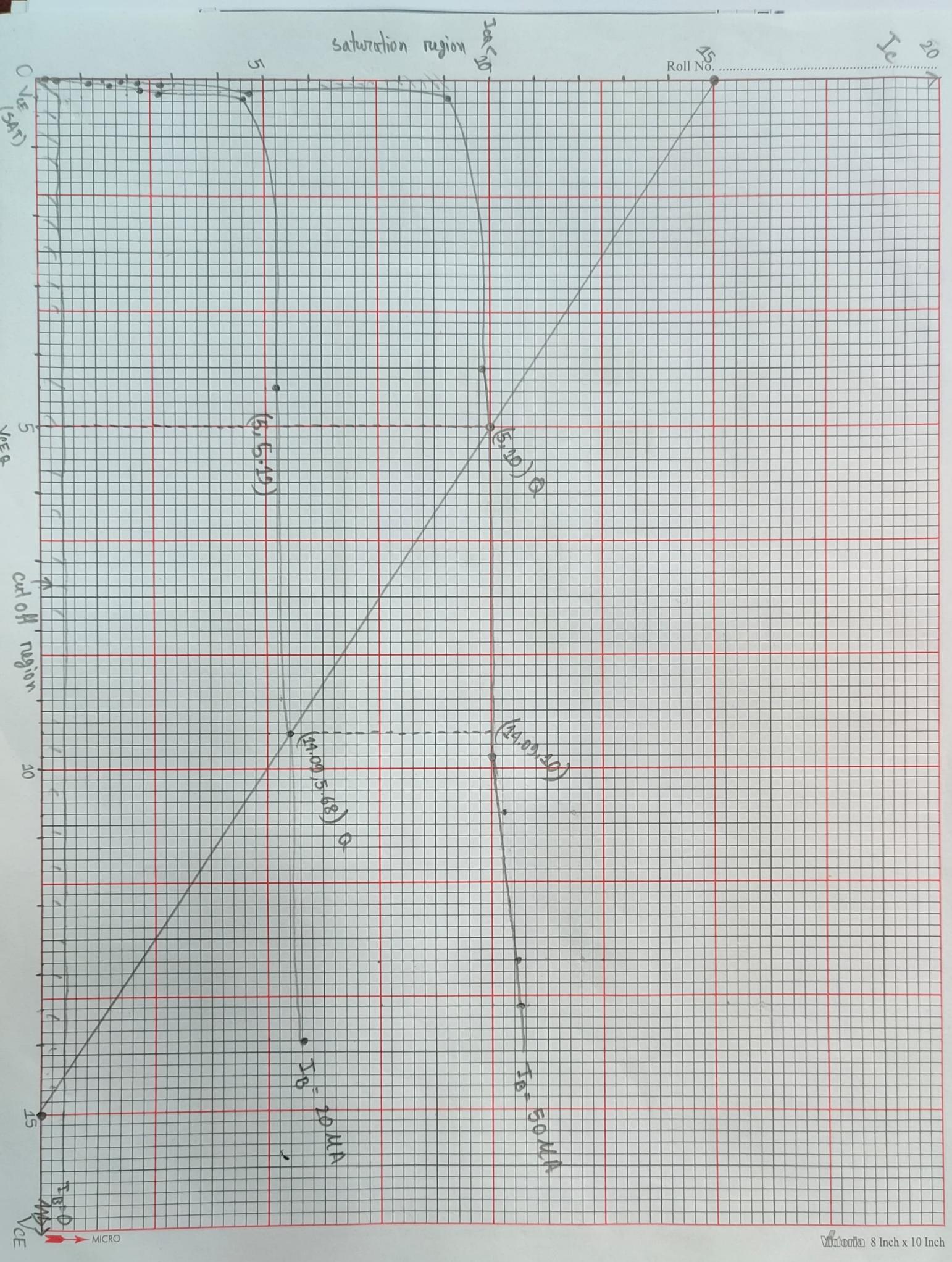


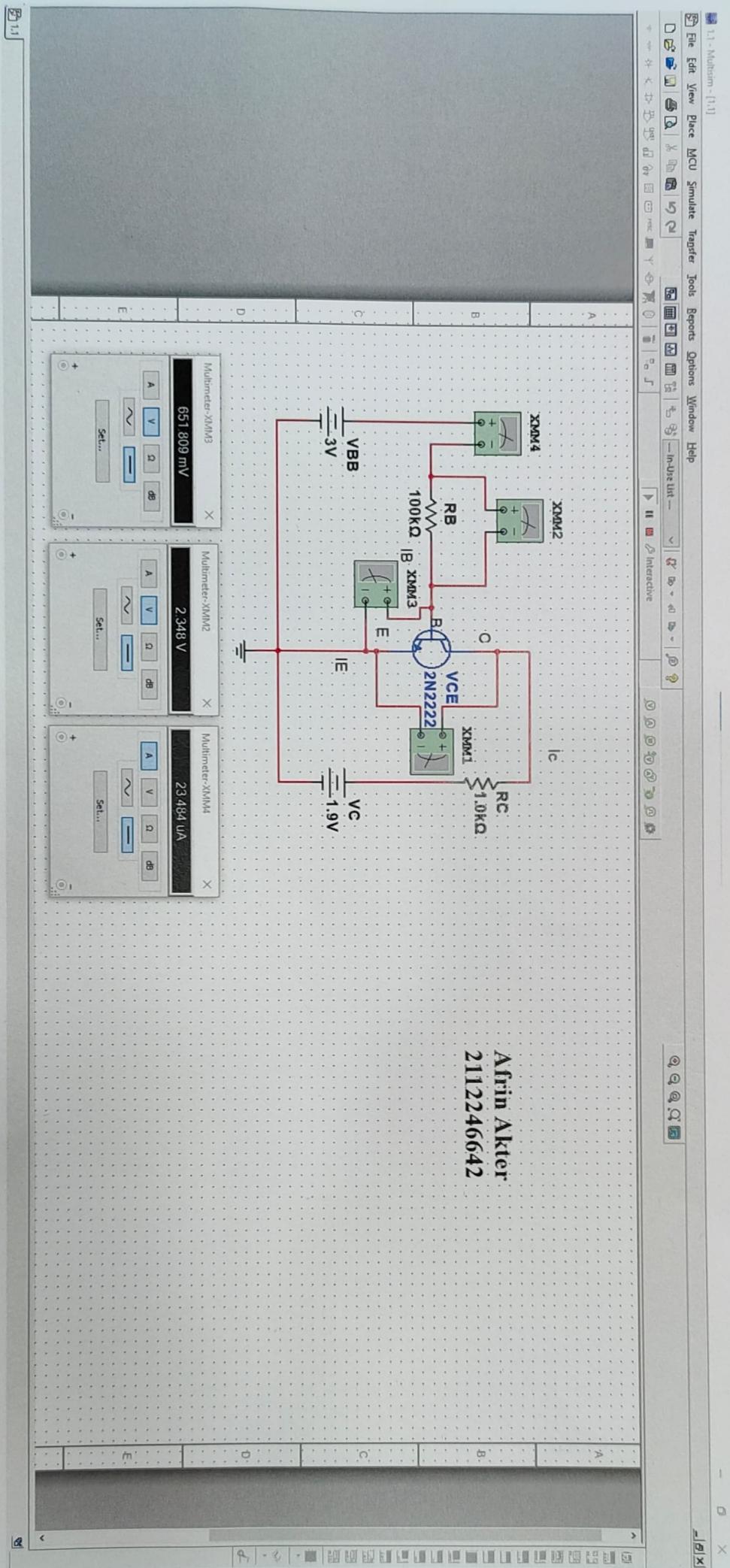

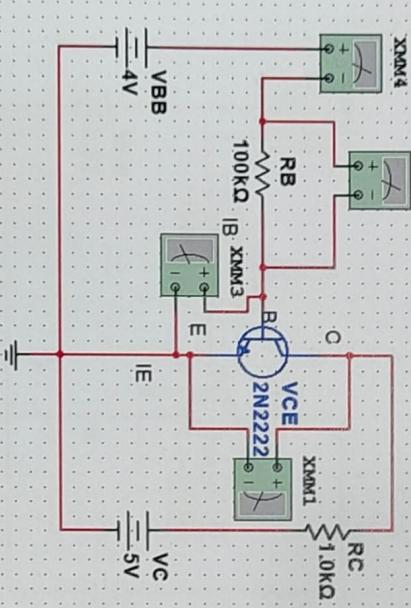

AIR Aktie
2112246642

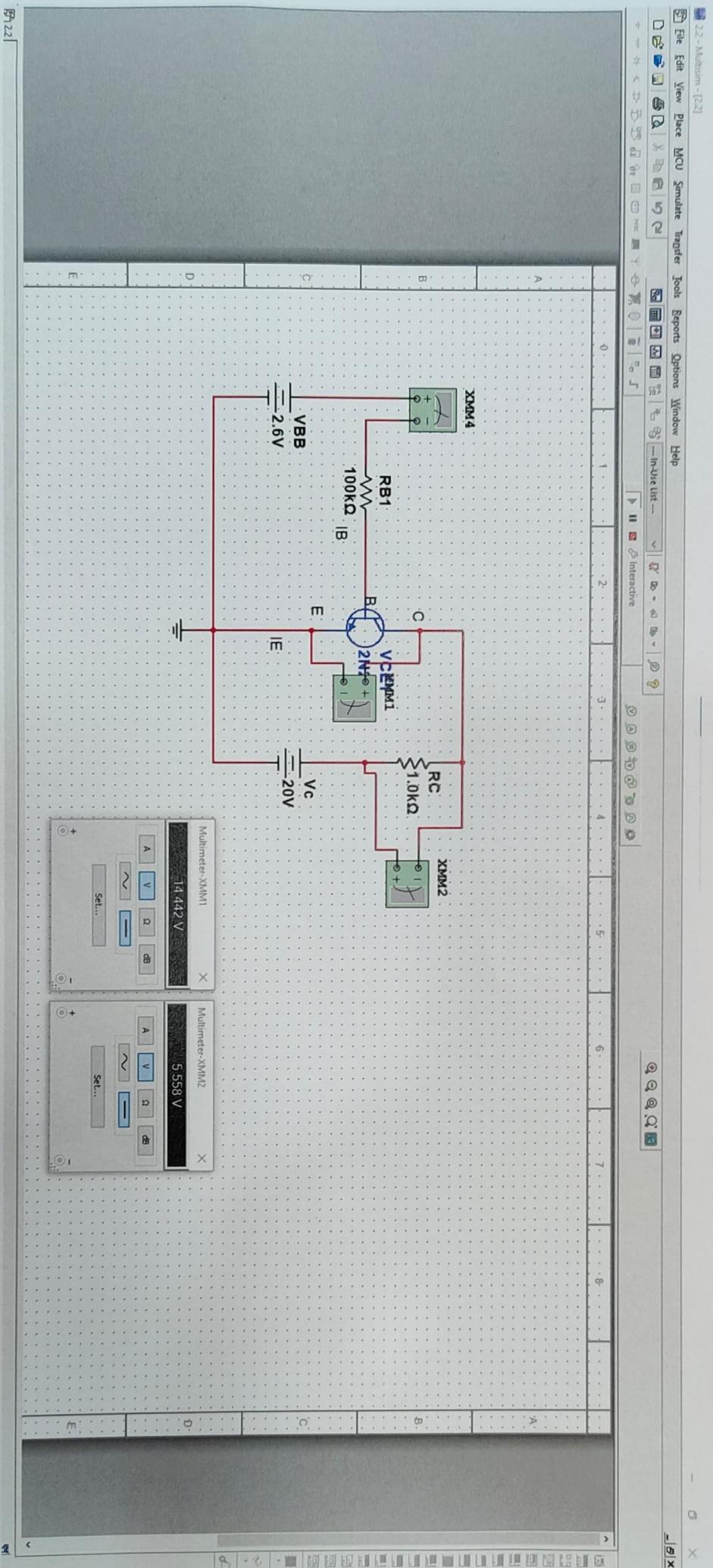

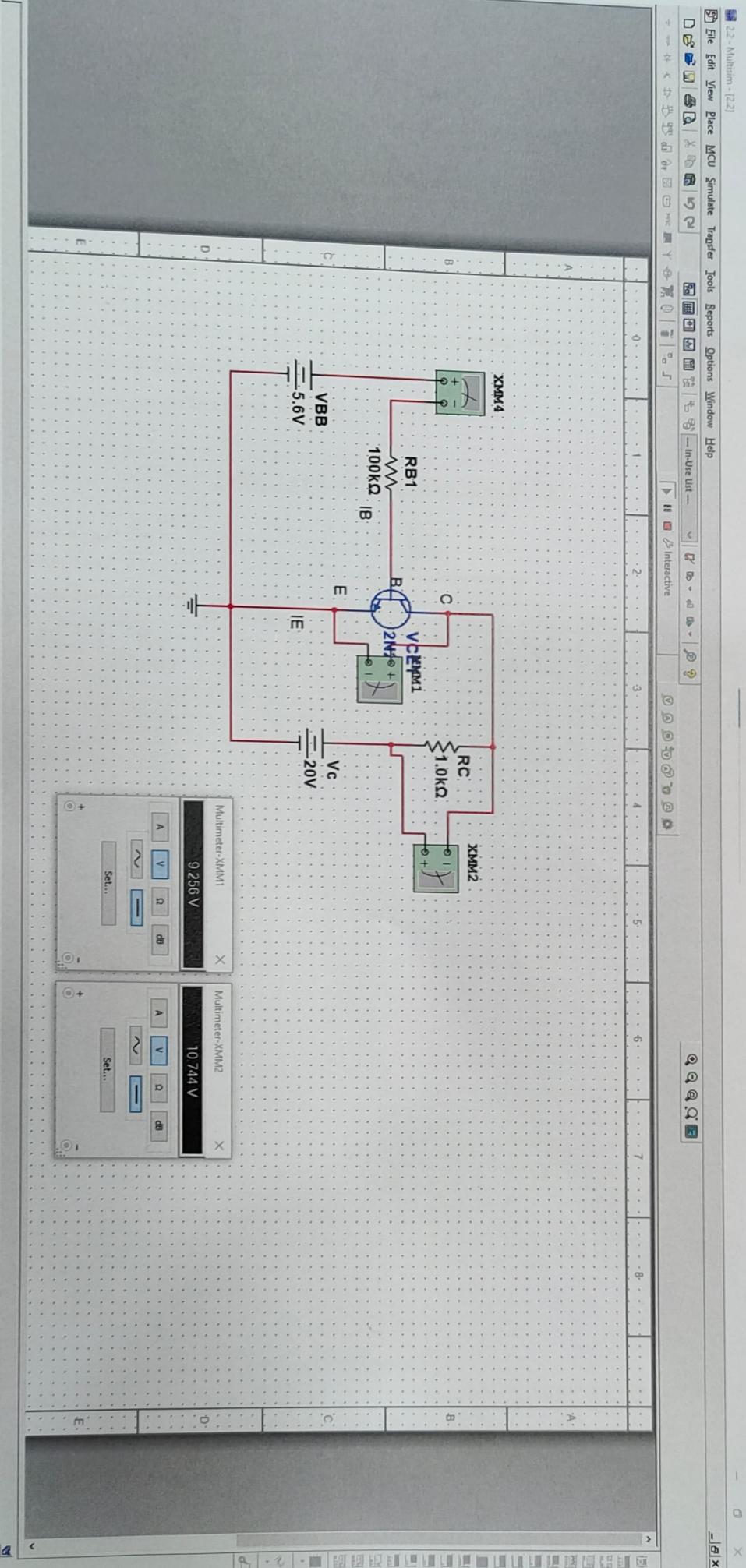

NORTH SOUTH UNIVERSITY
DEPARTMENT OF ELECTRICAL & COMPUTER ENGINEERING

Output Characteristics:

1. Connect the circuit as shown in the circuit diagram.
2. By varying V_{BB} , make $V_{RB} = 2V$. This makes $I_B = 20\mu A$.
3. Varying V_{CC} gradually in steps, measure Collector-Emitter Voltage, V_{CE} and V_{RC} . Calculate $I_C = \frac{V_{RC}}{R_C}$. Fill up Table-2.
4. Repeat above procedure (step 3) for $I_B = 50\mu A$ [$V_{RB} = 5V$].

2.03

Table 2: Output Characteristics of BJT

- When $V_{RB} = 2V \rightarrow V_{BB} = 2.6V$
- When $V_{RB} = 5V \rightarrow V_{BB} = 5.6V$

V_{CC}	$I_B = 20\mu A$			$I_B = 50\mu A$			
	V_{CE} (Volts)	V_{RC} (Volts)	$I_C = \frac{V_{RC}}{R_C}$ (Amp)	V_{CC}	V_{CE} (Volts)	V_{RC} (Volts)	$I_C = \frac{V_{RC}}{R_C}$ (Amp)
0.1	0.0037V	0.0172	0.0167mA	0.1	0.0070	0.0409	0.0397mA
0.2	0.094V	0.0752	0.0730mA	0.2	0.0103	0.9102	0.1070mA
0.3	0.0340V	0.1945	0.1888mA	0.3	0.0174	0.1612	0.1571mA
0.4	0.0438V	0.3160	0.3067mA	0.4	0.02380	0.2179	0.2600mA
0.5	0.0510V	0.3980	0.3370mA	0.5	0.0285	0.3964	0.3818mA
0.6	0.1012V	0.4440	0.4310mA	0.6	0.0321	0.4680	0.4543mA
0.7	0.1223	0.5700	0.5530mA	0.7	0.0357	0.6160	0.5980mA
0.8	0.0649	0.6280	0.6097mA	0.8	0.0385	0.6510	0.6320mA
0.9	0.0558	0.7360	0.7339mA	0.9	0.0417	0.7970	0.7737mA
1.0	0.2691	0.8270	0.8029mA	1.0	0.0446	0.9210	0.8941mA
1.2	0.0756	1.0800	1.04850mA	1.2	0.0495	1.0970	1.0650mA
1.5	0.0825	1.3120	1.2805mA	1.5	0.0564	1.3780	1.3378mA
2.0	0.0975	1.7920	1.7398mA	2.0	0.0654	1.8770	1.8223mA
2.5	0.1094	2.3320	2.1640mA	2.5	0.0729	2.3250	2.2570mA
3.0	0.1193	2.8050	2.7233mA	3.0	0.0790	2.8750	2.7864mA
5.0	0.1891	4.7200	4.6504mA	5.0	0.1034	4.7800	4.6407mA
10.0	4.4800	5.4000	5.2427mA	10.0	0.1761	9.6500	9.3689mA
15.0	9.3100	5.6300	5.4660mA	15.0	0.28300	10.2300	9.9320mA
20.0	14.0900	5.8600	5.6893mA	20.0	0.42000	11.1800	10.8543mA
				23.0	10.2500	11.9000	10.1592mA
				26.0	12.9870	12.3600	10.3252mA
				30.0	13.5780	16.6500	10.6720mA

Report:

1. Plot I_B vs. V_{BE} for different values of V_{CE} .
- ✓ Plot I_C vs V_{CE} for different values of I_B . Show different regions of operations.
- ✓ Find β for each I_B [for active region only]
- ✓ For $V_{cc} = 15V$, draw the load line and write the coordinates of the Q-point.

NORTH SOUTH UNIVERSITY
 DEPARTMENT OF ELECTRICAL & COMPUTER ENGINEERING

Data Collection:

Signature of instructor:

Experiment: 6,
 Performed by Group# _____

Riddiana

23.09.23

- $R_B = \underline{100.2 \text{ k}\Omega}$
- $R_C = \underline{1.03 \text{ k}\Omega}$

Input Characteristics:

1. Connect the circuit as shown in the circuit diagram.
2. By varying V_{CC} , make $V_{CE} = 2\text{V}$.
3. Varying V_{BB} gradually, measure V_{RB} and base-emitter voltage V_{BE} .
4. Calculate $I_B = \frac{V_{RB}}{R_B}$. Complete Table 1.
5. Step size is not fixed because of non-linear curve. Initially vary V_{BB} in steps of 0.1V.
6. Repeat above procedure (step 3) for $V_{CE} = 5\text{V}$.

Table 1: Input Characteristics of BJT

- When $V_{CE} = 2\text{V}$ $\rightarrow V_{CC} = \underline{1.9\text{V}}$
- When $V_{CE} = 5\text{V}$ $\rightarrow V_{CC} = \underline{5.0\text{V}}$

$V_{CE} = 2\text{V}$				$V_{CE} = 5\text{V}$			
V_{BB} (Volts)	V_{BE} (Volts)	V_{RB} (Volts)	$I_B = \frac{V_{RB}}{R_B}$ (μA)	V_{BB} (Volts)	V_{BE} (Volts)	V_{RB} (Volts)	$I_B = \frac{V_{RB}}{R_B}$ (μA)
0.1	0.0106V	0V	0.01A	0.1	0.0295V	0V	0
0.2	0.178V	0V	0.01A	0.2	0.0610V	0V	0
0.3	0.1894V	0V	0.01A	0.3	0.2372V	0V	0
0.4	0.3496V	0V	0.01A	0.4	0.2899V	0V	0
0.5	0.3996V	0.0004V	0.0010	0.5	0.3842V	0V	0
0.6	0.5140V	0.0134V	0.1340	0.6	0.4940V	0.0185V	0.1846
0.7	0.5720V	0.0862V	0.8618	0.7	0.5600V	0.0600V	0.5988
0.8	0.5920V	0.1331V	1.3302	0.8	0.5870V	0.1243V	1.2405
0.9	0.6130V	0.2560V	2.5525	0.9	0.6110V	0.2430V	2.4251
1.0	0.6160V	0.2924V	2.9231	1.0	0.6330V	0.2852V	2.8630
1.2	0.6310V	0.3270V	3.3681	1.2	0.6663V	0.5490V	5.4790
1.4	0.6410V	0.3980V	3.9878	1.4	0.6840V	0.6780V	6.7665
1.6	0.6430V	1.1090V	1.0920	1.6	0.6950V	0.8820V	8.8024
1.8	0.6460V	1.3470V	13.4673	1.8	0.6980V	1.0540V	10.5190
2.0	0.6480V	1.5350V	15.3469	2.0	0.6930V	1.2960V	12.9341
3.0	0.6510V	2.3220V	23.2853	3.0	0.6980V	2.2440V	22.3952
4.0	0.6560V	3.2950V	32.9434	4.0	0.6930V	3.3150V	33.0838
5.0	0.6560V	4.3500V	43.4913	5.0	0.6910V	4.3300V	43.632X

0.036