

L-1 / 20.07.2023 /


Analog Electronics

Analog Signal \Rightarrow Infinite amplitude


Digital Signal \Rightarrow Finite amplitude

$$\text{Level} = 2^n$$

DC Signal \Rightarrow

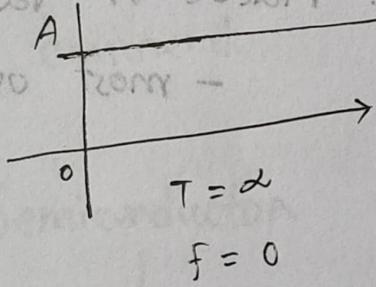

AC Signal \Rightarrow

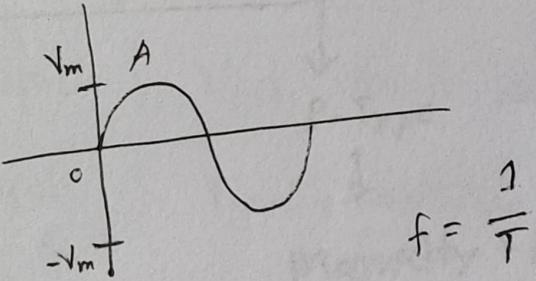

$$f = \frac{1}{T}$$

$$T = ? \text{ finite}$$

Passive Components \Rightarrow consume power only


Active Components \Rightarrow consume power and ~~amp~~
amplify power.

Seacal-D

Calcium Carbonate (From Coral Source) and
Vitamin D₃ (Colecalciferol)

Seacal-DX

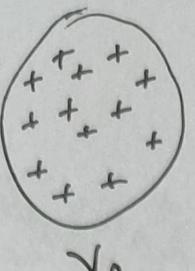
Calcium Carbonate (From Coral Source)
and Vitamin D₃ (Colecalciferol)



$$\nabla = \nabla_A - \nabla_B$$

$$I = \frac{dQ}{dt} \quad (\text{changes of current})$$

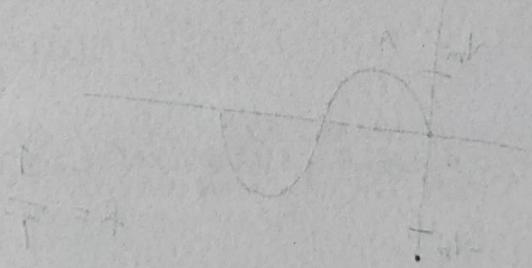Valence Electron : Placed on Valence shell
- most outer shell




$$\sin \theta = T$$

L-2 / 22.07.2023 /

④ Electron Current: The movement of free electrons create a current is called electron current.

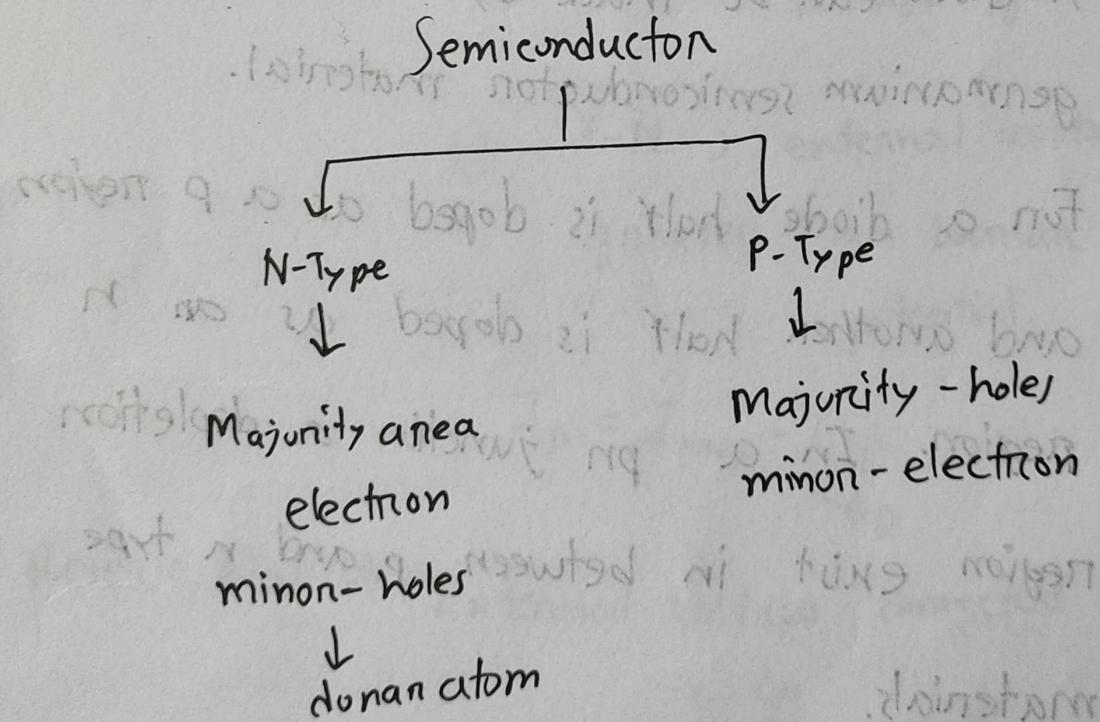⑤ Hole current: The hole has moved from one place to another in the crystal structure it is called hole current.



Seacal-D


Calcium Carbonate (From Coral Source) and Vitamin D₃ (Colecalciferol)

realme

Shot by Legend_T.JOY

Seacal-DX

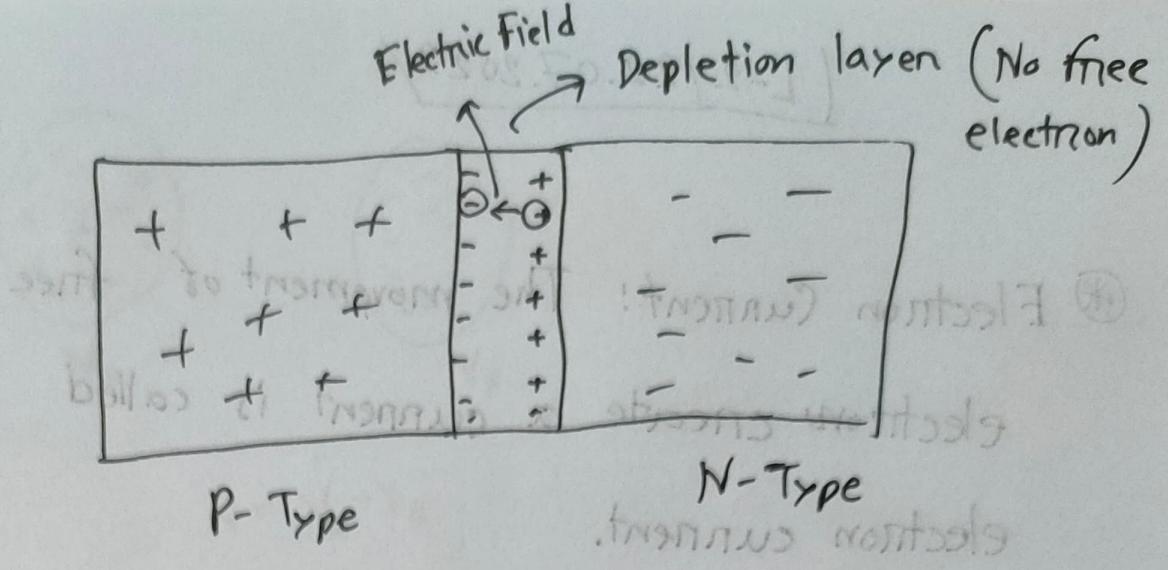Calcium Carbonate (From Coral Source) and Vitamin D₃ (Colecalciferol)




am mith bspn wsl slrf gft : mnnus slff
 ti stntnste btrwrs ant ni mntns et swlg
 ☺ Construction of Diode: (How?)

⇒ A diode can be made by a silicon or a
 genmanium semiconductor material.

For a diode half is doped as a p region
 and another half is doped as an n
 region. In a pn junction a depletion
 region exist in between p and n type
 materials.

(*) Representation of Diode:

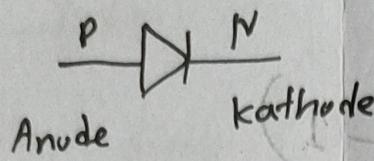

Diode Operating Condition

No bias \Rightarrow All normal and no external voltage

Forward bias \Rightarrow External voltage given in

$(+) (-)$ P-N ; external voltage

greater than barrier

potential.

$$I_D = I_{D0} = I_{max} - I_s \rightarrow_0$$

Reverse bias \Rightarrow External voltage connected as

$(-) (+)$
P-N

$$I_D = I_{D0} = I_{max} - I_s \rightarrow_0$$


Seacal-D

Calcium Carbonate (From Coral Source) and
Vitamin D₃ (Colecalciferol)

Seacal-DX

Calcium Carbonate (From Coral Source)
and Vitamin D₃ (Colecalciferol)

Diode Equation
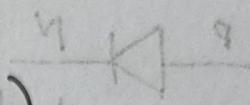
$$I_D = I_s (e^{\frac{V_D}{nV_T}} - 1)$$


diode

$$V_T = \frac{kT_K}{q}$$

V_D = applied forward bias voltage

I_s = reverse current

n = identity factor (1)

V_T = thermal voltage

$$k = 1.38 \times 10^{-23} \text{ J/K}$$

T_K = absolute temperature in kelvins


q = magnitude of electron charge

$$= 1.6 \times 10^{-19} \text{ C}$$

Lecture - 2 - Page - 12



$$\sum I_{out} = qI$$

1 L-3 / 27.07.2023 /

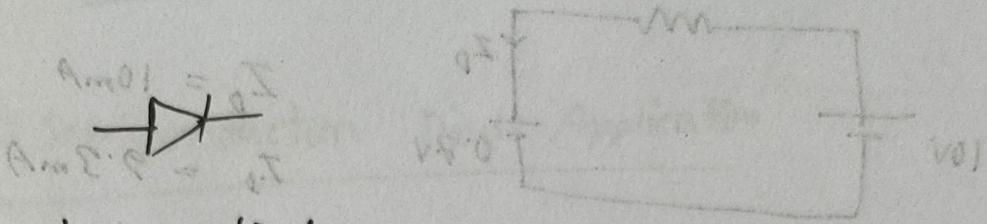


⇒ That is diode

⇒ Biasing
Forward
Reverse

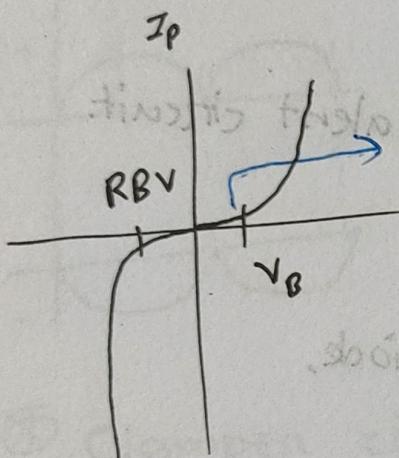
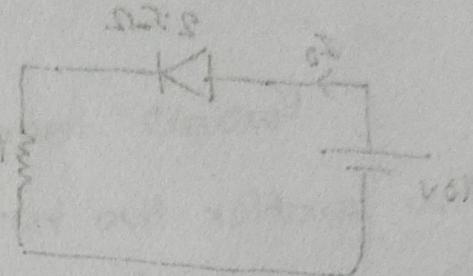


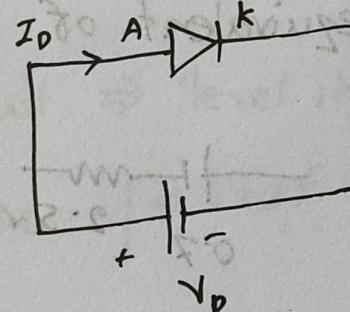Thermal effect ($I_s = \text{minority current}$)




$$V_D > 0$$

⊗ Reverse Break down Voltage

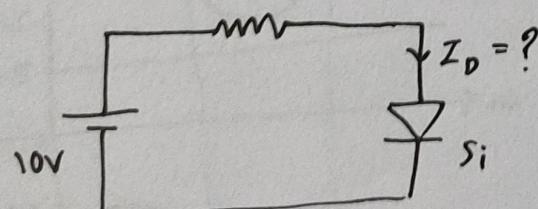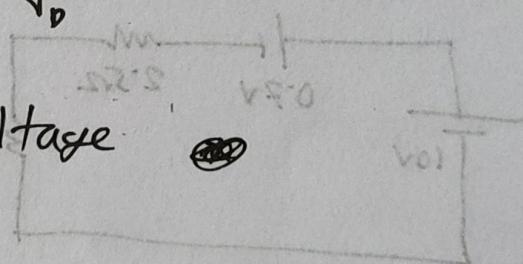

to value with

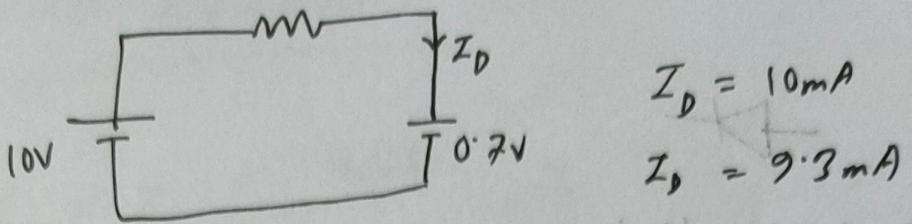
⊗ Ideal case, remove the diode and calculate.



$$I_D = 10 \text{ mA}$$


$$I_D = 9.3 \text{ mA}$$

gibet in fort

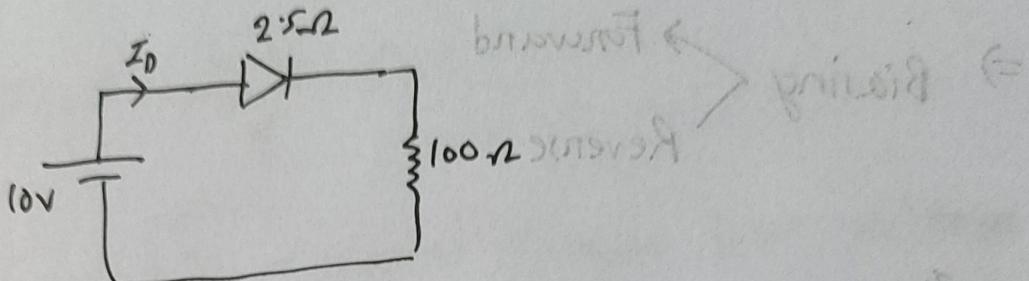


Find I_D using piecemeal equivalent circuit.

⊗ Forward Bias equivalent of Diode,

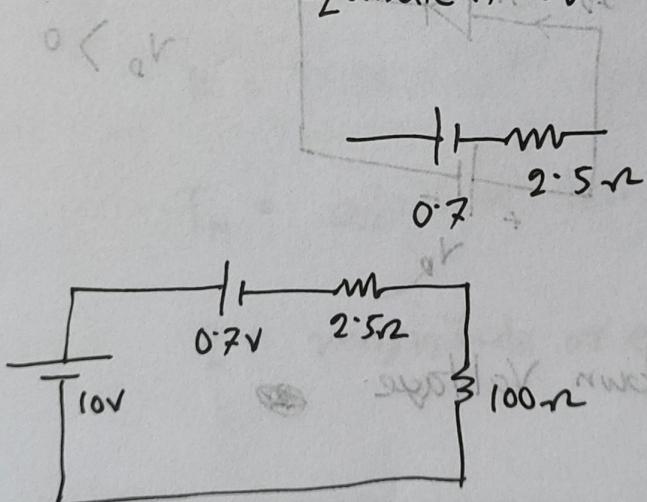


Now solve it

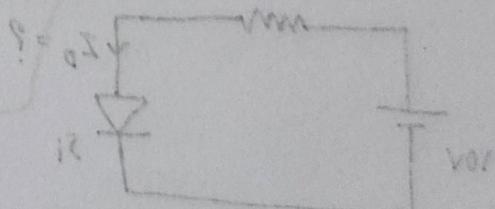

④ Semiconductor Diode Application

① Rectifier (AC to DC)

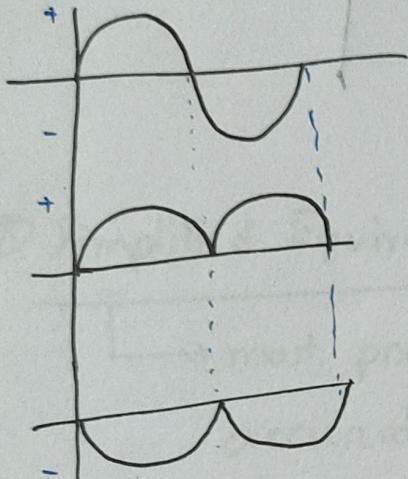


② Clipper circuit

\Rightarrow cut out voltage without changing waveform.


③ Clamper circuit \Rightarrow level shift

$$V = 5 + 5 \sin \omega t \quad | \omega = \omega f$$

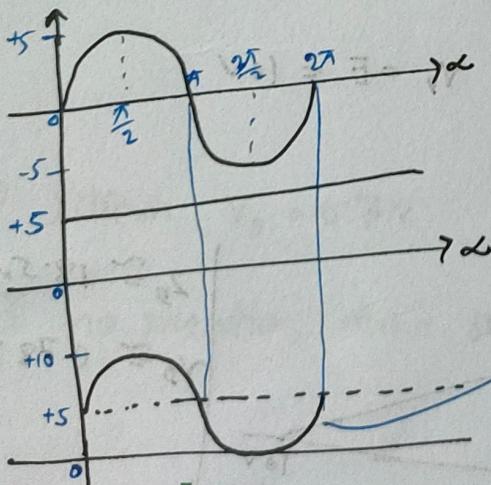
$\frac{DC}{AC} = \frac{5}{5 \sin \omega t}$



Level shifted

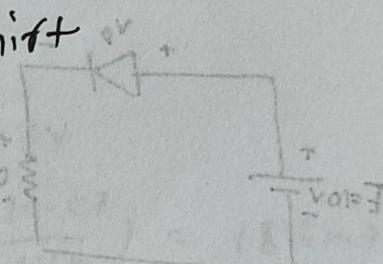

(*) Load Line analysis: 30.80 | P-1

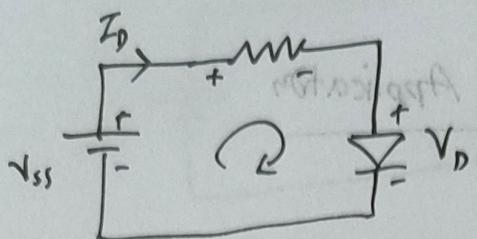


$$V_{ss} = -I_D R - V_D = 0$$


$$V_{ss} = I_D R + V_D$$

two solution for two cases
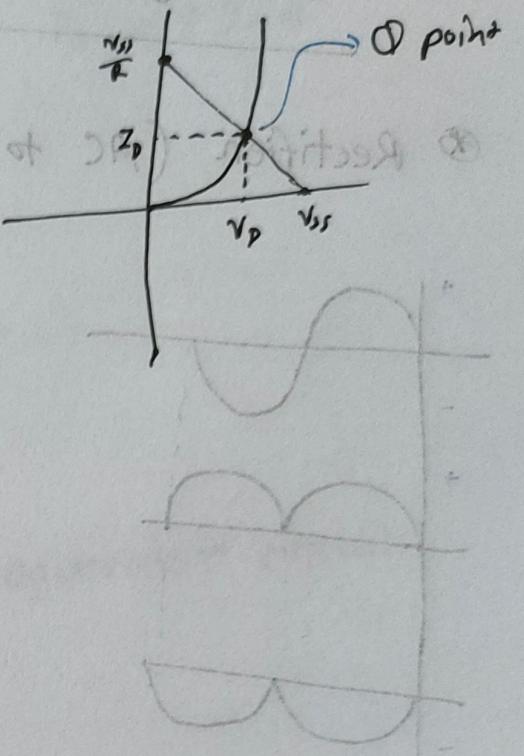
$$\begin{cases} V_D = 0; I_D = \frac{V_{ss}}{R} \\ I_D = 0; V_D = V_{ss} \end{cases}$$



(*) Load Line analysis:

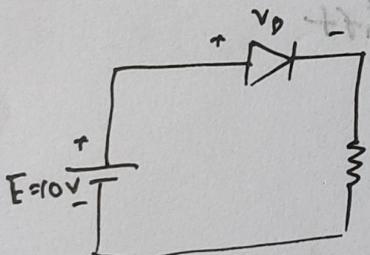


$$E - V_D - I_D R = 0$$


$$E = I_D R + V_D$$

$$V_D = 0; Z_D = \frac{E}{R} = \frac{10}{0.5 \text{ k}\Omega} = 20 \text{ mA}$$

$$I_D = 0; V_D = E = 10 \text{ V}$$

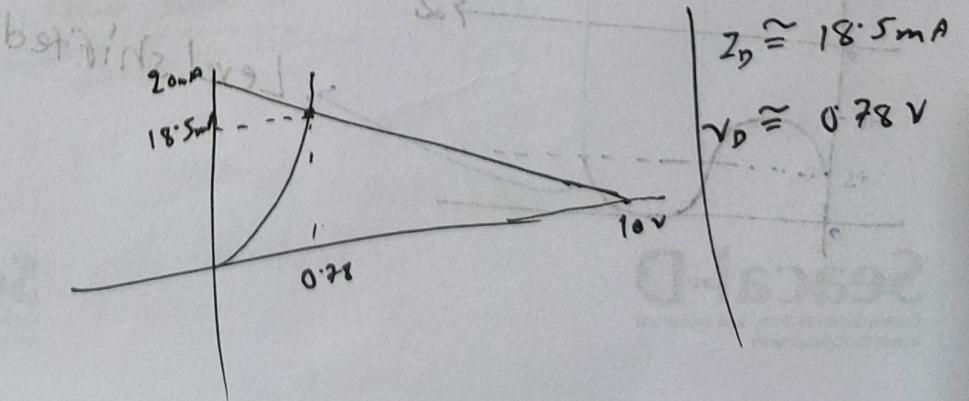


④ Ideal Equivalent Circuit:

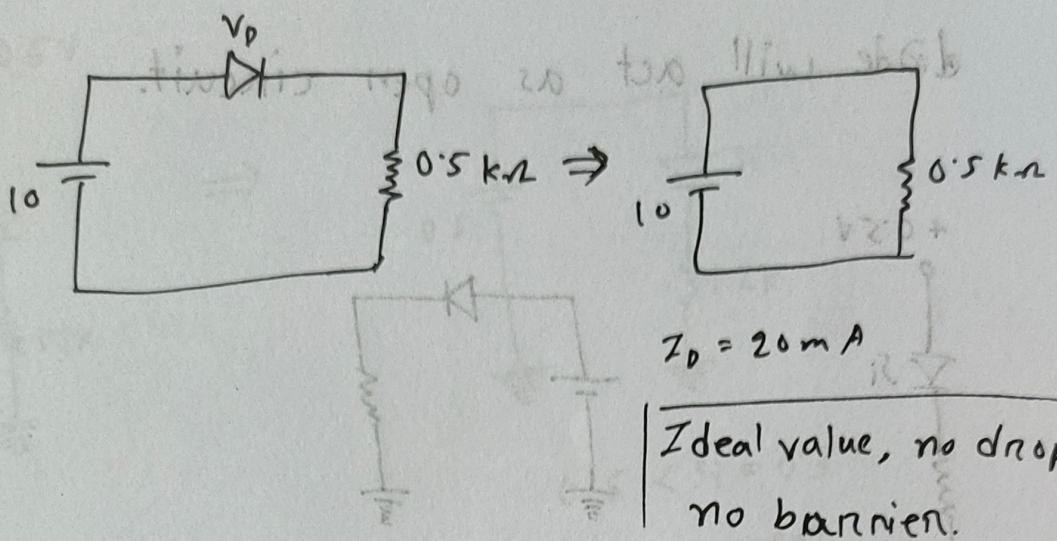

④ Simplified Equivalent Circuit:

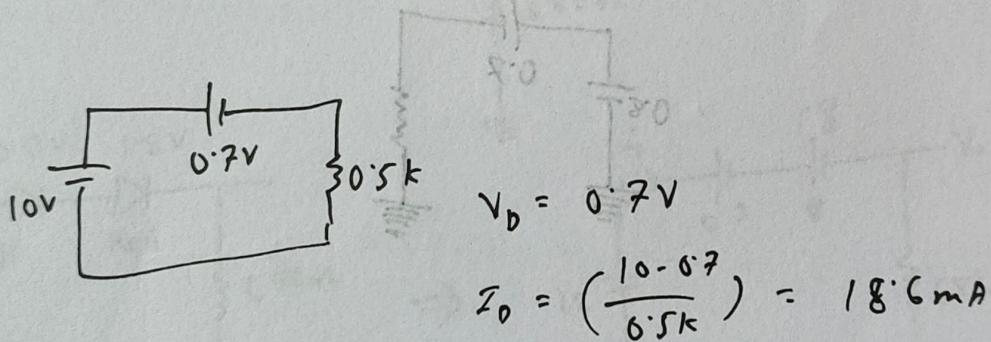→ most preferable for calculation and almost accurate result for complex circuit.



⇒ Approximately same as
Load Line analysis.

④ Silicon, $V_D = 0.7V$

If no mention, take as ideal case.


Seacal-D

Calcium Carbonate (From Coral Source) and
Vitamin D₃ (Colecalciferol)

Seacal-DX

Calcium Carbonate (From Coral Source)
and Vitamin D₃ (Colecalciferol)

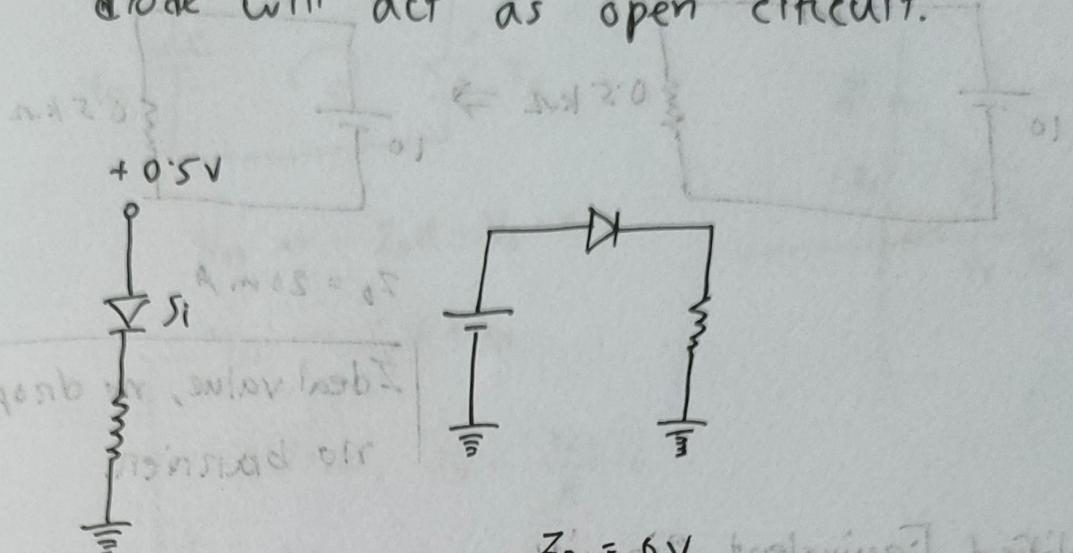
① Applied voltage less than barrier voltage, the diode will act as open circuit.



$$Z_D = 6\text{V}$$

barrier br. if, $V = 0.8\text{V} \rightarrow$ forward bias replace

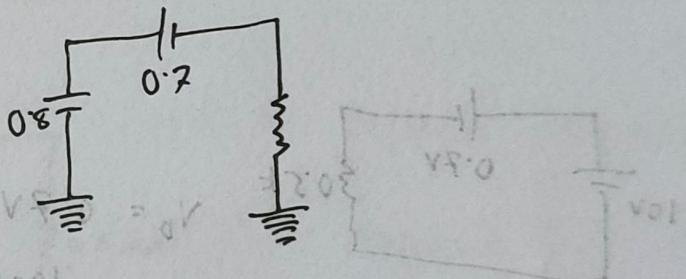Let's consider the circuit for source voltage V_{aus}



$$R_{aus} = \left(\frac{0.2}{0.2+0.2} \right) = 0.2$$


so small - diodeverbrauch <

indirekt wird gross


$$V_F = 0.3\text{V}, \text{ max!}$$

so bei we sent mit einer 11

L-5 / 05.08.2023 /




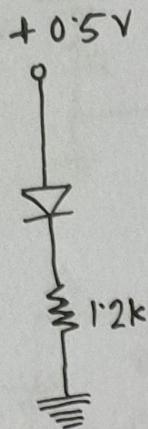


\Rightarrow

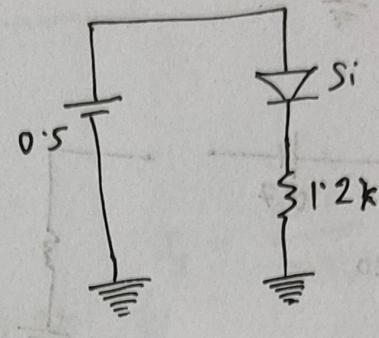



$$0.5 < s_i = 0.7$$

\therefore No current

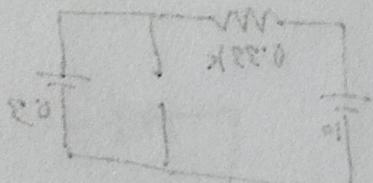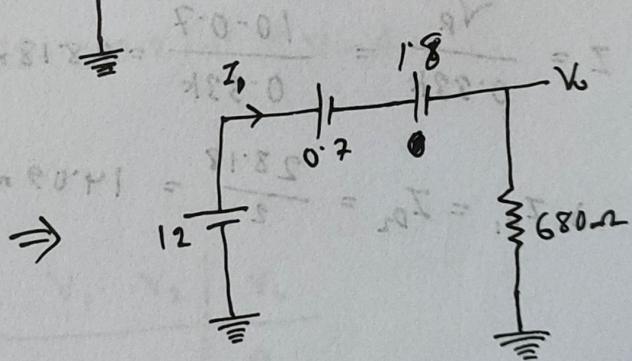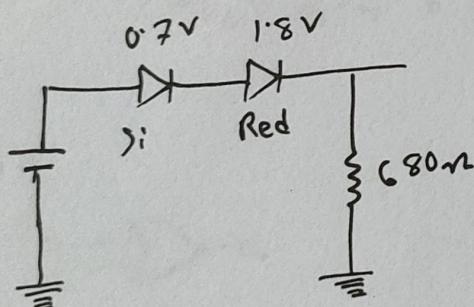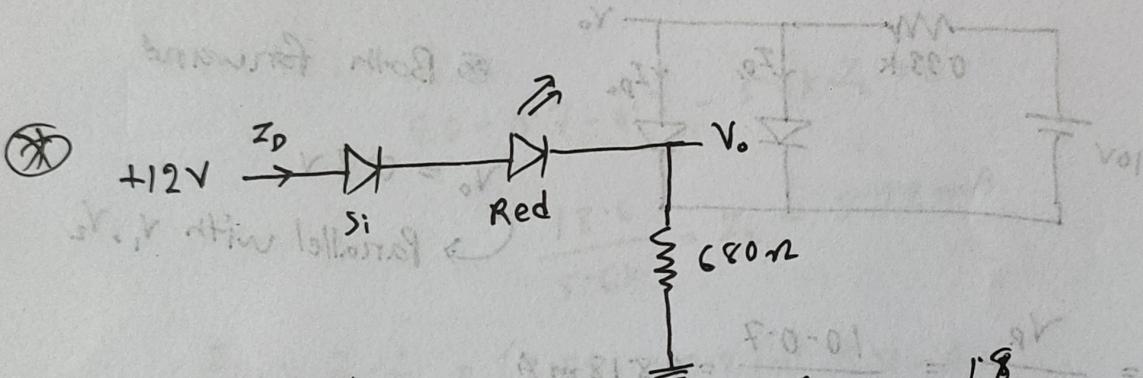

$$V_o = 9.5 \text{ V}$$

$$I_D = \frac{9.5}{0.68} \text{ mA}$$

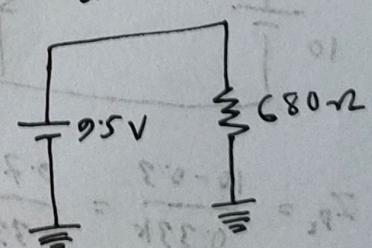
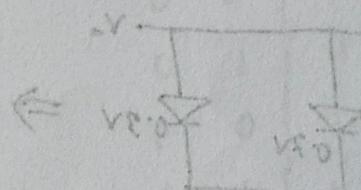


Seacal-D

Calcium Carbonate (From Coral Source) and
Vitamin D₃ (Colecalciferol)


Seacal-DX

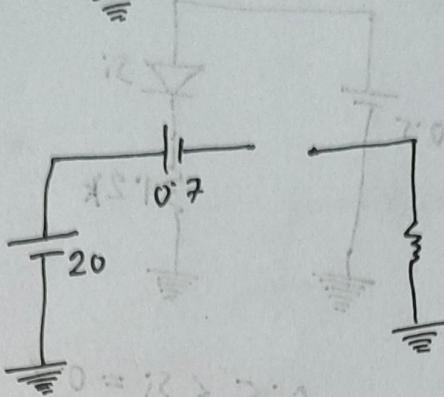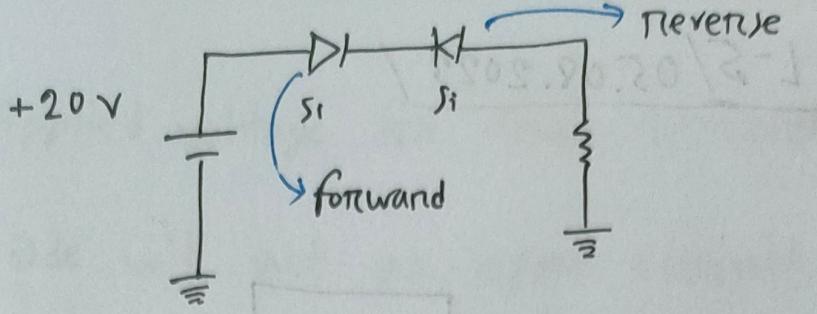Calcium Carbonate (From Coral Source)
and Vitamin D₃ (Colecalciferol)






$$I_D = 0$$

$$V_{D2} = 20V$$

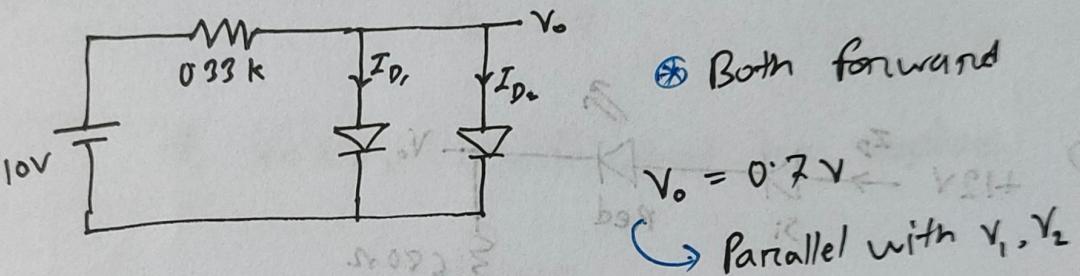



$$I = \frac{V_R}{0.33k} = \frac{10 - 0.7}{0.33k} = 28.18 \text{ mA}$$
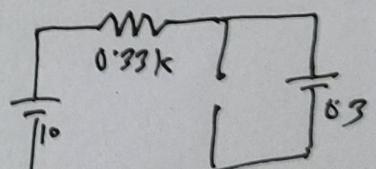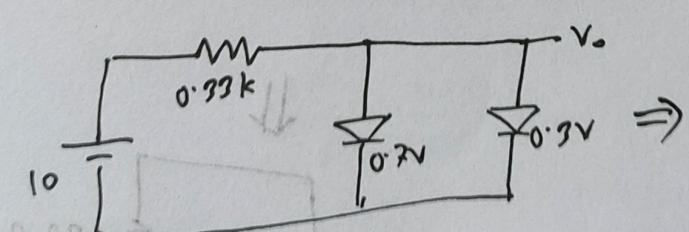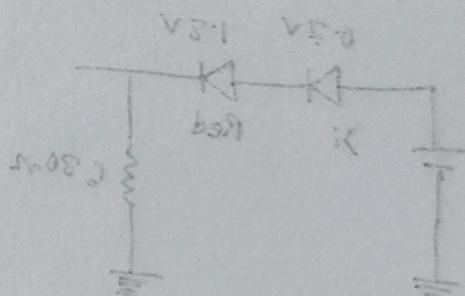
$$I_{D1} = I_{D2} = \frac{28.18}{2} = 14.09 \text{ mA}$$



$$I_{D2} = \frac{10 - 0.3}{0.33k} = 28.18 \text{ mA}$$

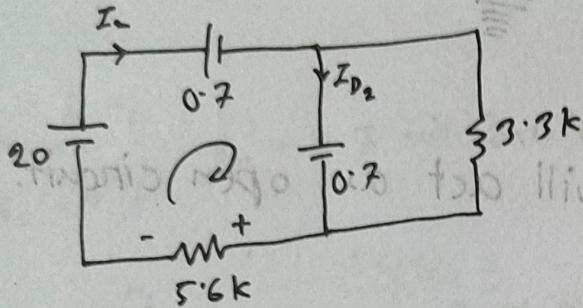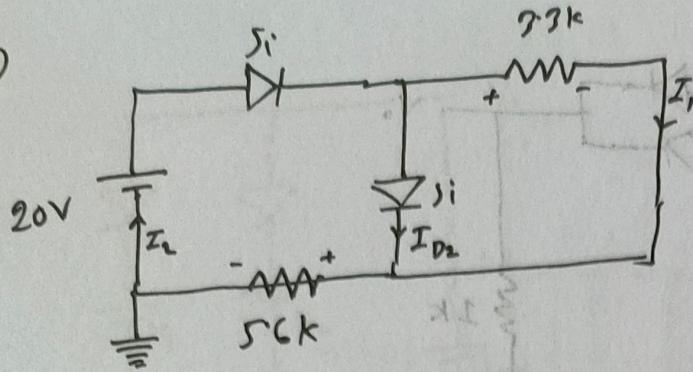Current will follow the shunted and easiest path.




$$I_1 = \frac{0.7}{7.3k} = 0.212 \text{ mA}$$

Parallel with D_2

$$20 - 0.7 - 0.7 - 5.6k \cdot I_2 = 0$$

$$\frac{18.6}{5.6k} = I_2 = 3.32 \text{ mA}$$
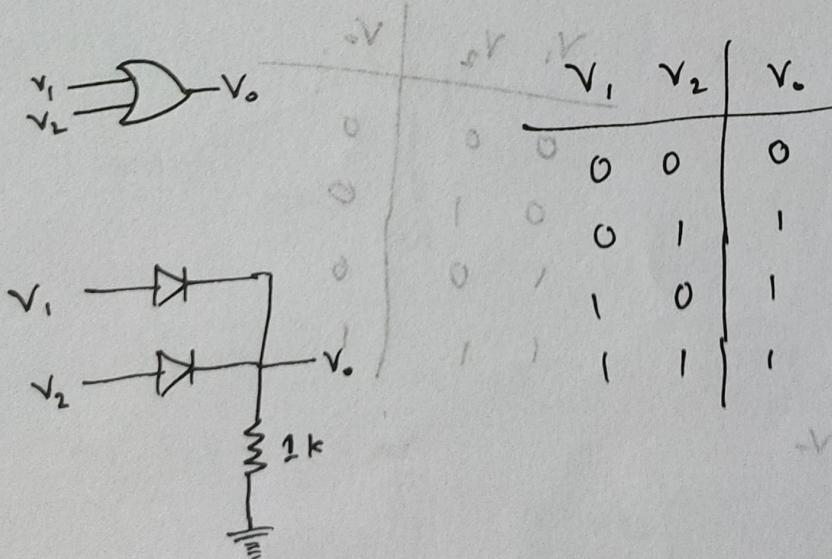
$$I_{D_2} = I_2 - I_1 = (3.32 - 0.212) = 3.11 \text{ mA}$$




V_1	V_2	V_0
0	0	0
0	1	1
1	0	1
1	1	0

Seacal-D

Calcium Carbonate (From Coral Source) and
Vitamin D₃ (Colecalciferol)

Seacal-DX

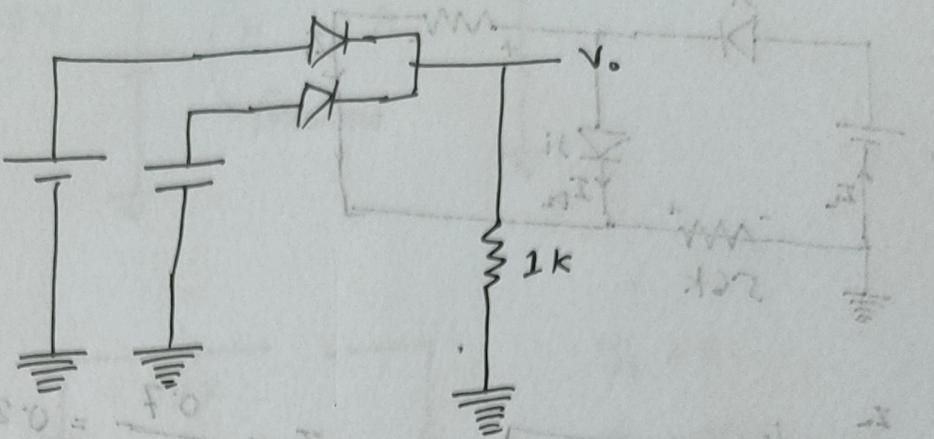Calcium Carbonate (From Coral Source)
and Vitamin D₃ (Colecalciferol)




$\Rightarrow \begin{cases} V_1 = 0 \\ V_2 = 0 \end{cases}$ Diode will act as open circuit.


$$\begin{cases} V_1 = 0 \\ V_2 = 5 \end{cases} \quad \begin{array}{l} D_1 = \text{Open} \\ D_2 = 0.7 \text{ (forward)} \end{array} \Rightarrow V_0 = 5 - 0.7 = 4.3V$$

$$\begin{cases} V_1 = 5 \\ V_2 = 5 \end{cases} \quad \begin{array}{l} D_1 = 0.7 \\ D_2 = 0.7 \end{array} \quad \text{Both forward} \Rightarrow V_0 = 4.3V$$

$$V_1 = V_0$$

	V_1	V_2	V_0
0	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

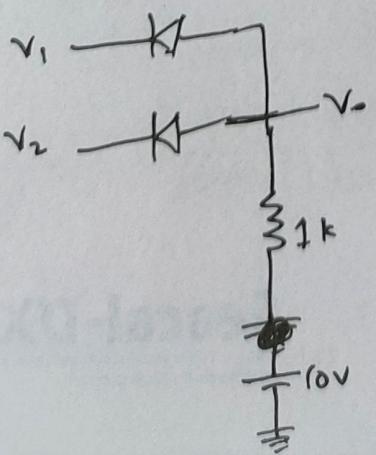

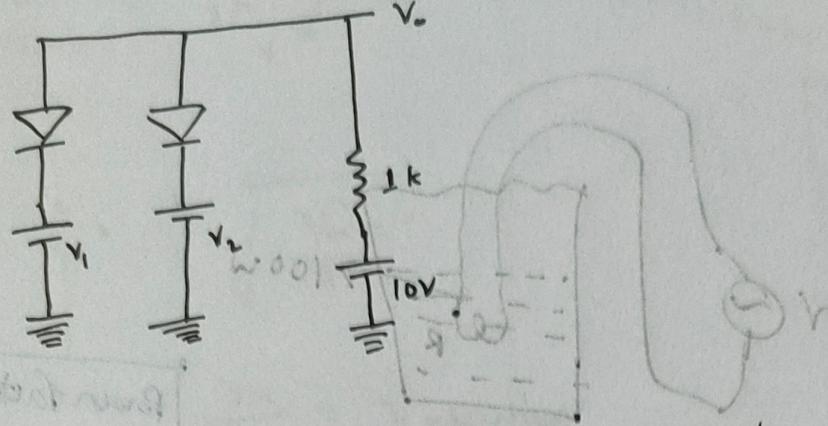


$$\left. \begin{array}{l} V_1 = 0 \\ V_2 = 0 \end{array} \right\} V_o = 0.7 \Rightarrow \text{Parallel with } V_1, V_2$$

$$\frac{V}{A} = 0.9$$

$$\left. \begin{array}{l} V_1 = 10 \\ V_2 = 0 \end{array} \right\} V_o = 0.7 \xrightarrow{\text{V}_1 = \text{Open}} \frac{V}{A} = 0.9$$

$$\left. \begin{array}{l} V_1 = 10 \\ V_2 = 10 \end{array} \right\} V_o = 10V \xrightarrow{\text{V}_1 = \text{V}_2 = \text{Open}} \frac{V}{A} = 0.9$$
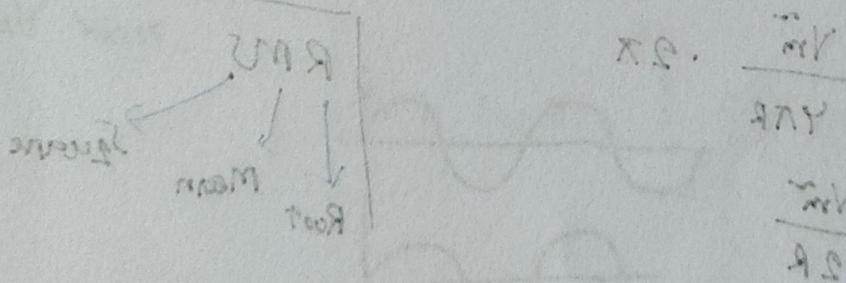
$$\text{tew b} (\text{tew s cos } -1) \left(\frac{V}{A} \right) = 0.9$$



$$(0.9) \text{ prod} = 0.9$$

$$0.9 \text{ prod} = \frac{mV}{A} = \frac{mV}{45} = \frac{V}{A}$$


Seacal-D

Calcium Carbonate (From Coral Source) and
Vitamin D₃ (Colecalciferol)

Seacal-DX

Calcium Carbonate (From Coral Source)
and Vitamin D₃ (Colecalciferol)

L-6 / 10.08.2023 /

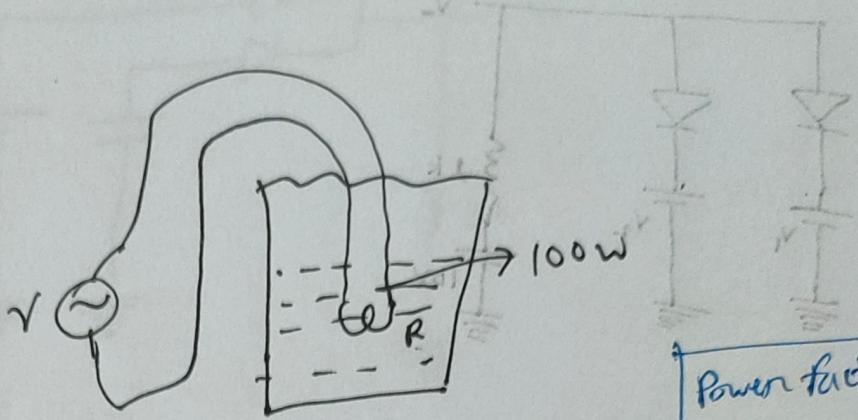

Power factor
P.F. ≈ 1
is most efficient

$$P_{DC} = \frac{V}{R}$$

$$P_{AC} = \frac{V}{R} = \frac{\sqrt{V_m}}{R} \cdot \frac{2 \sin \omega t}{2R}$$

$$= \frac{\sqrt{V_m}}{2R} (1 - \cos 2\omega t)$$

$$P_{avg} = \frac{\sqrt{V_m}}{4\pi R} \int_0^{2\pi} (1 - \cos 2\omega t) d\omega t$$

$$P = VZ \cos \theta$$

P.F.

$$= \frac{\sqrt{V_m}}{4\pi R} \cdot 2\pi$$

$$= \frac{\sqrt{V_m}}{2R}$$

RMS
Root Mean Square

$$P_{DC} = P_{avg} (AC)$$

$$\frac{V}{R} = \frac{\sqrt{V_m}}{2R} \therefore V_{\text{effective}} = \frac{\sqrt{V_m}}{\sqrt{2}} = 0.707 V_m$$

$$\sqrt{V_{RMS}} = \frac{V_m}{\sqrt{2}}$$

$\sin \omega t$ (alternating voltage)

$V_o = V_m \sin \omega t$

$= \frac{V_m}{\sqrt{2}} = V_{\text{effective}}$

$$V_o = V_m \sin \omega t$$


$$dV = mV$$

Rectifier




→ Half Wave


→ Full Wave

→ Bridge

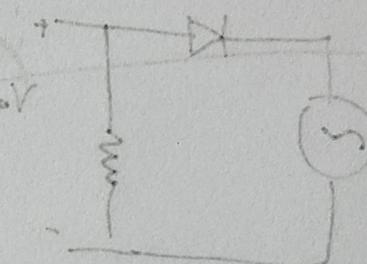


Half Wave

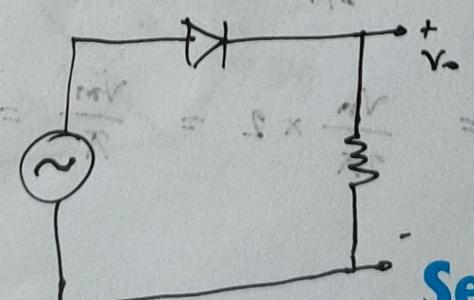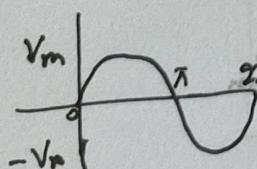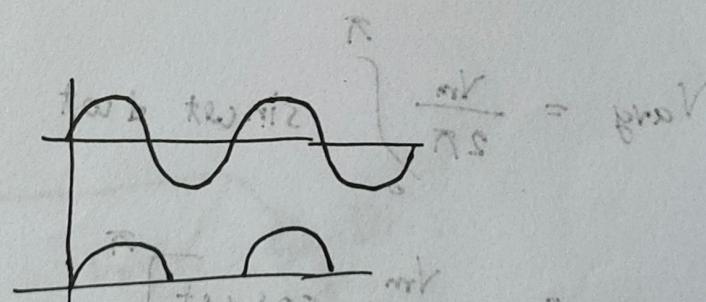

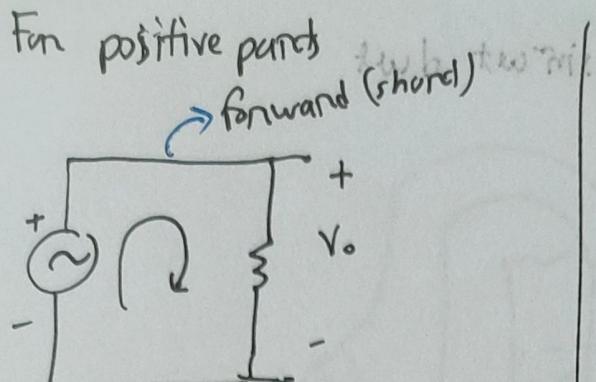


$$V_m - V_o = 0$$

$$V_m = V_o$$

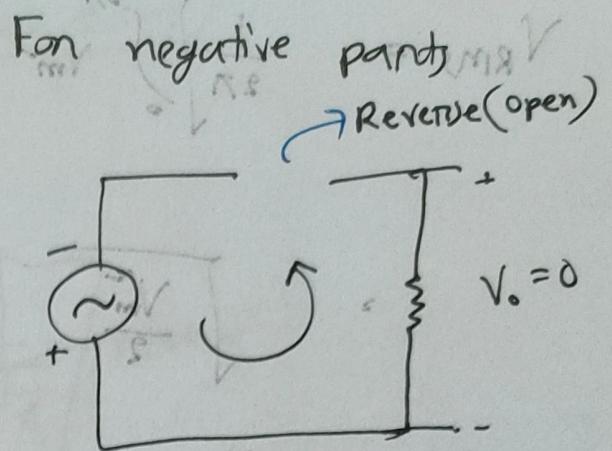

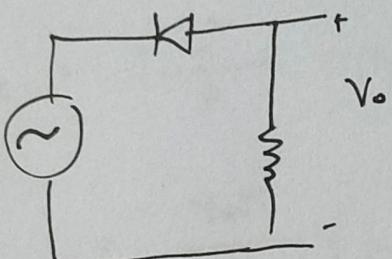
$$\text{av. voltage } V = \frac{mV}{2} = \frac{V_m}{2}$$



For positive \Rightarrow reverse (open)


For negative \Rightarrow forward (short)

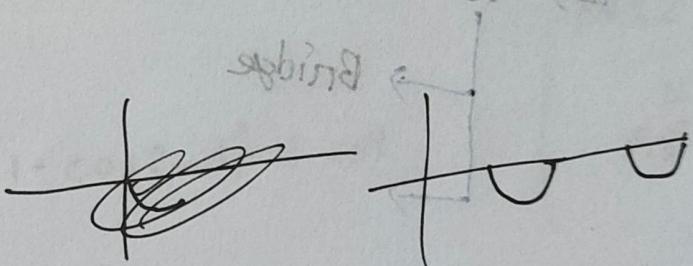


\otimes


$$V_{\text{avg}} = \frac{V_m}{2\pi} \int_0^{\pi} \sin wt \, dwt$$
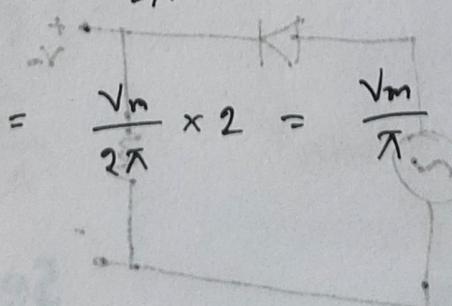
$$= - \frac{V_m}{2\pi} \left[\cos wt \right]_0^\pi$$



now find \otimes

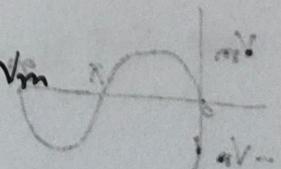

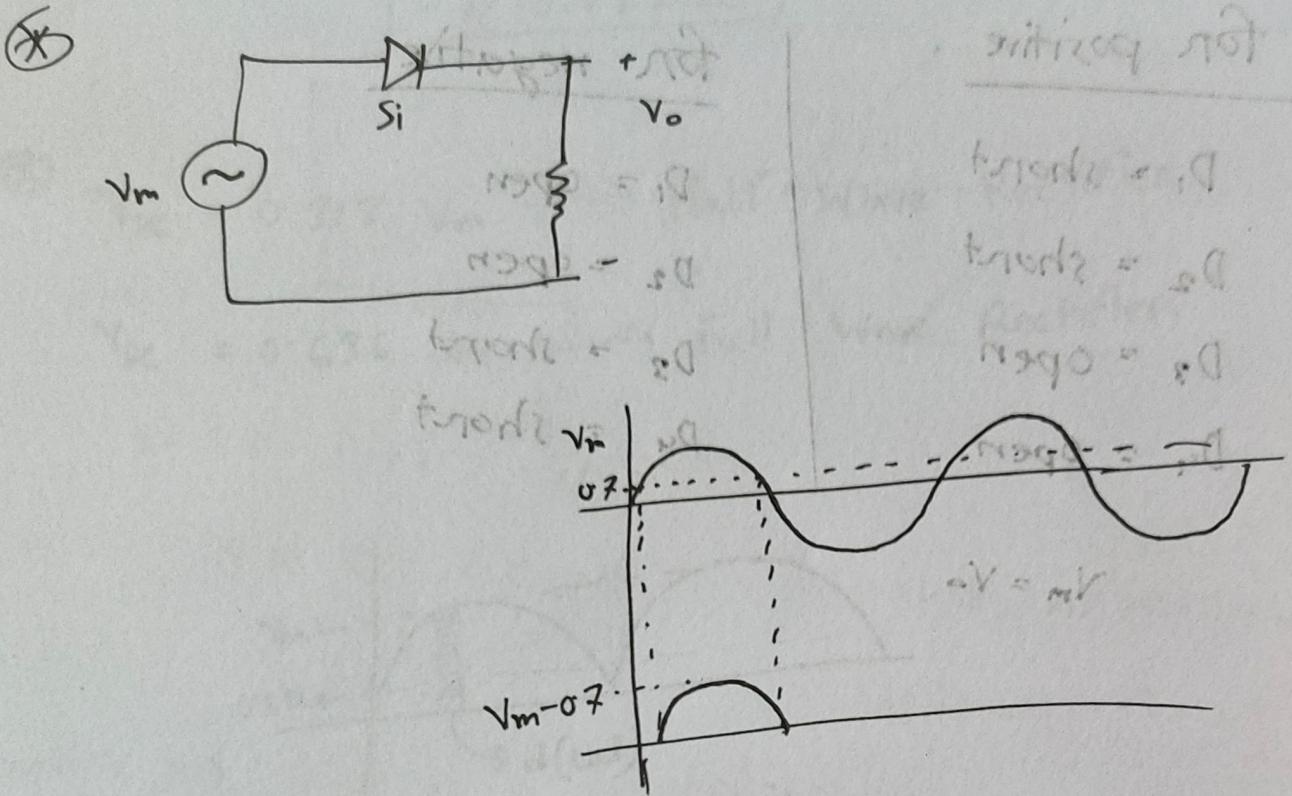


$$V_{avg} = 0.318 V_m$$

$$= 0.318 (V_m - 0.7)$$

~~(*)~~ Diode Rating

~~(*)~~ Full Wave:

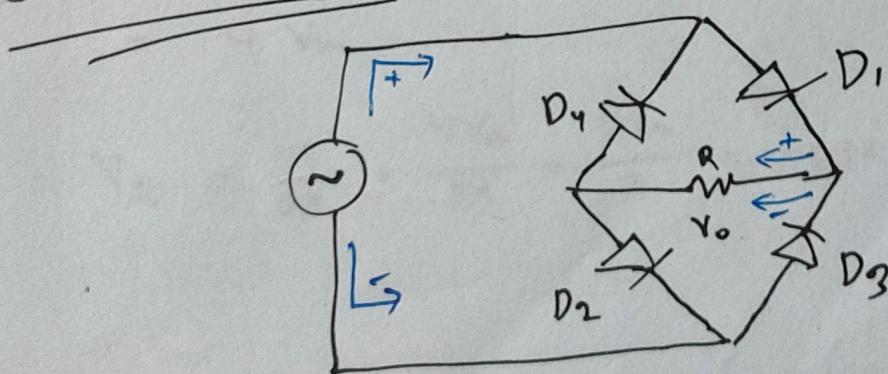

Seacal-D

Calcium Carbonate (From Coral Source) and
Vitamin D₃ (Colecalciferol)

Seacal-DX

Calcium Carbonate (From Coral Source)
and Vitamin D₃ (Colecalciferol)

for positive

$D_1 = \text{short}$

$D_2 = \text{short}$

$D_3 = \text{open}$

$D_4 = \text{open}$

$$V_m = V_o$$

for negative

$D_1 = \text{open}$

$D_2 = \text{open}$

$D_3 = \text{short}$


$D_4 = \text{short}$

$$V_m = -V_o$$

$$0.318 V_o = V_o$$

$$(V_o - 0.318) = 0.318 V_o$$

Diode positive

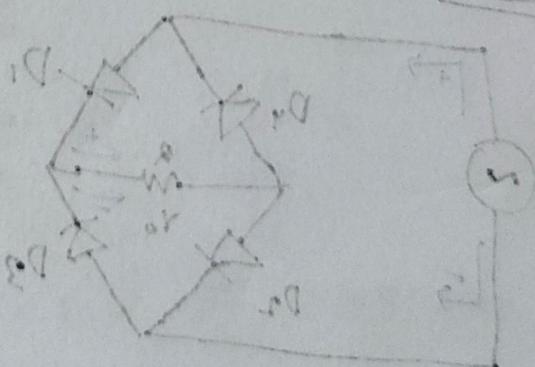


Full Wave

L-7 / 12-08-2023

⊗ $V_{DC} = 0.318 V_m \rightarrow$ Half Wave Rectifier

$V_{DC} = 0.636 V_m \rightarrow$ Full Wave Rectifier

$$0 = F.O. - iV = F.O. - iV \Leftarrow$$

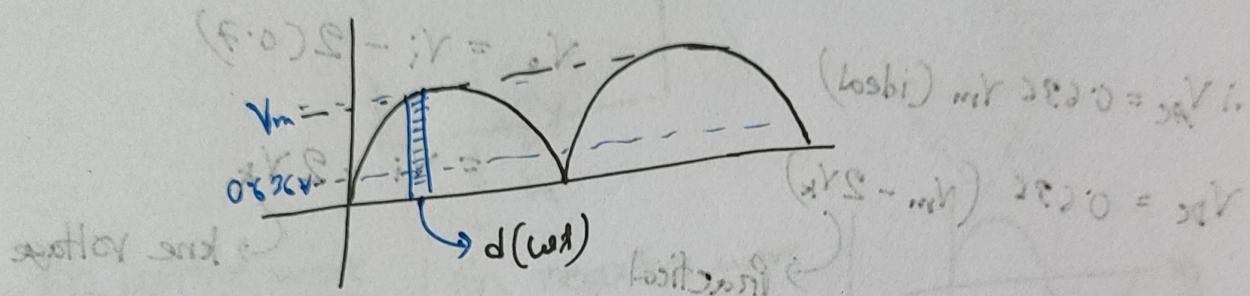

⊗
$$\int_0^{2\pi} V_m \sin \omega t dt$$

$= V_m \left[\int_0^{\pi} \sin \omega t dt + \int_{\pi}^{2\pi} \sin \omega t dt \right]$

$= -V_m \left[\cos \omega t \Big|_0^{\pi} + \cos \omega t \Big|_{\pi}^{2\pi} \right]$

$= -V_m \left\{ (-1-1) + (-1-1) \right\}$

$= 4 V_m$



$$\therefore V_{DC} = \frac{A}{2\pi} = \frac{4V_m}{2\pi} = \frac{2V_m}{\pi} = 0.636 V_m$$

Seacal-D

Calcium Carbonate (From Coral Source) and
Vitamin D₃ (Colecalciferol)

Seacal-DX

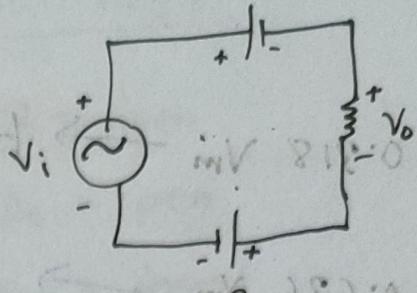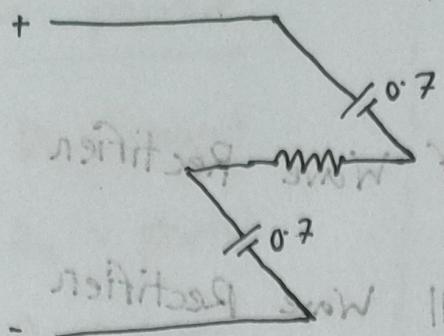Calcium Carbonate (From Coral Source)
and Vitamin D₃ (Colecalciferol)



$$\Rightarrow V_i - 0.7 - V_o - 0.7 = 0$$

$\therefore V_{AC} = 0.63 \times V_m$ (ideal)

$V_{DC} = 0.63 \times (V_m - 2V_k)$

Practical


$$V_o = V_i - 2(0.7)$$

$$= V_i - 2V_k$$


(hw) b e

kne voltage


~~Diode Rating~~

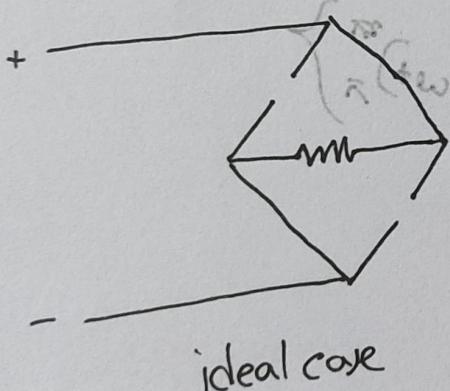

ideal case

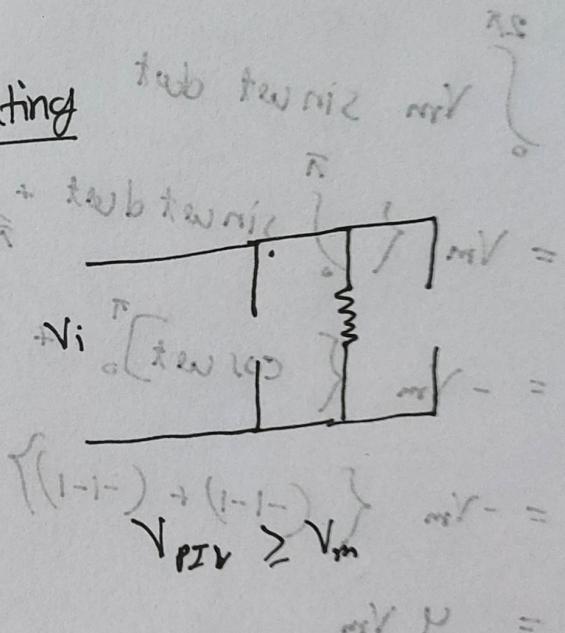

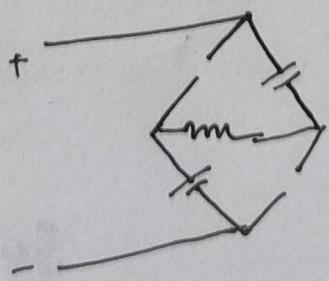
$$\Rightarrow \text{Practical Case} \quad V_{PZV} = \frac{mV}{R} = \frac{mV}{R_L} = \frac{A}{R_L} = 20V$$



$$\text{then, } V_{PZV} \geq (V_m - V_k)$$

④ Center tapped transformer

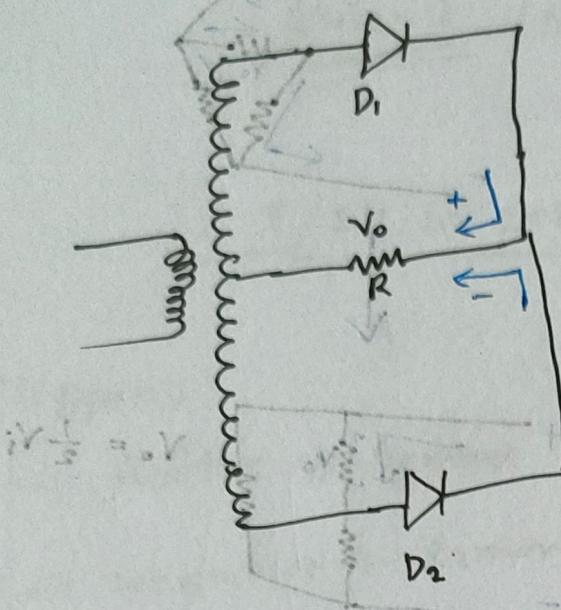

④ it's costly, used on low power source and for efficiency.

for positive wave


D₁ = short

D₂ = open


for negative wave

D₁ = open

D₂ = short

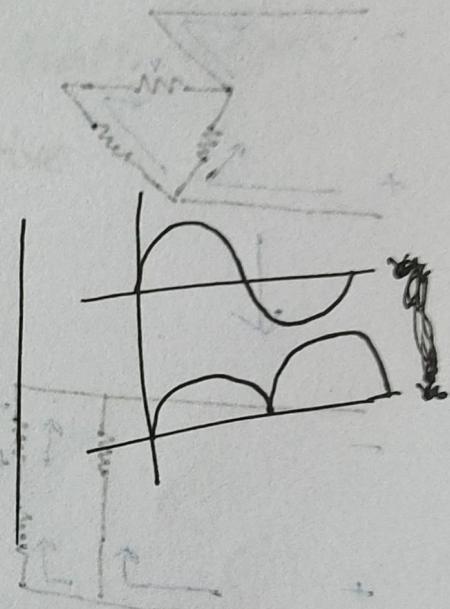

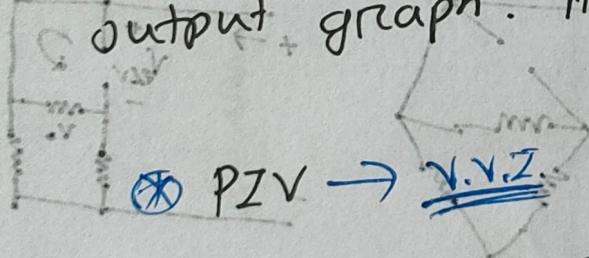④ Question Pattern: Real Diode effect with output graph. it will reduce by V_k.



④ PZV → Z.V.I.

for negative,

$$V_{ZV} - V_i + V_{PZV} - V_o = 0$$

in D₁ position

$$V_{PZV} = V_i + V_o = V_i + V_i = 2V_m$$





Seacal-D

Calcium Carbonate (From Coral Source) and Vitamin D₃ (Colecalciferol)

Seacal-DX


Calcium Carbonate (From Coral Source) and Vitamin D₃ (Colecalciferol)

+ — no bypassing (coupling) (X)

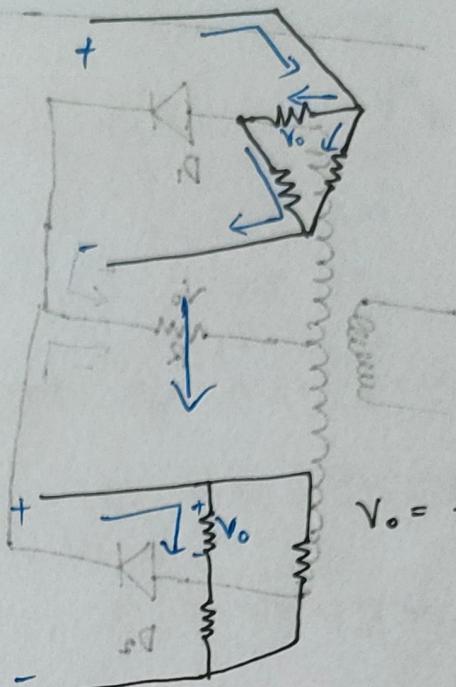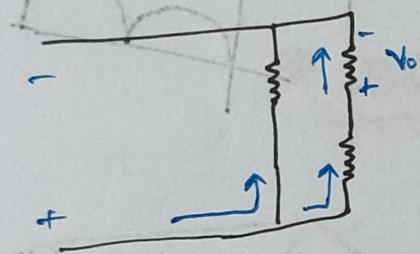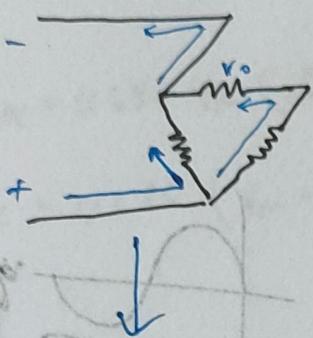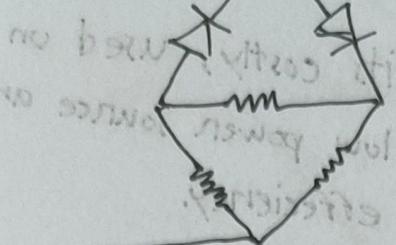


$$V_o = \frac{1}{2} V_i$$

less exciting more

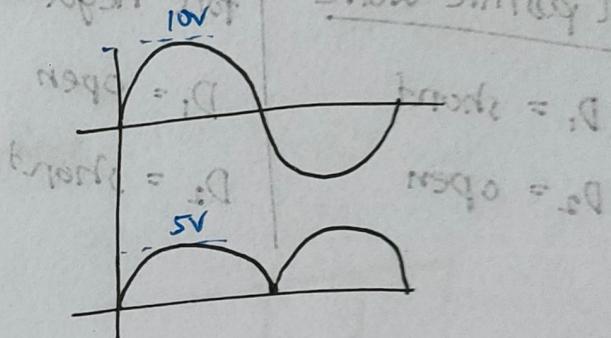

$$V_o = \frac{1}{2} V_i$$

more flux less exciting

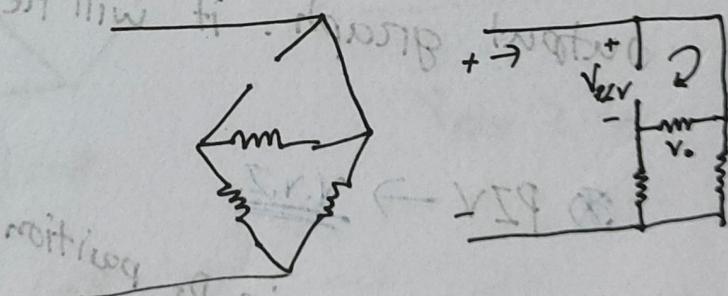

$$V_o = V_{PEV}$$

$$V_{PEV} = \frac{1}{2} V_m = 5V$$

Quiz-1
Next Secondary Saturation
L 1-4

Practical Application

L-8 / 19.08.2023 /


Quiz-1 / No class

(iv)


L-9 / 24.08.2023 /

Clippers

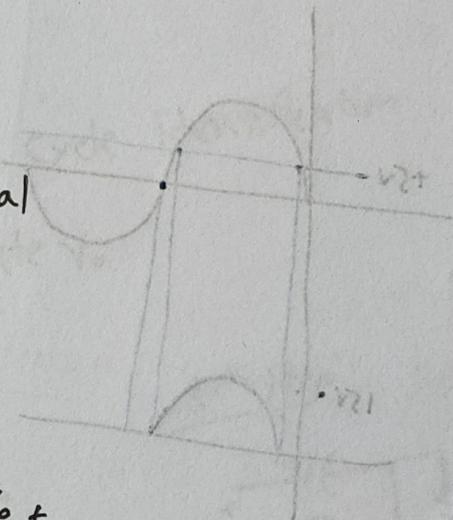- Positive \Rightarrow Remove positive half cycle
- Negative \Rightarrow Remove negative
- Biased
- Combinational




Biased

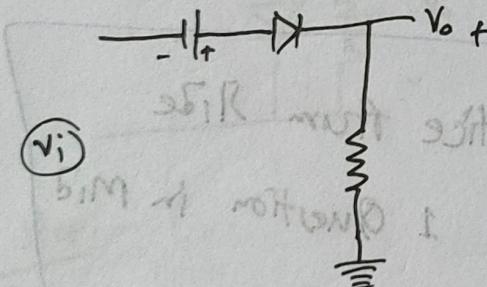

$$V_{in} + 5 - V_o = 0$$

$$V_o = 5 + V_{in}$$


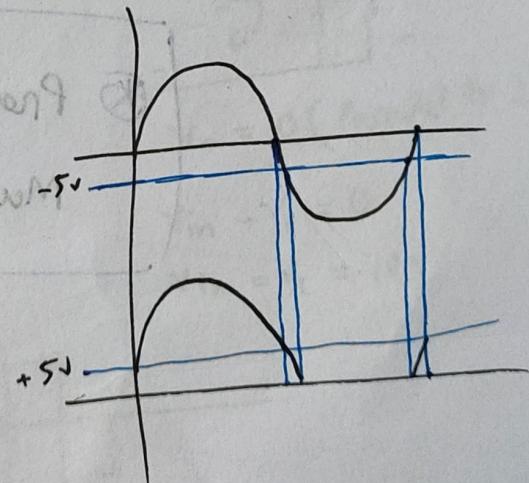


Seacal-D


Calcium Carbonate (From Coral Source) and
Vitamin D₃ (Colecalciferol)

Seacal-DX

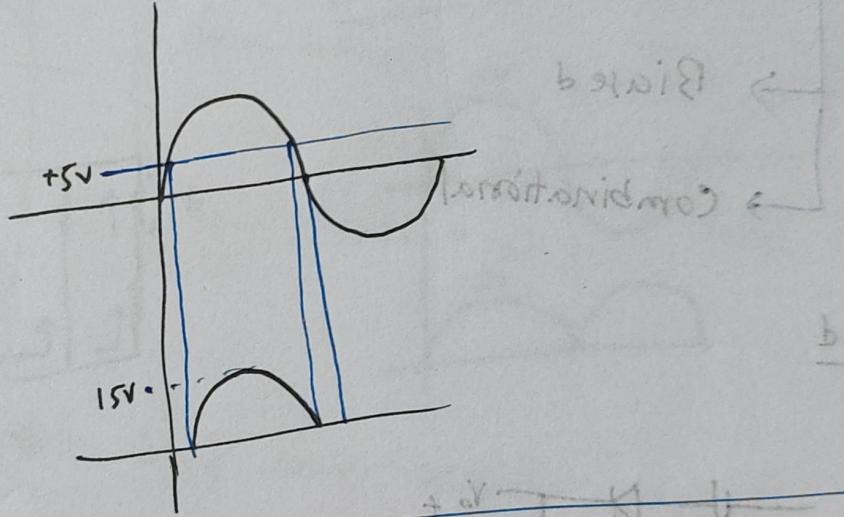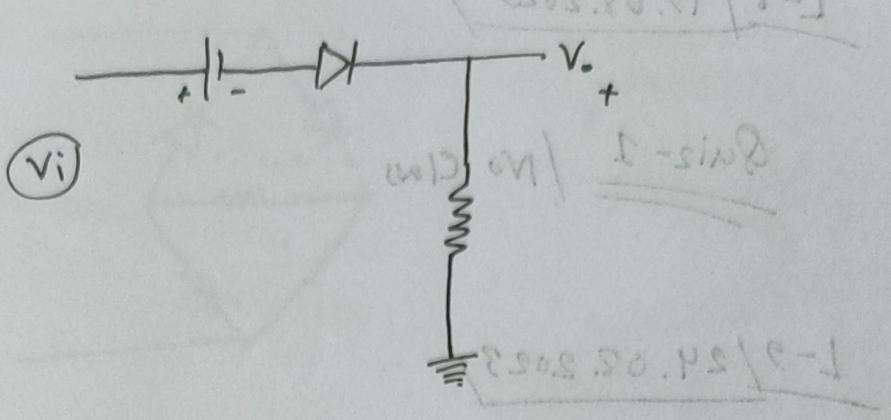Calcium Carbonate (From Coral Source)
and Vitamin D₃ (Colecalciferol)



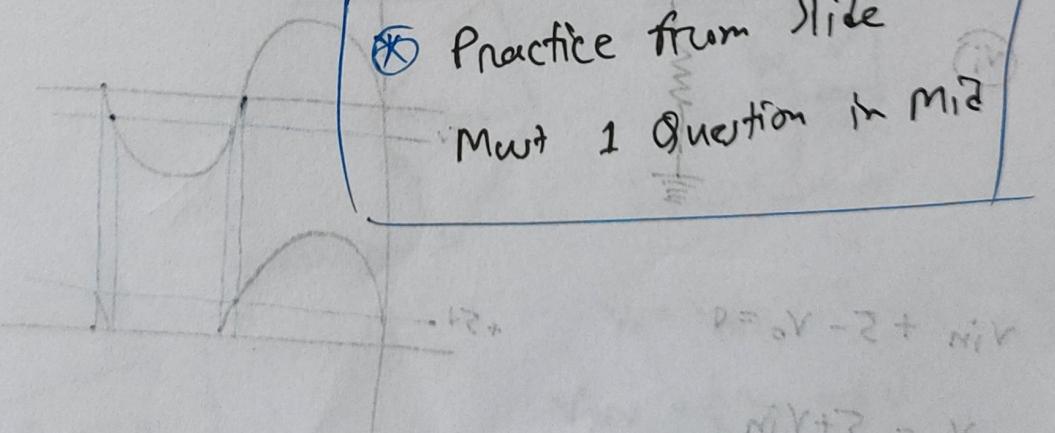Practice from slide
Ques 1 Question in Mid



L-10/26.08.2023/

Clampen Circuit

① Solving Step:

1st Step:

⇒ Forward Cycle identification


⇒ calculate V_o

⇒ calculate V_c


2nd Step:

⇒ Reverse Cycle identification


⇒ calculate V_o

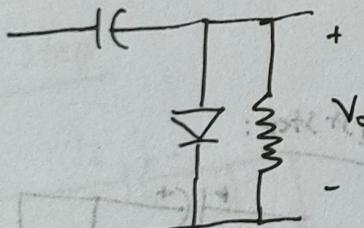

1st Step

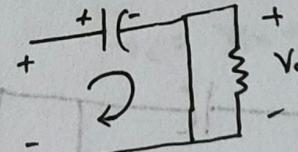

2nd Step:

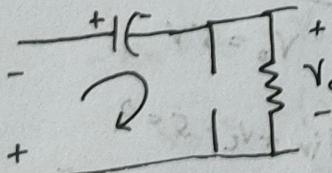

$$-V_{in} - V_c - V_o = 0$$


$$V_o = -(V_{in} + V_c)$$

$$= -20V$$

$V_o = 0$ (Parallel to short)

$$V_{in} - V_c = 0$$

$$V_{in} = V_c = 10V$$

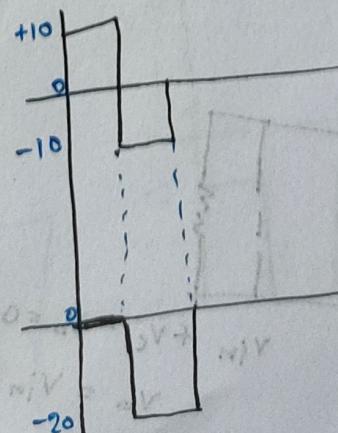


Seacal-D

Calcium Carbonate (From Coral Source) and Vitamin D₃ (Colecalciferol)


Seacal-DX

Calcium Carbonate (From Coral Source) and Vitamin D₃ (Colecalciferol)


⑧

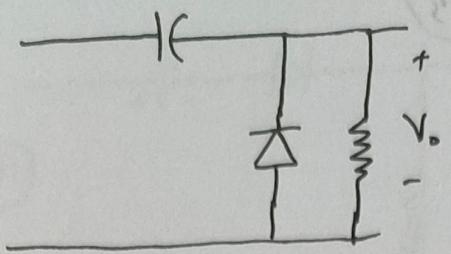

1st Step

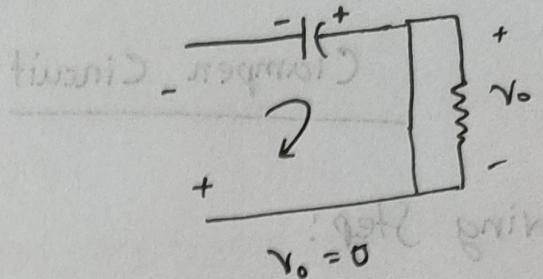

2nd Step:

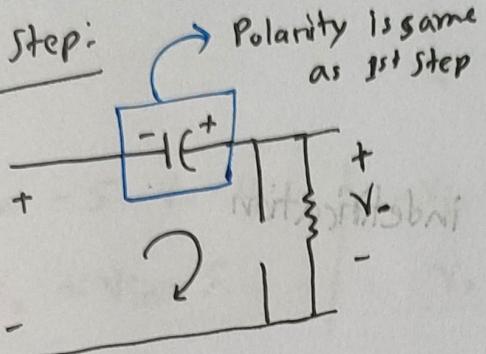


$$V_{in} + V_c - V_o = 0$$



$$V_o = V_{in} + V_c$$

$$= 20 \text{ V}$$

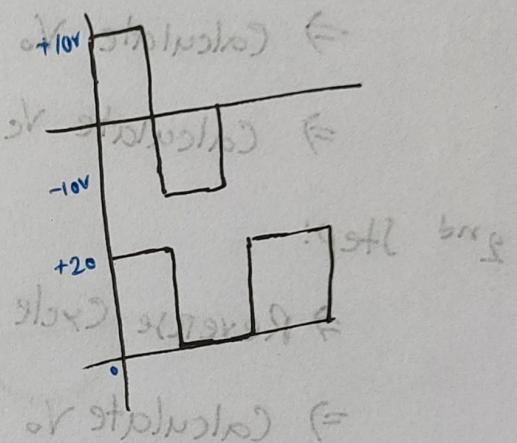
$$-V_{in} + V_c = 0 \Rightarrow V_c = V_{in} = 10 \text{ V}$$




⑨ Biased Clamper Circuit:

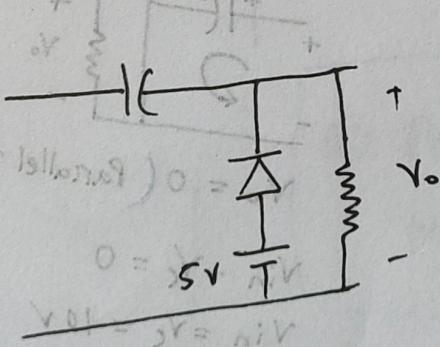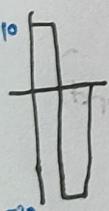

1st Step:

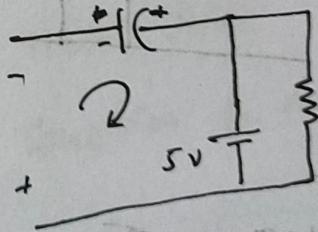

2nd Step

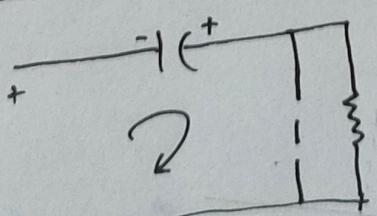


$$V_{in} + V_c - V_o = 0$$

$$V_o = V_{in} + V_c = 10 + 25 = 35$$


$$-V_{in} + V_c - 5 = 0$$

$$0 = V_c = V_{in} + 5$$



$$(10 + 5) = 15$$

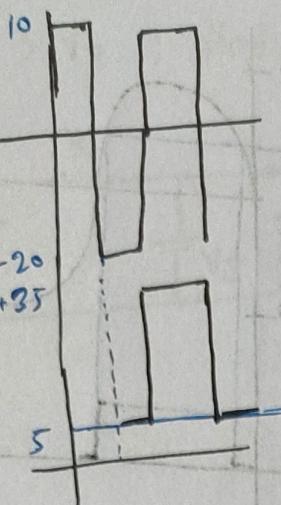


Practice more from
Slide

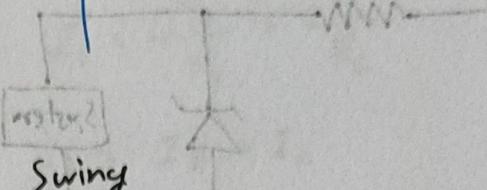
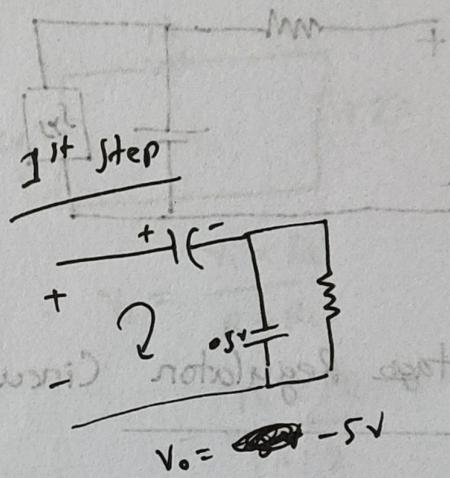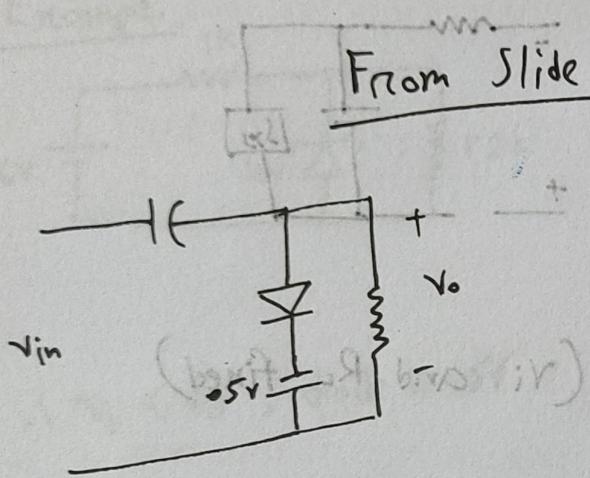
$$\begin{aligned} 10 + 20 &= 30 \\ 35 - 5 &= 30 \end{aligned} \quad \left. \begin{array}{l} \text{Authentication} \\ \text{Successful} \end{array} \right\}$$



2nd Step

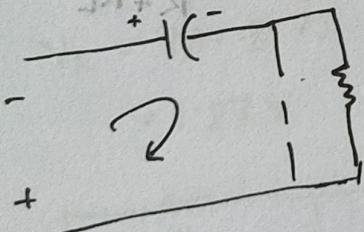


$$-V_{in} - V_c - V_o = 0$$

$$\begin{aligned} V_o &= -(V_{in} + V_c) \\ &= -(10 + 15) \\ &= -25V \end{aligned}$$

2nd Step

$$V_{in} - V_c + 5 = 0$$

$$V_c = V_{in} + 5 = 15V$$

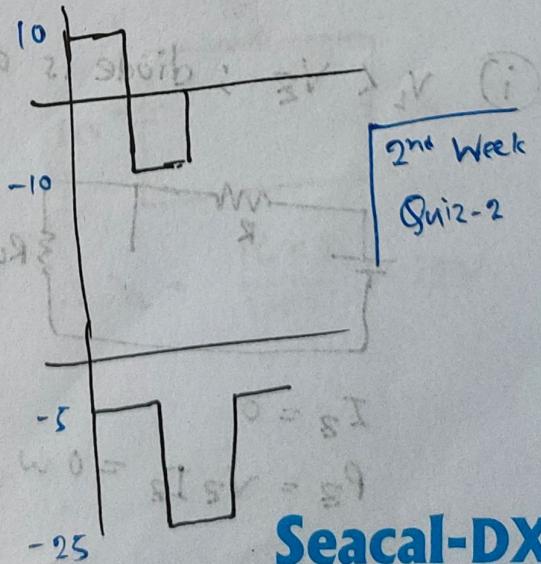

Swing

$$10 + 10 = 20$$

$$-5 + 25 = 20$$

Seacal-D

Calcium Carbonate (From Coral Source) and
Vitamin D₃ (Colecalciferol)





Seacal-DX

Calcium Carbonate (From Coral Source)
and Vitamin D₃ (Colecalciferol)


L-11 / 31.08.2023 /

most common situations

ab712

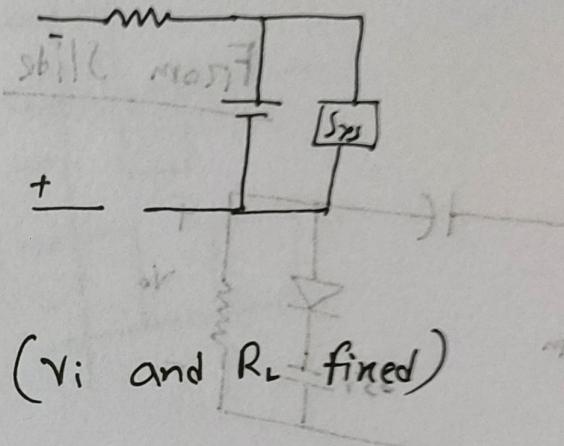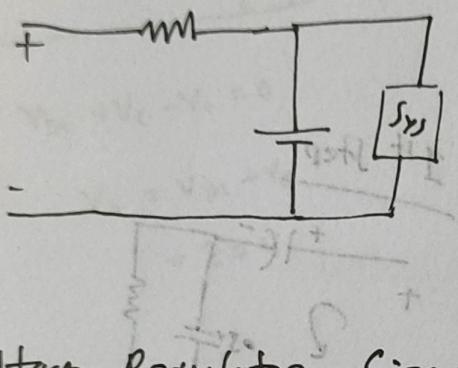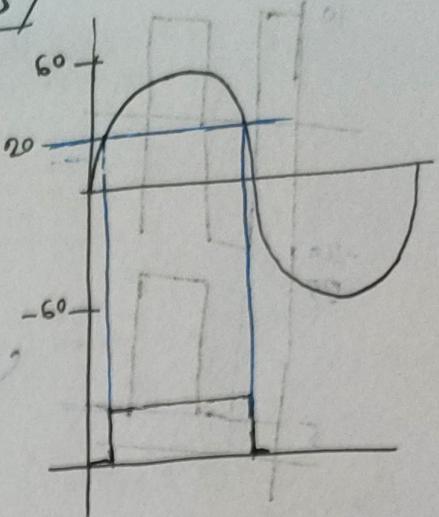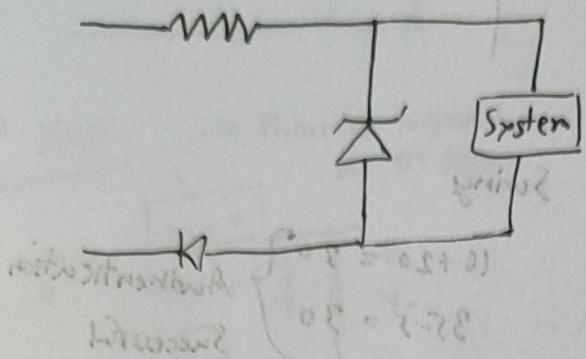


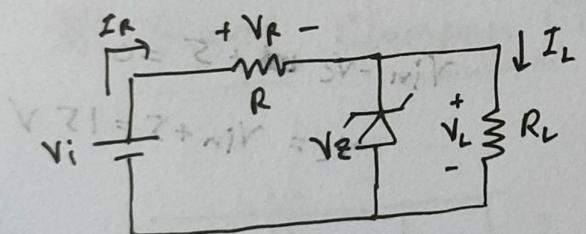* Voltage Regulation Circuit (V_i and R_L fixed)



$$V_L = \frac{V_i \times R_L}{R + R_L}$$

i) $V_L < V_Z$; diode is off

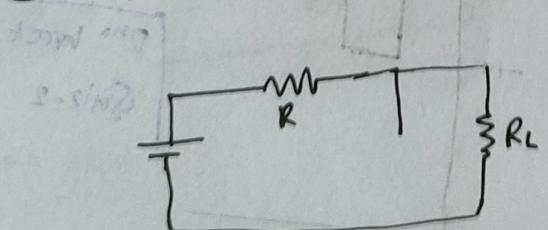

$$I_Z = 0$$

$$P_Z = V_Z I_Z = 0 \text{ W}$$


$$(V_i + nV) - V_Z = 0$$
$$(2.8 + 0.1) - 2.7 = 0$$

$$V_L = 0.1 \text{ V}$$

$$10 + 10 = 20$$
$$2.8 + 2.8 = 5.6$$

$$10 + 10 = 20$$
$$2.8 + 2.8 = 5.6$$

ii) $V_L > V_Z$; diode is On

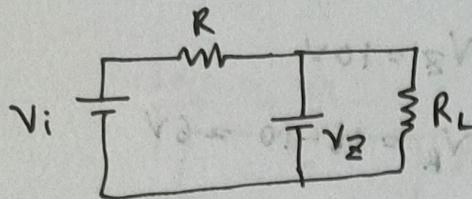

$$I_R = \frac{V_R}{R} = \frac{V_i - V_Z}{R}$$



$$I_L = \frac{V_L}{R_L} = \frac{V_Z}{R_L}$$

$$I_R = I_Z + I_L$$

$$I_Z = I_R - I_L$$

$$P_Z = V_Z I_Z$$

Example:

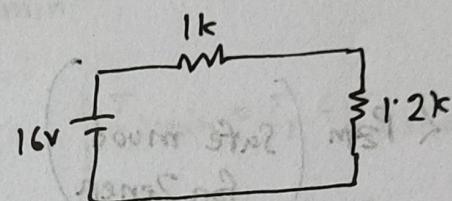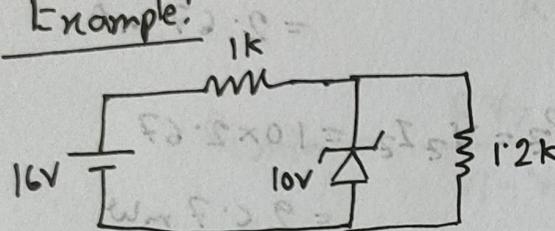



$\rightarrow V_L < V_Z$; diode is off

$$\therefore I_Z = 0$$

$$P_Z = 0 \text{ W}$$

$$V_R = 10 - 8.73$$

$$= 1.27 \text{ V}$$

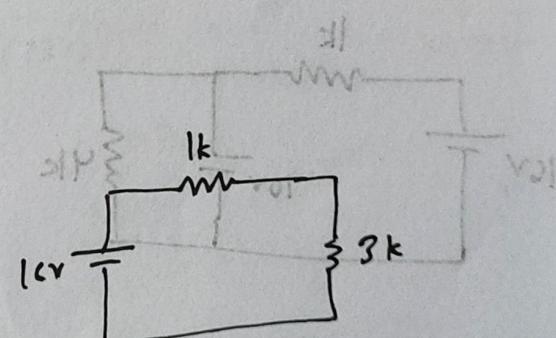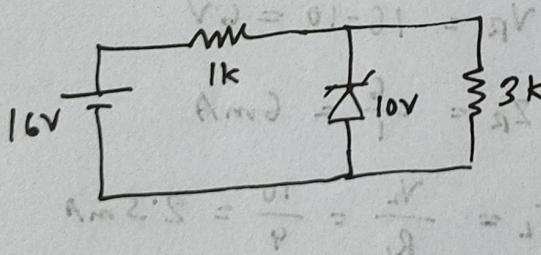

$$\therefore V_L = \frac{16 \times 3}{1+3} = 12 \text{ V}$$


$V_L > V_Z$; diode is On.

Seacal-D

Calcium Carbonate (From Coral Source) and
Vitamin D₃ (Colecalciferol)

Seacal-DX

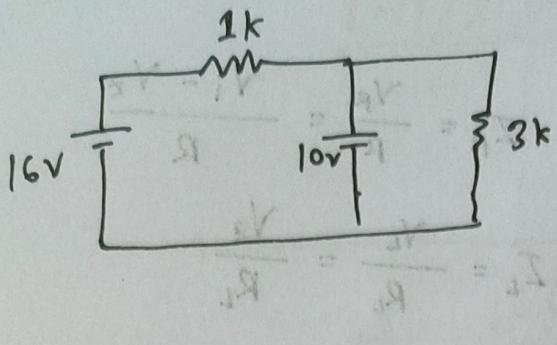Calcium Carbonate (From Coral Source)
and Vitamin D₃ (Colecalciferol)



$$\text{no di. abil. : } 5V < V \quad (ii)$$

$$V_L = 12V$$

$$V_Z = 10V$$

$$V_R = 16 - 10 = 6V$$

$$I_R = \frac{6}{1} = 6mA$$


$$I_L = \frac{V_L}{R_L} = \frac{10}{3} = 3.33mA$$

$$I_Z = I_R - I_L = 6 - 3.33$$

$$= 2.67mA$$

$\therefore P_Z < P_{ZM}$ (Safe mood for Zener)

$$P_Z = V_Z I_Z = 10 \times 2.67$$

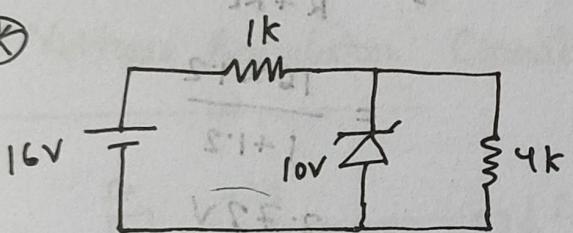

$$V_L = \frac{16 \times 4}{1+4} = 12.8V$$

-> Diode is on

$$\therefore V_L = 12.8V$$

$$V_R = 16 - 10 = 6V$$


$$I_R = \frac{6}{1} = 6mA$$

$$I_L = \frac{V_L}{R_L} = \frac{10}{4} = 2.5mA$$


$$I_Z = I_R - I_L = 6 - 2.5 = 3.5mA$$

$$P_Z = V_Z I_Z = 10 \times 3.5 = 35mW$$

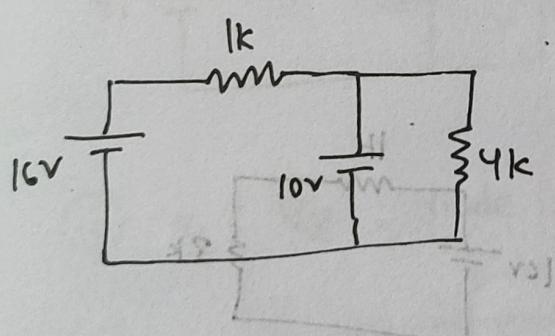$\therefore P_Z > P_{ZM}$ (Not safe, Zener diode will be damage)



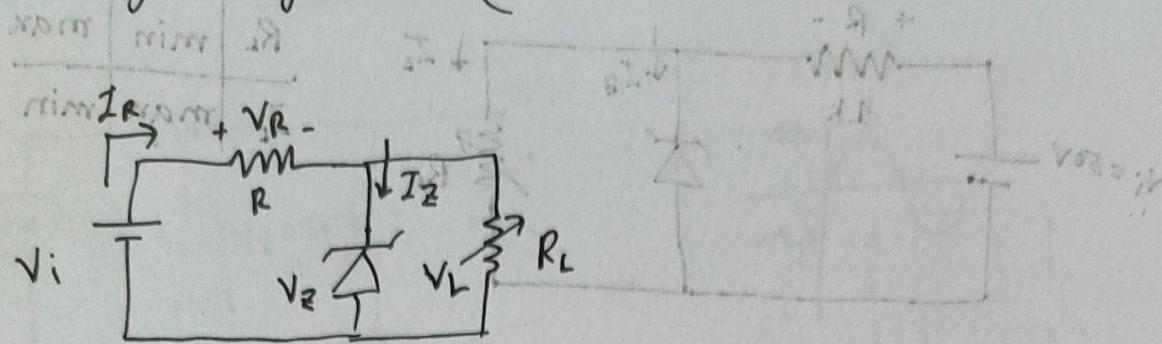(*) Voltage Regulator (V_i fixed & R_L variable)



$$V_Z = V_L = \frac{V_i \times R_{L\min}}{R + R_{L\min}} \Rightarrow V = \text{const}$$

$$R_{L\min} = \frac{R V_Z}{V_i - V_Z} \quad | \quad I_{L\min} = I_R - I_{Z\max}$$

$$I_{L\max} = \frac{\sqrt{V_{Z01} + R_{01}}}{R_{L\max}} \quad | \quad P_{Zm} = V_Z I_{Z\max}$$

$$I_{Z\min} = I_R - I_{L\max} \quad | \quad R_{L\max} = \frac{V_L}{I_{Z\min}}$$

~~$$A_{vOP} = \frac{10}{0.82} = \frac{10}{0.82} = 12 = \text{normal}$$~~

$$A_{vON} = \frac{0.1 - 0.2}{0.11} = \frac{0.1}{0.11} = \frac{10}{11} = 0.91 = 9.1$$

~~$$\frac{0.1 - 0.2}{0.11} = \frac{0.1}{0.11} = \frac{10}{11} = 0.91 = 9.1$$~~