



North South University
Department of Electrical & Computer Engineering
LAB REPORT- 03

Course Code: CSE 231L

Course Title: Digital Logic Lab

Section: 08

Lab Number: 03

Experiment Name: Combinational Logic Design (Canonical Form)

Combinational Logic Design (Canonical Form)

Experiment Date: 06 March, 2023

Date of Submission: 13 March, 2023

Submitted by Group Number: 05

Group members:

Name	ID	Obtained Mark Simulation [5]	Obtained Mark Lab Report [15]
1. Syed Tashriful Alam	2212623042		
2. Sazid Hasan	2211513642		
3. Joy Kumar Ghosh	2211424642		
4. Md. Nifat Hossain	2212923042		
5. Md. Rafawat Islam	2122343642		

Course Instructor: Dr. Md. Abdur Razzak (Azz)

Submitted To: Pritthika Dhar

Experiments Name : Combinational Logic Design (canonical Form)

Objective :

- Become familiarized with the analysis of combinational logic networks.
- Learn the implementation of networks using two canonical forms.

Apparatus:

- 1x IC 7411 Triple 3-input AND gates
- 2x IC 4075 Triple 3-input OR gates
- 1x IC 7409 Hex Inverters (NOT gates)

Theory:

Minterms and Maxterms: A minterm is a product of term that includes all the variables in the function.

where each variable appears either in its direct or complemented form. For example, in a function of two

variables, the minterms are:

- $A'B'$

- $A'B$

- AB'

- AB

A maxterm, on the other hand, is a sum term that includes all the variables in the function, where each variable appears either in its direct or complemented form. For example, in a function of two variables, the maxterms are:

- $(A+B)$
- $(A'+B)$
- $(A+B')$
- $(A'+B')$

It is important to note that minterms and maxterms are complements of each other. That is, the minterm expression for a given Boolean function can be obtained by taking the complement of its maxterm expression, and vice versa.

The four minterms and maxterms for 2 variables, together with symbolic designations, are listed in Table 1.

		Minterms		Maxterms	
A	B	Term	Designation	Term	Designation
0	0	$\bar{A}\bar{B}'$	m_0	$A+B$	m_0
0	1	$\bar{A}B$	m_1	$A+B'$	m_1
1	0	$A\bar{B}'$	m_2	$\bar{A}+B$	m_2
1	1	AB	m_3	$\bar{A}+B'$	m_3

Table 1


Canonical Forms:

In digital logic, a canonical form is a unique and standard representation of a Boolean function using either minterm or maxterms. There are two types of canonical forms: sum of products (SOP) and product of sums (POS).

A Boolean function expressed in SOP canonical form is a sum of minterms, where each minterm represents a unique combination of input variables that produces a logic high output. For example, the Boolean function $F(A, B, C) = A'B'C + ABC + ABC'$ can be expressed in SOP canonical form as $F(A, B, C) = m(1, 2, 6)$, where $m(i)$ denotes the i -th minterm.

A Boolean function expressed in POS canonical form is a product of maxterms, where each maxterm represents a unique combination of input variables that produces a logic low output. For example, the Boolean function $F(A, B, C) = (A+B+C)$ can be expressed in POS canonical form as $F(A, B, C) = M(0, 3, 4, 5, 7)$, where $M(i)$ denotes the i -th maxterm.

Circuit Diagram:

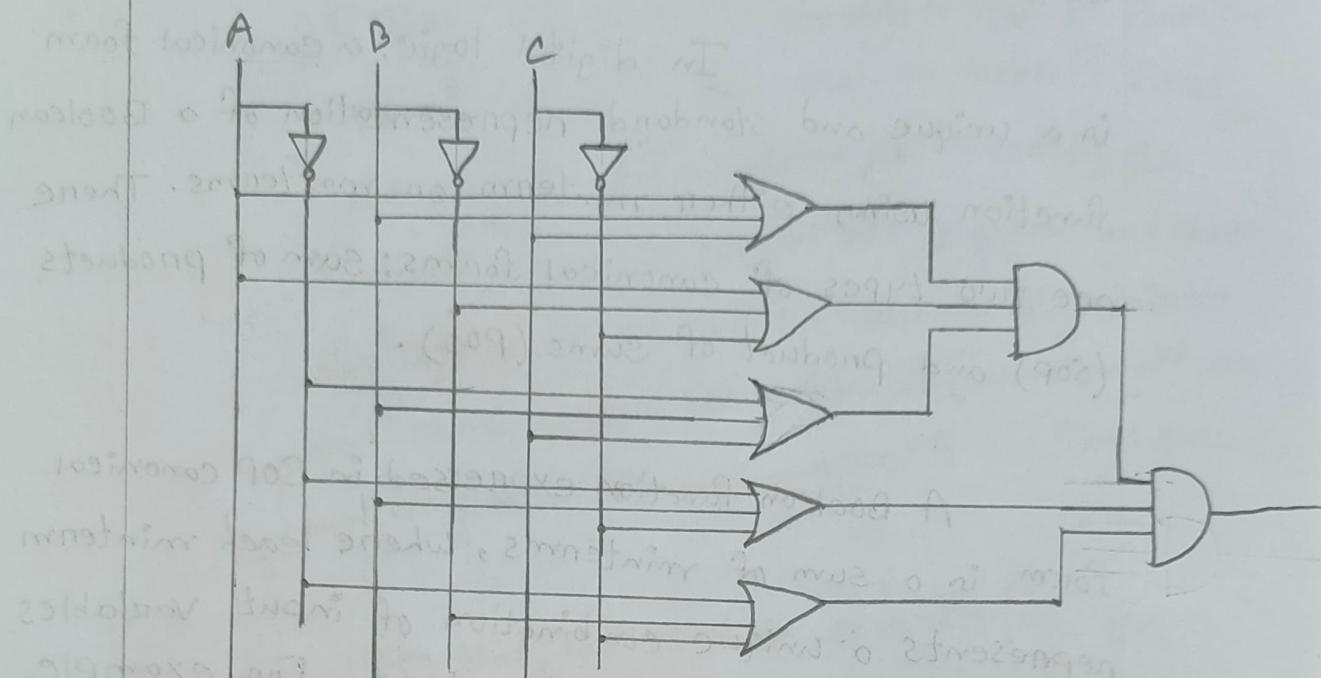

Experimental Procedure:

01. First, we write down all minterms and maxterms of three inputs ABC in Table F.1.

Table F.1.

02. Then, we express the function in 1st and 2nd Canonical forms and write it in Table F.2.

03. After that, we draw two circuit diagram for 1st and 2nd Canonical forms, with PIN labels in Figure F.1.

04. Then, we start to construct the 1st Canonical Form circuit in the trainer board. First, we connect one minterm and verify its output. Then, we connect 2nd minterm and check for output. One by one we connect all minterm and check output for each. Then we connect all minterm in an OR gate and check the final output.

05. After that, we start to construct the 2nd Canonical Form circuit in the trainer board. First, we connect one maxterm and verify its output. Then, we connect 2nd maxterm and check for output. One by one we connect all maxterm and check output for each. Then we connect all maxterm in an AND gate and check the final output.


Simulation: Attached

Experimental Data Table:


Input reference	A	B	C	F	Min term	Max term
0	0	0	0	0	$A'B'C$	$A+B+C$
1	0	0	1	1	$A'B'C'$	$A+B+C'$
2	0	1	0	1	$A'BC'$	$A+B'+C$
3	0	1	1	0	$A'BC$	$A+B'C'$
4	1	0	0	0	ABC'	$A'+B+C$
5	1	0	1	0	ABC	$A'+B+C'$
6	1	1	0	1	$AB'C'$	$A'+B'+C$
7	1	1	1	0	ABC	$A'+B'+C'$

Table F.1 Truth table to a combinational circuit

	Shorthand Notation	Function
1 st Canonical Form	$F = \Sigma(1, 2, 6)$	$F = A'B'C + A'B'C' + ABC'$
2 nd Canonical Form	$F = \Pi(0, 3, 4, 5, 7)$	$F = (A+B+C)(A+B'+C')(A'+B+C)(A'+B+C')(A'+B'+C)$

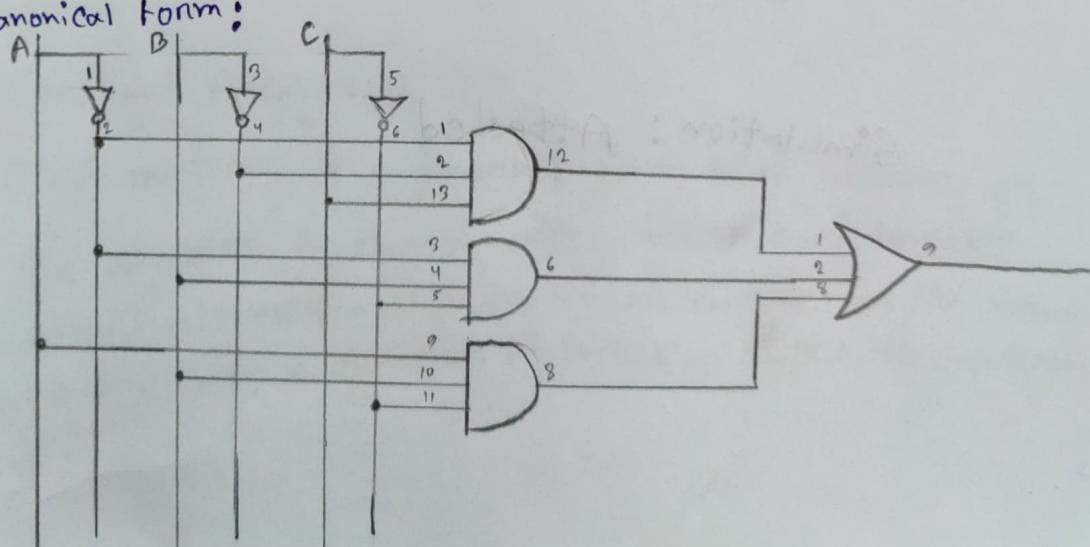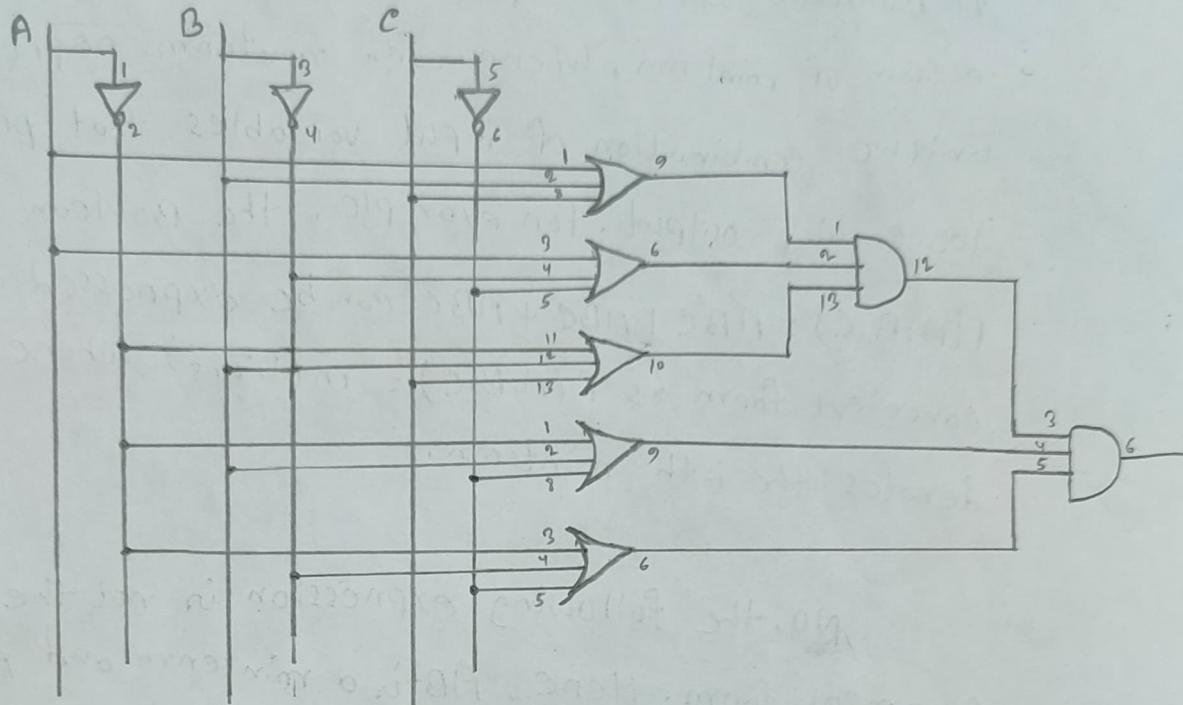Table F.2 1st and 2nd Canonical forms of combinational circuit of Table F.11st Canonical Form:

$$\therefore AB$$

2nd Canonical Form:

Results:

After constructing two circuits of the 1st and 2nd Canonical forms, we found that both outputs are the same. That means we can express a function in either the 1st Canonical Forms or the 2nd Canonical Form; both outputs will be the same. We can check which Form takes fewer gates than others and then reduce the cost of building the circuit.

Questions and Answers (Q/A):

Q1. A minterm is a product term that includes all the variables in the function, where each variable appears either in its direct or complemented form. For example, in a function of two variables, the minterm one:

- $A'B'$
- $A'B$
- AB'
- AB

A Boolean function expressed in SOP Canonical form is a sum of minterms, where each minterm represents a unique combination of input variables that produces a logic high output. For example, the Boolean function $F(A,B,C) = A'B'C + A'BC' + ABC'$ can be expressed in SOP canonical form as $F(A,B,C) = m(1,2,6)$, where $m(i)$ denotes the i -th minterm.

No, the following expression is not the first canonical form. Here, AB' is a minterm and ABC' is also a minterm. And two minterms are connected by OR gate. So, it's a sum of products. But it's not a standard SOP. So, we can't call it by 1st canonical form.

Q2. No, just because a Boolean expression is in Canonical form does not necessarily mean that it is in minimal form. Canonical form simply represents a unique and standard representation of a Boolean function using either minterms or maxterms. On the other hand, the minimal form represents the simplest possible expression of that function in terms of its variables and operations.

It is possible for Boolean expression to be in Canonical form but not be in its minimal form, meaning that there may be a simpler expression that represents the same function. For example, consider the Boolean function $F(A, B, C) = A'B'C + ABC + A'BC + AB'C$. Consider the Boolean function $F(A, B, C) = A'B'C + ABC + A'BC + AB'C$ in SOP canonical form. We can simplify this expression using Boolean algebra as:

$$\begin{aligned} F(A, B, C) &= A'B'C + ABC + A'BC + AB'C \\ &= A'B'C + ABC + AB(C + C') \\ &= A'B'C + ABC + AB \end{aligned}$$

In summary, while Canonical form provides a standardized way to represent a Boolean function, it does not necessarily ensure that the expression is in its minimal form.

Q3. List of all the minterm and maxterm of 4 binary variables are given below:

Input Reference	A	B	C	D	F		
0	0	0	0	0	1	$A'B'C'D'$	$A + B + C + D$
1	0	0	0	1	0	$A'B'C'D$	$A+B+C+D'$
2	0	0	1	0	1	$A'B'C'D'$	$A+B+C'+D$
3	0	0	1	1	1	$A'B'C'D$	$A+B+C'+D'$
4	0	1	0	0	1	$A'B'C'D'$	$A+B'+C+D$
5	0	1	0	1	0	$A'B'C'D$	$A+B'+C+D'$
6	0	1	1	0	0	$A'B'C'D'$	$A+B'+C'+D$
7	0	1	1	1	1	$A'B'C'D$	$A+B'+C'+D'$
8	1	0	0	0	0	$A'B'C'D'$	$A'+B+C+D$
9	1	0	0	1	1	$A'B'C'D$	$A'+B+C+D'$
10	1	0	1	0	1	$A'B'C'D'$	$A'+B+C'+D$
11	1	0	1	1	1	$A'B'C'D$	$A'+B+C'+D'$
12	1	1	0	0	1	$A'B'C'D'$	$A'+B'+C+D$
13	1	1	0	1	1	$A'B'C'D$	$A'+B'+C+D'$
14	1	1	1	0	0	$A'B'C'D'$	$A'+B'+C'+D$
15	1	1	1	1	0	$A'B'C'D$	$A'+B'+C'+D'$

Given,

$$\text{product of Maxterm : } (A+B'+C+D')(A'+B'+C'+D)(A'+B+C+D)(A'+B'+C'+D') \\ (A+B+C+D')(A+B'+C+D)$$

$$\therefore \text{Sum of Minterm : } A'B'C'D' + A'B'C'D + A'B'C'D + A'B'C'D' + A'B'C'D + A'B'C'D \\ + A'B'C'D + A'B'C'D + A'B'C'D' + A'B'C'D$$

04.

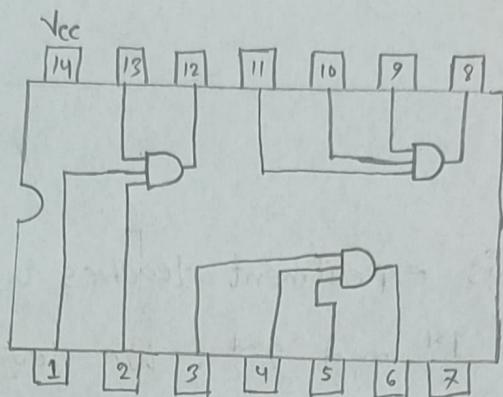
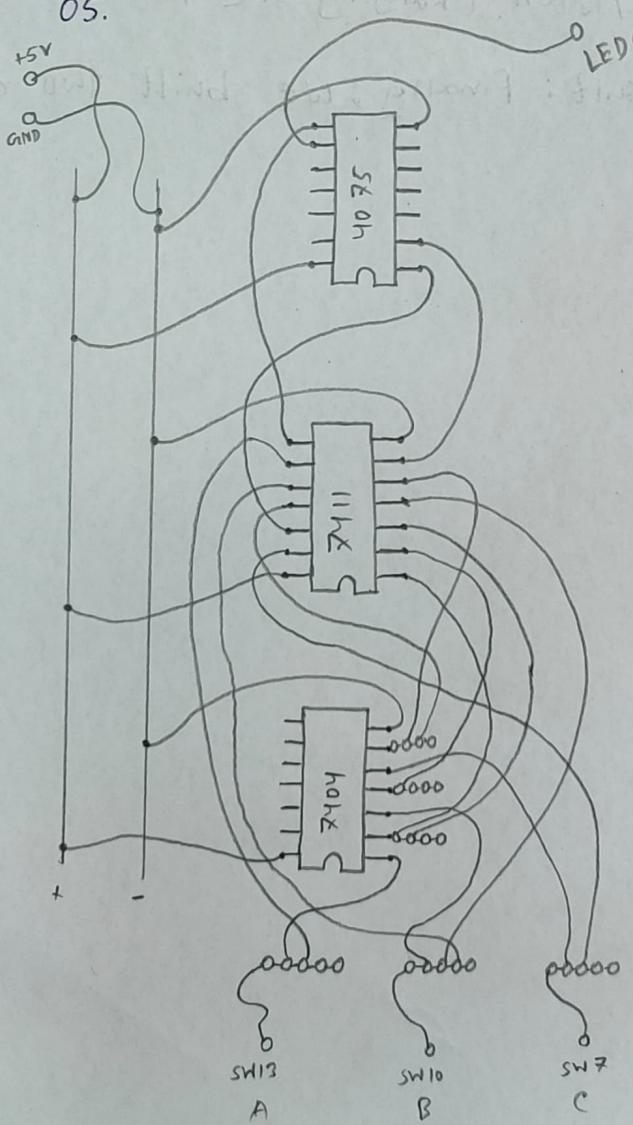


Fig.: Internal gates of the 7411 IC.


05.


Fig.: IC diagram of 1st Canonical form

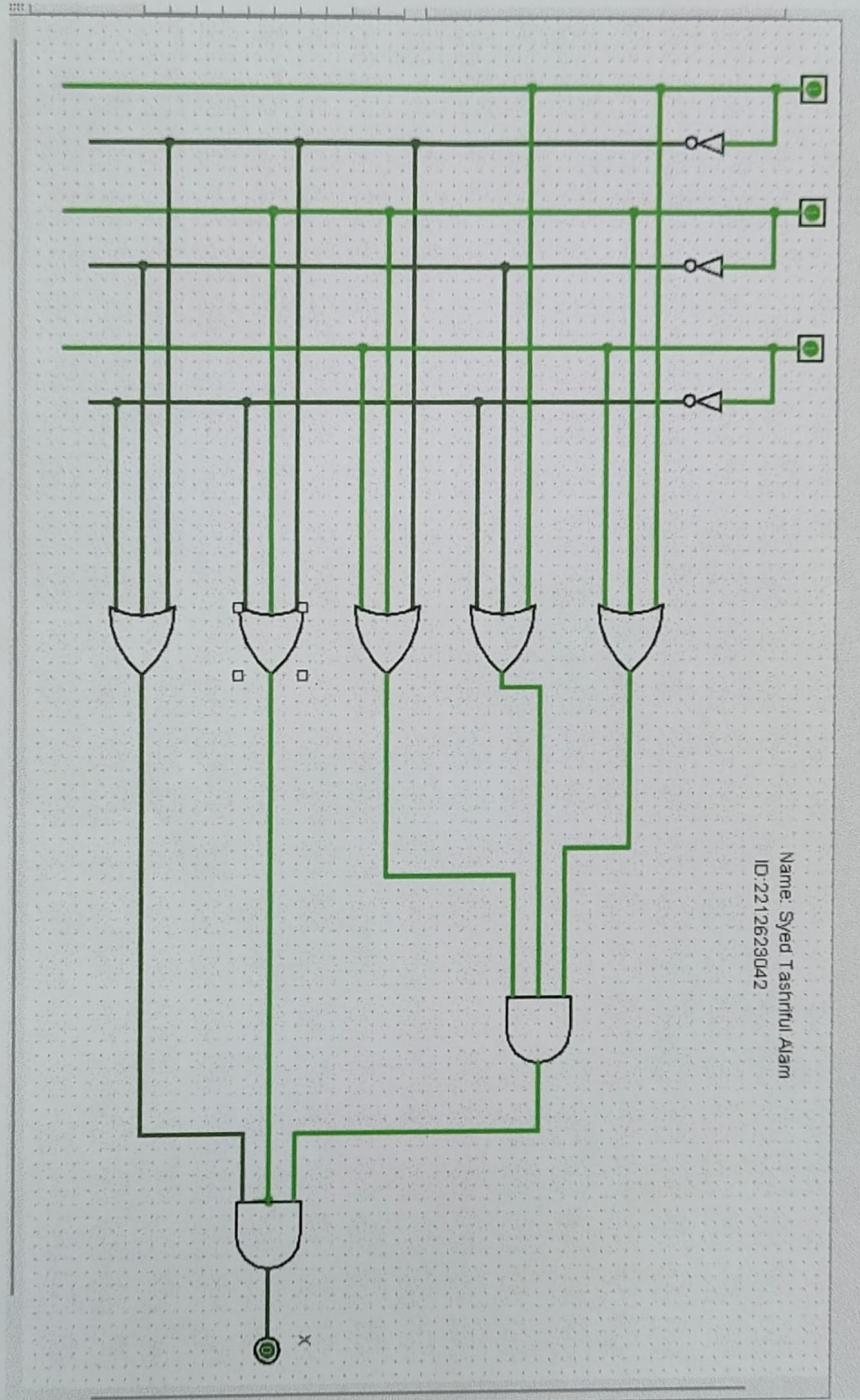Q6. Simulation Attached

Discussion :

This experiment teaches us about two Canonical forms, 1st and 2nd. We learn how to build a combinational circuit using the canonical form. We also verify that two canonical forms give us the same output. While constructing the 1st canonical form in this experiment, we face some problems with the NOT IC. After changing the NOT IC, we get the accurate result. Finally, we built two circuits successfully.



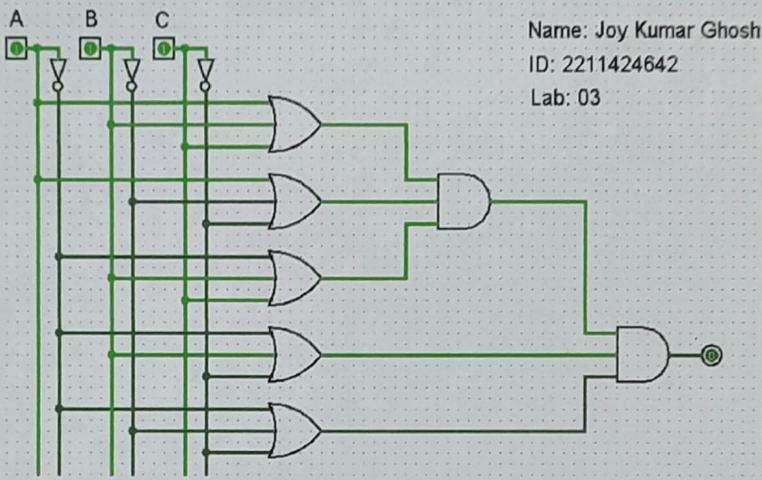

Name: Joy Kumar Ghosh
ID: 2211424642
Lab: 03



E. Experimental Data

Input Reference	A B C	F	Min term	Max term
0	0 0 0	0	$A'B'C'$	$A+B+C$
1	0 0 1	1	$A'B'C$	$A+B+C'$
2	0 1 0	1	$A'BC'$	$A+B'+C$
3	0 1 1	0	$A'BC$	$A+B'+C'$
4	1 0 0	0	$AB'C'$	$A'+B+C$
5	1 0 1	0	$AB'C$	$A'+B+C'$
6	1 1 0	1	ABC'	$A+B+C$
7	1 1 1	0	ABC	$A'+B'+C'$

Table F.1 Truth table to a combinational circuit

	Shorthand Notation	Function
1 st Canonical Form	$F = \Sigma(1, 2, 6)$	$F = A'B'C + A'BC' + ABC'$ ✓
2 nd Canonical Form	$F = \Pi(0, 3, 4, 5, 7)$	$F = (A+B+C)(A+B'+C')(A'+B+C)(A'+B+C')(A'+B+C')$ ✓

Table F.2 1st and 2nd canonical forms of the combinational circuit of Table F.1

Priti Bhikha Dhar

06/03/23

Bonus → 2

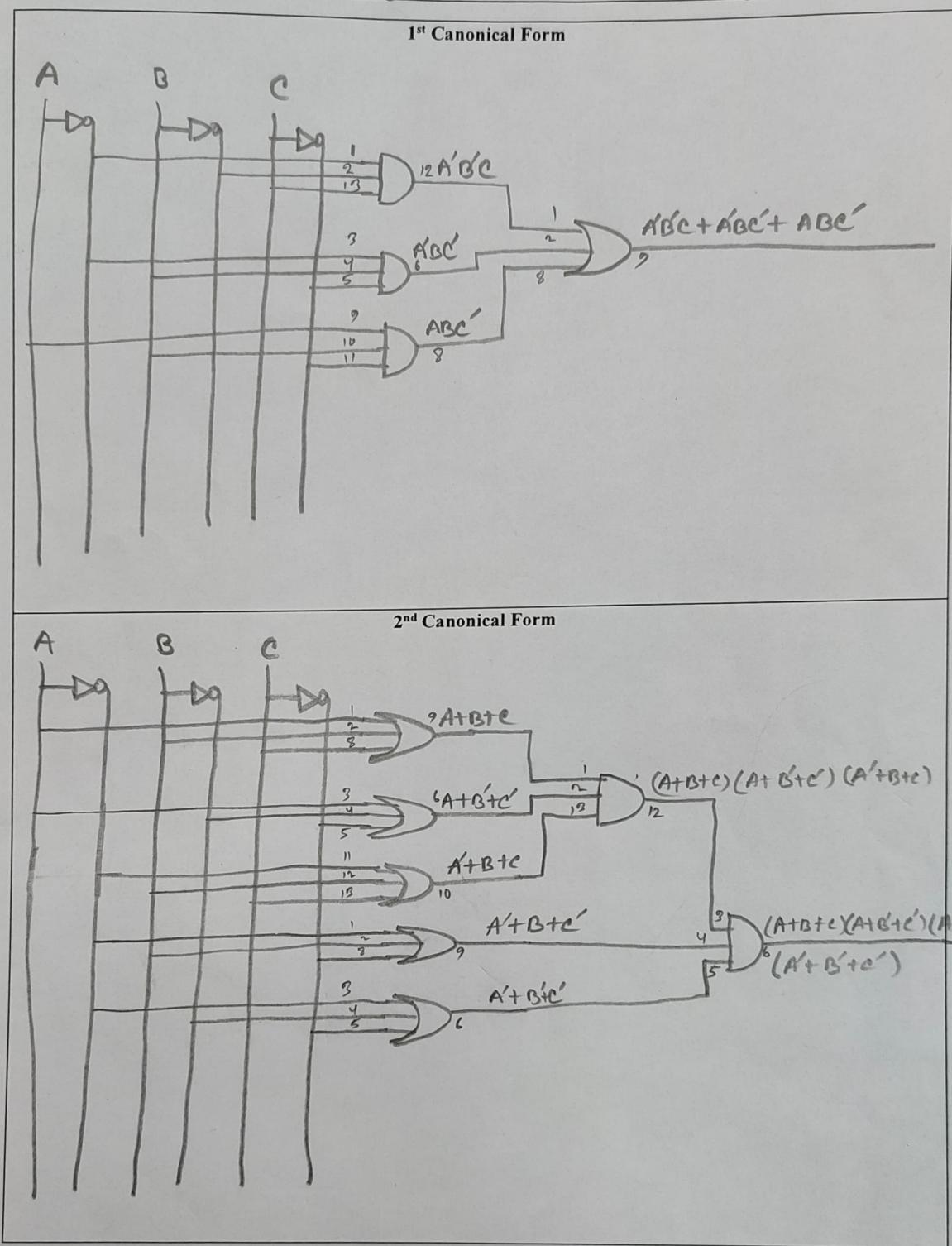


Figure F.1 1st and 2nd canonical circuit diagrams of the combinational circuit of Table F.1