

Summer 2023

EEE/ETE 111L

Analog Circuits-I Lab (Sec-11)

Faculty: Professor Dr. Monir Morshed (DMM)

Instructor: Rokeya Siddiqua

Lab Report 03: Diode rectifier circuits.

<p>Date of Performance: 26 August 2023</p> <p>Date of Submission: 02 September 2023</p>	<p>Group no.: 05</p> <ul style="list-style-type: none">1. Mahmudul Hasan- 20115510432. Sabrina Haque Tithi- 20312656423. Afrin Akter- 21122466424. Joy Kumar Ghosh – 22114246425. Sazid Hasan- 2211513642
---	--

Experiment No : 03

Experiment Name : Diode Rectifiers circuits .

Objective :

Study of different diode rectifier circuits .



Theory :

A diode flows current in one direction only in reverse bias if becomes open so no current passes . The current flows in forward bias only . A rectifier converts an AC signal into a DC signals . When an alternative voltage is applied across a diode it allows only the half cycle . Positive or negative it depends on the orientation of the diode . During forward bias , the negative side won't be in consideration .

There are two types of diode rectifiers -

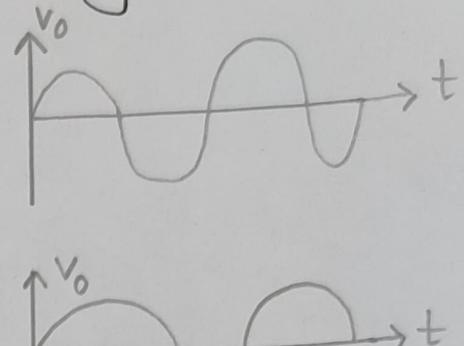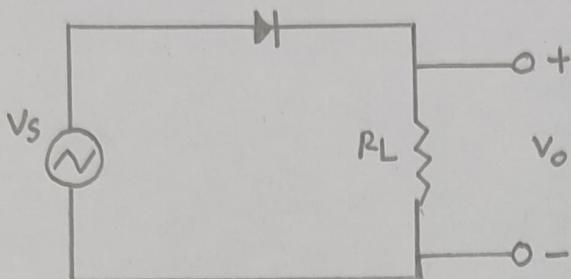- 1) Half wave rectifiers .
- 2) Full wave rectifiers .


Half wave rectifier:
It can be build by using one signal diode



Output receives half of the input. Average dc voltage is low. Output voltage is not smooth due to ripple.

Full wave Rectifier:

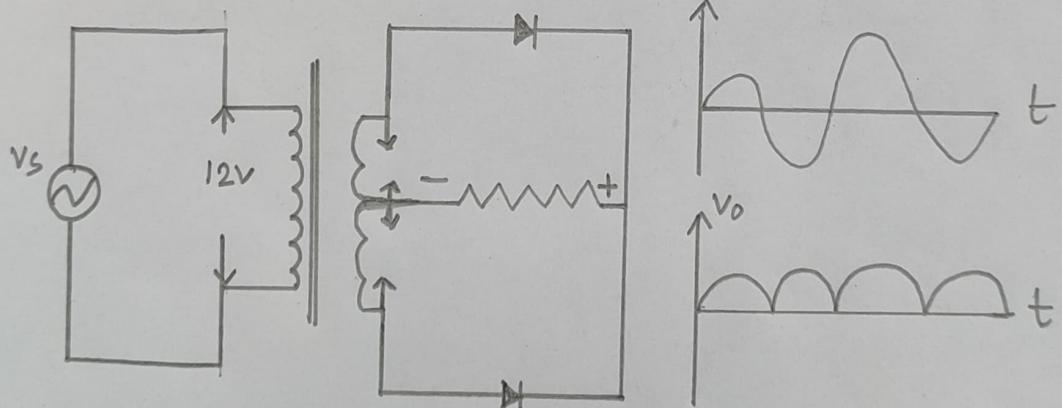
In this both the half cycle is present in the output.



full wave rectifier using
Centered tapped transformers .

Full wave rectifier requires more space and it is not cost effective.

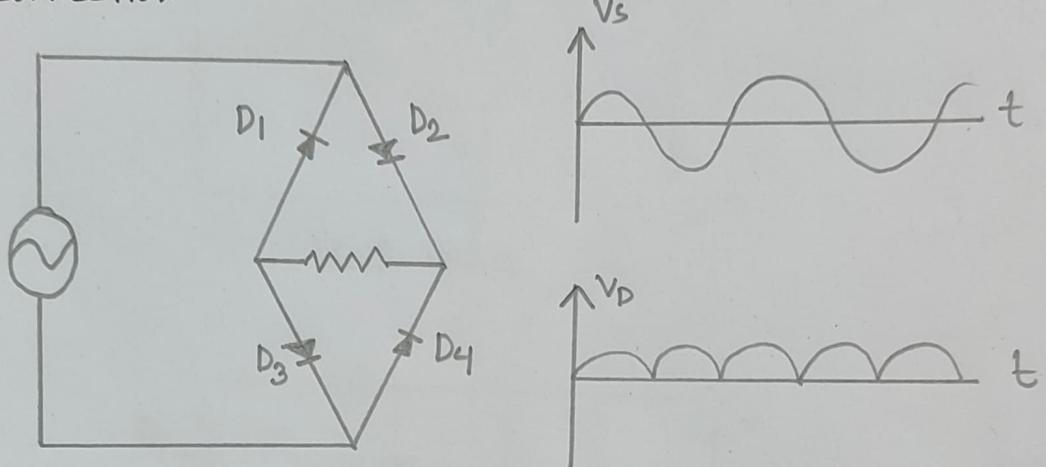To solve the problem full-wave bridge rectifier. In this four diodes will be connected as bridge connection.




full wave bridge rectifier.

List of Equipment :

1. P-n junction diode \rightarrow IN4007 \rightarrow 4 pieces.
2. Resistors \rightarrow 10 k Ω \rightarrow 1 piece
3. capacitors \rightarrow 0.22 μ F, 10 μ F \rightarrow 1 piece each
4. signal generators \rightarrow 1 unit.
5. Trainer Board \rightarrow 1 unit.
6. Oscilloscope \rightarrow 1 unit
7. Digital Multimeter \rightarrow 1 unit
8. chords & wire \rightarrow per requirement.


Circuit Diagram :

(1)

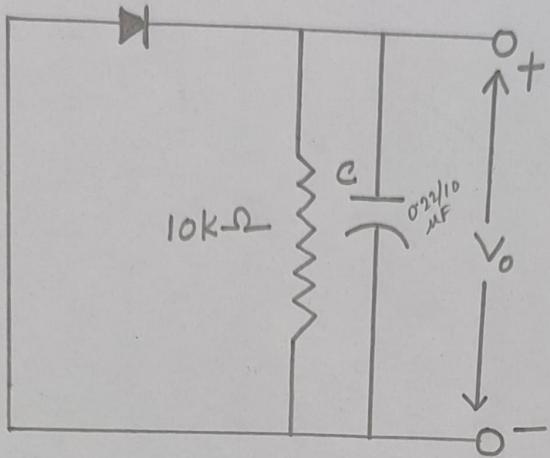

Half wave

(2)

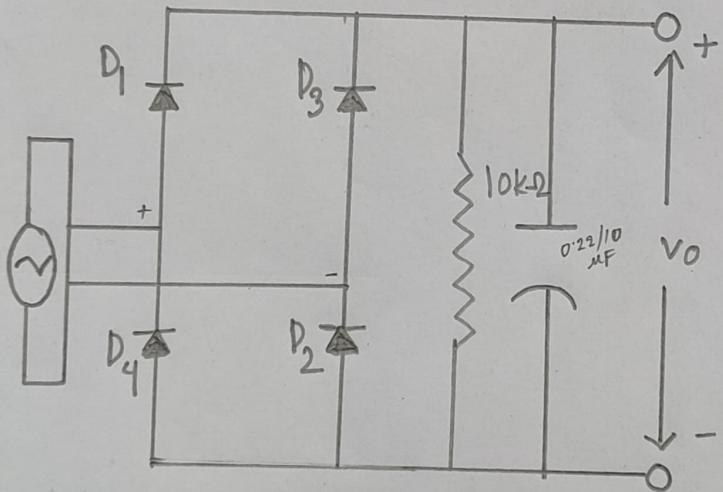

full wave

Data Table :

	Half wave Rectifier	full wave Rectifier
V ₀ (P-P) (without capacitor)	5.00 V	
V ₀ (P-P) (with 0.22 μF)	1.60 V	
V ₀ (P-P) (with 10μF)	0.20 V	

Ans: to the Q: NO-01

For Fig 2.4 & Fig 2.5, draw the input-output wave
shape without capacitor, with $0.22\mu F$ capacitor
and $10\mu F$ capacitor.

Ans: Graph is attached with the report.

Ans: to: the: Q: NO-02

Compare the change in the wave-shape and Peak to peak values for no capacitor at the Output to $0.22\text{ }\mu\text{F}$ to $10\text{ }\mu\text{F}$.

Ans: In comparison to the ripple wave-form created with a $0.22\text{ }\mu\text{F}$, the output wave form obtained with $10\text{ }\mu\text{F}$ produces a straight horizontal line.

There is a considerable difference in frequency from 10 kHz to 100 Hz . The output curve shifts from a straight line to a curved line. When the capacitance is changed from 10 kHz to 100 Hz , the line becomes a tripling wave. When the waveforms are compared it is clear that the output voltage waveform is different can be seen. The output waveform is produced by $10\text{ }\mu\text{F}$.

The half wave rectifier value is $\frac{500\text{ V}}{ }$.

The full wave rectifier value is $\frac{ }{ }$.
Then for voltage 0.22 mF capacitor, the half-wave rectifier value is $\frac{1.60}{ }$ v. & the full wave rectifier value is $\frac{ }{ }$ mv. for voltage-out with a $10\text{ }\mu\text{F}$ capacitor, the half-wave rectifier value is $\frac{0.20}{ }$ v. & the full-wave rectifier value is $\frac{ }{ }$ v.

Ans: to the Q: NO-03

Explain the effect on the output signal for changing the frequency of the input signal.

Ans: from the graph we can see, some graphs showing the input and output But they are quietly changing at the time of charging.

In the 1st case, if we add 0.22uf the in the output graph we see the V_{max} and V_{min} is increasing drastically and if more charge added in the result is the same as they are increasing. The V_{pp} & V_{max} also increasing but if we add more charge to it then after a certain period the V_{pp} also starts decreasing.

Ans: to: the: Q: No—04

Between half wave and full wave which circuit produces smoother output ? Briefly explain in context with data collection .

Ans: At first, when we do the experiment we made circuit for half wave rectifier . then we found some value and ~~a~~ input-output with out capacitor graph . After doing the Half-wave circuit we can see that the Half-wave circuit is not the have not that smoother output .

and, then when we started doing full-wave circuit we faced some technical issues , we have all our circuits and connections fixed properly . and cheaked lot of time with our lab instructor also ; But due to some water problem and some technical problem we could not complete the full wave rectifier circuit .

But through theoretical knowledge we can say that and after seeing some full wave rectifier graph we can say that, the Between half wave and full wave circuit "Full-wave" makes produces smoother output .

Discussion:

In our 3rd Experiment (Diode Rectifier circuit) we learnt about diode rectifier circuit.

In the theory part we saw types of rectifiers and their advantages and disadvantages.

Some alternative uses also noticed. Such as half-wave rectifier, full-wave rectifier, full-wave bridge rectifier. We ~~saw~~ two did two circuit in multism.

Observed wave form for different frequencies.




Also observed the output with capacitors and without capacitors than we collects all the output for report purpose. But in this Experiment we faced some technical issues while doing full-wave rectifier circuits. we fixed all our connections and circuit properly. And we have checked it lot of time also with out lab instructors. But Due to some technical problem we ~~can't~~ should not complete the full-wave rectifier circuit.




Contribution:-



SN	Name	ID	Contribution
01	Sabrina Haque Tithi	2031265642	Report Writing & Data writing
02	Sazid Hasan	2211513642	1st circuit building & Operating Oscilloscope
03	Afrin Akter	2112246642	Simulation, graph & Operating function generator.
04	Joy Kumar Ghosh	2211424642	2nd circuit building, helped in operating Oscilloscope
05	Mahmudul Hasan	2011551043	Absent due to fever.




Attachment:

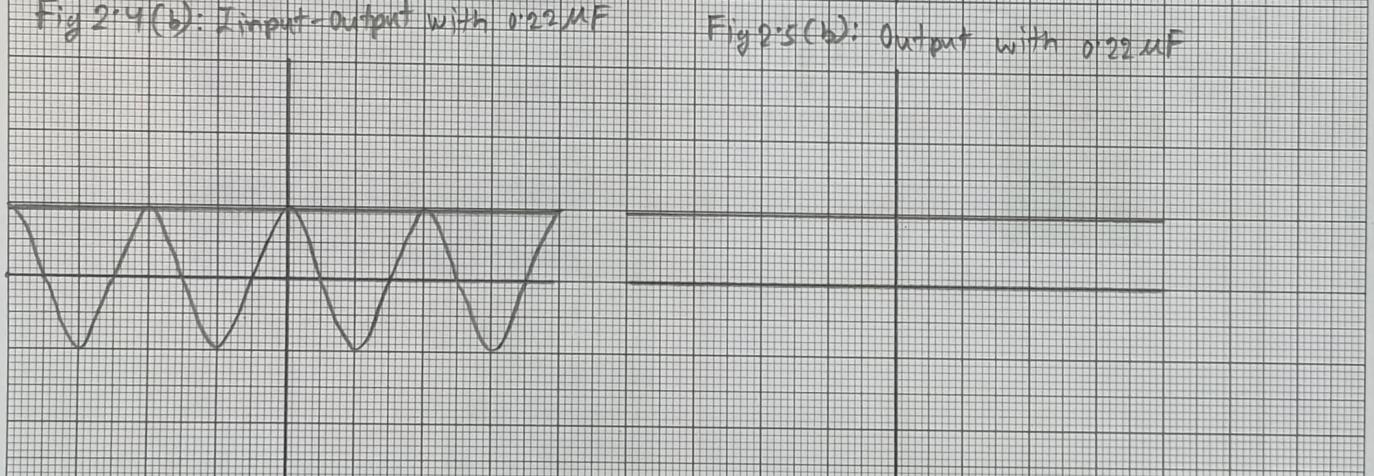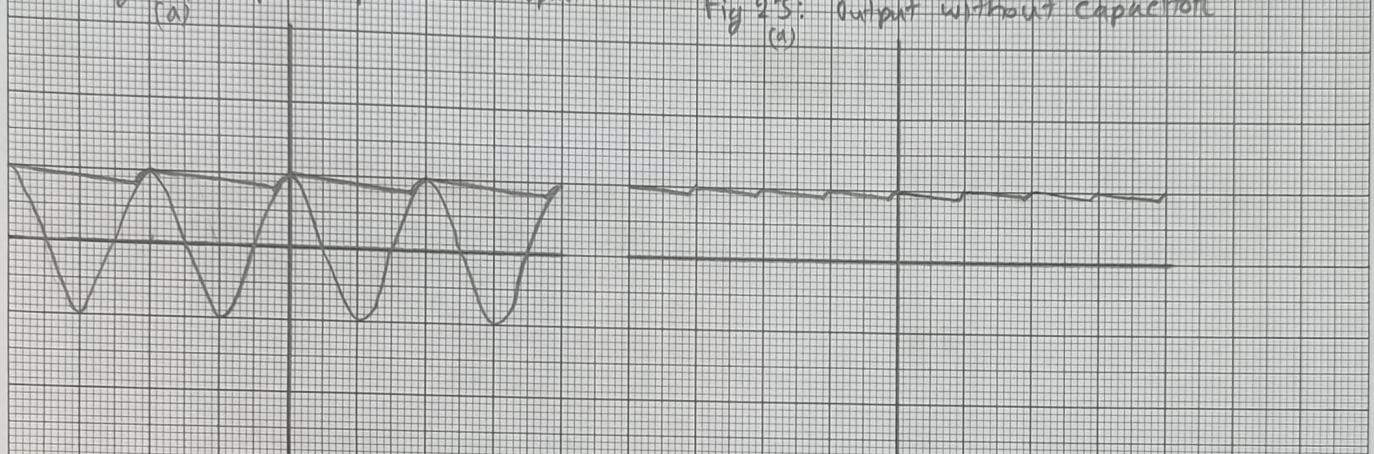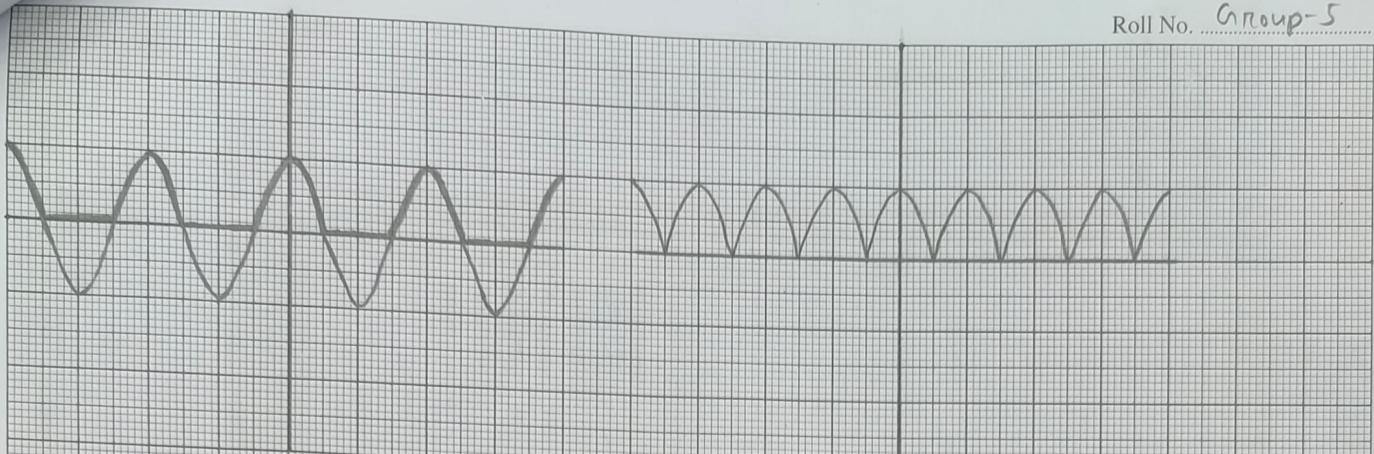- 1) Simulation
- 2) Graph
- 3) Oscilloscope Picture
- 4) Data sheet.



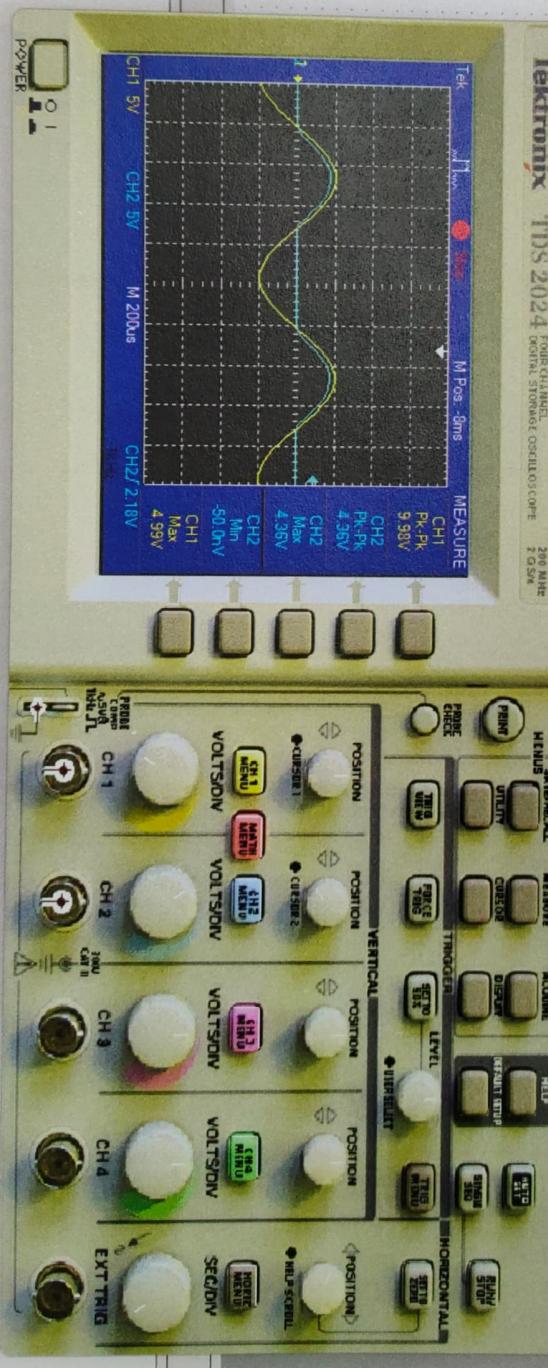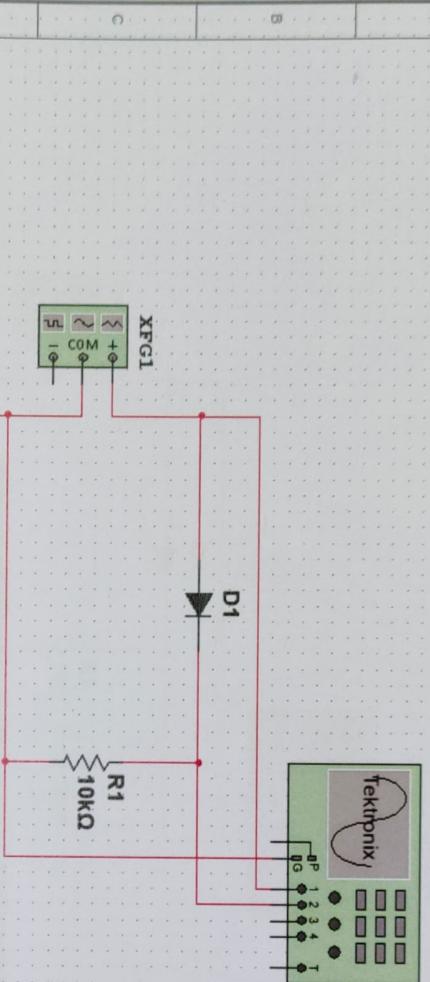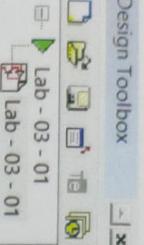

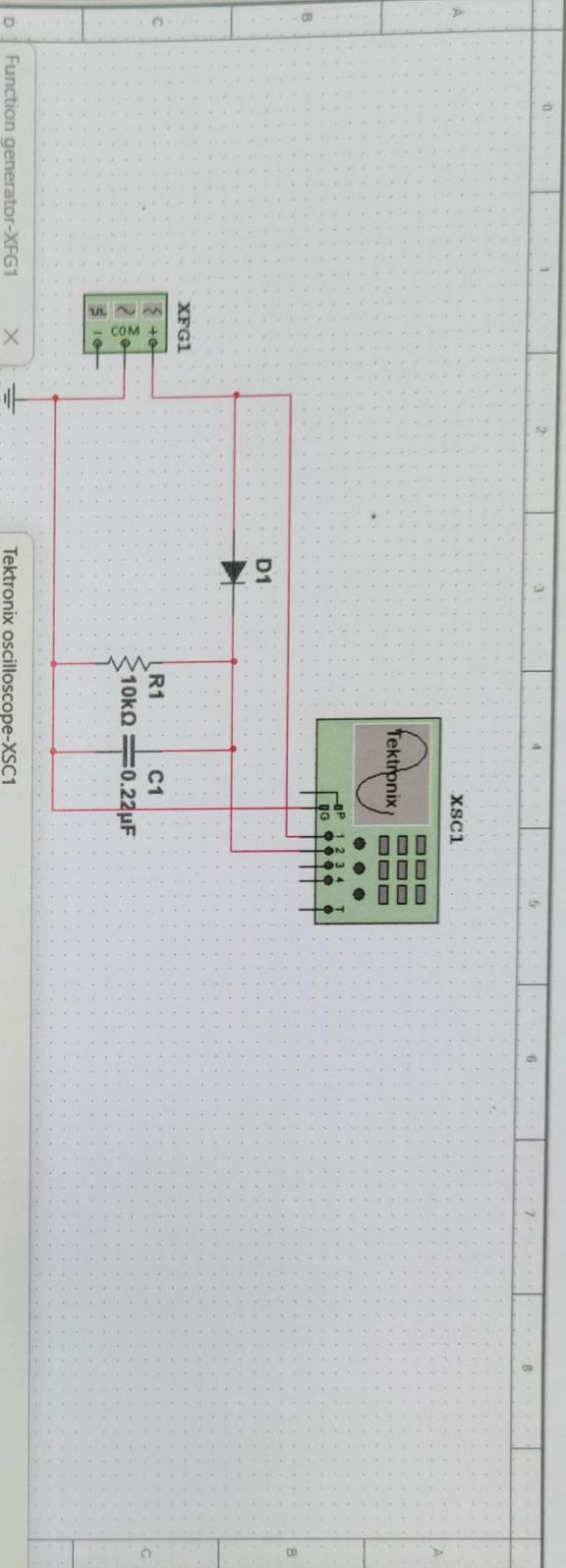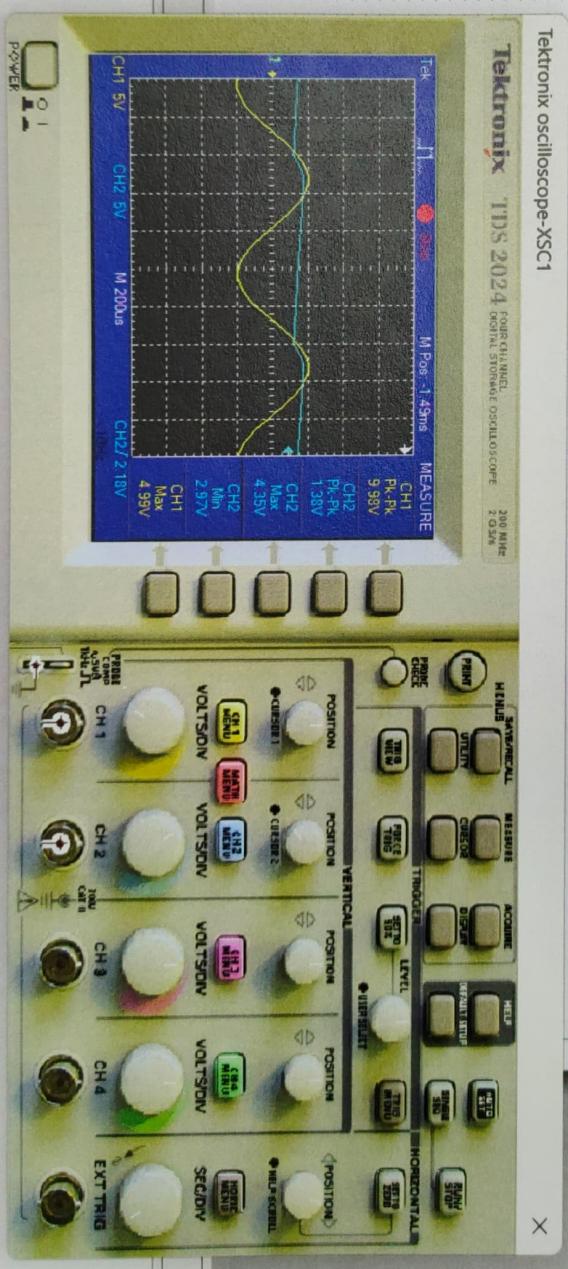

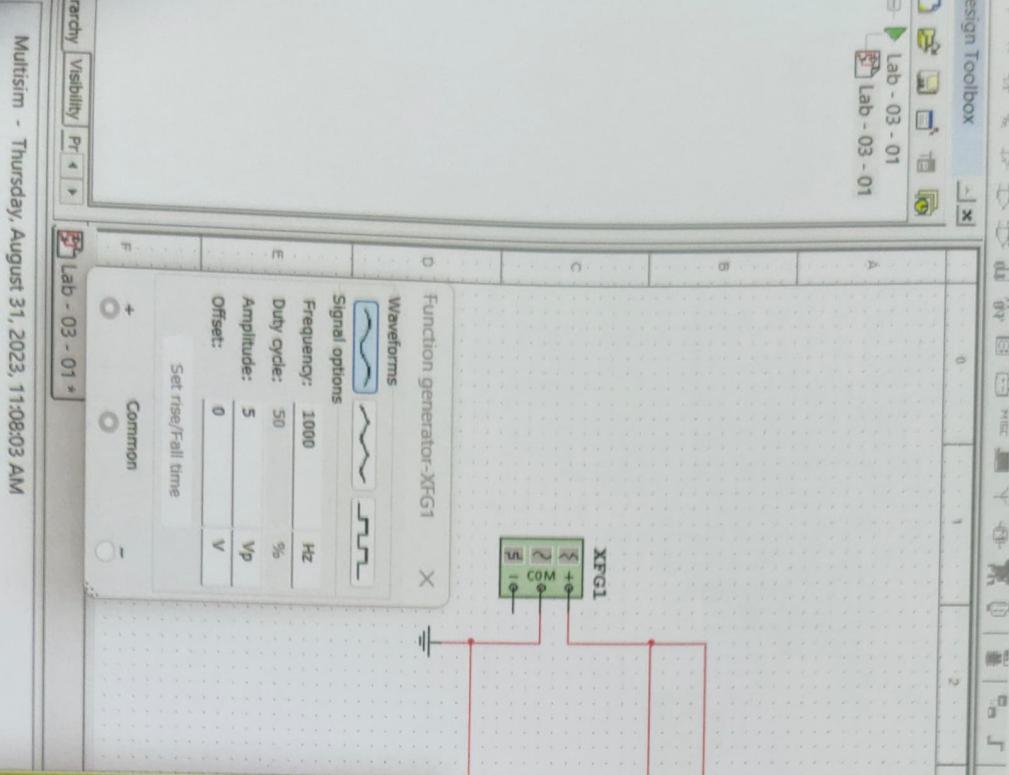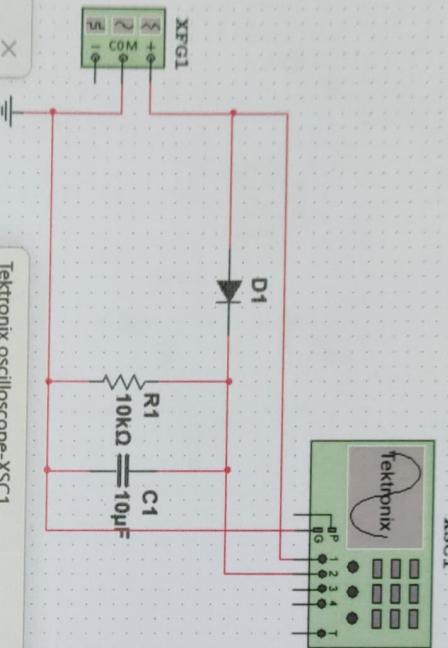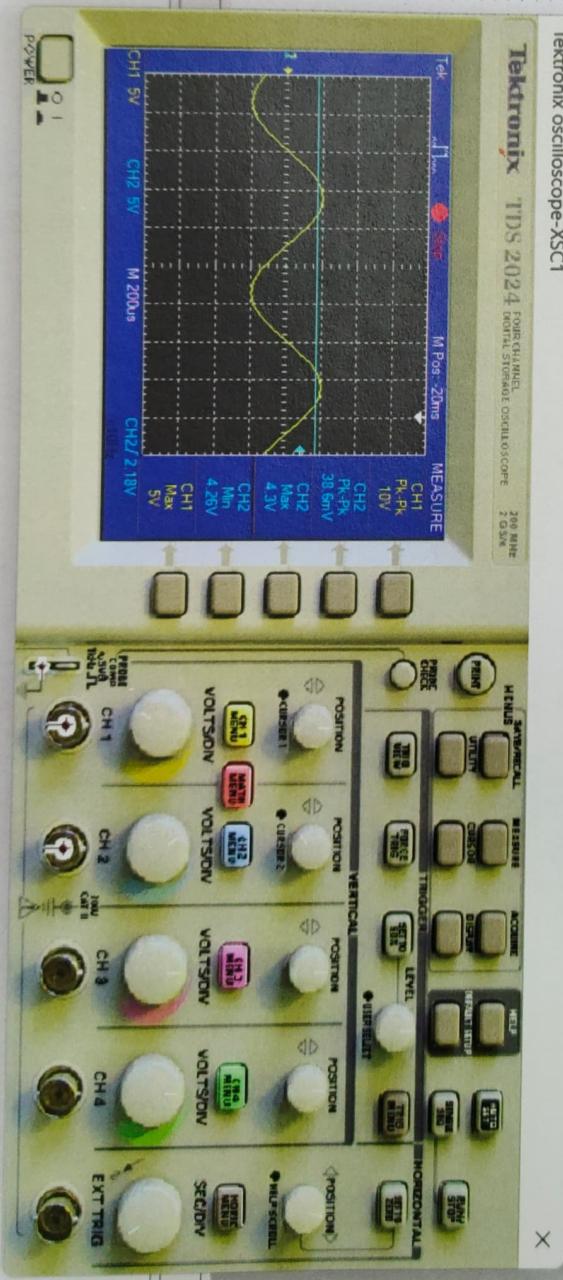


Design Toolbox


- Lab - 03 - 01
- Lab - 03 - 02
- Lab - 03 - 02



XSC1

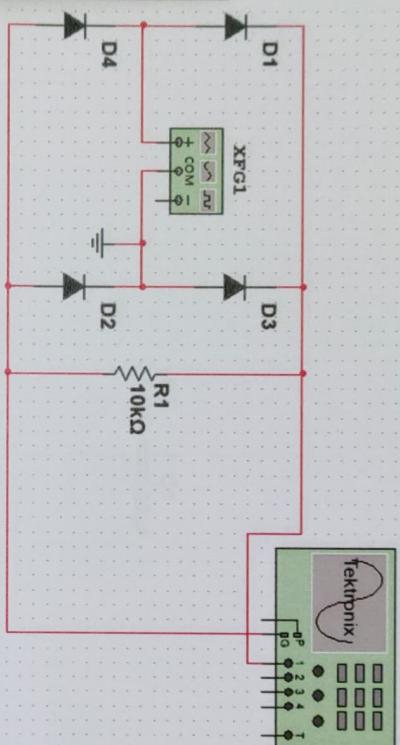

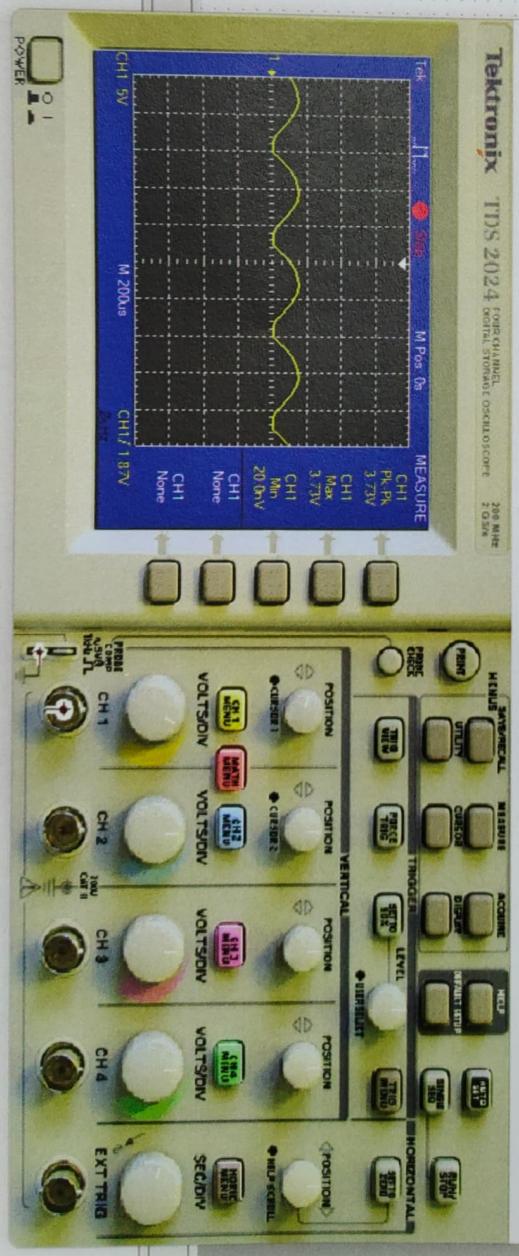Tektronix TDS 2024 FOUR CHAN. 200 MHz, 2 G/Sa




Multisim - Thursday, August 31, 2023, 11:08:03 AM

Design Toolbox

- Lab - 03 - 01
- Lab - 03 - 01
- Lab - 03 - 02
- Lab - 03 - 02

XSC1

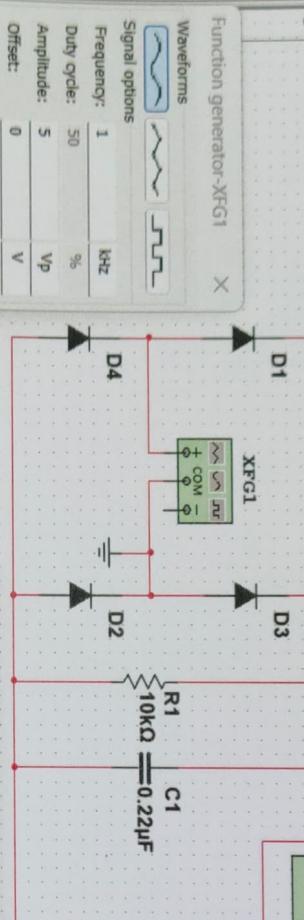

Tektronix oscilloscope-XSC1

Tektronix

TDS 2024 FOUR CHANNEL DIGITAL STORAGE OSCILLOSCOPE

200 MHz

2 GSa/s

56mV

CH1

Pk-Pk

3.71V

CH1



Min

3.15V

CH1

None

CH1

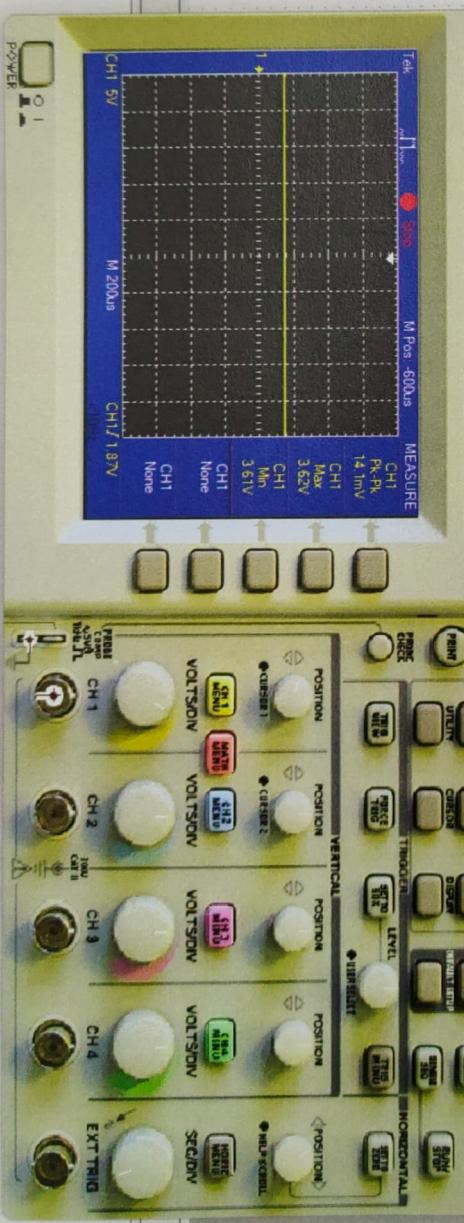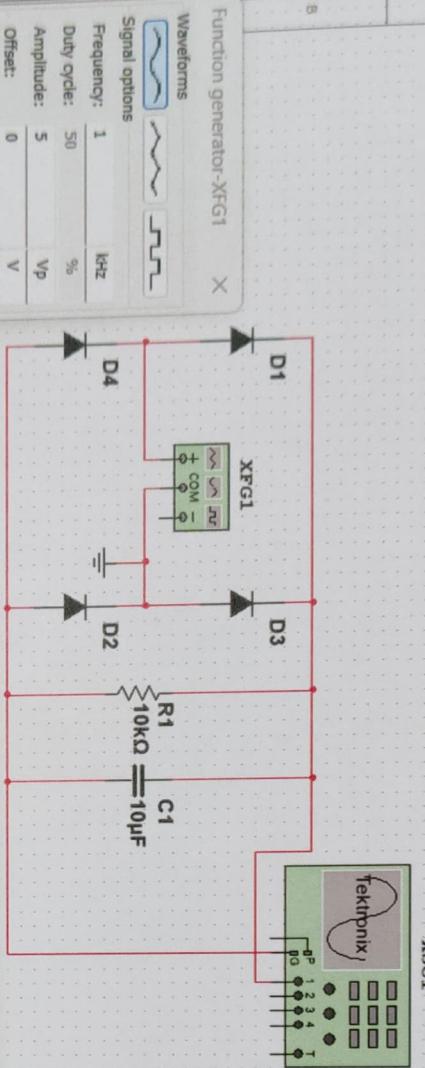


BK PRECISION

2190D

Digital Storage Oscilloscope

100 MHz
1 GSa/s

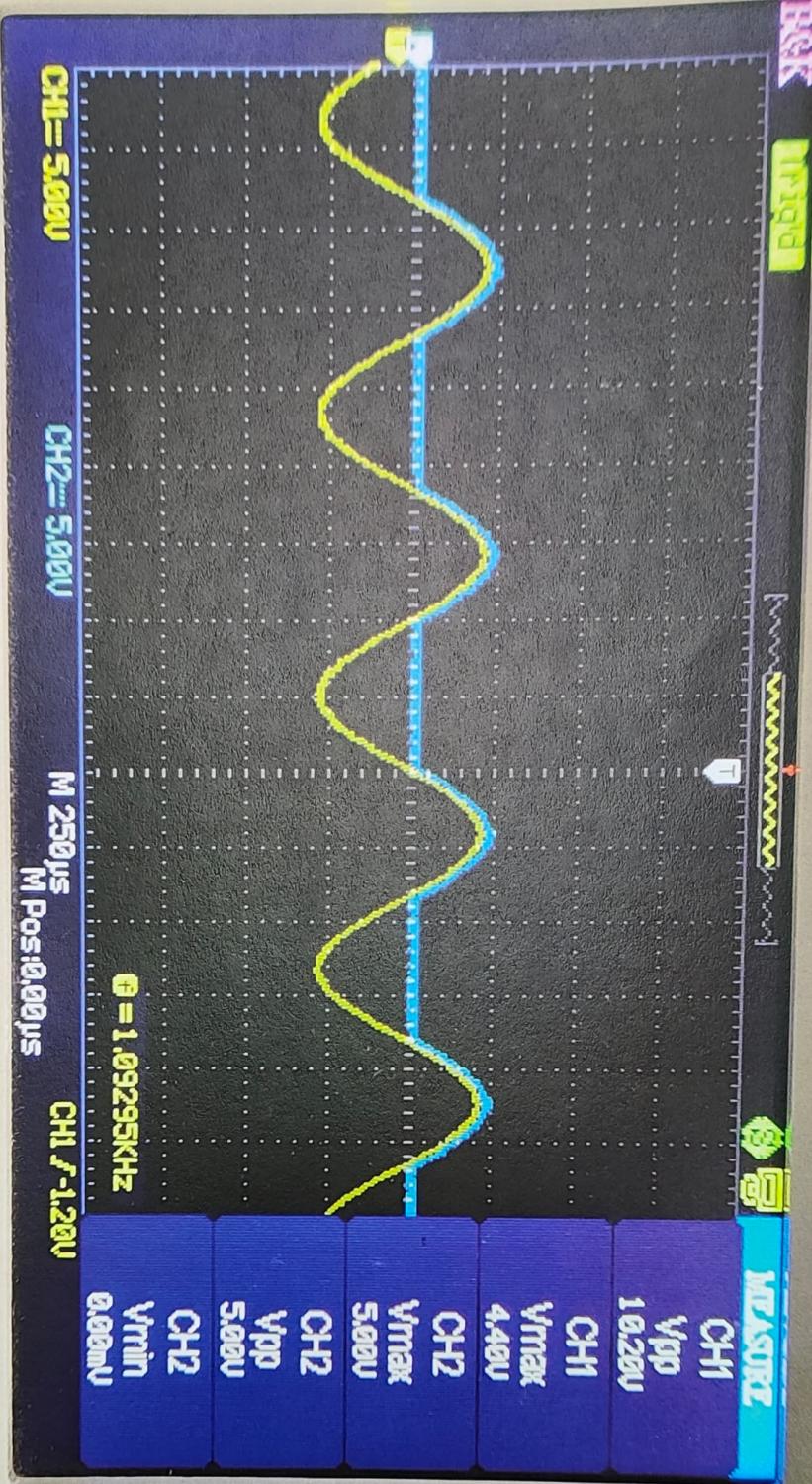

PRINT
MENU
ON/OFF

PRINT


CH1

BK PRECISION

2190D

Digital Storage Oscilloscope

100 MHz
1 GSa/s

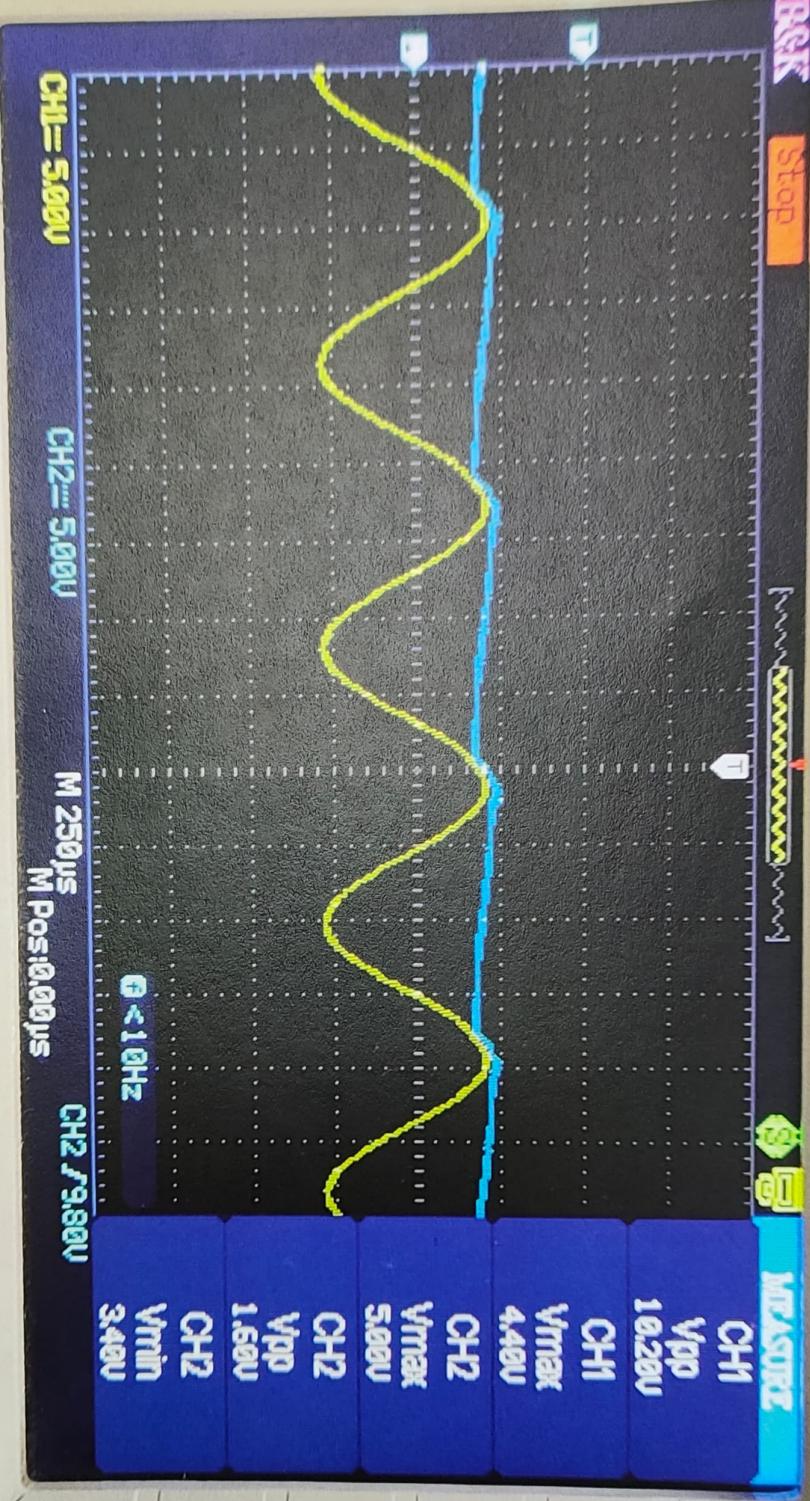

PRINT


ON/OFF

BK PRECISION

2190D

Digital Storage Oscilloscope

100 MHz
1 GSa/s

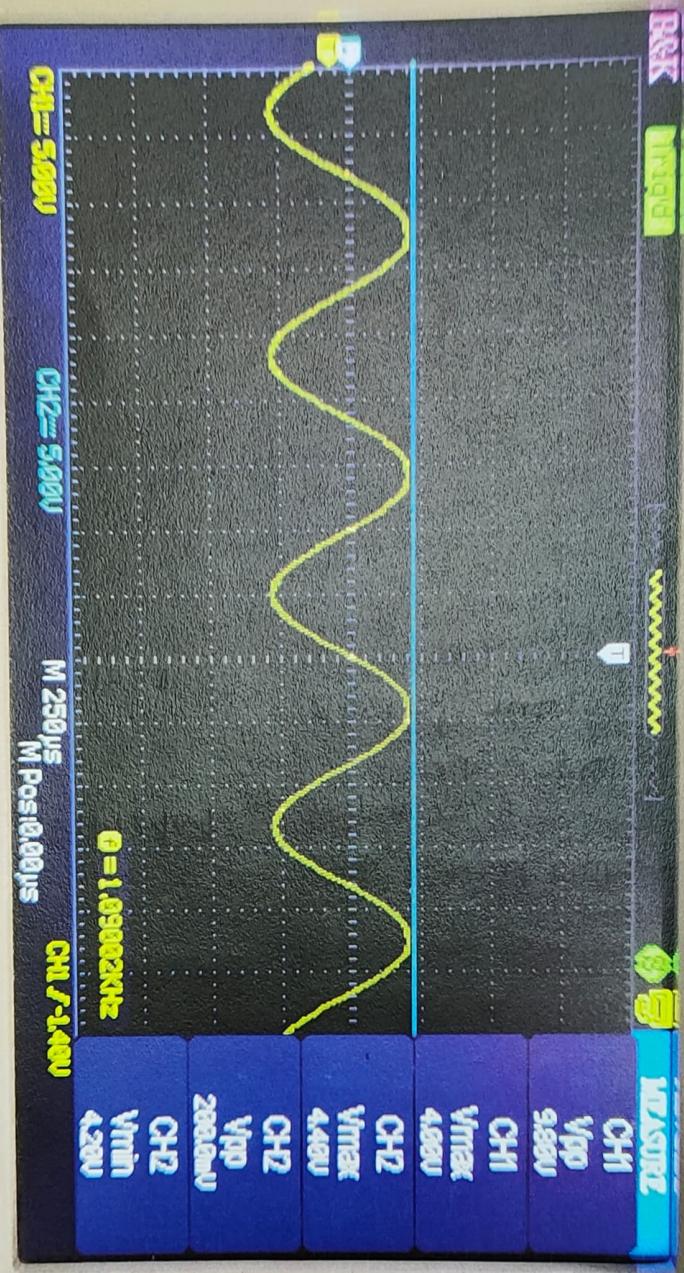


PRINT

ON/OFF



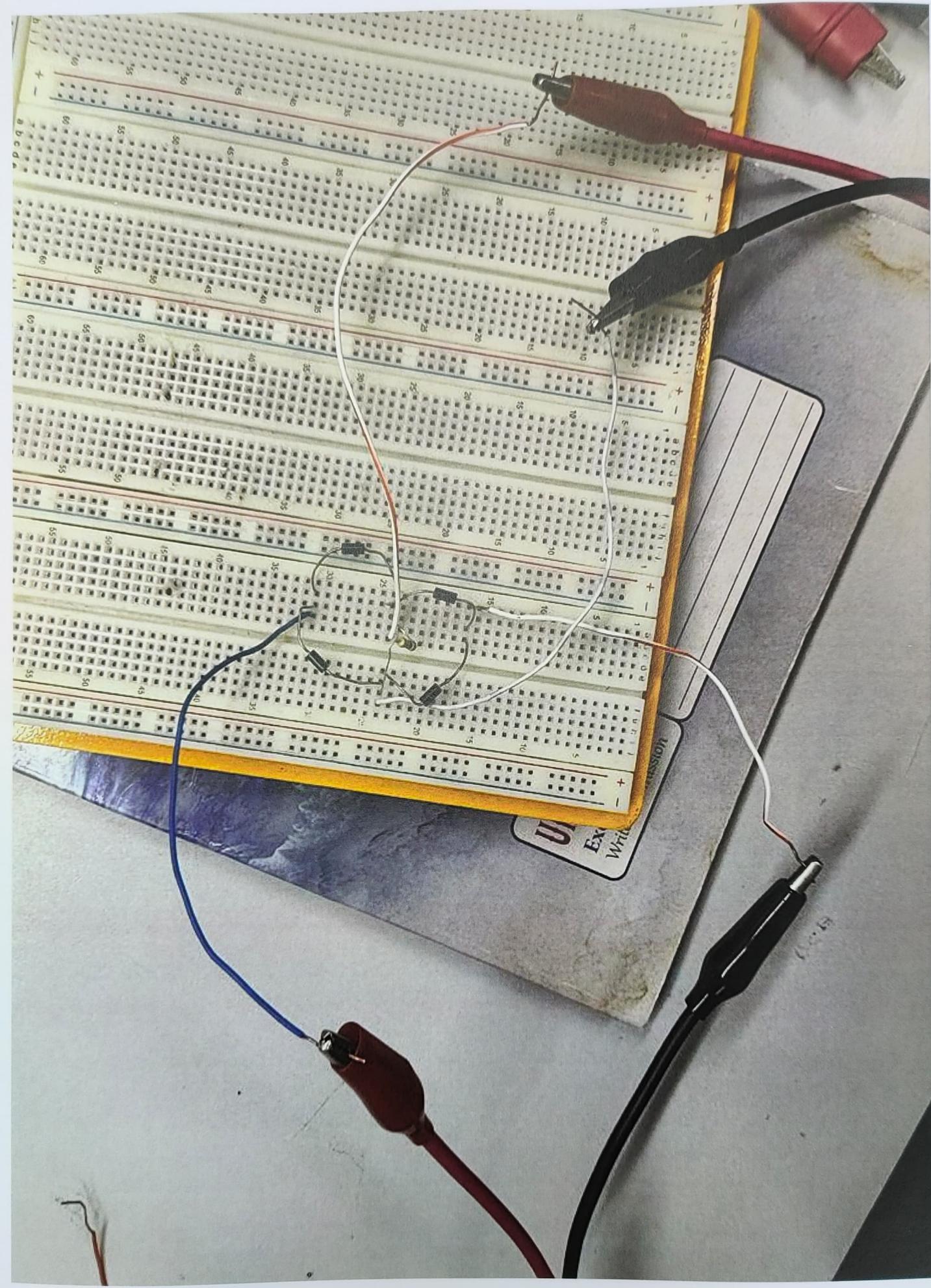realme
Shot by Legend_TJOY
realme GT NEO 2
2023 08 26 17:37



BK PRECISION

2190D



Digital Storage Oscilloscope

100 MHz
1 GS/s



PRINT

ON/Off

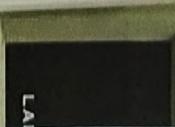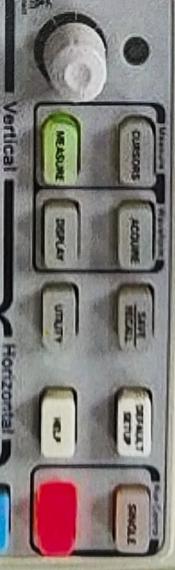

L

A

MCP

POWER
ON OFF

FINE

CU

NORTH SOUTH UNIVERSITY

DEPARTMENT OF ELECTRICAL & COMPUTER ENGINEERING

Equipment and Components:

Serial no.	Component Details	Specification	Quantity
1.	p-n junction diode	1N4007	4 piece
2.	Resistor	10KΩ	1 piece
3.	Capacitor	0.22μF, 10μF	1 piece each
4.	Signal generator		1 unit
5.	Trainer Board		1 unit
6.	Oscilloscope		1 unit
7.	Digital Multimeter		1 unit
8.	Chords and wire		as required

Experimental Setup:

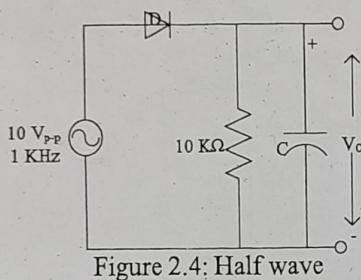


Figure 2.4: Half wave

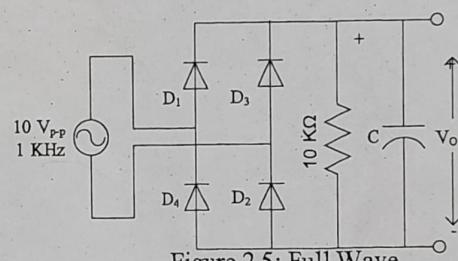


Figure 2.5: Full Wave

Procedure:

- First, connect the circuit in breadboard as shown in figure 2.4 without any capacitor.
- Apply 1 KHz 10V (p-p) sinusoidal input signal from signal generator.
- Connect channel 1 of oscilloscope to the input side, and channel 2 of oscilloscope to output side. Observe the wave shapes and p-p values inputs and outputs and draw them in the graph paper with proper p-p values.
- Connect the 0.22μF capacitor and repeat step 3. [decrease the Volts/DIV for proper wave-shape]
- Now keeping capacitor fixed at 0.22 μF, Observe the change in output wave shape by 1st varying the frequency lower than 1 KHz and then higher than 1 khz.
- Connect the 10μF capacitor and repeat step 3 and step 5. [decrease the Volts/DIV for proper wave-shape]
- Repeat steps 1-6 for Figure 2.5.

Data Collection:

Signature of instructor:


Experiment: 2,

Performed by Group# 5


Theoretical value: R = 10 kΩ

Measured value: R = 9.89 kΩ

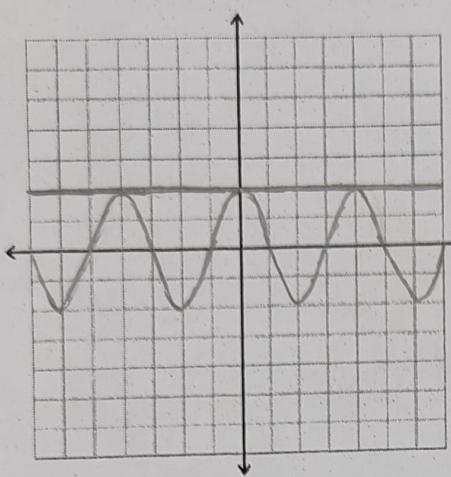NORTH SOUTH UNIVERSITY
DEPARTMENT OF ELECTRICAL & COMPUTER ENGINEERING



c) Input-output with $10\mu F$ (fig 2.4)

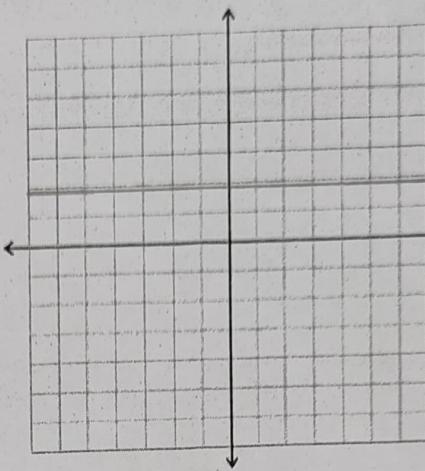

f) Input-output with $10\mu F$ (fig 2.5)

Report:

1. For Fig 2.4 and Fig 2.5, draw the input-output wave-shape without capacitor, with $0.22\mu F$ capacitor and $10\mu F$ capacitor.
2. Compare the change in the wave-shape and peak to peak values for no capacitor at the output to $0.22\mu F$ to $10\mu F$.
3. Explain the effect on the output signal for changing the frequency of the input signal
4. Between half wave and full wave which circuit produces smoother output? Briefly explain in context with your data collection.