

Spring 2023
EEE/ETE 141L
Electrical Circuits-I Lab (Sec-19)
Faculty: Mr. Saif Ahmed (SfA)
Instructor: Md. Rabiul Karim Khan

Lab Report 06: Verification of Thevenin's, and Norton's Theorem.

<p>Date of Performance: 09 April 2023</p> <p>Date of Submission: 30 April 2023</p>	<p><u>Group no.: 05</u></p> <ul style="list-style-type: none">1. Joy Kumar Ghosh – 22114246422. Sarith Chowdhury - 22125516423. Anindita Das Mishi - 22113646424. Md. Mehedi Hossain – 19222256425. Anisa Akter Meem - 2212538042
--	--

Experiment Name: Verification of Thevenin's, and Norton's Theorem.

Objectives:

- Experimentally perform Thevenin's theorem, Norton theorem.
- Perform theoretical calculations.
- Verify the experimental values with theoretical values.

Apparatus:

- Breadboard
- Resistors ($1 \times 10\text{ k}\Omega$, $1 \times 5.0\text{ k}\Omega$, $2 \times 10\text{ k}\Omega$)
- Digital Multimeter (DMM)
- DC Power Supply
- Wires

Circuit Diagram:

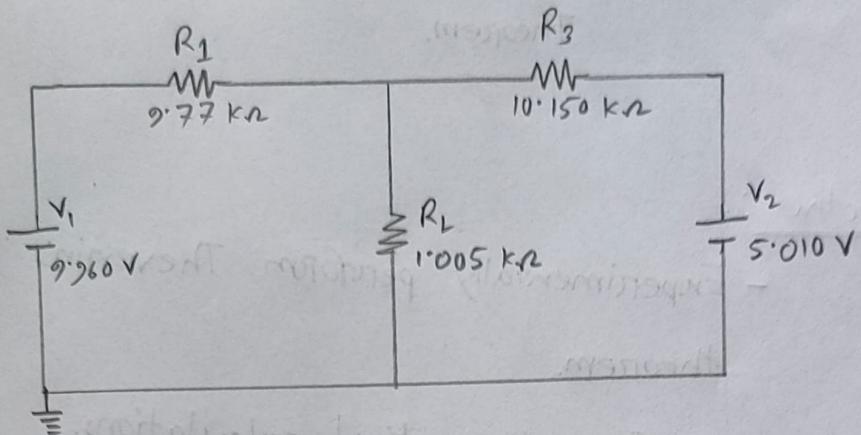


Fig.: Original Circuit

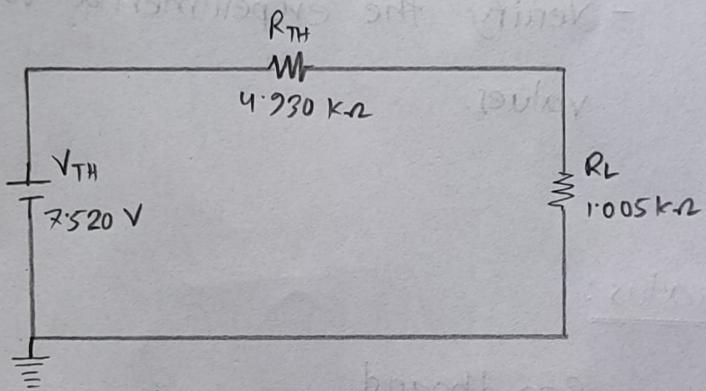


Fig.: Thevenin's Equivalent circuit

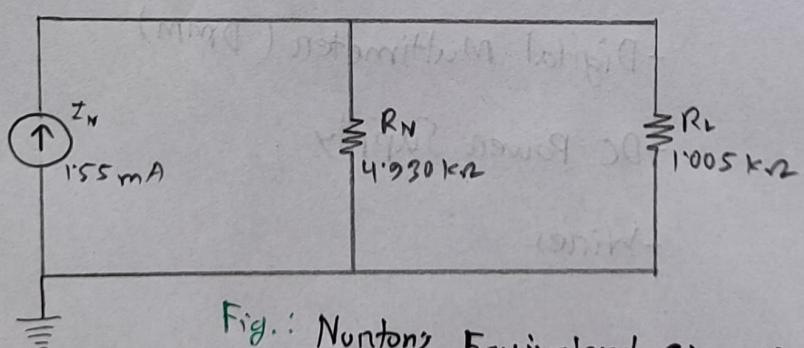


Fig.: Norton's Equivalent circuit

Data Table & Calculation:

Table - 1 :

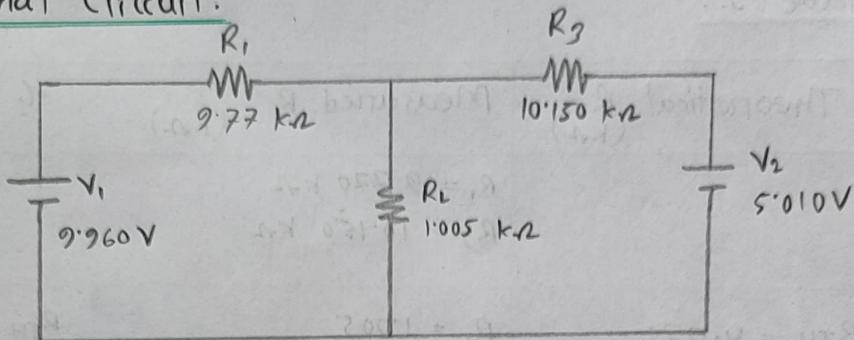
Theoretical R (k Ω)	Measured R (k Ω)	% Error
	$R_1 = 9.770 \text{ k}\Omega$ $R_2 = 10.150 \text{ k}\Omega$	
$R_{TH} = 4.978$	$R_L = 1.005$ $R_{TH} = 4.930$	$R_{TH} = 0.96\%$

Table - 2 : Original Circuit


Value	Measured	Theoretical	% Error
$V_L (\text{v})$	1.263	1.265	0.16%

Table - 3 :

Measurement	Measured	Theoretical	% Error
$V_{TH} (\text{v})$	7.520	7.532	0.16%
$I_N (\text{mA})$	1.520	1.513	0.46%
$R_{TH} = R_N (\text{k}\Omega)$	4.980	4.978	0.04%
$V_L (\text{v})$ $_{TH\text{-circuit}}$	1.274	1.273	0.08%
$I_N (\text{mA})$	1.550	1.513	2.45%
$V_L (\text{v})$ $_{N\text{-circuit}}$	1.293	1.294	0.08%


Calculation :Original Circuit:

Using Super Position theorem,

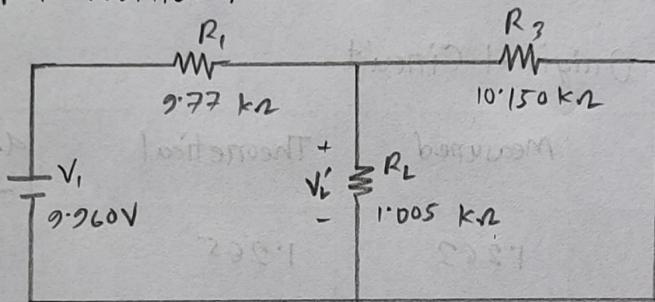

$$V'_L = \frac{\left(\frac{1}{1.005} + \frac{1}{10.150}\right)^{-1}}{9.77 + \left(\frac{1}{1.005} + \frac{1}{10.150}\right)^{-1}} \times 9.960$$

$$= 0.852\text{ V}$$

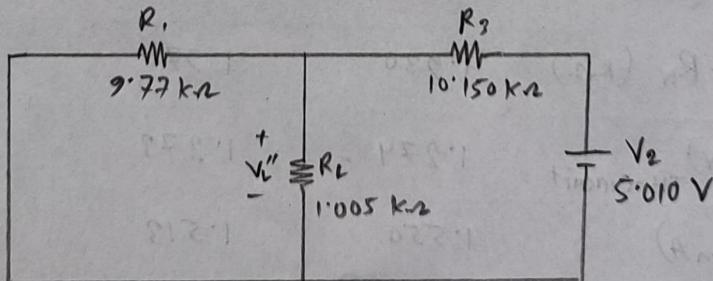


$$V''_L = \frac{\left(\frac{1}{1.005} + \frac{1}{9.77}\right)^{-1}}{10.150 + \left(\frac{1}{1.005} + \frac{1}{9.77}\right)^{-1}} \times 5.010$$

$$= 0.413\text{ V}$$


$$\begin{aligned}\therefore V_L &= V'_L + V''_L \\ &= (0.852 + 0.413) V \\ &= 1.265 V\end{aligned}$$

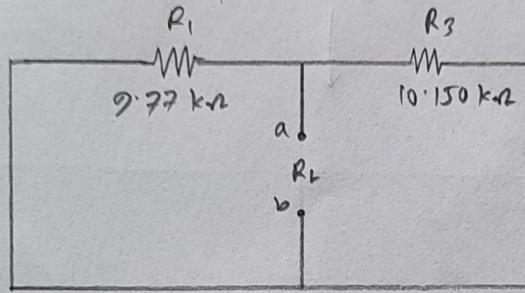Thevenin's & Norton's Equivalent $R_{TH} = R_N$:





$$\begin{aligned}\therefore R_{TH} = R_N &= \left(\frac{1}{9.77} + \frac{1}{10.150} \right)^{-1} \\ &= 4.978 \text{ k}\Omega\end{aligned}$$

Thevenin's equivalent voltage, V_{TH} :


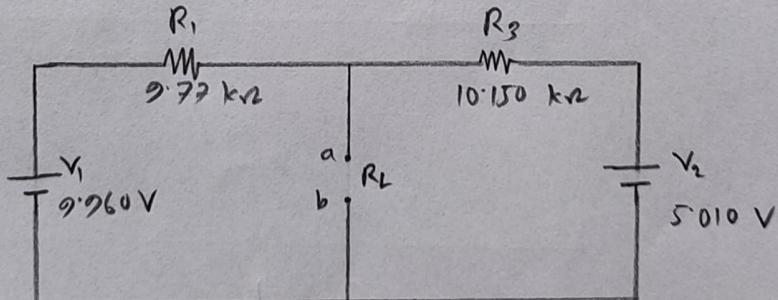


Using Super Position theorem:

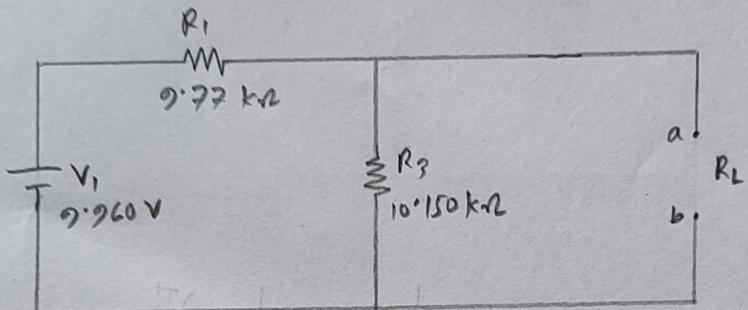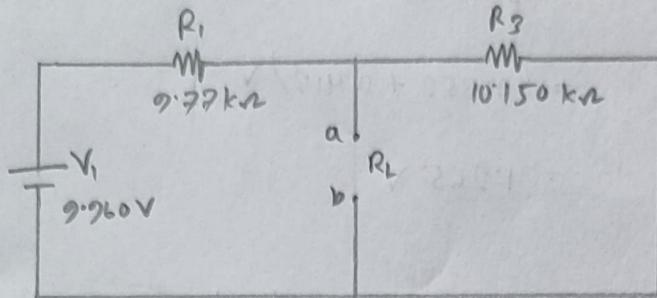

$$\therefore V_{TH}' = \frac{10.150}{9.77 + 10.150} \times 9.960$$


$$= 5.075 \text{ V}$$

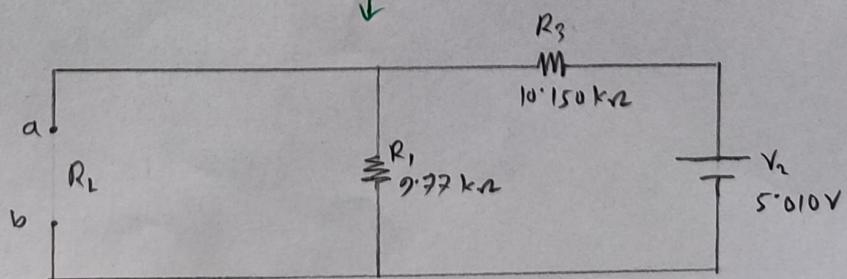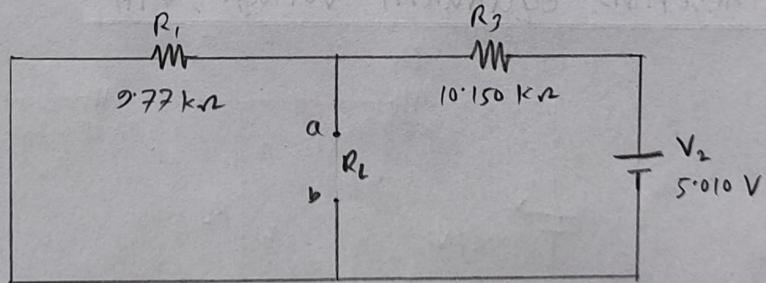

$$\therefore V_{TH}'' = \frac{0.77}{0.77 + 10.150} \times 5.010 \\ = 2.457 \text{ V}$$


$$\therefore V_{TH} = V_{TH}' + V_{TH}'' \\ = 5.075 + 2.457 \\ = 7.532 \text{ V}$$

Thevenin equivalent circuit:

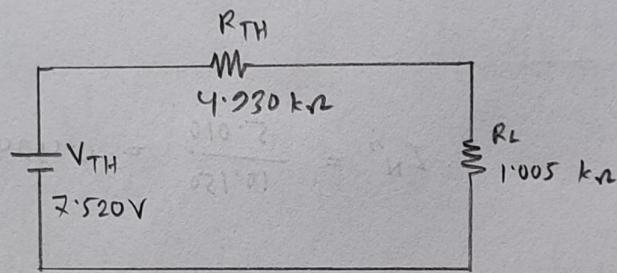


$$\therefore V_L (\text{TH-Circuit}) = \frac{1.005}{4.930 + 1.005} \times 7.520 \\ = 1.273 \text{ V}$$


Norton's equivalent current, I_N :

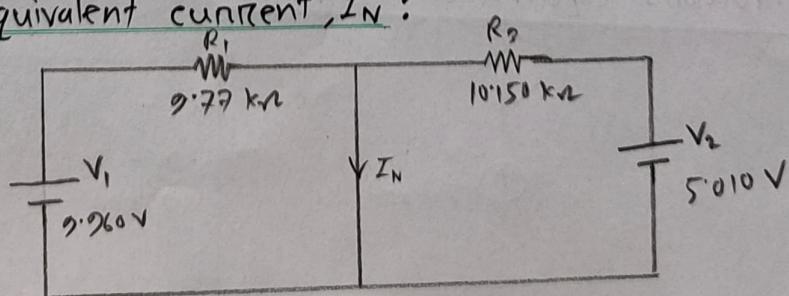

Using Super Position theorem,

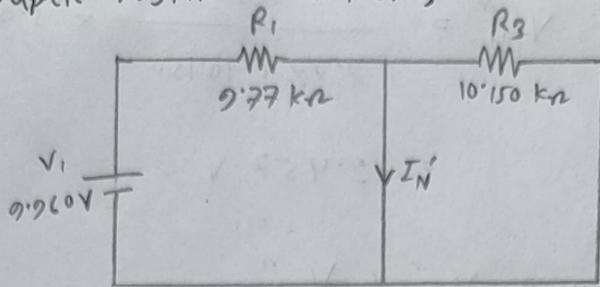

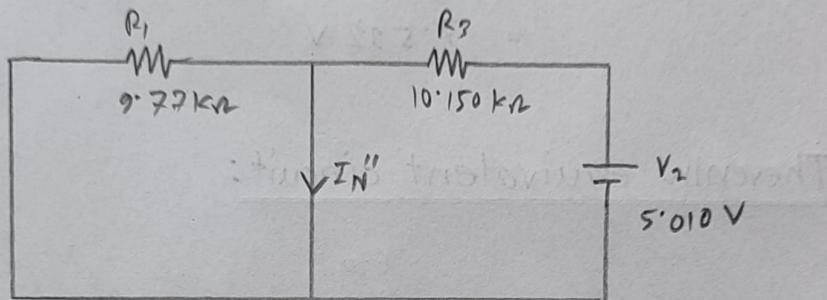
$$\therefore I_{N'} = \frac{9.960}{9.77} = 1.019 \text{ mA}$$



$$\therefore I_{N''} = \frac{5.010}{10.150} = 0.494 \text{ mA}$$

$$\begin{aligned} \therefore I_N &= I_{N'} + I_{N''} \\ &= 1.019 + 0.494 \\ &= 1.513 \text{ mA} \end{aligned}$$

Norton's equivalent circuit:

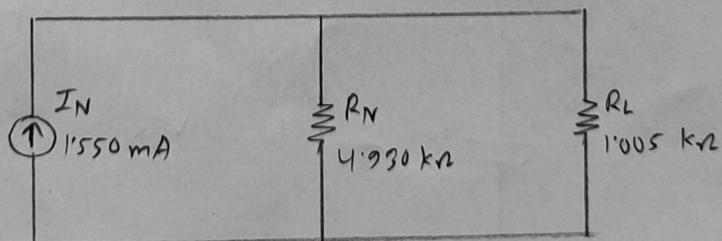

$$\therefore I_{R_L} = \frac{\left(\frac{1}{4.930} + \frac{1}{1.005}\right)^{-1}}{1.005} \times 1.550 \\ = 1.288 \text{ mA}$$

$$\therefore V_L (\text{N-circuit}) = (1.288 \times 1.005) \text{ V} \\ = 1.294 \text{ V}$$

Error Calculation:

We know,

$$\text{Error} = \left| \frac{\text{Theoretical Value} - \text{Measured Value}}{\text{Theoretical Value}} \right| \times 100\%$$

$$V_{TH} = \left| \frac{7.532 - 7.520}{7.532} \right| \times 100\% \\ = 0.161.$$

$$I_N = \left| \frac{1.513 - 1.520}{1.513} \right| \times 100\% \\ = 0.461.$$

$$R_{TH} = \left| \frac{4.978 - 4.980}{4.978} \right| \times 100\% \\ = 0.041.$$

$$V_L (\text{TH}) = \left| \frac{1.273 - 1.274}{1.273} \right| \times 100\% \\ = 0.08\%$$

$$I_N = \left| \frac{1.513 - 1.550}{1.513} \right| \times 100\% \\ = 2.45\%$$

$$V_L = \left| \frac{1.294 - 1.293}{1.294} \right| \times 100\% \\ = 0.08\%$$

Graph: N/A.

Result Analysis:

From the data table of this experiment, we found that the theoretical and measured values are the same. We also get that the V_L or the original circuits and Thevenin's equivalent circuits, also Norton's equivalent circuits are the same.

Therefore, our circuit completely follow Thevenin's and Norton's theorem.

Questions and Answers:



1. Already showed in Data Table section.
2. Already showed in Data Table section.

Discussion:


After completing this experiment, we learnt to verify Thvenin's and Norton's Theorem. Now we can convert a complex circuit into a simple circuit using these two theorems. We need to remove the load and measure the R_T and the voltage for Thvenin's Theorem and the current for Norton's Theorem at points a and b. In this experiment, we don't face any difficulties. We completed this experiment on time.


Attachment:

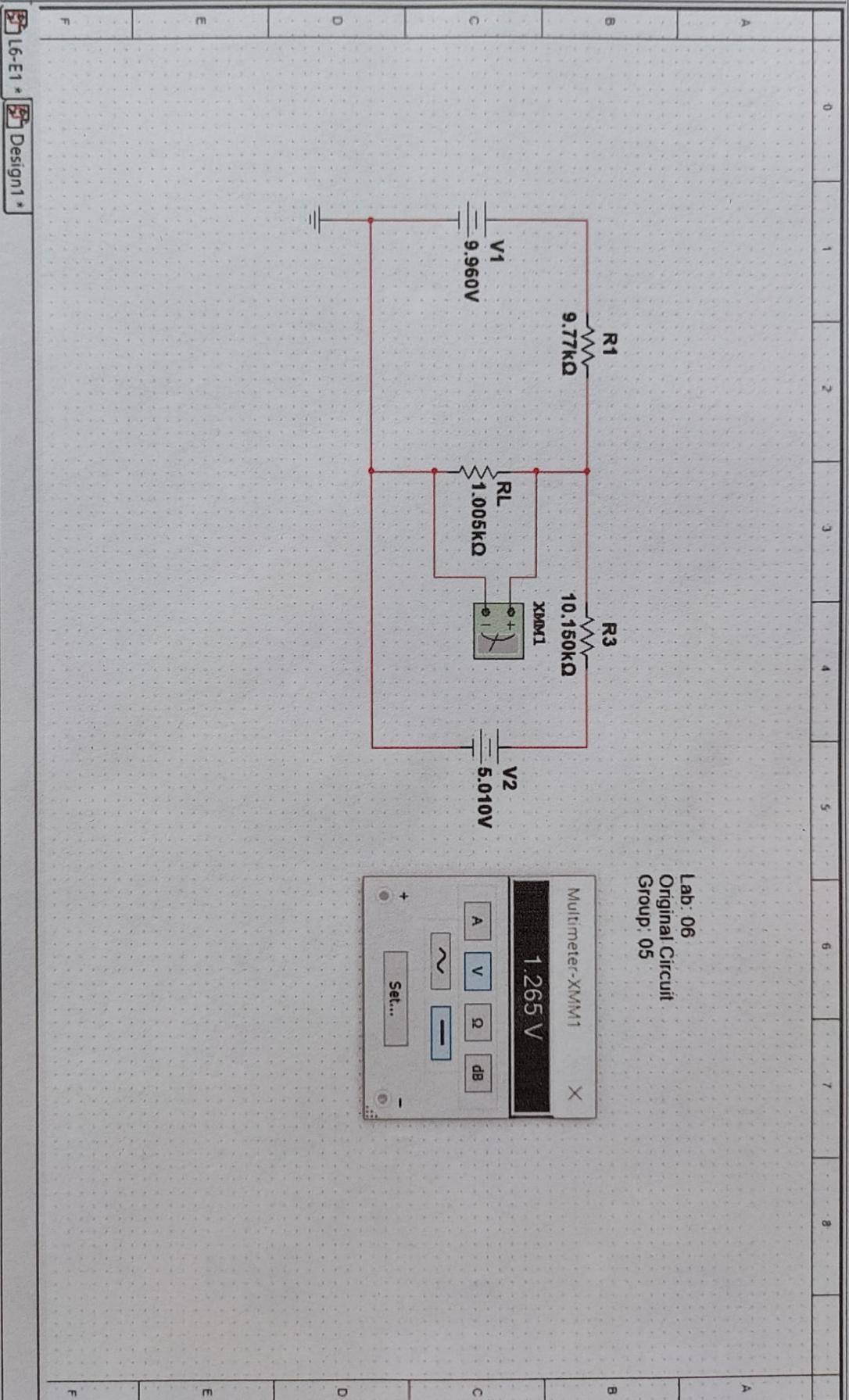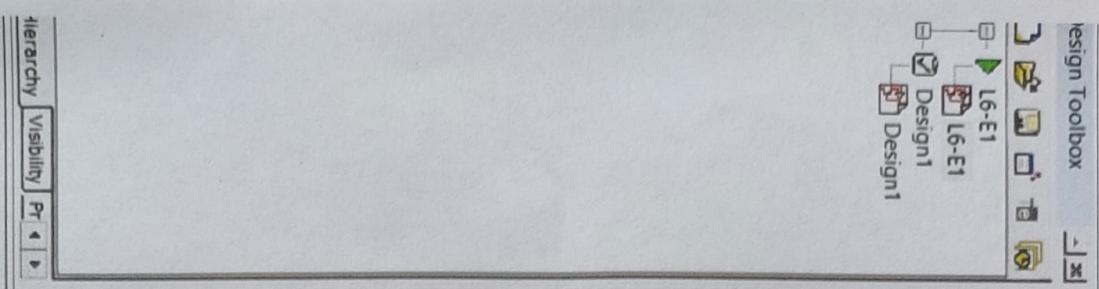1. Signed Data Table.
2. Simulation using Multisim.





L6-E1 * Design1 *

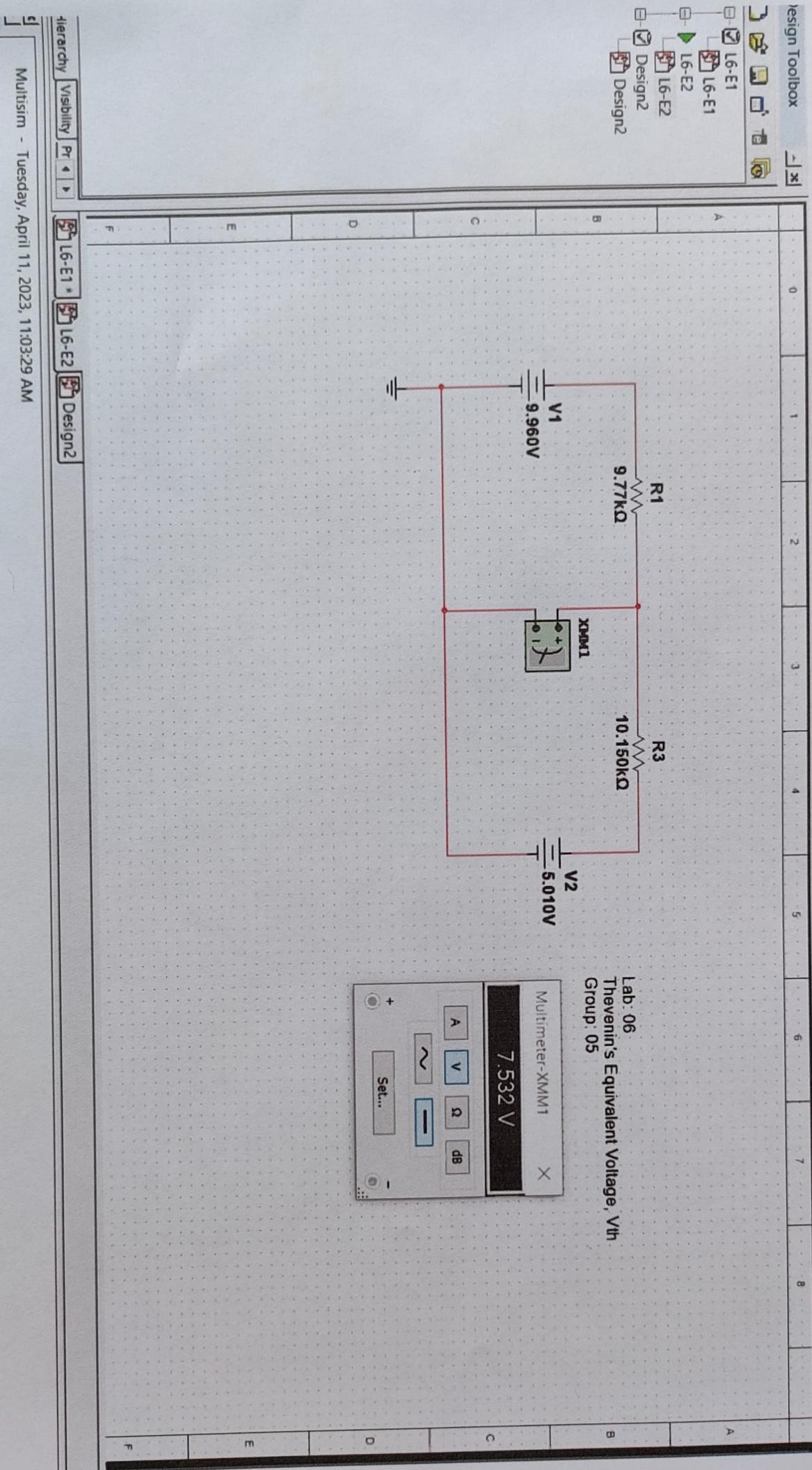


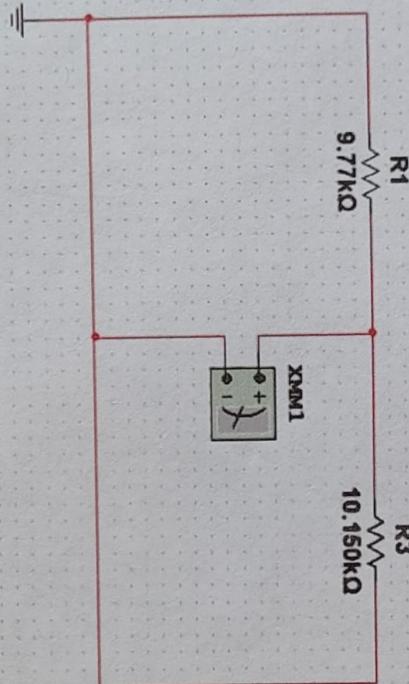


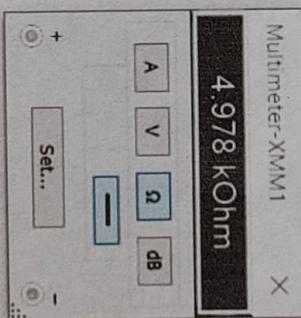Lab. 10
Thevenin's Equivalent Resistance, R_{th}
Group: 05




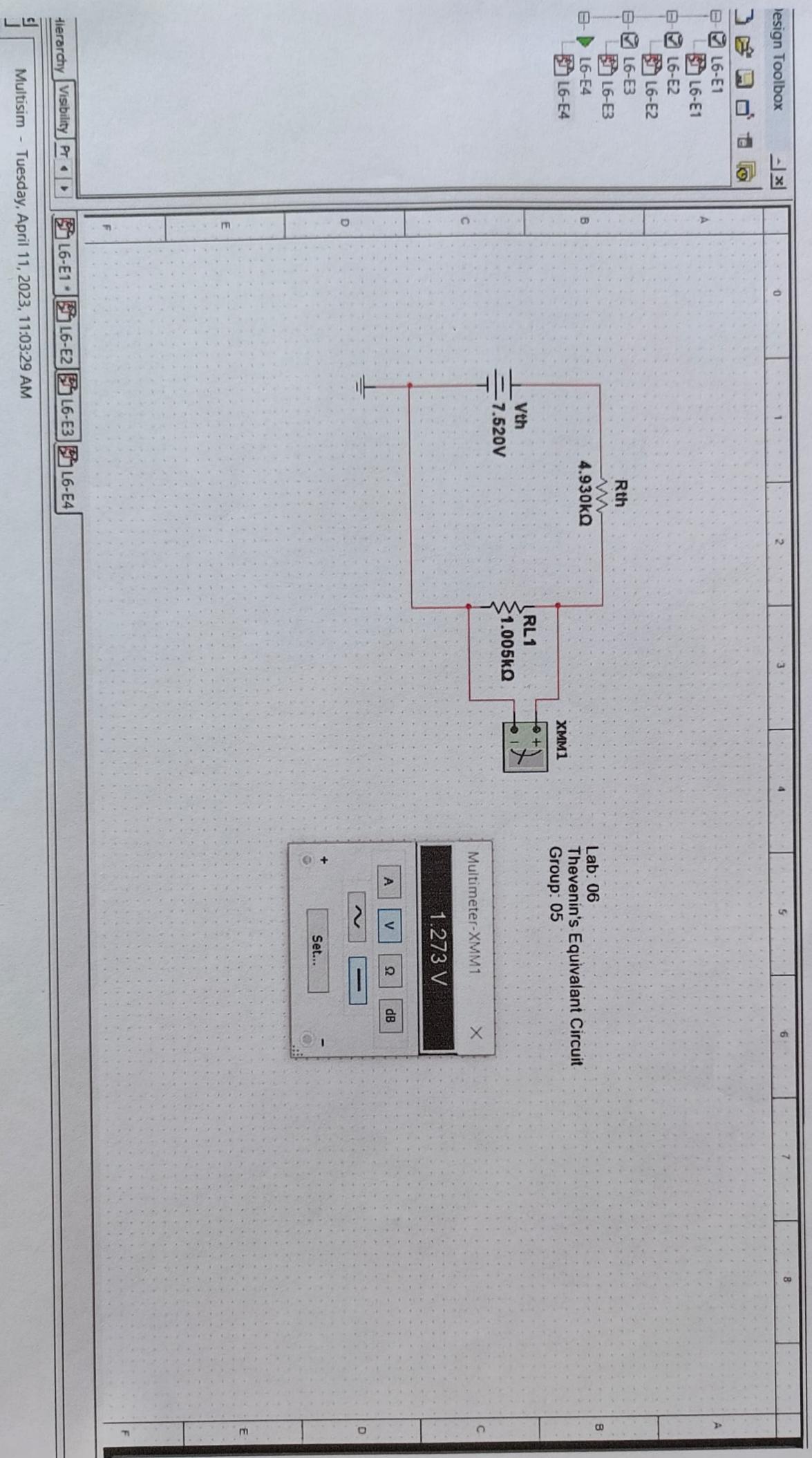

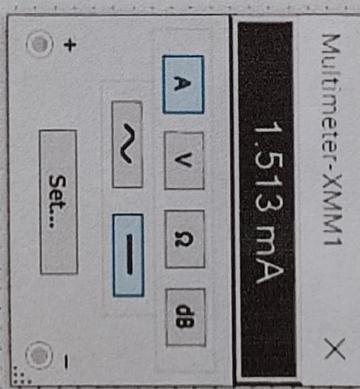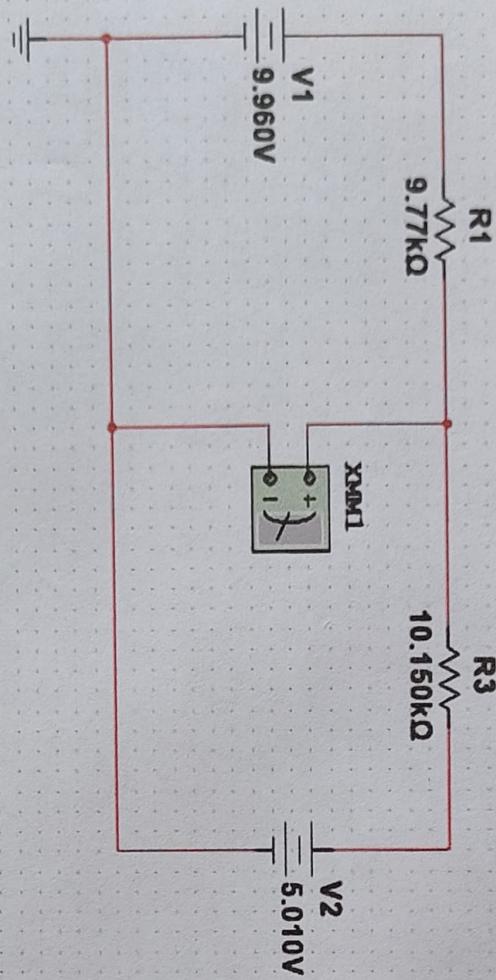
Lab: 06
Norton's Equivalent Current, I_N
Group: 05



Design Toolbox

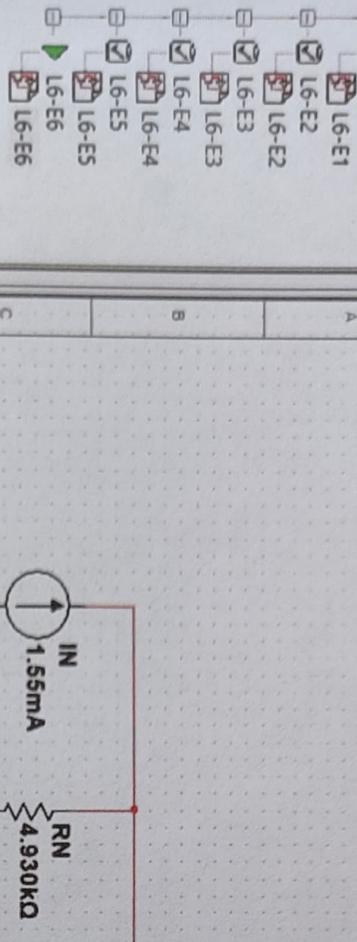


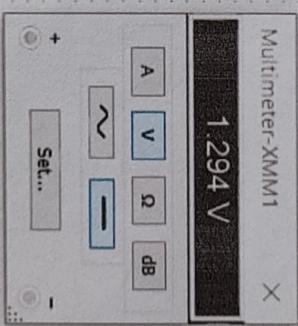Lab: 06
Norton's Equivalent Circuit
Group: 05



L6-E1 L6-E2 L6-E3 L6-E4 L6-E5 L6-E6

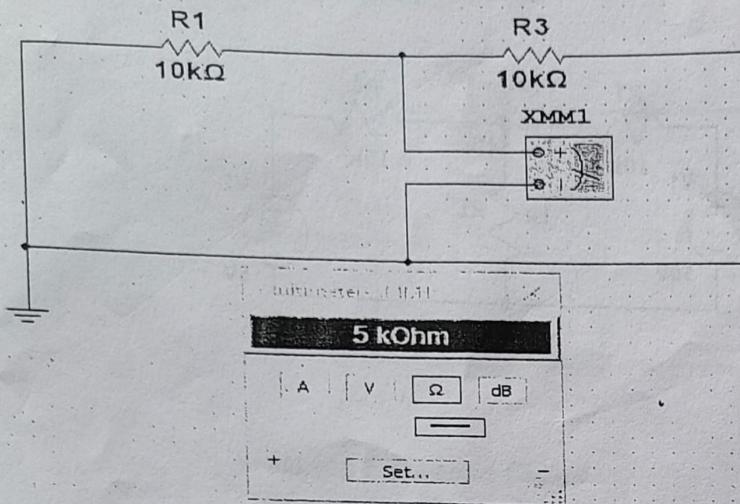Thevenin's equivalent resistance, R_{TH} :



Data Collections:

Group No. _____
Instructor's Signature _____

Table 1:

Theoretical R	Measured R	% Error
	$R_1 = 9.77\text{k}\Omega, R_3 = 10.150\text{k}\Omega$	
	$R_L = 1.005\text{k}\Omega, R_{TH} = 4.930\text{k}\Omega$	

Table 2:

Value	Measured	% Error
$V_L(V)$	1.263V	
$I_L(\text{mA})$		


Table 3:

Measurement	Measured	Calculated	% Error
$V_{TH}(V)$	7.520		
$I_N(\text{mA})$	1.520		
$R_{TH}(\text{k}\Omega) = R_N(\text{k}\Omega)$	4.980		
$V_L(V)$	1.274		
$I_L(\text{mA})$			

$$I_m = 1.55 \text{ mA}$$

$$\sqrt{R_L} = 1.293 \text{ V}$$

Norton's equivalent circuit:

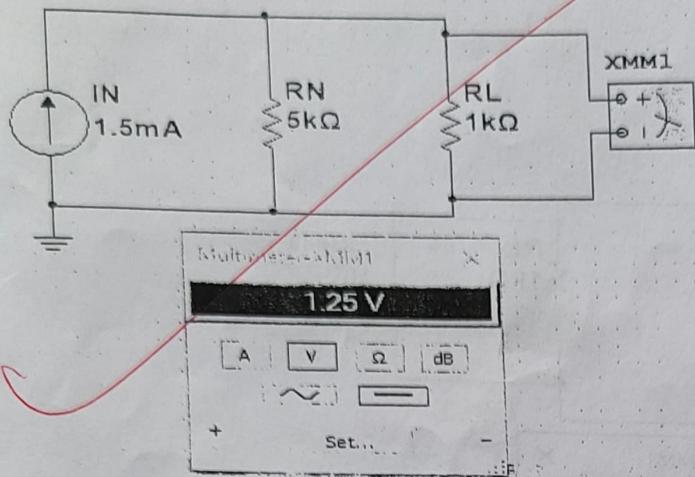

Rahayu
9/4/23