

Spring 2023  
EEE/ETE 141L  
Electrical Circuits-I Lab (Sec-19)  
Faculty: Mr. Saif Ahmed (SfA)  
Instructor: Md. Rabiul Karim Khan

**Lab Report 03:** Loading Effect of Voltage Divider Circuit.

Date of Performance:  
12 March, 2023

Date of Submission:  
02 April, 2023

**Group no.:** 05

1. Anindita Das Mishi – 2211364642
2. Sarith Chowdhury – 2212551642
3. Joy Kumar Ghosh – 2211424642
4. Md. Mehedi Hossain - 1922225642
5. Anisa Akter Meem - 2212538042

## Experiment Name: Loading Effect of Voltage Divider Circuit


### Objectives:

- To analyze how the voltage divider circuit behaves when there is no load resistance connected.
- Evaluate the performance of voltage divider circuit due to loading.

### Apparatus:

- Breadboard
- Resistors ( $2 \times 560\Omega$ )
- Variable Resistor ( $0-10\text{ k}\Omega$ )
- Digital Multimeter (DMM)
- DC Power Supply
- Wires

### Circuit Diagram:

 



## Data Table:

Table 01:

RL	Vout (V) (Measured)	Vout (V) (calculated)	% Error
No Resistor	4.91	4.94	0.61%.
1.01K	3.87	3.88	0.26%.
3.99K	4.60	4.62	0.43%.
6.99K	4.73	4.75	0.42%.
10.02K	4.80	4.81	0.21%.

## Theoretical Vout Calculation:

$$V_{in} = 9.92 \text{ V}$$

$$R_1 = 0.553 \text{ k}\Omega$$

$$R_2 = 0.548 \text{ k}\Omega$$

Without load,

$$V_{out} = V_{in} \frac{R_1}{R_1 + R_2}$$

$$= 9.92 \times \frac{0.548}{(0.553 + 0.548)}$$

$$= 4.94 \text{ V}$$

$$\text{Error} = \left| \frac{4.94 - 4.91}{4.94} \right| \times 100\%$$

$$= 0.61\%$$

With load,

When,  $R_3 = 1.01 \text{ k}\Omega$

$$V_{out} = V_{in} \frac{(R_2 || R_3)}{R_1 + (R_2 || R_3)}$$

$$= 9.92 \times \frac{(1/0.548 + 1/1.01)^{-1}}{0.553 + (1/0.548 + 1/1.01)^{-1}}$$

$$= 3.88 \text{ V}$$

$$\text{Error} = \left| \frac{3.88 - 3.87}{3.88} \right| \times 100\%$$

$$= 0.26\%$$

When,  $R_3 = 3.99 \text{ k}\Omega$

$$V_{out} = V_{in} \frac{(R_2 || R_3)}{R_1 + (R_2 || R_3)}$$

$$= 9.92 \times \frac{(1/0.548 + 1/3.99)^{-1}}{0.553 + (1/0.548 + 1/3.99)^{-1}}$$

$$= 4.62 \text{ V}$$

$$\text{Error} = \left| \frac{4.62 - 4.60}{4.62} \right| \times 100\%$$

$$= 0.43\%$$



When,  $R_3 = 6.99 \text{ k}\Omega$

$$\begin{aligned}
 V_{out} &= V_{in} \frac{(R_2 \parallel R_3)}{R_1 + (R_2 \parallel R_3)} \\
 &= 9.92 \times \frac{(1/0.548 + 1/6.99)^{-1}}{0.553 + (1/0.548 + 1/6.99)^{-1}} \\
 &= 4.75 \text{ V}
 \end{aligned}$$

$$\begin{aligned}
 \text{Error} &= \left| \frac{4.75 - 4.73}{4.75} \right| \times 100\% \\
 &= 0.42\%
 \end{aligned}$$

When,  $R_3 = 10.02 \text{ k}\Omega$

$$\begin{aligned}
 V_{out} &= V_{in} \frac{(R_2 \parallel R_3)}{R_1 + (R_2 \parallel R_3)} \\
 &= 9.92 \times \frac{(1/0.548 + 1/10.02)^{-1}}{0.553 + (1/0.548 + 1/10.02)^{-1}} \\
 &= 4.81 \text{ V}
 \end{aligned}$$

$$\begin{aligned}
 \text{Error} &= \left| \frac{4.81 - 4.80}{4.81} \right| \times 100\% \\
 &= 0.21\%
 \end{aligned}$$

Graph:

N/A

### Result Analysis:

After this experiment, we found that the voltage across a component suddenly drops whenever we add a resistor parallel to that component. Then, when we increase the resistor value, the total resistor increases, and the voltage rises. So, we can control the voltage of a component by adding a variable resistor parallel to that component.

### Questions and Answers:

01. When there was no loading resistor in our circuit,  $V_{out}$  in  $R_2$  was 4.91 volts. Whenever, we add the variable resistor with a value of 1.01 K ohms in parallel, the total resistance at that point decreases and the voltage drops to 3.87 volts. Then, when we increase and the voltage rises to 4.60 volts. As we connected the variable resistor in parallel connection, the total resistance of that point must be less than the lower resistor. In this case, the lower resistor is  $R_2$ . So we can't get the previous voltage again, but we can control the voltage up to  $< 4.91$  volts. So, we can now control the voltage of  $R_2$  by changing the value of the variable resistor.




02. All calculation showed in Data Table Section.
03. Our measured data and theoretically calculated data are approximately the same. We found a minimal margin of error of about 0.21-0.61%. Only. This error may happen due to wires resistance; variable resistors may increase by a bit of resistance so, our voltage divider circuit supports the theory of the loading effect.

### Discussions

In this experiment, we analyze the voltage divider circuit behaves when there is a loading resistance connected in parallel connection. We saw how the voltage changes with the loading resistance value. Most importantly, we can now control the voltage of a component by adding a variable resistor in a parallel connection. In this experiment, we face some problems related to the variable resistor. To set its value at a particular point was too difficult; sometimes, it auto changed its resistance. We managed to keep it steady and completed the experiment within the time.

### Attachment:

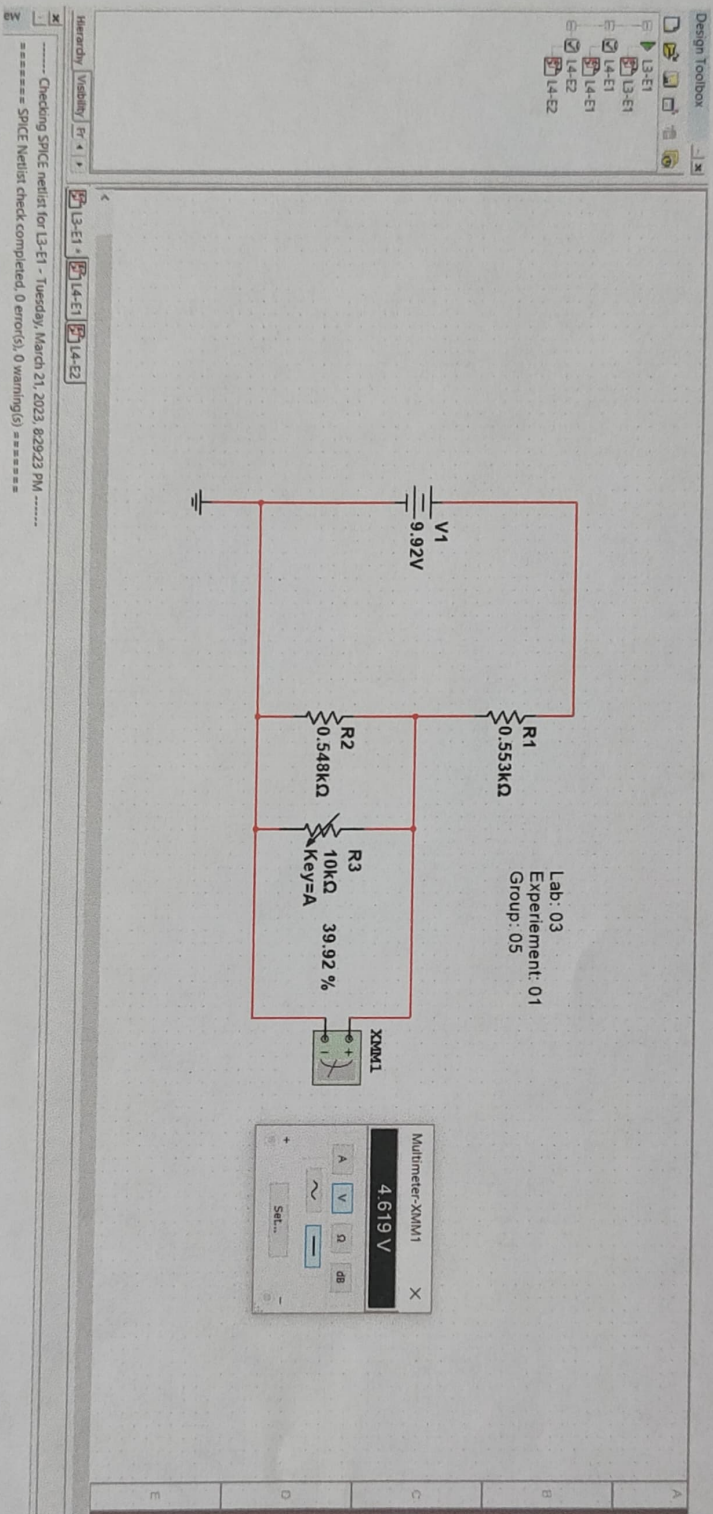01. Signed Data Table.
02. Simulation using multisim.







## Electrical Circuit I Lab

- Now say we connect an output load,  $R_3$  in parallel to  $R_2$  :

 


Figure 2: With Output Load Connected.

⇒ Do you think keeping the values of resistors same would still give  $V_{out}=3V$  from  $V_{in}=5V$  ?  
Let's check:

Since you have a Load resistance parallel to  $R_2$  , your Voltage divider formula to find  $V_{out}$  is:

$$V_{out} = V_{in} \frac{(R_2 // R_3)}{R_1 + (R_2 // R_3)} \quad (2)$$

Let  $R_3 = 10k$ .  
 $R_2 // R_3 = 2.31k$


$$\rightarrow V_{out} = 2.68 \text{ v}$$

So, our Designed value was 3v, but connecting a load resistor reduced it to 2.68v.

### Design Criteria:

To minimize the loading effect, choose the load resistor to be much larger than its parallel resistor.  
If  $R_3$  is much greater than  $R_2$  then  $R_2 // R_3$  (parallel combination of  $R_2$  and  $R_3$  ) is approximately equal to  $R_2$

### Circuit Diagram:

 

# NORTH SOUTH UNIVERSITY

DEPARTMENT OF ELECTRICAL & COMPUTER ENGINEERING



Electrical Circuit I Lab

## Data Collection for Lab 3:

Group No. \_\_\_\_\_

Instructor's Signature \_\_\_\_\_

*12/03/27*

Table 1:

RL	Vout (Measured)	Vout (Calculated)	%Error
No resistor	4.91	4.94	0.61%
1k (1.01)	3.87	3.88	0.26%
4k (3.99)	4.60	4.62	0.43%
7k (6.99)	4.73	4.75	0.42%
10k (10.02)	4.80	4.81	0.21%

### Report Question:

1. Explain the loading effect of your circuit (i.e explain how does your Vout vary with increasing Load resistor)
2. Showing all steps in details, theoretically calculate the value of Vout for each load resistor.
3. Comparing the theoretical data to the experimental data, comment how far the loading effect of your circuit supports the theory.