

Summer 2023  
EEE/ETE 111L  
Analog Circuits-I Lab (Sec-11)  
Faculty: Professor Dr. Monir Morshed (DMM)  
Instructor: Rokeya Siddiqua

Lab Report 07: BJT biasing circuits.

**Date of Performance:**  
29 September 2023

**Date of Submission:**  
14 October 2023

**Group no.: 05**

1. Mahmudul Hasan- 2011551043
2. Sabrina Haque Tithi- 2031265642
3. Afrin Akter- 2112246642
4. Joy Kumar Ghosh – 2211424642
5. Sazid Hasan- 2211513642

Experiment no-07

Name of the Experiment:

The BJT Biasing circuits

Objective:

Study of the BJT biasing circuits

Theory:

Bipolar junction Transistor are semiconductor devices commonly used in electronic circuits for amplification and switching purposes. BJT biasing is a crucial aspect of designing BJT circuits to ensure proper transistor operation and desired circuit performance.

~~There are~~ Biasing is essential to establish a stable Q point in the active region of a BJT. The Q-point determines the DC operating point of the transistor and it is crucial for faithful reproduction of the input signal.



Achieving a stable Q-point is vital to ensure that the transistor responds linearly to small input signals. In the lab, we learned about the fixed bias circuit and self bias circuit. In the fixed bias circuit  $I_C$  is determined by the ~~base~~ resistance,  $I_C = \frac{V_C}{R_C}$ . The main drawback is its susceptibility to  $\beta$  variations leading to Q point instability.

The self bias circuit overcomes the  $\beta$  sensitivity issue by incorporating a self-biasing resistor  $R_E$  connected to the emitter terminal. In the lab, studying both fixed bias and self bias circuits provides valuable scenario between stability and simplicity. Self bias circuits, though more complex, offer better stability in achieving a reliable Q point for faithful signal production.

## List of equipments:

1. NPN Transistor - C828, BD 135  $\rightarrow$  1 piece
2. Resistor -  $470\Omega$ ,  $560\Omega$ ,  $220\Omega$   $\rightarrow$  1 piece each
3. POT -  $10\text{ k}\Omega$  - 1 unit
4. Trainer board - 1 unit
5. Dc power supply  $\rightarrow$  1 unit
6. Digital multimeter  $\rightarrow$  1 unit
7. Cords and wire  $\rightarrow$  as required

## Circuit Diagram:

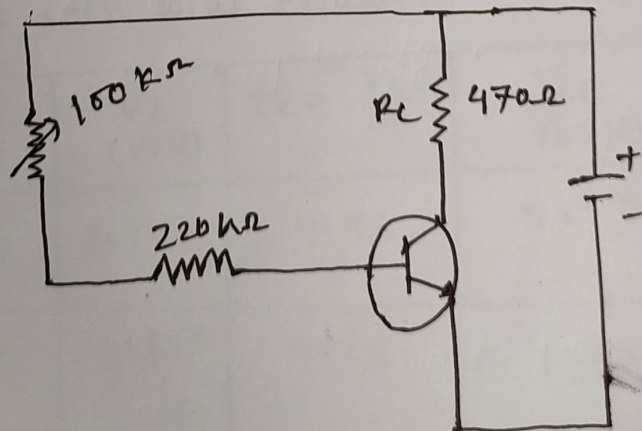


Figure 7.1: Circuit 1



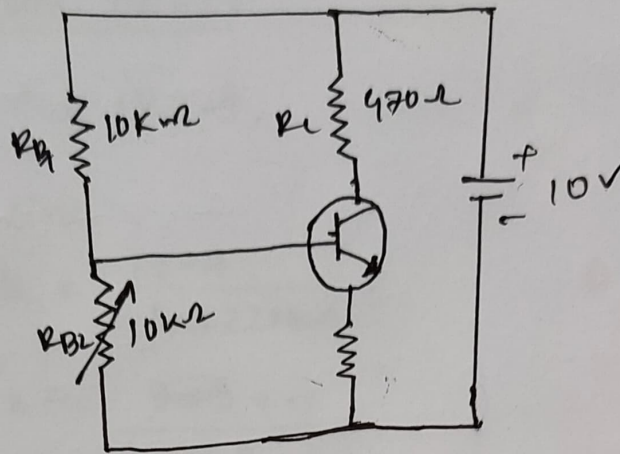


Figure: 7-2 : circuit 2

Data table:

Data for fixed bias circuit

Transistor	$R_C$ (Ω)	$V_C$ (Volt)	$I_C = \frac{V_C}{R_C}$ mA	$V_{CE}$ (Volt)	Q-point
C828	460	4.96	10.78	5.01	(5.01, 10.78)
BD135	460	4.20	9.13	5.61	(5.61, 9.13)

Data for self Bias circuit

Transistor	$R_C$ (Ω)	$V_C$ (Volt)	$I_C = \frac{V_C}{R_C}$	$V_{CE}$ (Volt)	Q-point
C828	460	2.107	4.58	5.00	(5.00, 4.58)
BD135	460	2.155	4.68	4.98	(4.98, 4.68)

Answer the ques: no-1:

From the CKT-1,


DC load line,

$$i_{Bb} = \frac{10 - V}{R_a + 220k\Omega}$$

$$i_b = \frac{9.3}{(220 + R_a)k\Omega}$$

$i_c = \beta i_b$  for active region

$$i_c = \frac{10 - V_{CE}}{470}$$

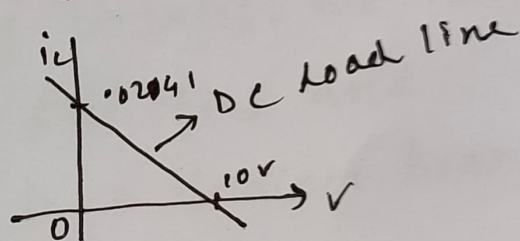

for  $V_{CE} = 0$ ,  $i_c = 0.241A$

The circuit is fixed bias circuit whose stability is given by  $S = 1 + \beta$

stability factor should be low for better performance,  $S = 101$

Circuit-2 is called safe bias circuit.

$$\text{Here, } R_B = R_{B1} \parallel R_{B2}$$

$$S = \frac{(1 + \beta) + \left(\frac{R_B}{R_E} + 1\right)}{1 + \beta + \frac{R_B}{R_E}} = \frac{101 \left(\frac{5000}{500} + 1\right)}{101 + \frac{5000}{500}} = 9.122$$



So, circuit-2 shows better stability.

2. Ans:

+ Graph attached

Discussion:




In this lab, we experienced the analysis of BJT biasing circuits. We have covered fixed bias and self bias and build up two circuits in a trainer board. We used two transistors in the lab, For the ~~first~~ <sup>both</sup> circuit, we used C828 and for the ~~second~~ <sup>both</sup> ckt, we used BD135 transistors. We have used POT which was  $R_B = 10k\Omega$ . For the first ckt, we measured  $R_E$  and set  $R_B$  to maximum value and decreasing POT  $R_B$  gradually, so that  $V_{CE} = V_{CC}/2$ . For both circuit we have measured  $V_{CE}$  and  $I_E$  and recorded Q-point.




After finishing the recorded Q-point, we ~~have~~ got some error for fixed bias circuit. ~~How~~ then we build up the circuit again and measured the value of  $I_C$  and  $V_{CE}$  and found the Q-point.

### Contribution:

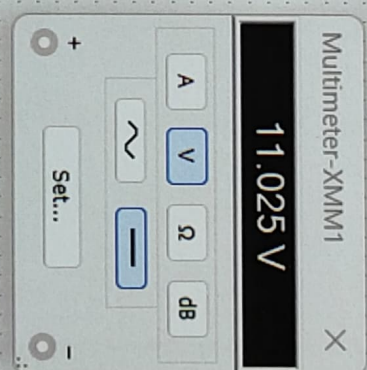
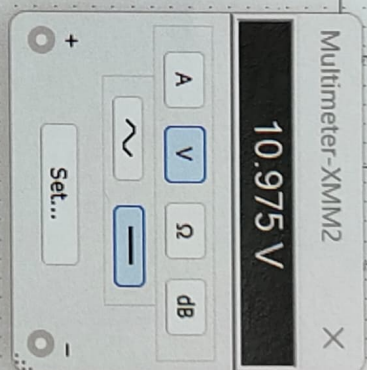
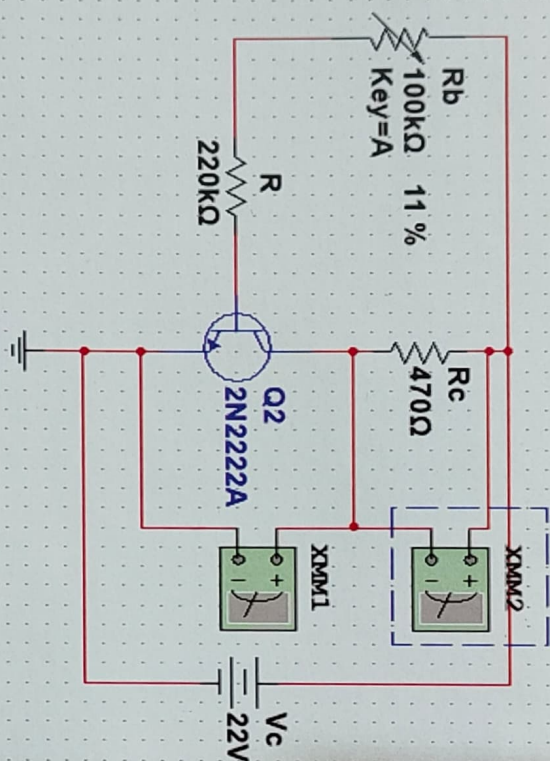
1. Mahmudul Hasan  
Id-2011551043 → Full report writing, help to build circuit-1
2. Sazid Hasan  
ID-2211513642 → 1st circuit build and took measurements
3. Sabrina Haque Rithi  
ID-2031265642 → operating DC power supply and POT
4. Joy Kumar Ghosh  
Id- ~~2112246642~~  
2211424642 → Multisim 2nd ckt build up and took measurement
5. Afrin Akter  
Id-2112246642 → Help to took measurement and report writing.






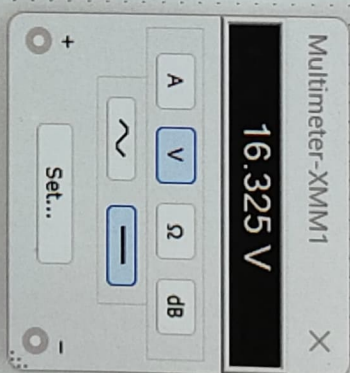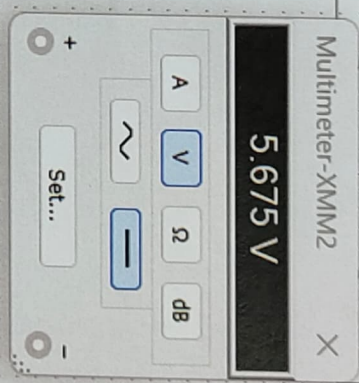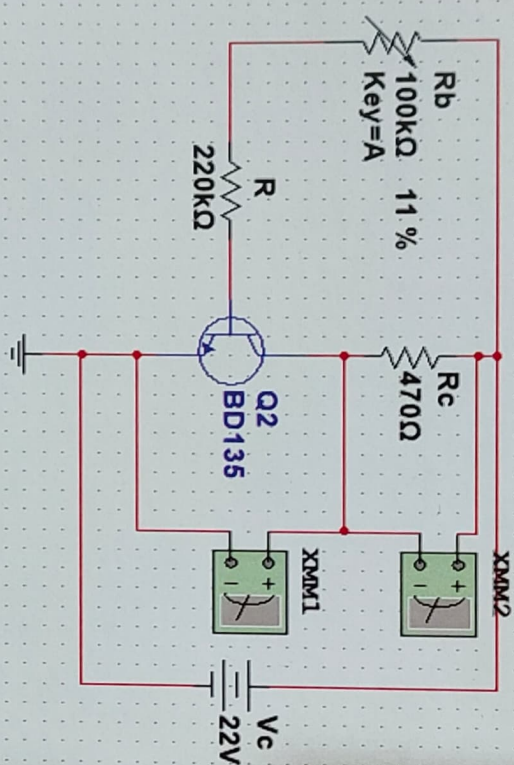



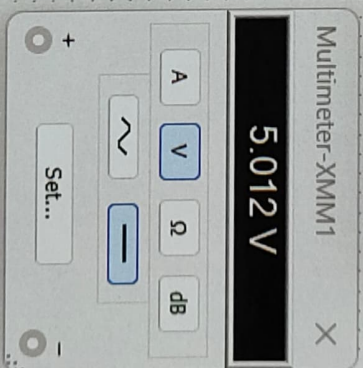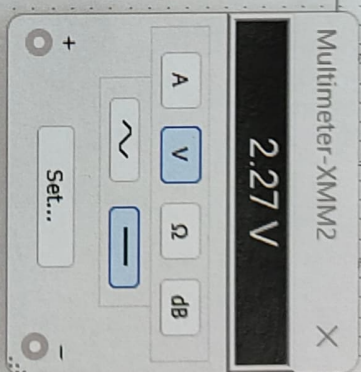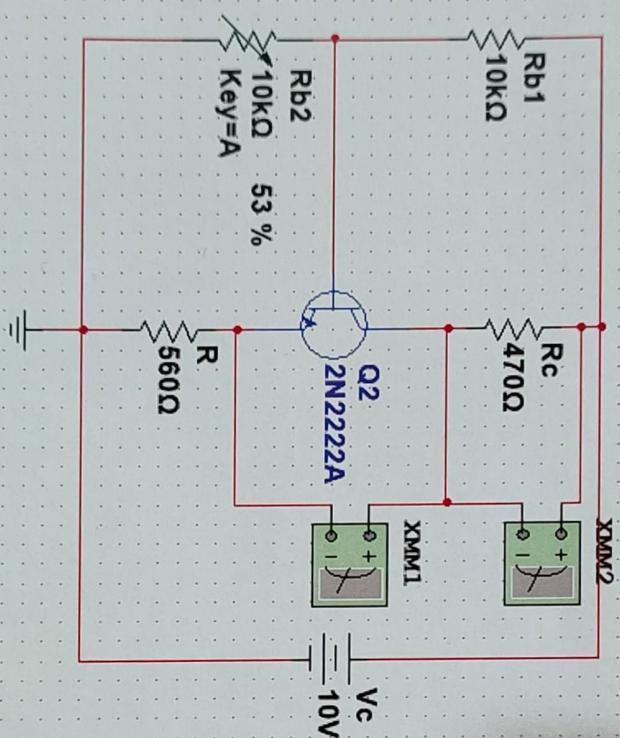

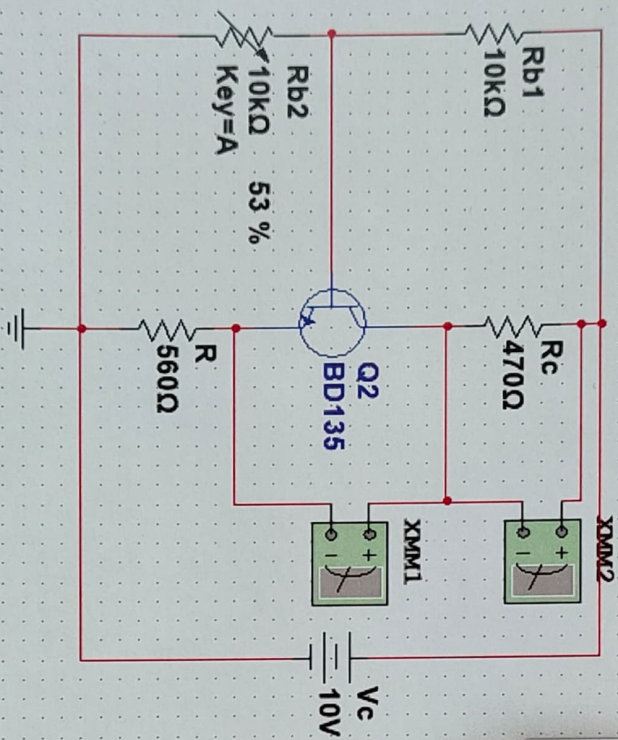

Multimeter-XMM2

2.235 V

A V  $\Omega$  dB

~ —

Set...

Multimeter-XMM1

5.082 V

A V  $\Omega$  dB

~ —

Set...



# NORTH SOUTH UNIVERSITY

DEPARTMENT OF ELECTRICAL & COMPUTER ENGINEERING

## Data Sheet:

Table 7.1 : Data for Fixed Bias Circuit.

Riddiqua  
30.09.23

Transistor	$R_C$ ( $\Omega$ )	$V_C$ (volt)	$I_C = V_C / R_C$ m(Amp)	$V_{CE}$ (volt)	Q-point
C828	460	4.96	10.78	5.01	(5.01, 10.78)
BD135	460	4.20	9.13	5.61	(5.61, 9.13)

Table 7.2 : Data for Self Bias Circuit.

Transistor	$R_C$ ( $\Omega$ )	$V_C$ (volt)	$I_C = V_C / R_C$ m(Amp)	$V_{CE}$ (volt)	Q-point
C828	460	2.108	4.58	5.00	(5.00, 4.58)
BD135	460	2.155	4.68	4.28	(4.28, 4.68)

## Report:

1. Which circuit shows better stability? Explain in the context of the results obtained in the laboratory.
2. Draw the DC load line for both the circuits and show the Q-point.

